



UNSW
SYDNEY


Australia's
Global
University

School of Electrical Engineering &
Telecommunications

ELEC1111

Topic 3: Circuit Theorems

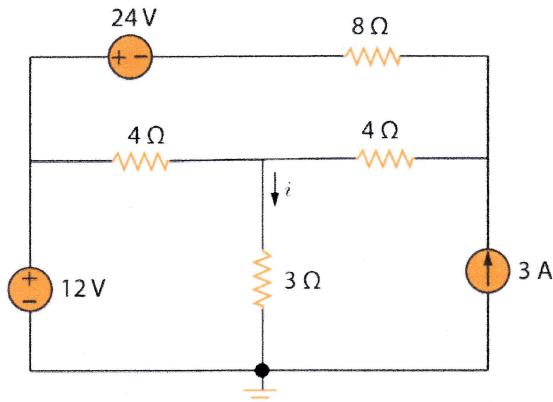- Find the current i in the following circuit by using superposition principle.





Answer: $i = i' + i'' + i''' = 2 \text{ A}$, where $i' = 2 \text{ A}$, $i'' = -1 \text{ A}$, and $i''' = 1 \text{ A}$ are the responses due to 12-V, 24-V, and 3-A sources.

Solution: Let's find the response to each source individually by setting the other independent source to zero. Note that there is NO dependent source.

* i' due to 12-V source

Set 24-V and 3-A sources to zero
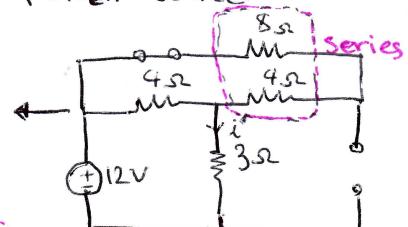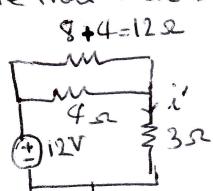
$$\text{KVL: } -12 \times (3 + 4) / 12 i' = 0 \\ i' = \frac{12}{6} = 2 \text{ A}$$





* i'' due to 24-V Source

Set 12-V and 3-A sources to zero

Use Mesh analysis:
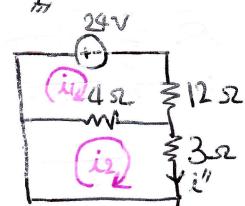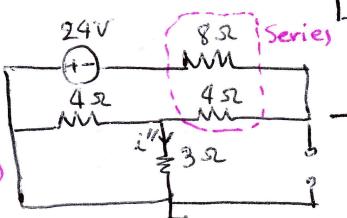
$$\text{KVL @ m1: } 24 + 12i_1 + 4(i_1 - i_2) = 0 \quad \text{(I)} \\ \text{KVL @ m2: } -4(i_1 - i_2) + 3i_2 = 0 \quad \text{(II)}$$



(I) $i_1 = \frac{7}{4} i_2$


$$(I) \quad 16i_1 - 4i_2 = -24 \rightarrow 4 \times \frac{7}{4} i_2 - i_2 = -6 \rightarrow i_2 = i'' = -1 \text{ A}$$

* i''' due to 3-A Source

Using Nodal Analysis Set 12-V and 24-V sources to zero

$$\text{KCL @ } V_1: \frac{V_1}{4} + \frac{V_1}{3} = \frac{V_2 - V_1}{4}$$
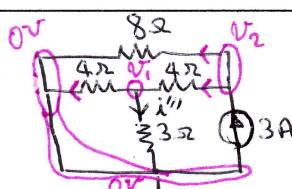
$$\times 12 \rightarrow 3V_1 + 4V_1 = 3V_2 - 3V_1 \rightarrow V_2 = \frac{10V_1}{3}$$




$$\text{KCL @ } V_2: 3 = \frac{V_2}{8} + \frac{V_2 - V_1}{4} \rightarrow 3V_2 - 2V_1 = 24$$

$$i''' = \frac{V_1}{3} = 1 \text{ A}$$

$$\Rightarrow \text{Thus } i = i' + i'' + i''' = 2 + (-1) + 1 = 2 \text{ A}$$

Contribution of 3 Sources.
Via Superposition

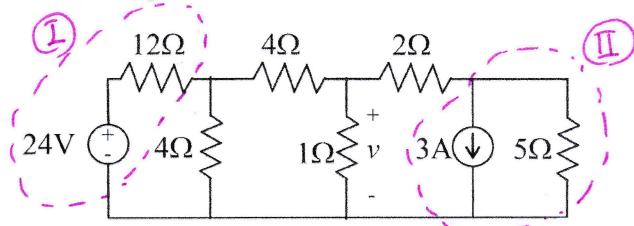2. (Final Exam, S1, 2014) Use source transformations to determine the voltage v shown in the following circuit.



Answer: $v = -1 \text{ V}$

Solution: first transform ① and ④

$$V = 1 \times \frac{\frac{7}{2}}{1 + \frac{7}{2}} \times \frac{9}{7} = \frac{-7}{9} = -1 \text{ V}$$


Current division

or

$$\frac{15-6}{7} = \frac{9}{7} \text{ A}$$


Combine Sources

$$\frac{6}{7} = \frac{6}{7} \text{ A}$$

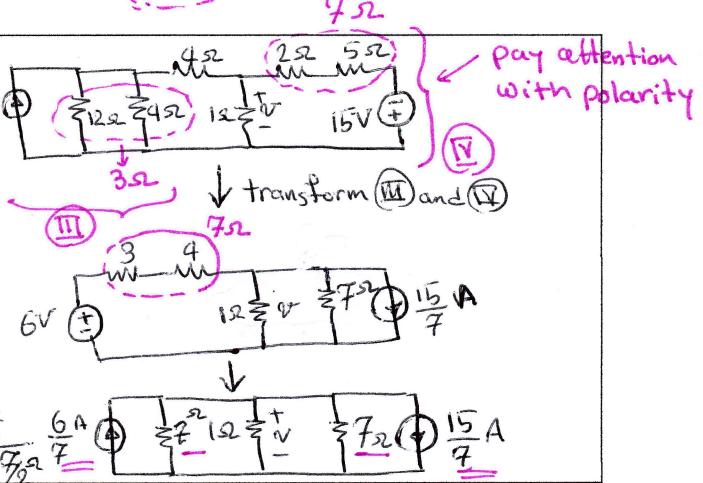



pay attention with polarity

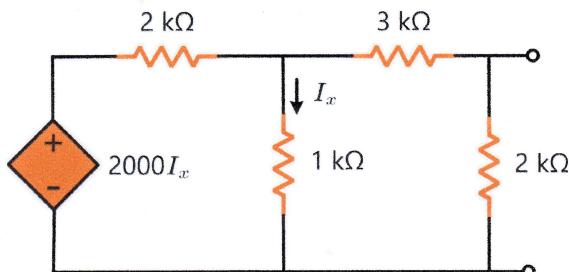3. Determine R_{Th} for the following circuit. What is the value of the Thevenin equivalent voltage? Why can we find this value without any calculations?



Answer: $V_{Th} = 0 \text{ V}$, $R_{Th} = \frac{10}{7} = 1.428 \text{ k}\Omega$

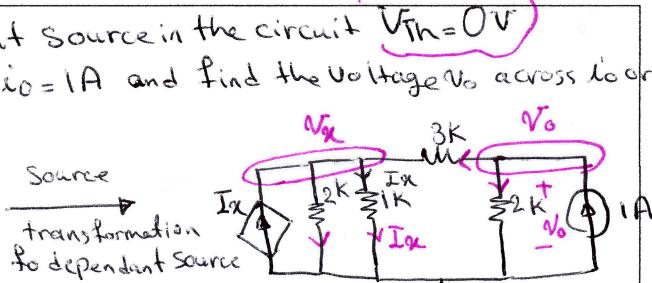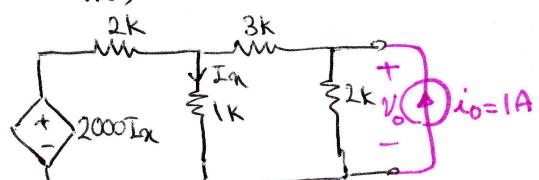Solution: Since there is no independent source in the circuit $V_{Th}=0 \text{ V}$. For R_{Th} , attach a current source $i_0=1 \text{ A}$ and find the voltage V_0 across the $2\text{k}\Omega$.



$$\text{Use KCL at } V_x: 1 = \frac{V_0}{2k} + \frac{V_0 - V_x}{3k} \xrightarrow{x6} 5V_0 - 2V_x = 6 \quad \textcircled{I}$$

$$\text{Analysis KCL at } V_x: I_x + \frac{V_0 - V_x}{3k} = \frac{V_x}{2k} + \frac{V_x}{1k} \xrightarrow{x6} 2V_x = 5V_0 \rightarrow V_x = \frac{2}{5}V_0 \quad \textcircled{II}$$


$$\text{Sub } \textcircled{II} \text{ into } \textcircled{I}: 5V_0 - \frac{4}{5}V_0 = 6 \rightarrow V_0 = \frac{30}{21} = \frac{10}{7} \text{ KV}$$

Careful that all resistors are in $\text{k}\Omega$ and with $i_0=1 \text{ A}$, the voltage will be in KV


$$\Rightarrow R_{Th} = \frac{V_0}{i_0} = \frac{\frac{10}{7} \text{ KV}}{1 \text{ A}} = \frac{10}{7} \text{ k}\Omega$$

↑ pay attention

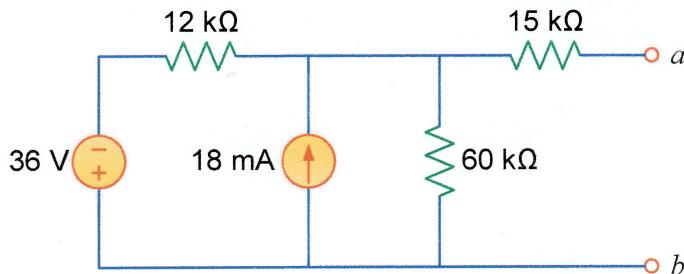4. (Final Exam - S2, 2015) Find the Norton equivalent of the following circuit.




Norton equivalent circuit

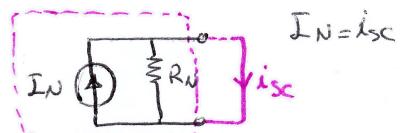

Answer: $I_N = 6\text{mA}$, $R_{Th} = 25\text{k}\Omega = R_N$

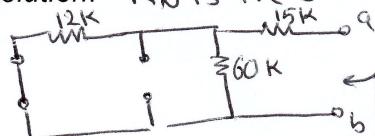
Solution: R_N is the same as R_{Th} . Set all independent sources to zero (No dependent source)




$$R_{Th} = R_N = 15\text{k} + \frac{12 \times 60}{72} = 15 + 10 = 25\text{k}\Omega$$

$R_N \parallel R_{Th}$

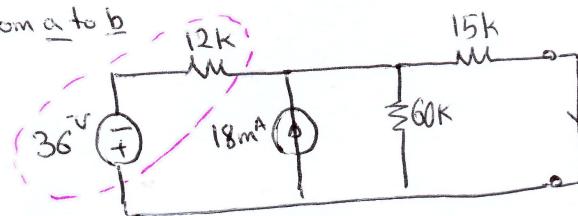To find I_N , short circuit the terminals and find the short-circuit current flowing from a to b



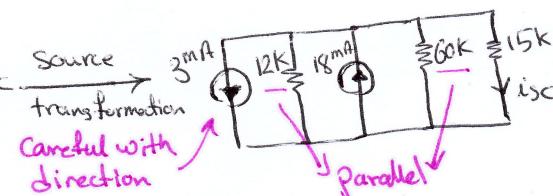Source transformation
Careful with direction
parallel




$$\begin{aligned} \text{Combine current Sources and } 12\text{k} \parallel 60\text{k} & \rightarrow 18 - 3 = 15 \text{ mA} \\ & \text{Sources and } 10\text{k} \parallel 15\text{k} \rightarrow i_{sc} \\ & \text{Current division} \\ I_N = i_{sc} &= \frac{10\text{k}}{10\text{k} + 15\text{k}} \times 15\text{ mA} \\ &= 6\text{ mA} \end{aligned}$$

Norton equivalent circuit

5. (Mid-session Exam – S2, 2016) For the circuit below, find the current i in the $4\text{-}\Omega$ resistor using,

(a) The superposition principle.

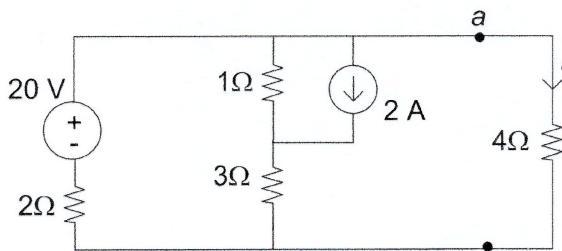(b) The Thevenin equivalent of the circuit to the left of terminal pair $a-b$.



Answer: $i = i' + i'' = 2.375\text{ A}$, where $i' = 2.5\text{ A}$ and $i'' = -0.125\text{ A}$ are the responses due to 20-V and 2-A sources.


b) $V_{Th} = 12.66\text{ V}$, $R_{Th} = \frac{4}{3}\text{ }\Omega = 1.33\text{ }\Omega$

Solution: Let's find the response to each source individually by setting the other independent sources to zero


$$5.a) i = i' + i''$$

* i' due to 20V Source

Set 2-A source to zero

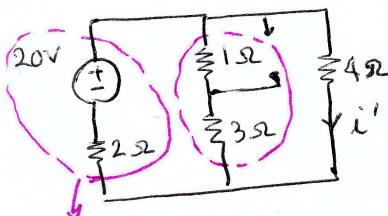


by setting the other

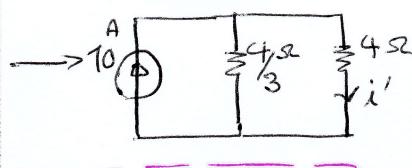


current division

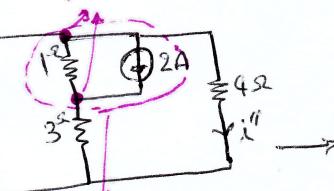
$$i' = \frac{4}{\frac{4}{3} + 4} \times 10 = \frac{40}{16} = 2.5 \text{ A}$$



Terminal

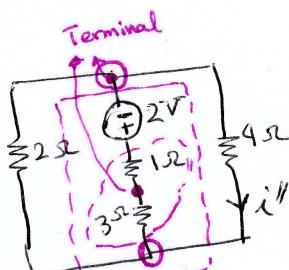

Source transformation

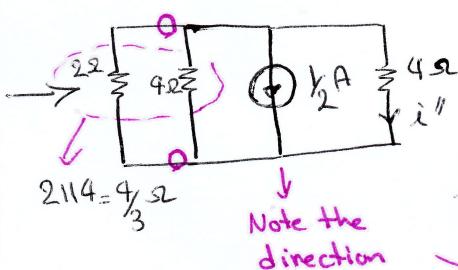

Note the direction

Current division


$$i'' = \frac{\frac{4}{3}}{\frac{4}{3} + 4} \times -4 = \frac{-4}{16 \times 2} = -0.125 \text{ A}$$

superposition

$$\text{Thus } i = i' + i'' = 2.5 - 0.125 = 2.375 \text{ A}$$

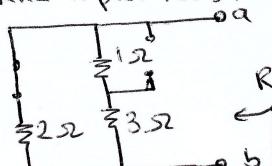
5.b) First detach the load (4Ω) from the circuit.

Then check for dependent sources, if not, set all independent sources to zero and find input resistance, R_{th}




$$R_{th} = R_{in} = 2(1+3) = \frac{4}{3} \Omega$$

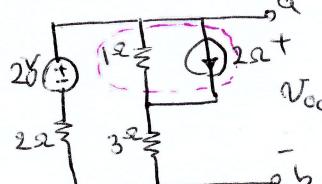For V_{th} , find the open-circuit voltage after detaching the load, $V_{th} = V_{oc}$



source transformation

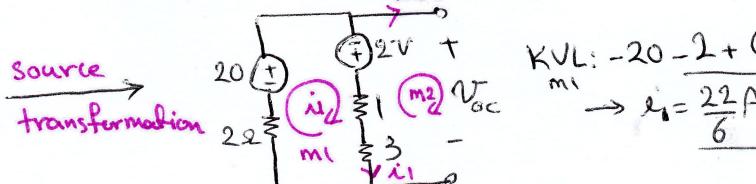


$$\text{KVL: } -20 - 2 + (1+3+2)i_1 = 0 \rightarrow i_1 = \frac{22}{6} \text{ A}$$

$$\text{KVL in: } V_{oc} - (1+3)i_1 + 2 = 0 \rightarrow V_{oc} = 4 \times \frac{22}{6} - 2 = \frac{38}{3} = 12.66 \text{ V}$$


$$\Rightarrow V_{th} = V_{oc} = 12.66 \text{ V}$$

Using Thévenin
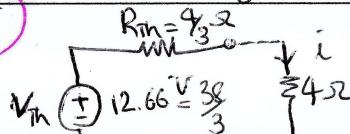
$$\Rightarrow i = \frac{V_{th}}{R_{th} + 4} = \frac{\frac{38}{3}}{\frac{4}{3} + 4} = \frac{38}{16} = 2.375 \text{ A}$$



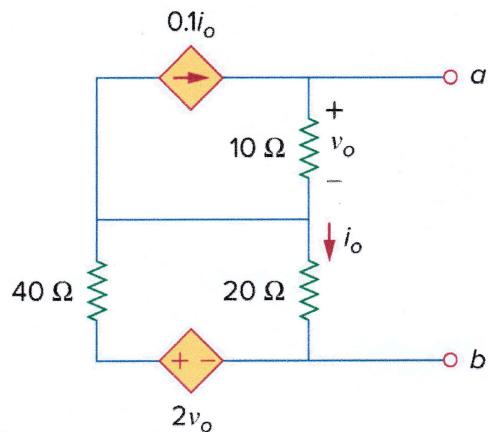
6. Find the Thevenin equivalent of the circuit given below.



Answer: $V_{Th} = 0 \text{ V}$, $R_{Th} = 31.73 \text{ k}\Omega$

Solution: Since there is no independent source in the circuit, $V_{Th} = 0 \text{ V}$

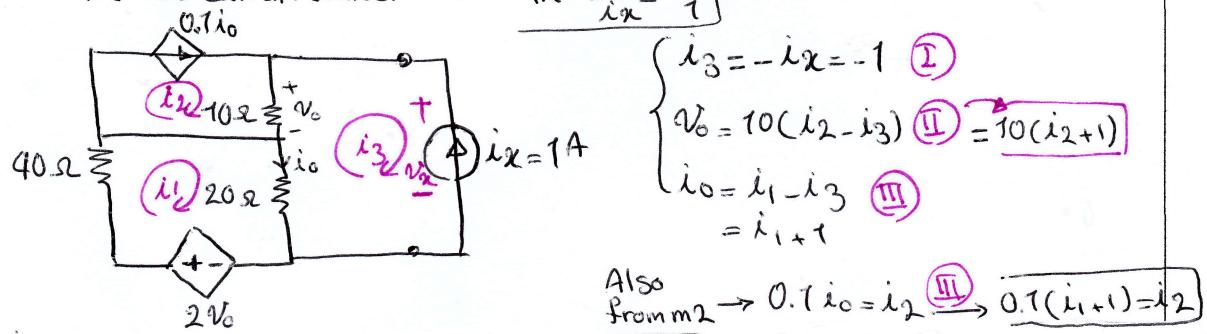For R_{Th} , attach a current source $i_x = 1 \text{ A}$ and then find the voltage v_x across the new current source. Then $R_{Th} = \frac{V_x}{i_x} = \frac{V_x}{1}$



Using Mesh Analysis : $\star KVL_{in m_1} : 40i_1 + 20i_o - 2v_o = 0$

$$\begin{aligned} \text{From } \text{m}_1 &\rightarrow 40i_1 + 20(i_1 + 1) - 2 \times 10(i_2 + 1) = 0 \\ &\rightarrow 60i_1 - 20i_2 = 0 \rightarrow 3i_1 = i_2 \quad \star \star \quad \star \star \\ \Rightarrow 30i_1 &= i_1 + 1 \Rightarrow i_1 = \frac{1}{29} \text{ A} \quad \Rightarrow i_2 = \frac{3}{29} \text{ A} \quad \Rightarrow 3i_1 = 0.7(i_1 + 1) \end{aligned}$$


$KVL_{in m_3} : V_x - 20i_o - v_o = 0 \quad \text{III} \quad \Rightarrow V_x = 20(i_1 + 1) + 10(i_2 + 1) \quad \text{IV} \quad \Rightarrow V_x = 20i_1 + 20 + 30i_1 + 10$

$$\Rightarrow V_x = 50i_1 + 30 = \frac{50}{29} + 30 = 31.73 \text{ V} \quad (\text{All resistors are in } \Omega)$$

$$\Rightarrow R_{Th} = \frac{V_x}{i_x} = 31.73 \Omega$$

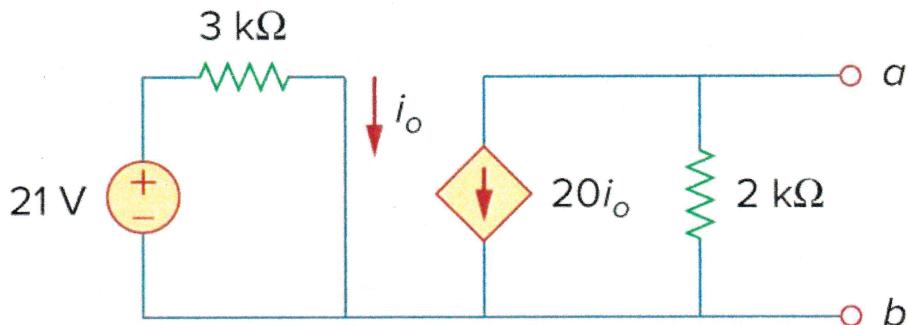7. For the transistor model given below, do the following,


- Obtain the open-circuit voltage v_{oc} across terminals a-b.
- Calculate the short-circuit current i_{sc} at terminals a-b.
- Find the equivalent resistance R_{eq} seen from the terminals a-b
(use the results from previous parts)



Answer:


- $v_{oc} = -280 \text{ V}$
- $i_{sc} = -140 \text{ mA}$
- $R_{eq} = 2 \text{ k}\Omega$

Solution:

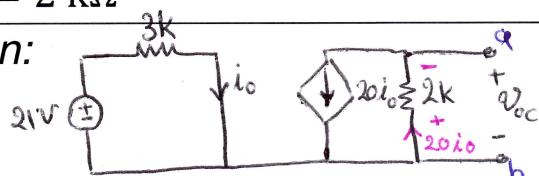

$$\text{a) } i_o = \frac{21V}{3k} = 7 \text{ mA} \quad \text{Note the polarity}$$
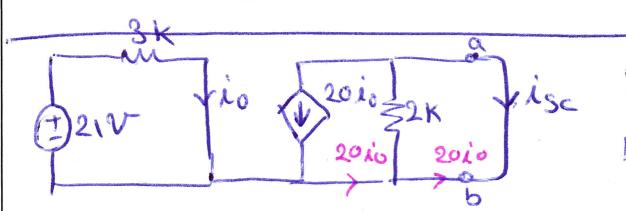
$$v_{oc} = -2k \times 20i_o = -280 \text{ V}$$




$$\text{b) } i_{sc} = 20i_o \xrightarrow[\text{from part (a)}]{i_o = 7 \text{ mA}} i_{sc} = -140 \text{ mA}$$

Note the directions

$$R_{eq} = \frac{v_{oc}}{i_{sc}} = \frac{-280 \text{ V}}{-140 \text{ mA}} = 2 \text{ k}\Omega$$

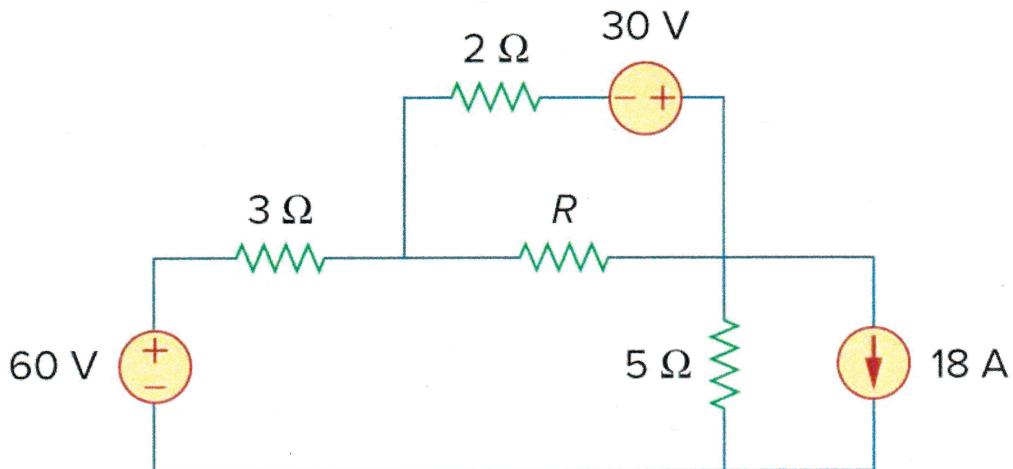8. In the following circuit, find the maximum power that can be delivered to the resistor R in the circuit below. What should be the value of R for maximum power transfer?





Answer: $R_{Th} = 1.6 \Omega$, $V_{Th} = 6 V$, $P_{max} = 5.625 W$, $R = 1.6 \Omega$

Hint: Find the Thevenin equivalent circuit from the terminals across the load R .

Solution: No dependent source \rightarrow Set all Independent Sources to zero and find Req . (The objective is to find Thevenin equivalent circuit) Remove R and find the equivalent resistance first.

$$Req = R_{Th} = (3 + 5) // 2 = 1.6 \Omega$$

Now, find V_{oc} across the terminals

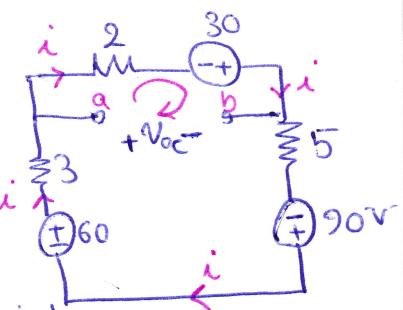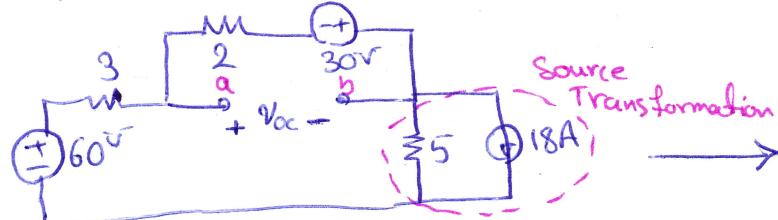


Assign the current i and write KVL in the main loop

* KVL: $-90 - 60 + 3i + 2i - 30 + 5i = 0 \rightarrow 10i - 180 = 0 \rightarrow i = 18 A$ (I)

Now write KVL in top mesh or bottom mesh

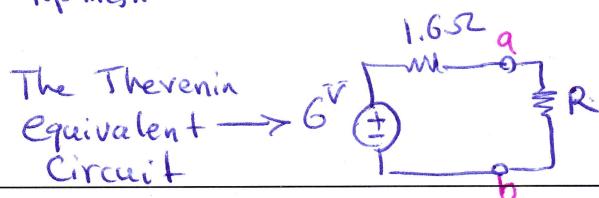* KVL in top mesh: $-V_{oc} + 2i - 30 = 0 \xrightarrow{(I)} V_{oc} = 6 V$




for Max Power Transfer $R = R_{Th} = 1.6 \Omega$

$$P_{max} = \frac{V_{Th}^2}{4R_{Th}} = \frac{6^2}{4 \times 1.6} = 5.625 W$$

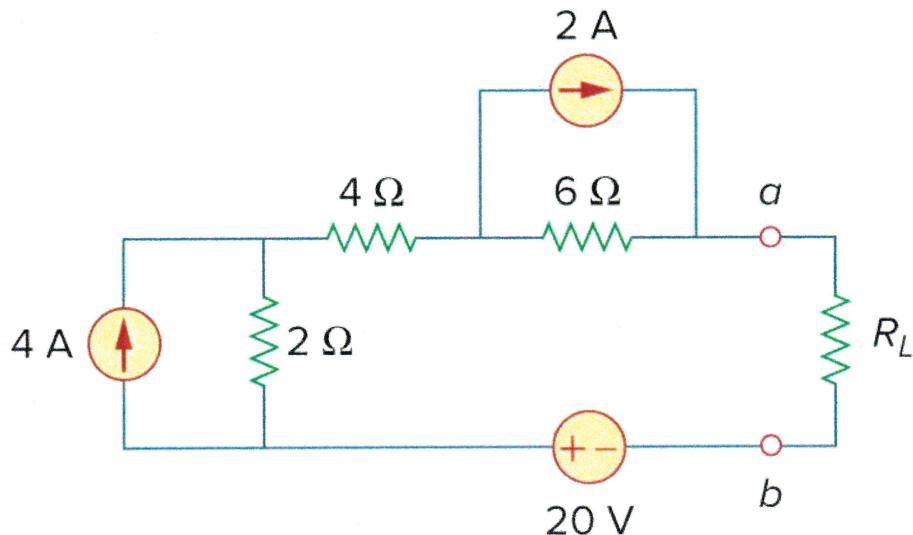9. For the circuit below,

- Obtain the Norton equivalent circuit at terminals a-b.
- Calculate the current in $R_L = 13 \Omega$.
- Find R_L for maximum power deliverable to R_L .
- Determine that maximum power.



Answer:

a) $R_N = 12 \Omega, I_N = \frac{10}{3} = 3.33 \text{ A}$


b) $I_L = \frac{8}{5} = 1.6 \text{ A}$

c) $R_L = 12 \Omega$



d) $P_{\max} = \frac{100}{3} = 33.33 \text{ W}$

Solution: No dependent source \rightarrow Set all independent sources to zero.

Then find $R_N = R_{\text{eq}}$ from the terminals a-b

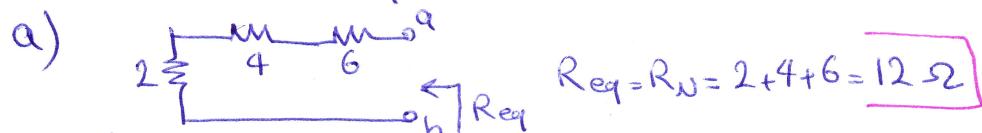
a) 

Now find Short-circuit Current

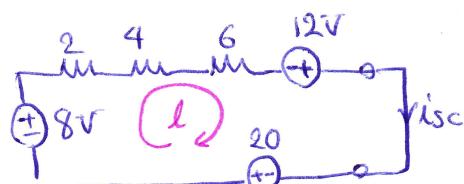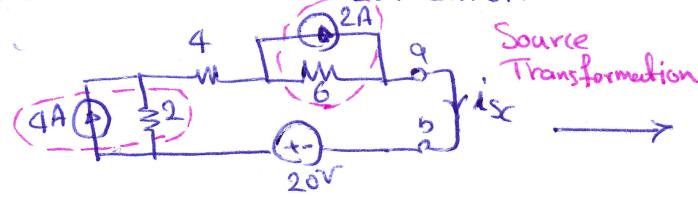

* KVL in loop l: $-12 - 20 - 8 + i_{sc}(2+4+6) = 0 \rightarrow i_{sc} = \frac{10}{3} \text{ A} = I_N$


b) Use Norton equivalent circuit

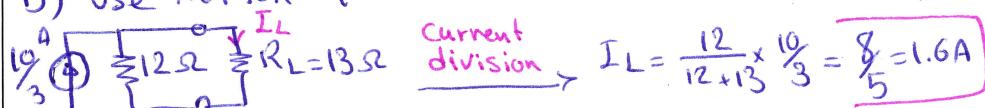

Current division: $I_L = \frac{12}{12+13} \times \frac{10}{3} = \frac{8}{5} = 1.6 \text{ A}$

c) Max Power Transfer $R_L = R_{\text{Th}} = R_N = 12 \Omega$

$P_{\max} = \frac{V_{\text{Th}}^2}{4R_{\text{Th}}} = \frac{40^2}{4 \times 12} = \frac{100}{3} \text{ W}$

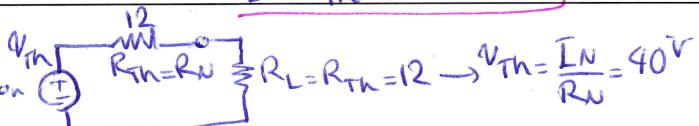d) Source Transformation 

$V_{\text{Th}} = \frac{I_N}{R_N} = 40 \text{ V}$