

Topic 8: AC Circuits II

1. Write nodal equations for the following circuits:

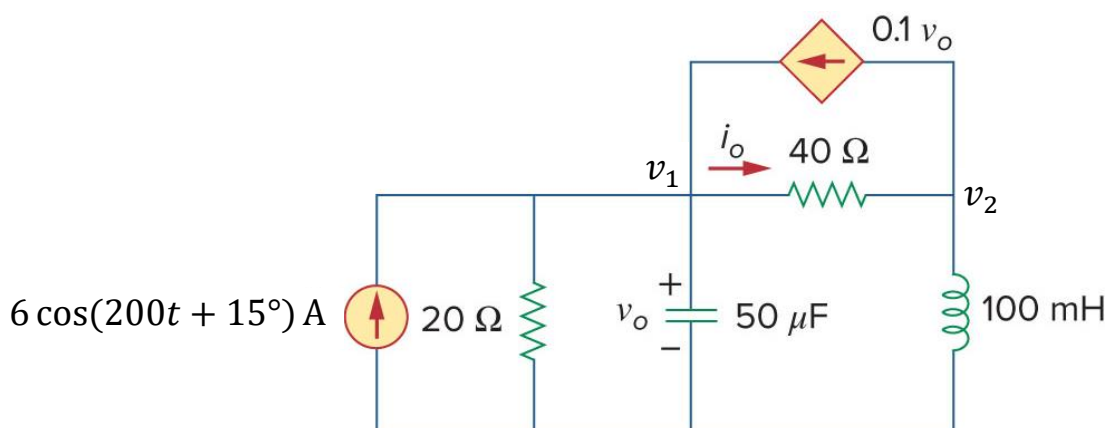


Fig. 1

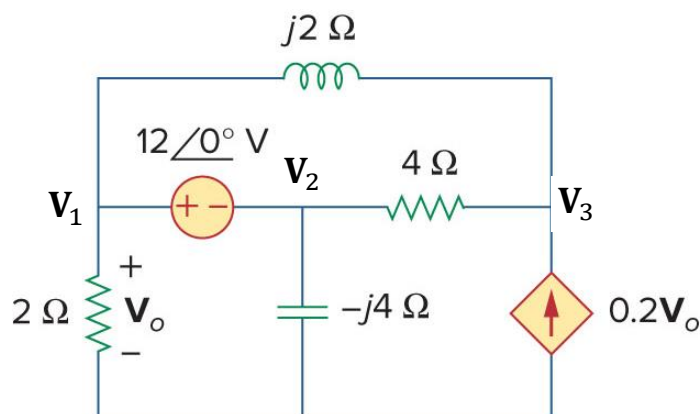


Fig. 2

Answer:

a) Fig. 1:
$$\begin{cases} (-2.5 + j1)V_1 - 2.5V_2 = 579.5 + j155.3 \\ 3V_1 + (1 - j2)V_2 = 0 \end{cases}$$

b) Fig. 2:
$$\begin{cases} (2 - j2)V_1 + (1 + j)V_2 + (-1 + j2)V_3 = 0 \text{ V} \\ (0.8 - j2)V_1 + V_2 + (-1 + j2)V_3 = 0 \text{ V} \\ V_1 - V_2 = 12 \end{cases}$$

2. Write mesh equations for the following circuits:

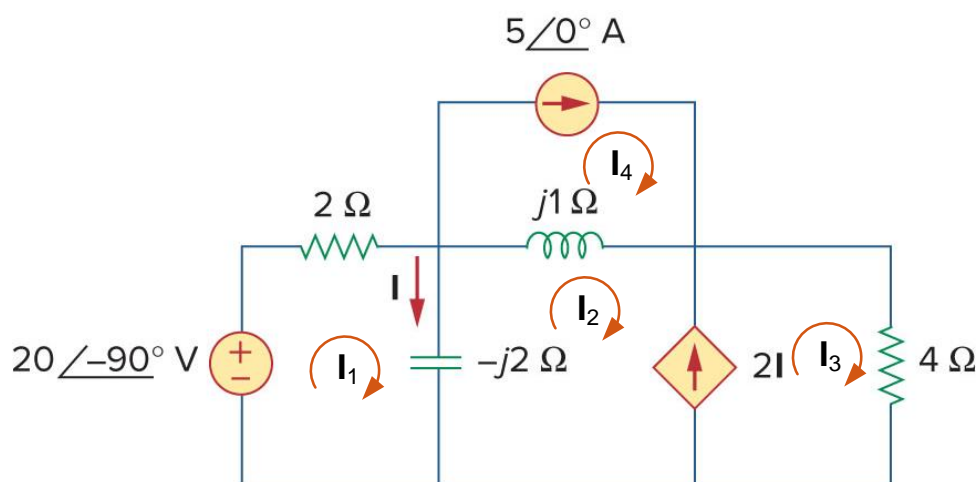


Fig. 1

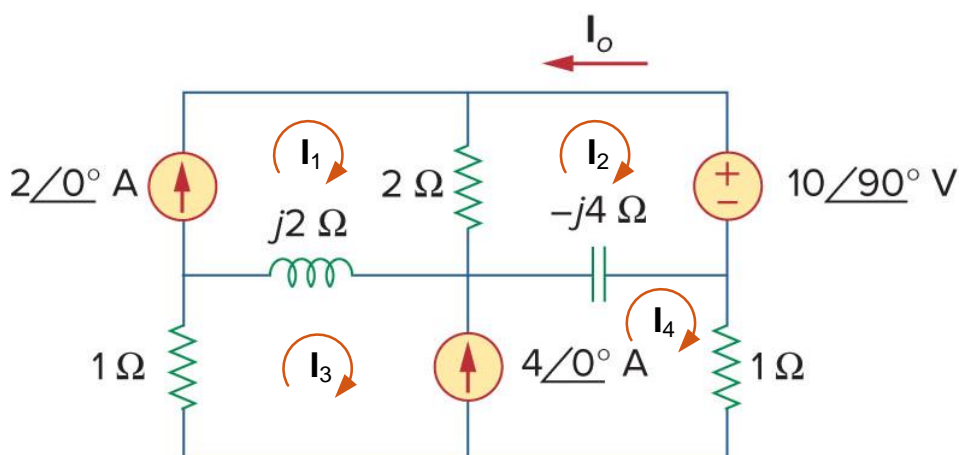


Fig. 2

Answer:

a) Fig. 1:
$$\begin{cases} (1-j)I_1 + jI_2 = -j10 \\ j2I_1 - jI_2 + 4I_3 = j5 \\ 2I_1 - I_2 - I_3 = 0 \\ I_4 = 5 \end{cases}$$

b) Fig. 2:
$$\begin{cases} I_1 = 2 \\ (1-j2)I_2 + j2I_4 = 2-j5 \\ j4I_2 + (1+j2)I_3 + (1-j4)I_4 = j4 \\ I_3 - I_4 = -4 \end{cases}$$

3. Use superposition principle to find i_x and v_x in the following circuits

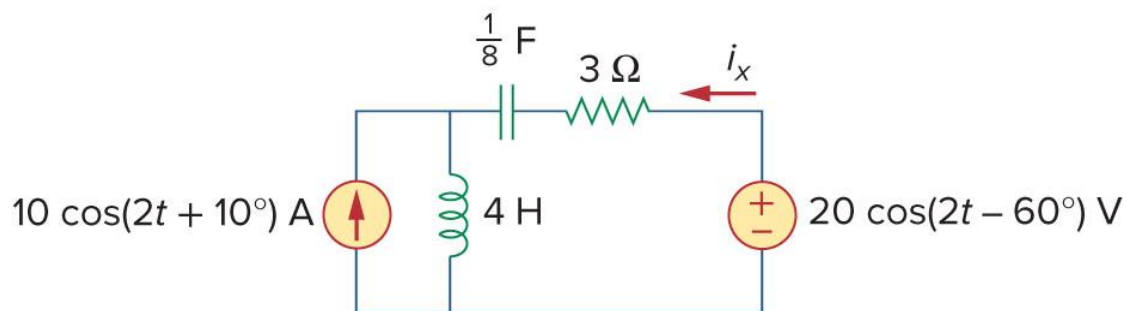


Fig. 1

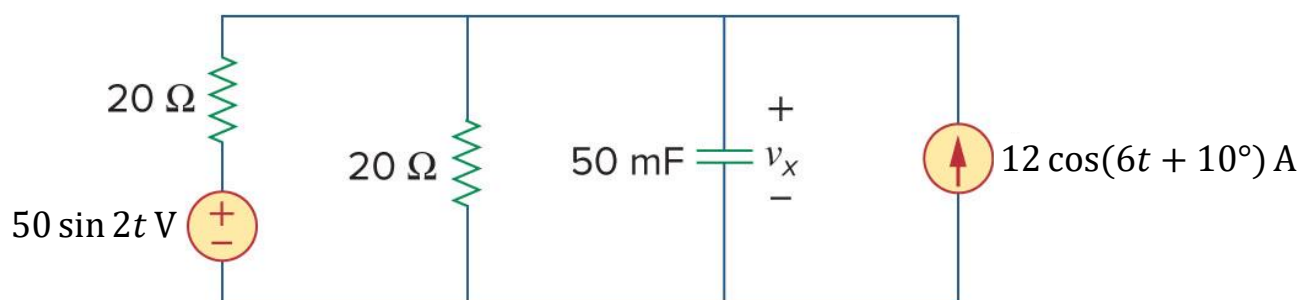



Fig. 2

Answer:

a) Fig.1: $i_x(t) = 19.8 \cos(2t - 129.1^\circ) \text{ A}$


b) Fig. 2: $v_x(t) = [17.678 \cos(2t - 135^\circ) + 37.95 \cos(6t - 61.5^\circ)] \text{ V}$

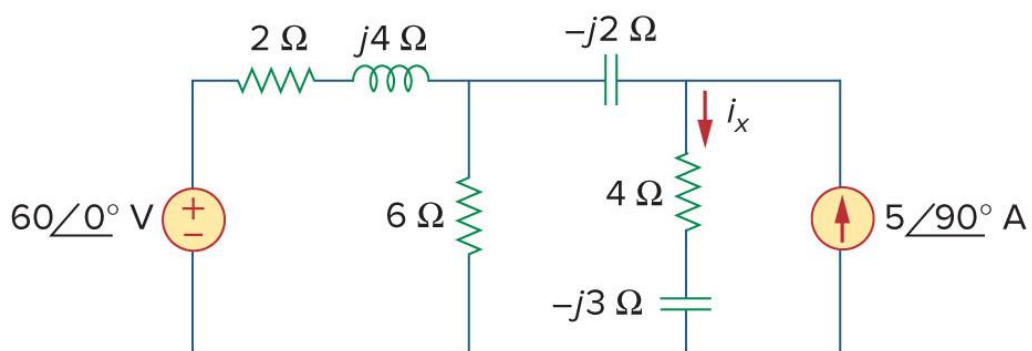4. Use source transformation to find I_x in the following circuit.




Answer: $I_x = 5.238 \angle 17.35^\circ \text{ A}$

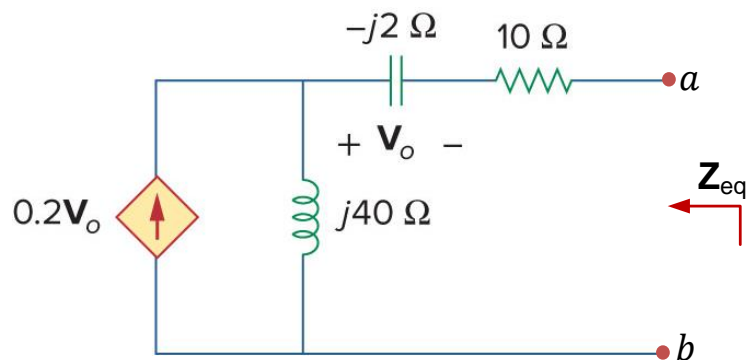5. Calculate the equivalent impedance of the following circuit from the terminals a - b .




Answer: $\mathbf{Z}_{eq} = -6 + j38\ \Omega$.

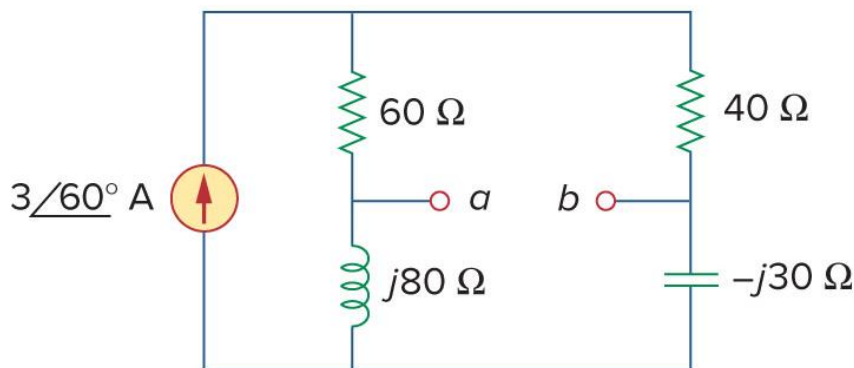6. For the following circuit, find the Thevenin and Norton equivalent circuits




Answer: $\mathbf{Z}_{eq} = 20 + j40\ \Omega = 44.72\angle 63.43^\circ\ \Omega$, $\mathbf{V}_{Th} = 134\angle 123.4^\circ\text{ V}$, $\mathbf{I}_N = 3\angle 60^\circ\text{ A}$

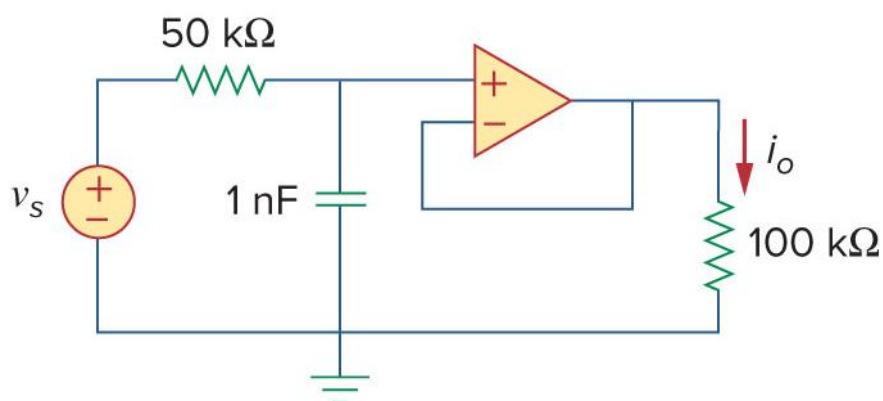7. Find $i_o(t)$ in the Op Amp circuit shown below if $v_s = 4\cos(10^4 t)\text{ V}$




Answer: $i_o(t) = 35.78\cos(10^4 t - 26.56^\circ)\ \mu\text{A}$

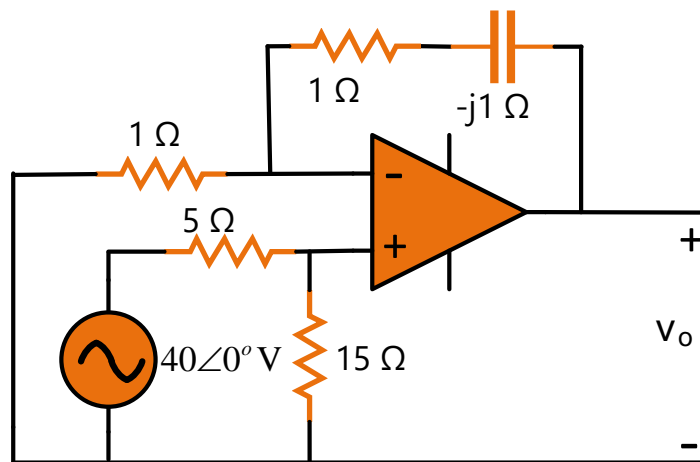8. (Final Exam – Summer, 2016-17) For the circuit shown in below, calculate the output voltage V_o .



Answer: $V_o = 67.08\angle(-26.56^\circ) \text{ V} = 60 - j30 \text{ V}$

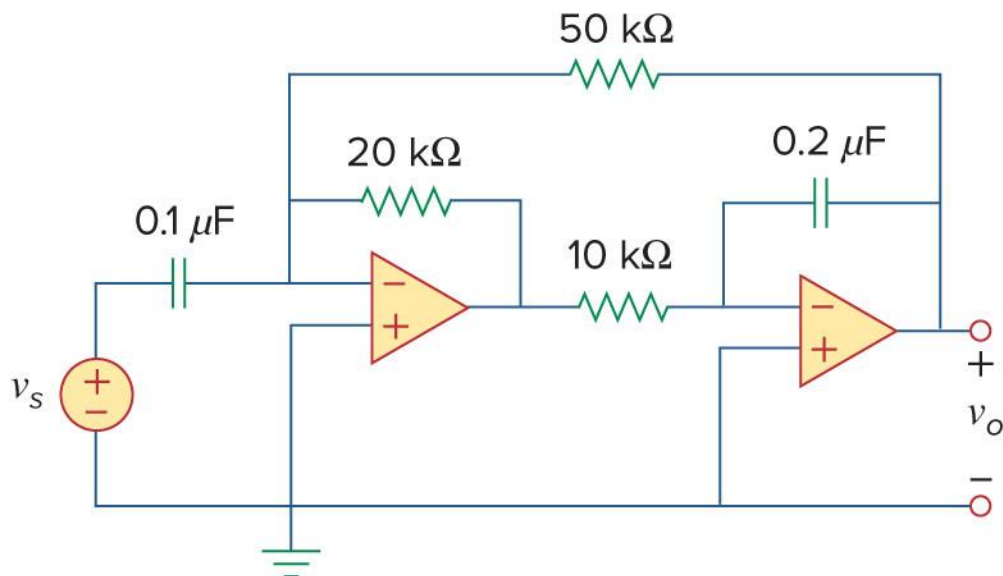9. Calculate $v_o(t)$ for the Op Amp circuit below if $v_s = 12 \cos(10^3 t - 60^\circ) \text{ V}$



Answer: $v_o(t) = 11.767 \cos(10^3 t - 71.31^\circ) \text{ V}$