

# Topic 4 recap

- A capacitor is a circuit element that stores energy in its electric field.
- The ratio of voltage to charge across a capacitor is its *capacitance* (F).

$$q = Cv$$

- Current in a capacitor is proportional to the time rate of change of its voltage.

$$i = C \frac{dv}{dt}$$

$$v(t) = \frac{1}{C} \int_{t_0}^t i(\tau) d\tau + v(t_0)$$

- Energy stored in a capacitor is proportional to the square of its voltage.

$$w_c = \frac{1}{2} Cv^2$$

- Capacitor acts as an open circuit to DC voltage.
- Parallel combination of capacitors is similar to series resistors.

$$C_{eq} = C_1 + C_2 + \cdots + C_N$$

- Series combination of capacitors is similar to parallel resistors.

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} \cdots + \frac{1}{C_N}$$

# Topic 4 recap

- Natural response of RC circuits
  - Behaviour of the circuit (in terms of voltage or current) due to initial energy stored.
  - If the capacitor has a initial voltage  $v(0) = V_0$ , the natural response of the RC circuit is:

$$v(t) = V_0 e^{\frac{-t}{RC}}$$

- The natural response decay to zero exponentially.
- The speed at which the voltage decays is given by the *time constant*.
  - Time constant is the time required for the response to decay to a factor of  $1/e$  or **36.8%** of its **initial value** or to reach **63.2%** of its **final value**.
  - For an RC circuit  $\tau = RC$ .
  - After **5 time constant**,  $5\tau$ , the capacitor voltage is considered to have reached its final value.
  - The higher the resistance and capacitance, the longer it would take for the capacitor to charge or discharge.
  - The resistance for the time constant is the **Thevenin equivalent resistance** as seen from the capacitor terminals.

# Topic 4 recap

- Step response of RC circuits

- The unit step function can be used in electric circuits to model switching.

$$u(t) = \begin{cases} 0, & t < 0 \\ 1, & t > 0 \end{cases}$$

- The step response is the response to a sudden change in the input sources.
- The capacitor voltage over time is obtained as an exponential function:

$$v(t) = \begin{cases} V_0, & t < 0 \\ V_s + (V_0 - V_s)e^{-\frac{t}{\tau}}, & t > 0 \end{cases}$$

- If the initial voltage  $v(0) = 0$  V , the response is known as **forced response**.
- The step response with non-zero initial condition is known as **complete response**.
  - It can be described as the sum of **transient** and **steady state responses**.
- The solution to the step response of RC circuits can be given as follows:

$$v(t) = v(\infty) + [v(0) - v(\infty)]e^{-\frac{t}{\tau}}, \quad t > 0$$

- $v(0)$ : **Initial voltage** at  $t = 0$ .
- $v(\infty)$ : **Final or steady-state value** at  $t \rightarrow \infty$ .
- $\tau = R_{Th_\infty}C$ : Time constant at  $t \rightarrow \infty$ .