
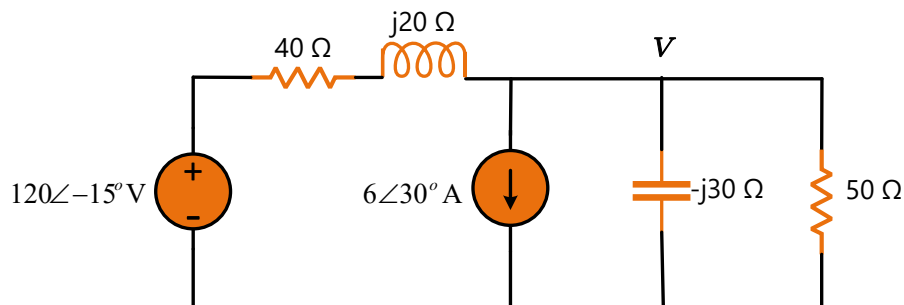


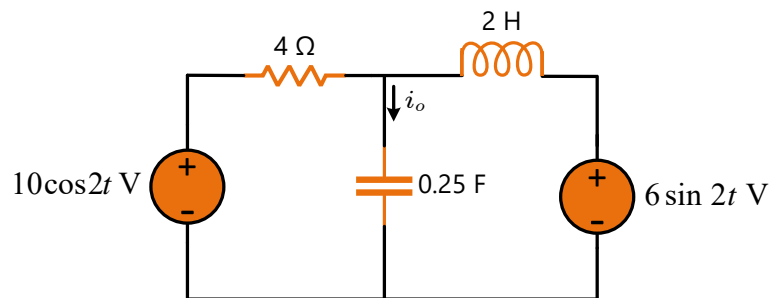
- Using nodal analysis, calculate the voltage V in the following circuit.




- Using mesh analysis, calculate i_o in the following circuit.



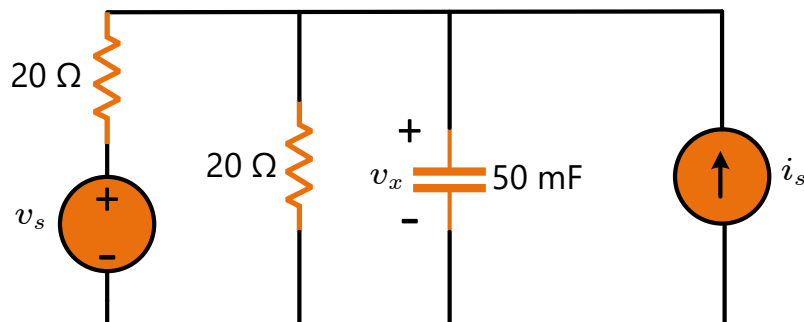
- Using the principle of superposition, calculate v_x in the following circuit, if $v_s = 50\sin 2t \text{ V}$ and $i_s = 12\cos(6t + 10^\circ) \text{ A}$.



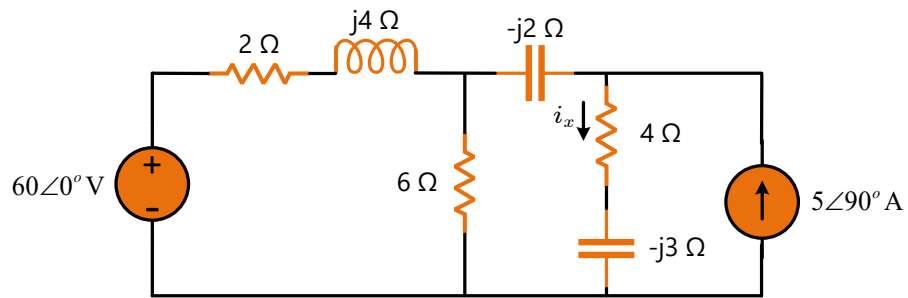
4. Using source transformation, calculate the current $\mathbf{I_x}$ in the following circuit.



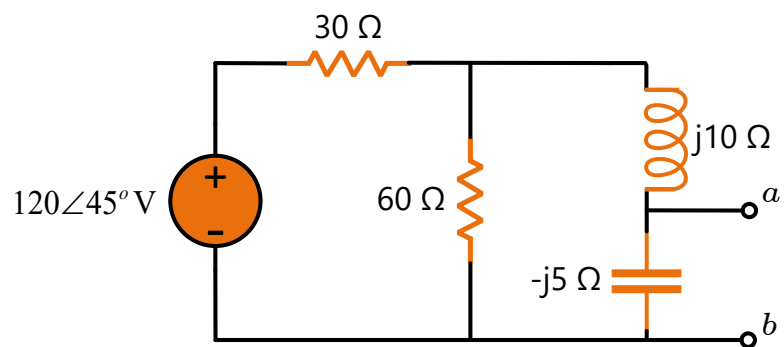5. Calculate the Thevenin and Norton equivalent circuits at terminals a and b of the following circuit.



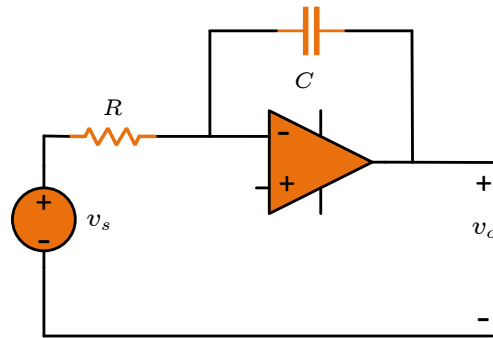6. For the integrator of the following figure, calculate V_o/V_s .



7. Evaluate the voltage gain $A_v = V_o/V_s$ in the following circuit. Find the gain when $\omega = 0$ and when $\omega \rightarrow \infty$.

