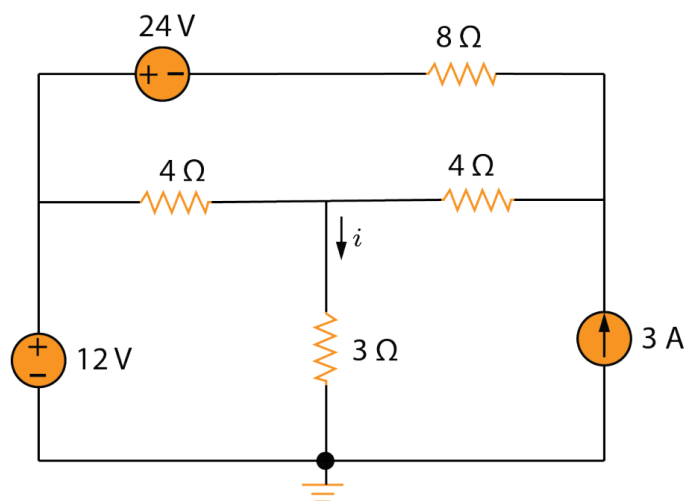



Topic 3: Circuit Theorems

- Find the current i in the following circuit by using superposition principle.




Answer: $i = i' + i'' + i''' = 2 \text{ A}$, where $i' = 2 \text{ A}$, $i'' = -1 \text{ A}$, and $i''' = 1 \text{ A}$ are the responses due to 12-V, 24-V, and 3-A sources.

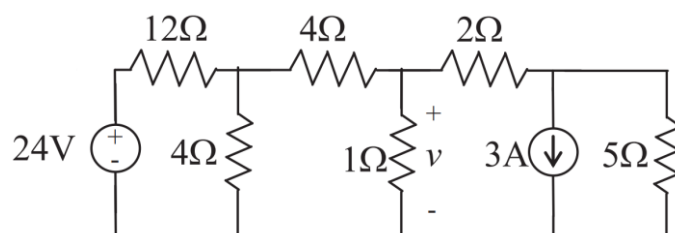- (Final Exam, S1, 2014) Use source transformations to determine the voltage v shown in the following circuit.




Answer: $v = -1 \text{ V}$

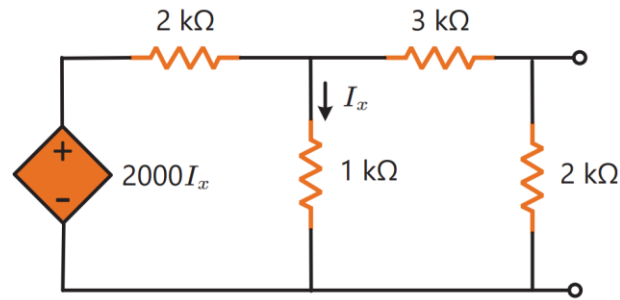3. Determine R_{Th} for the following circuit. What is the value of the Thevenin equivalent voltage? Why can we find this value without any calculations?




Answer: $V_{Th} = 0 \text{ V}$, $R_{Th} = \frac{10}{7} = 1.428 \text{ k}\Omega$

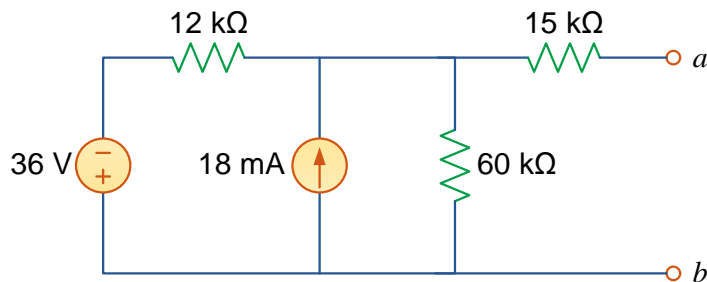4. (Final Exam - S2, 2015) Find the Norton equivalent of the following circuit.



Answer: $I_N = 6 \text{ mA}$, $R_N = R_{Th} = 25 \text{ k}\Omega$

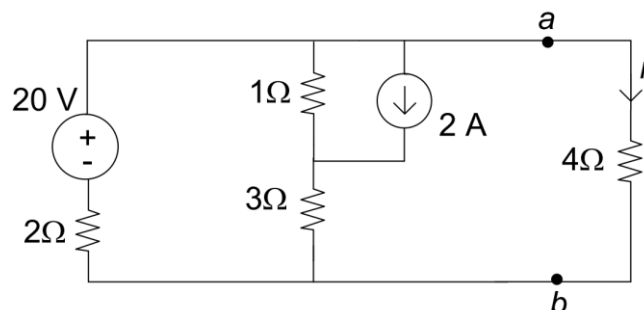
5. (Mid-session Exam – S2, 2016) For the circuit below, find the current i in the 4- Ω resistor using,
 (a) The superposition principle.
 (b) The Thevenin equivalent of the circuit to the left of terminal pair a - b .



Answer:

- (a) $i = i' + i'' = 2.375 \text{ A}$, where $i' = 2.5 \text{ A}$ and $i'' = -0.125 \text{ A}$ are the responses due to 20-V and 2-A sources.
 (b) $V_{Th} = 12.66 \text{ V}$, $R_{Th} = \frac{4}{3} = 1.33 \text{ k}\Omega$

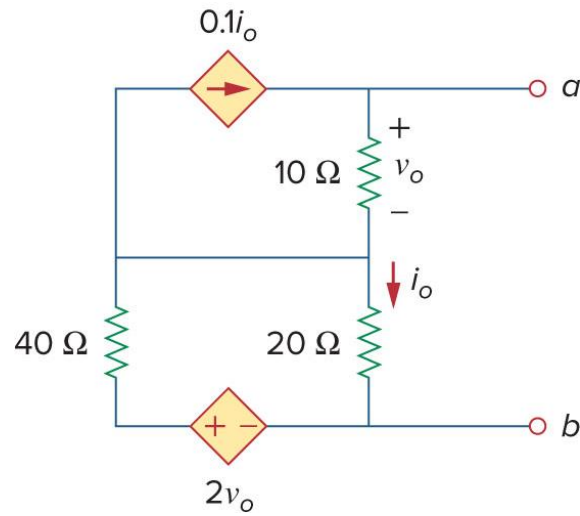
6. Find the Thevenin equivalent of the circuit given below.



Answer: $V_{Th} = 0 \text{ V}$, $R_{Th} = 31.73 \text{ k}\Omega$

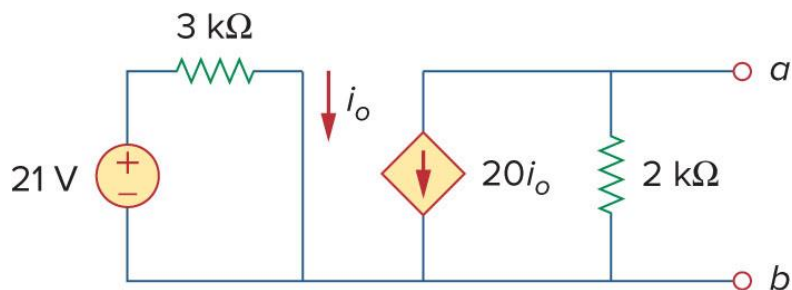7. For the transistor model given below, do the following,


- Obtain the open-circuit voltage v_{oc} across terminals a-b.
- Calculate the short-circuit current i_{sc} at terminals a-b.
- Find the equivalent resistance R_{eq} seen from the terminals a-b (use the results from previous parts)



Answer:

- $v_{oc} = -280 \text{ V}$
- $i_{sc} = -140 \text{ mA}$
- $R_{eq} = 2 \text{ k}\Omega$

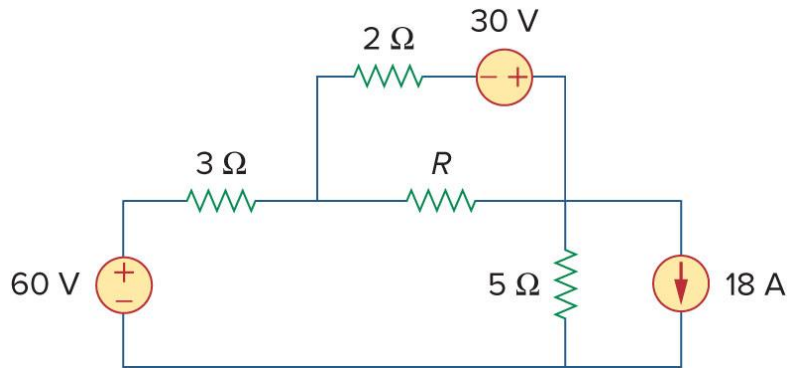8. In the following circuit, find the maximum power that can be delivered to the resistor R in the circuit below. What should be the value of R for maximum power transfer?




Answer: $R_{Th} = 1.6 \Omega$, $V_{Th} = 6 \text{ V}$, $P_{max} = 5.625 \text{ W}$, $R = 1.6 \Omega$

Hint: Find the Thevenin equivalent circuit from the terminals across the load R .

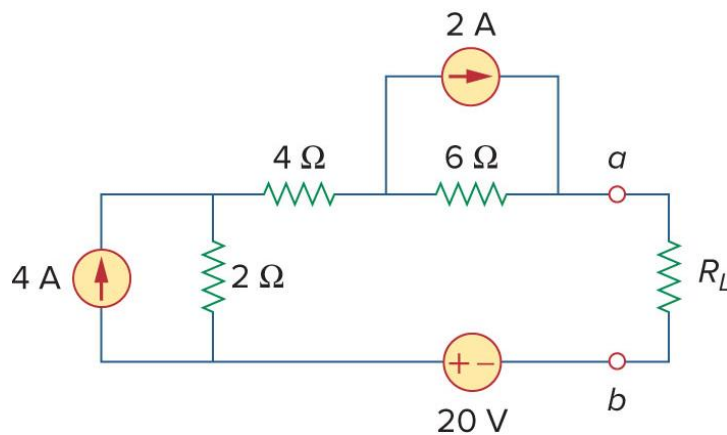9. For the circuit below,

- Obtain the Norton equivalent circuit at terminals a-b.
- Calculate the current in $R_L = 13 \Omega$.
- Find R_L for maximum power deliverable to R_L .
- Determine that maximum power.



Answer:

- $R_N = 12 \Omega$, $I_N = \frac{10}{3} = 3.33 \text{ A}$
- $I_L = \frac{8}{5} = 1.6 \text{ A}$
- $R_L = 12 \Omega$
- $P_{max} = \frac{100}{3} = 33.33 \text{ W}$