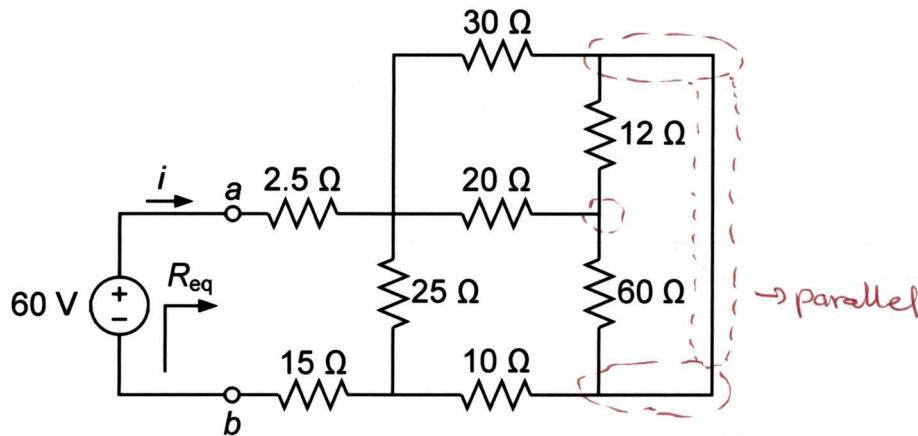


**QUESTION 1 [25 marks]**


(i) [12 marks] For the circuit shown in Figure 1,

- [10 marks] Calculate the equivalent resistance  $R_{eq}$  as seen from terminals a-b.
- [2 marks] Find the current  $i$  through the network using the result of part (a).




$$a) \frac{12\Omega \parallel 60\Omega}{12+60} = \frac{12 \times 60}{12+60} = \underline{\underline{10\Omega}} \Rightarrow$$

Figure 1

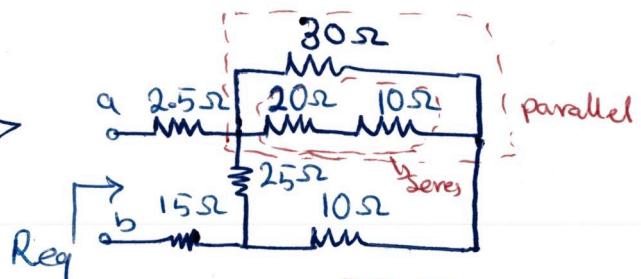


$$20+10=30 \rightarrow 30 \parallel 30 = \frac{30 \times 30}{30+30} = \underline{\underline{15\Omega}}$$
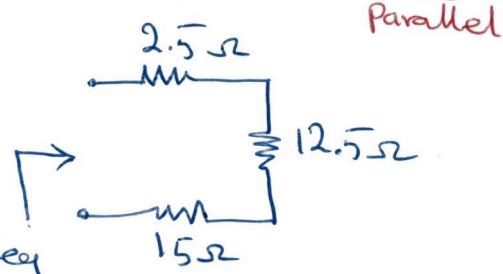
$$\Rightarrow 15+10=25 \rightarrow 25 \parallel 25 = \frac{25 \times 25}{25+25} = \underline{\underline{12.5\Omega}}$$



$$\Rightarrow R_{eq} = 2.5 + 12.5 + 15 = \underline{\underline{30\Omega}}$$

b) Equivalent circuit

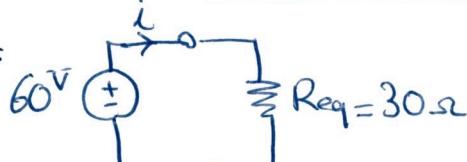

$$i = \frac{V}{R} = \frac{60}{R_{eq}} = \frac{60}{30} = \underline{\underline{2A}}$$

**QUESTION 1 [25 marks] Continued**

(ii) [13 marks] For the circuit shown in Figure 2,

- (10 marks) Calculate all the powers absorbed and/or supplied by the elements.
- (3 marks), Verify the law of conservation of energy.

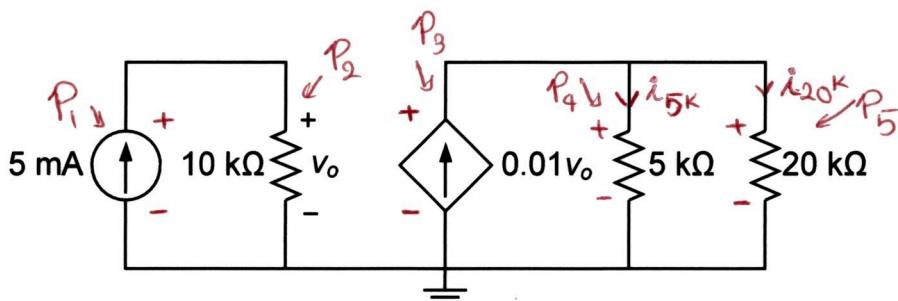


Figure 2

$$a) P = V \cdot i = \frac{V^2}{R} = R i^2 \quad (\text{passive sign convention})$$

$$V_o = 10^k \times 5^m = \boxed{50V} \quad \leftarrow \text{Ohm's Law}$$

$$i_{5k} = \frac{20^k}{5^k + 20^k} \times 0.01V_o = \frac{20 \times 0.5}{25} = \boxed{0.4A} \quad \leftarrow \text{Current division}$$

$$i_{20k} = 0.01V_o - i_{5k} = 0.5 - 0.4 = \boxed{0.1A} \quad \leftarrow \text{KCL}$$

$$V_{5k} = V_{20k} = V_{\text{dependent source}} = 5^k \times 0.4A = \boxed{2^k V = 2000V}$$

Now find powers of each element

$$* 5\text{mA source: } P_1 = V_o \cdot I = \boxed{\frac{V_o \cdot 5^m}{10^k} = \frac{50 \times 5^m}{10^k} = 250 \text{ mW} = 0.25 \text{ W}} \quad \text{Supplied (passive sign convention for active elements)}$$

$$* 10\text{-k}\Omega \text{ resistor: } P_2 = \frac{V_o^2}{10^k} = \boxed{10^k \times (5^m)^2 = 250 \text{ mW} = 0.25 \text{ W}} \quad \text{absorbed}$$

$$* 0.01V_o \text{ source: } P_3 = V_{5k} \times 0.01V_o = \boxed{2000 \times 0.01 \times 50 = 1000 \text{ W} = 1 \text{ kW}} \quad \text{Supplied}$$

$$* 5\text{-k}\Omega \text{ resistor: } P_4 = \boxed{5^k \times (i_{5k})^2 = 5^k \times (0.4)^2 = 800 \text{ W}} \quad \text{absorbed}$$

$$* 20\text{-k}\Omega \text{ resistor: } P_5 = \boxed{20^k \times (i_{20k})^2 = 20^k \times (0.1)^2 = 200 \text{ W}} \quad \text{absorbed}$$

b) Conservation of energy  $\rightarrow \sum P_{\text{supplied}} = \sum P_{\text{absorbed}}$

$$\Rightarrow 0.25^W + 1000^W = 0.25^W + 800^W + 200^W \Rightarrow 1000.25^W = 1000.25^W$$

Confirmed


**QUESTION 2 [30 marks]**

(i) [14 marks] For the circuit shown in Figure 3,

a. (10 marks) Apply nodal analysis and show that the nodal equations are given as below,

$$\begin{cases} 9v_1 - 5v_2 = 120 \\ v_1 - 5v_2 = -40 \end{cases}$$

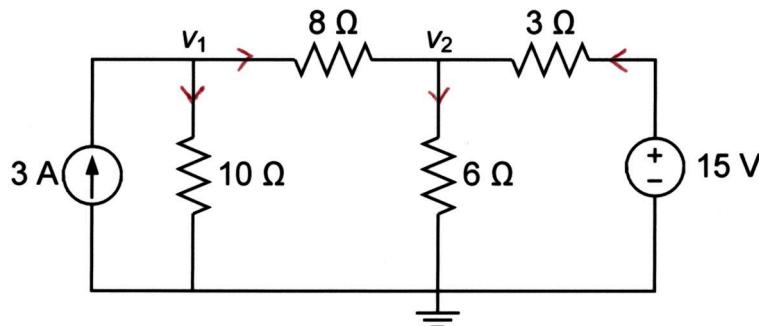b. (4 marks) Given the values of node voltages as  $v_1 = 20$  V and  $v_2 = 12$  V, calculate the total power supplied by the sources.



a)

Figure 3

$$\text{KCL at } v_1: 3 = \frac{v_1}{10} + \frac{v_1 - v_2}{8} \xrightarrow{\times 40} 120 = 4v_1 + 5v_1 - 5v_2$$

$$\Rightarrow \boxed{9v_1 - 5v_2 = 120}$$

$$\text{KCL at } v_2: \frac{v_1 - v_2}{8} + \frac{15 - v_2}{3} = \frac{v_2}{6} \xrightarrow{\times 24} 3v_1 - 3v_2 + 120 - 8v_2 = 4v_2$$

$$\Rightarrow 3v_1 - 15v_2 = -120 \xrightarrow{\times \frac{1}{3}} \boxed{v_1 - 5v_2 = -40}$$

b)  $P_{3A} = v_1 \times 3 = 20 \times 3 = 60 \text{ W supplied}$

$$P_{15V} = 15 \times \left( \frac{15 - v_2}{3} \right) = 5 \times (15 - 12) = 15 \text{ W supplied}$$

$$\Rightarrow P_{\text{Total}} = 60 + 15 = \boxed{75 \text{ W}} \text{ Supplied}$$


**QUESTION 2 [30 marks] Continued**

(ii) [16 marks] For the circuit shown in Figure 4,

a. (12 marks) Apply mesh analysis and show that the mesh equations are given as below,

$$\begin{cases} i_1 + 3i_2 - 2i_3 = 8 \\ i_1 + i_2 - 4i_3 = -1 \\ i_1 - i_2 = -4 \end{cases}$$

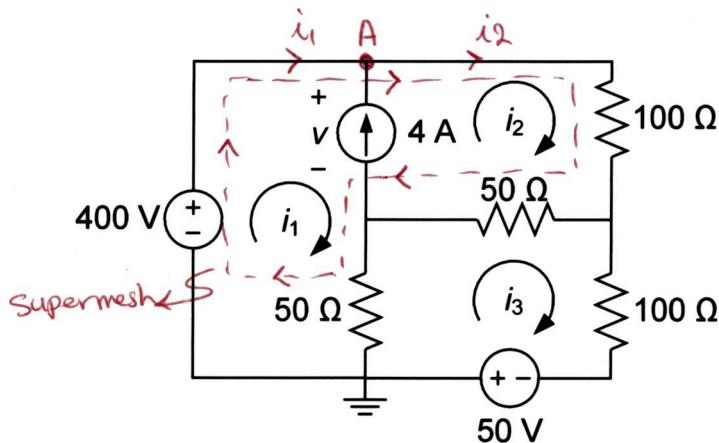b. (4 marks) Given the values of mesh currents as  $i_1 = -0.5$  A,  $i_2 = 3.5$  A, and  $i_3 = 1$  A, find the voltage  $v$  across 4-A current source.



a) \*KVL in supermesh:

$$-400 + 100i_2 + 50(i_2 - i_3) + 50(i_1 - i_3) = 0$$

$$\cancel{\times 50} \quad -8 + 2i_2 + i_2 - i_3 + i_1 - i_3 = 0$$

$$\Rightarrow \boxed{i_1 + 3i_2 - 2i_3 = 8}$$

Figure 4

(Polarities are chosen based on Passive sign Convention for each KVL)

(direction of currents in shared branches are chosen based on the mesh for which KVL is written)

\* KVL in mesh 3:  $-50 + 50(i_3 - i_1) + 50(i_3 - i_2) + 100i_3 = 0$

$$\cancel{\times 50} \quad -1 - i_1 + i_3 - i_2 + i_3 + 2i_3 = 0 \Rightarrow \boxed{i_1 + i_2 - 4i_3 = -1}$$

\* KCL @ node A:  $i_1 + 4 = i_2 \Rightarrow \boxed{i_1 - i_2 = -4}$


b) \* KVL in mesh 1:  $V_1 + 50(i_1 - i_3) - 400 = 0$

$$\frac{i_1 = -0.5}{i_3 = 1} \quad V = 50(1 + 0.5) + 400 = \boxed{475 \text{ V}}$$

**QUESTION 3 [25 marks]**

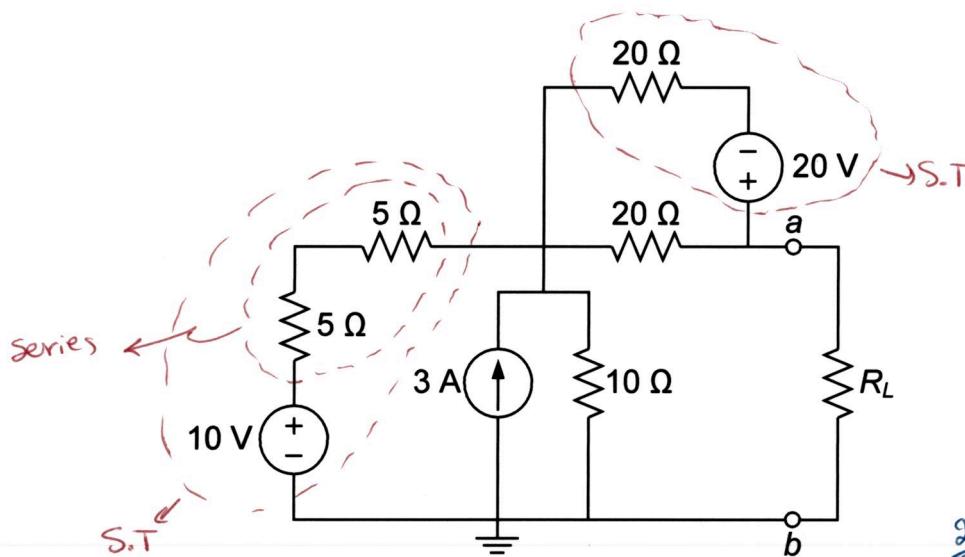(i) [15 marks] In the circuit of Figure 5,

- [12 marks] Use only **source transformation** to reduce the circuit into a single resistor in series with a single voltage source as seen from terminals a-b, and then determine Thevenin voltage  $V_{Th}$  and Thevenin resistance  $R_{Th}$  at the terminals a-b.
- [3 marks] Find the value of load resistance  $R_L$  for maximum power transfer, and then calculate the maximum power that can be delivered to  $R_L$ .



a) 2 Source Transformations (S.T.s)



$$5 + 5 = 10 \Omega$$

$$i_S = \frac{V_S}{R}$$

$$10/110 = \frac{10 \times 10}{10+10} = 5 \Omega$$

$$20/1120 = \frac{20 \times 20}{20+20} = 10 \Omega$$

$$1A + 3A = 4A$$

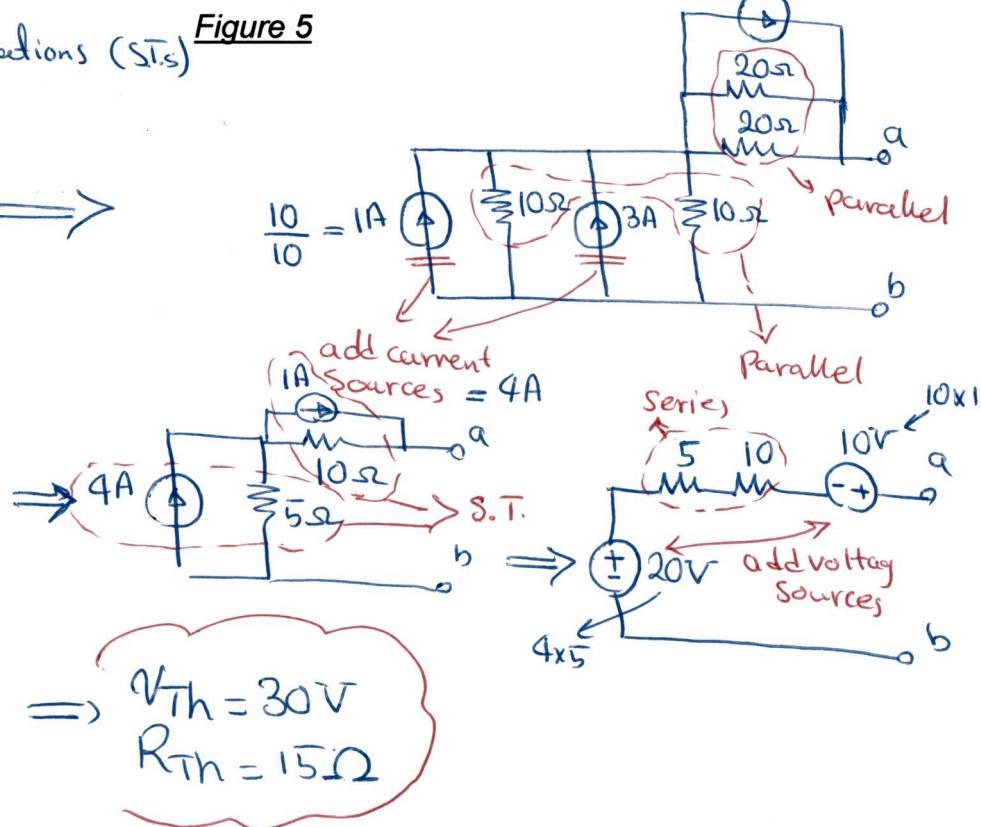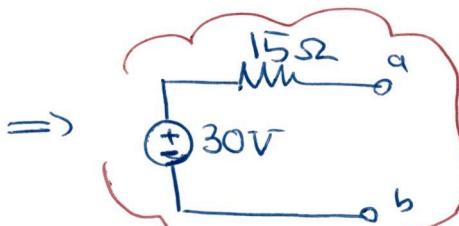

b)  $R_L = R_{Th} = 15 \Omega$  for max power transfer

$$P_{max} = \frac{V_{Th}^2}{4R_{Th}} = \frac{30^2}{4 \times 15} = 15 W$$

**QUESTION 3 [25 marks] Continued**

- (ii) [10 marks] For the circuit shown in Figure 6, obtain the Norton equivalent circuit as seen from terminal a-b and draw the Norton equivalent circuit.


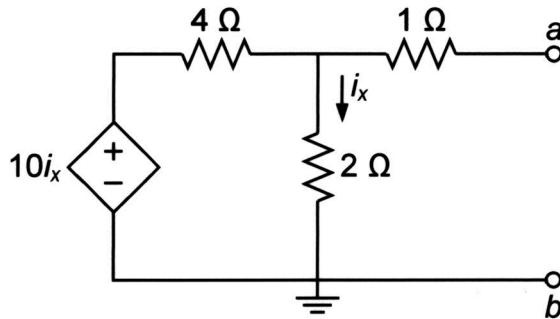


Figure 6

$I_N = 0 \text{ A}$  → No independent source

For  $R_N = R_{eq}$ , attach an external source

Method 1: Voltage Source

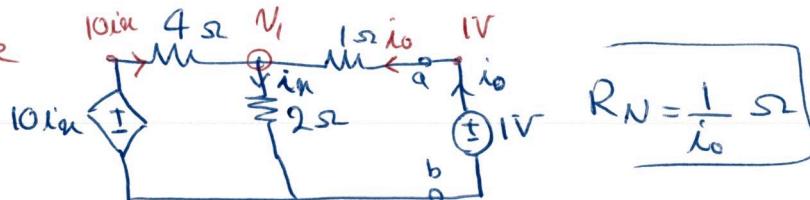

Nodal analysis:

$$\begin{aligned} & \text{find } V_1 \\ & \text{then find } i_0 \text{ to find } R_N \end{aligned}$$

$$\left\{ \begin{array}{l} \frac{10i_x - V_1}{4} + i_0 = \frac{V_1}{2} \\ i_0 = \frac{1 - V_1}{1}, \quad i_x = \frac{V_1}{2} \end{array} \right. \Rightarrow \frac{5V_1 - V_1}{4} + 1 - V_1 = \frac{V_1}{2}$$

$$\xrightarrow{\times 4} 4V_1 + 4 - 4V_1 = 2V_1 \Rightarrow V_1 = 2V \quad \boxed{\text{I}} \Rightarrow i_0 = \frac{1 - 2}{1} = -1A$$

$$\Rightarrow R_N = -1 \Omega = \frac{1}{-1}$$

Method 2: Current Source

Nodal analysis:


$$\begin{aligned} & \text{find } V_1 \\ & \text{then find } V_0 \text{ to find } R_N \end{aligned}$$

$$\left\{ \begin{array}{l} \frac{10i_x - V_1}{4} + 1 = \frac{V_1}{2} \\ i_x = \frac{V_1}{2}, \quad \frac{V_0 - V_1}{1} = 1 \end{array} \right. \Rightarrow \frac{5V_1 - V_1}{4} + 1 = \frac{V_1}{2} \xrightarrow{\times 4} 4V_1 + 4 = 2V_1$$


$$= V_1 = -2V \quad \boxed{\text{I}} \Rightarrow V_0 = 1 + V_1 = -1V$$

$$\Rightarrow R_N = -1 \Omega = \frac{-1}{1}$$

\* Norton equivalent Circuit

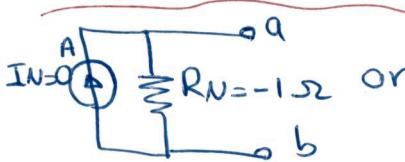


$$R_N = \frac{V_0}{I} = 1 \Omega$$

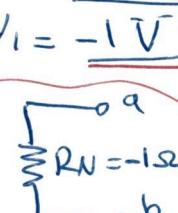

**QUESTION 4 [20 marks]**

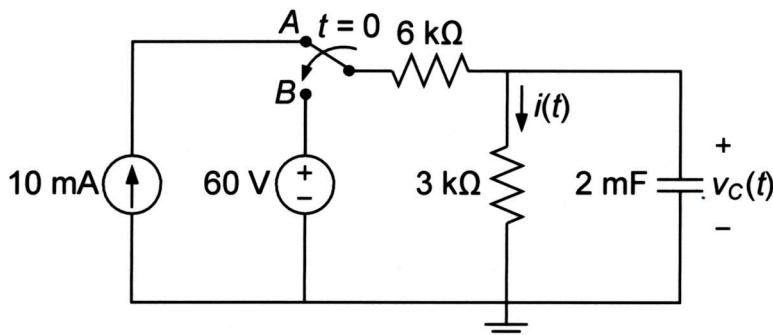- (i) [8 marks] In circuit shown in Figure 7, the switch has been in position A for a long time. At  $t = 0$ , the switch moves to position B.


- [4 marks] Find the voltage  $v_C(t)$  across the capacitor immediately after the switch changes to position B,  $v_C(0^+)$ , and its final voltage when  $t \rightarrow \infty$ ,  $v_C(\infty)$ .
- [3 marks] Derive an expression for the capacitor voltage  $v_C(t)$  for  $t > 0$ .
- [1 marks] Find the current  $i(t)$  through  $3\text{-k}\Omega$  resistor for  $t > 0$ .



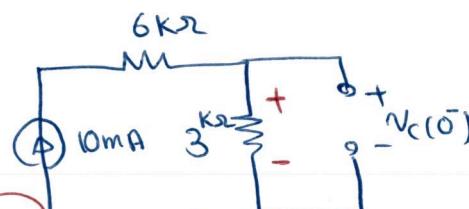a) \* for  $t < 0$


Switch is at A  
and  $v_C(0^+) = v_C(0^-)$  *Figure 7*  
No sudden change in  $v_C(t)$

$$\rightarrow v_C(0^-) = v_{3k\Omega} = 3 \times 10^m = 30V = v_C(0^+)$$



\* for  $t > 0$

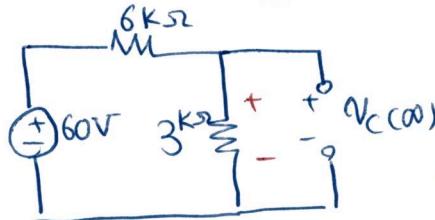
switch is at B  $\rightarrow$   
 $t \rightarrow \infty$



$$v_C(\infty) = \frac{3}{6+3} \times 60 = 20V$$

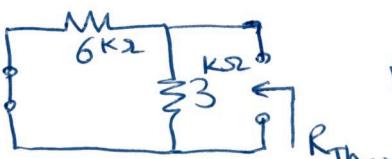b)  $v_C(t) = v_C(\infty) + [v_C(0^+) - v_C(\infty)] e^{-t/\tau}$   $t > 0$

$$\tau = R_{Th\infty} C \xrightarrow{t > 0}$$



$$R_{Th\infty} = 3 \parallel 6 = \frac{3 \times 6}{3+6} = 2\text{k}\Omega$$

$$\Rightarrow \tau = 2 \times 2 = 4s$$

$$\Rightarrow v_C(t) = 20 + [30 - 20] e^{-t/4} V = 20 + 10e^{-t/4} V \quad t > 0$$


c)  $i(t) = \frac{v_{3k}}{3k\Omega} = \frac{v_C(t)}{3k\Omega} \Rightarrow i(t) = \frac{20}{3} + \frac{10}{3} e^{-t/4} \text{mA} \quad t > 0$

$3k\Omega$  is parallel with capacitor


**QUESTION 4 [20 marks] Continued**

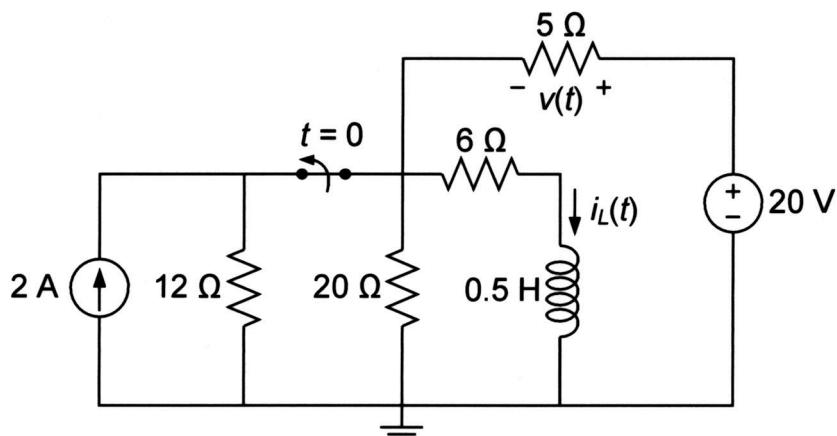(ii) [12 marks] In the circuit of Figure 8, the switch has been closed for a long time before being opened at  $t = 0$ .

- [10 marks] Derive an expression for the inductor current  $i_L(t)$  for all time (i.e., for both  $t < 0$  and  $t > 0$ ) and sketch  $i_L(t)$  as a function of time showing all critical points in the sketch.
- [2 marks] Find the total energy stored or released by the inductor for  $t \geq 0$ , i.e., from  $t = 0$  to  $t \rightarrow \infty$ .




a) \* For  $t < 0$

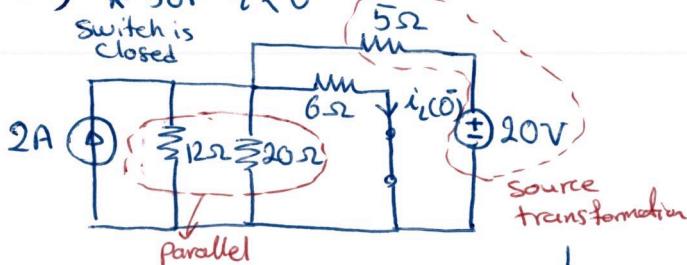

$$12/120 = \frac{12 \times 20}{12 + 20} = 7.5 \Omega$$

$$\Rightarrow \text{Current division} \rightarrow i_L(0^-) = \frac{3}{3+6} \times 6A = 2A$$

\* For  $t > 0$   
switch is open

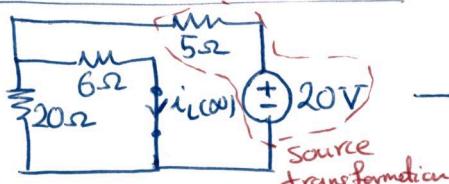

$$\Rightarrow \text{Current division} \rightarrow i_L(0^+) = \frac{4}{4+6} \times 4 = 1.6A$$

$$* C = \frac{L}{R_{Th\alpha}} \xrightarrow{t \gg 0}$$

$$\Rightarrow C = \frac{0.5H}{10\Omega} = \frac{1}{20} S = 50ms$$


$$\Rightarrow i_L(t) = 1.6 + (2 - 1.6)e^{-\frac{t}{50}} A = 1.6 + 0.4e^{-\frac{20t}{50}} A$$

→ next page

Figure 8


$$\begin{cases} i_L(t) = i_L(\infty) + [i_L(0^+) - i_L(\infty)] e^{-\frac{t}{C}} \\ C = \frac{L}{R_{Th\alpha}} \text{ and } i_L(0^+) = i_L(0^-) \end{cases}$$

no sudden change  
in  $i_L(t)$

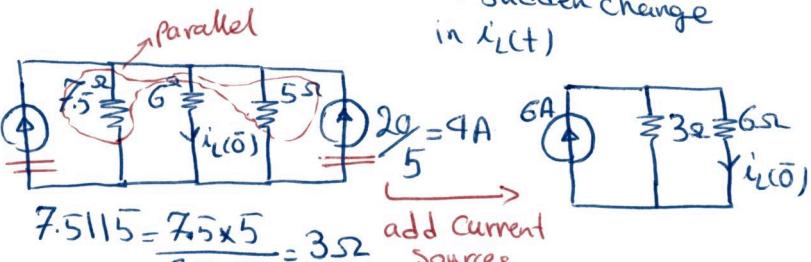

$$7.5/15 = \frac{7.5 \times 5}{7.5 + 5} = 3\Omega$$

add Current Sources

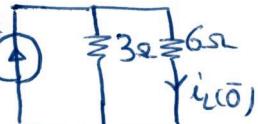

$$20/15 = \frac{20 \times 5}{20 + 5} = 4\Omega$$

parallel




$$R_{Th\alpha} = 6 + 5/20 = 6 + \frac{5 \times 20}{5 + 20} = 10\Omega$$

$$\Rightarrow i_L(t) = \begin{cases} 2A & t < 0 \\ 1.6 + 0.4e^{-\frac{20t}{50}} A & t \geq 0 \end{cases}$$

# Solutions of the Mid-semester exam, ELEC1111 Summer 2017-2018

Part (ii)-a Continued

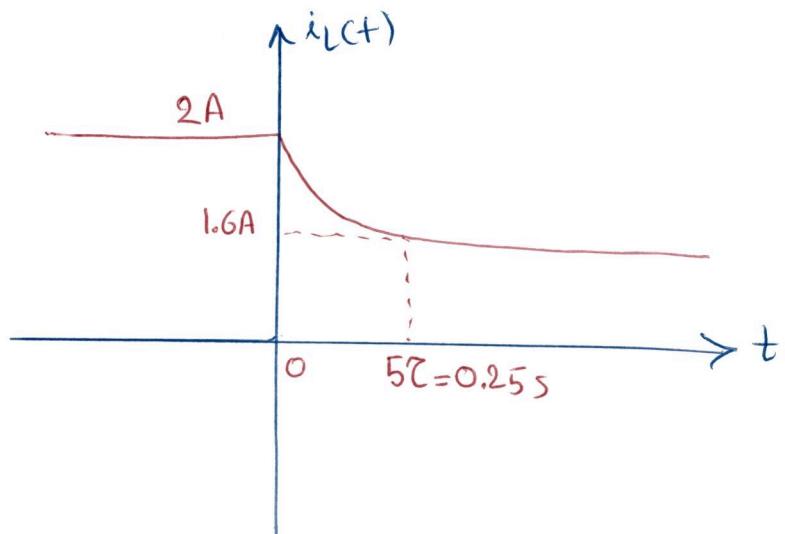

b)  $W_{\infty} = \frac{1}{2} L i_L^2(\infty)$  and  $W_0 = \frac{1}{2} L i_L^2(0)$  also  $W = \int_{-\infty}^t P(c) dc = \int_0^{\infty} L i_L^2 dt$

$$\Rightarrow W_T = \frac{1}{2} L (i_L^2(\infty) - i_L^2(0))$$

$$= \frac{1}{2} \times 0.5 (1.6^2 - 2^2) = -0.36 J$$

Assuming  $i_L(-\infty) = i_L(0)$

Thus, the inductor releases  $0.36 J$  from  $t=0$  to  $t \rightarrow \infty$