

Topic 8: AC Circuits II

1. Write nodal equations for the following circuits:

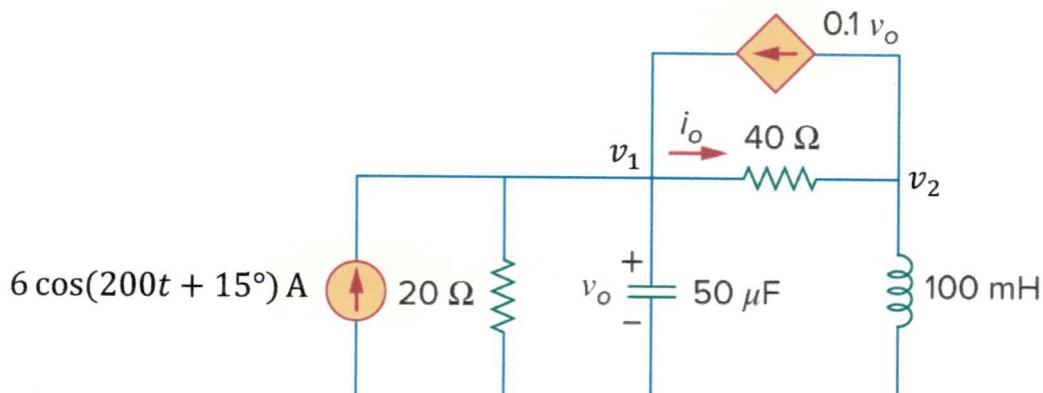


Fig. 1

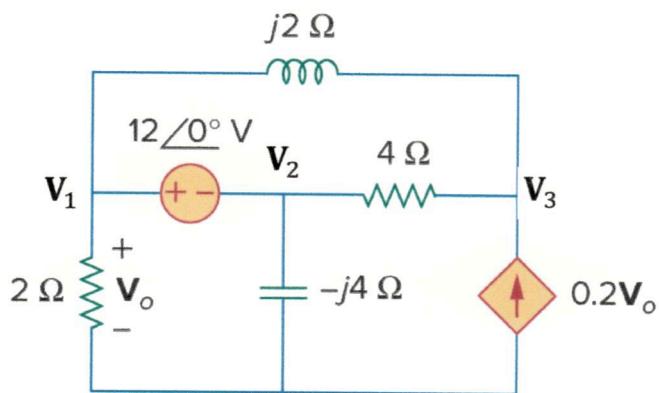


Fig. 2

Answer:

a) Fig. 1: $\begin{cases} (-2.5 + j1)V_1 - 2.5V_2 = 579.5 + j155.3 \\ 3V_1 + (1 - j2)V_2 = 0 \end{cases}$

b) Fig. 2: $\begin{cases} (2 - j2)V_1 + (1 + j)V_2 + (-1 + j2)V_3 = 0 \text{ V} \\ (0.8 - j2)V_1 + V_2 + (-1 + j2)V_3 = 0 \text{ V} \\ V_1 - V_2 = 12 \end{cases}$

Solution: Transform the circuit into phasor domain

$$\omega = 200 \frac{\text{rad}}{\text{s}}$$

$$6 \text{A} (200t + 15^\circ) = 6 \angle 15^\circ \text{A}$$

$$100 \text{mH} \rightarrow j\omega L = j20 \Omega \rightarrow 6 \angle 15^\circ \text{A}$$

$$50 \mu\text{F} \rightarrow -\frac{j}{\omega C} = -j100 \Omega$$

Note that $\underline{V_0} = \underline{V_1}$

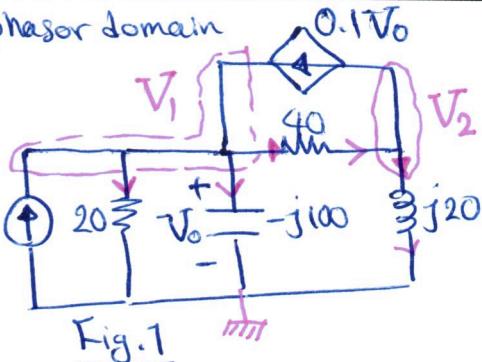


Fig.1

*KCL @ node 1: $6 \angle 15^\circ + 0.1 \bar{V}_0 = \frac{\bar{V}_1}{20} + \frac{\bar{V}_1 - \bar{V}_2}{-j100} + \frac{\bar{V}_1 - \bar{V}_2}{40} \xrightarrow{\times 100}$

$$600 \angle 15^\circ + \bar{V}_1 = 5\bar{V}_1 + j\bar{V}_1 + 2.5\bar{V}_1 - 2.5\bar{V}_2$$

Transform to
Polar form

$$(-2.5 + j1)\bar{V}_1 - 2.5\bar{V}_2 = \frac{600 \angle 15^\circ + j600 \sin 15^\circ}{579.5} \quad 155.3$$

*KCL @ node 2: $\frac{\bar{V}_1 - \bar{V}_2}{40} = 0.1\bar{V}_1 + \frac{\bar{V}_2}{j20} \xrightarrow{\times 40} \bar{V}_1 - \bar{V}_2 = 4\bar{V}_1 - j2\bar{V}_2$
 $\Rightarrow 3\bar{V}_1 + (1-j2)\bar{V}_2 = 0$

We have a supernode between \bar{V}_1 and \bar{V}_2

Note that $\underline{V_0} = \underline{V_1}$

*KCL @ supernode:

$$\frac{\bar{V}_3 - \bar{V}_2}{4} = \frac{\bar{V}_2}{-j4} + \frac{\bar{V}_1}{2} + \frac{\bar{V}_1 - \bar{V}_3}{j2} \xrightarrow{\times 4} \bar{V}_3 - \bar{V}_2 = j\bar{V}_2 + 2\bar{V}_1 - j2\bar{V}_1 + j2\bar{V}_3$$

$$\Rightarrow (2-j2)\bar{V}_1 + (1+j)\bar{V}_2 + (-1+j2)\bar{V}_3 = 0$$

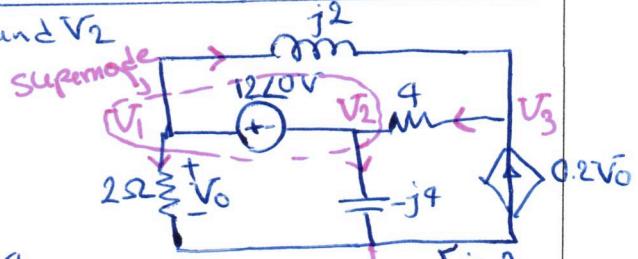


Fig.2

* KCL @ node 3:

$$0.2\bar{V}_1 + \frac{\bar{V}_1 - \bar{V}_3}{j2} = \frac{\bar{V}_3 - \bar{V}_2}{4} \xrightarrow{\times 4} 0.8\bar{V}_1 - j2\bar{V}_1 + j2\bar{V}_3 = \bar{V}_3 - \bar{V}_2$$

$$(0.8 - j2)\bar{V}_1 + \bar{V}_2 + (-1 + j2)\bar{V}_3 = 0$$

* Extra equation due to supernode (Voltage Source)

$$\bar{V}_1 - \bar{V}_2 = 12$$

2. Write mesh equations for the following circuits:

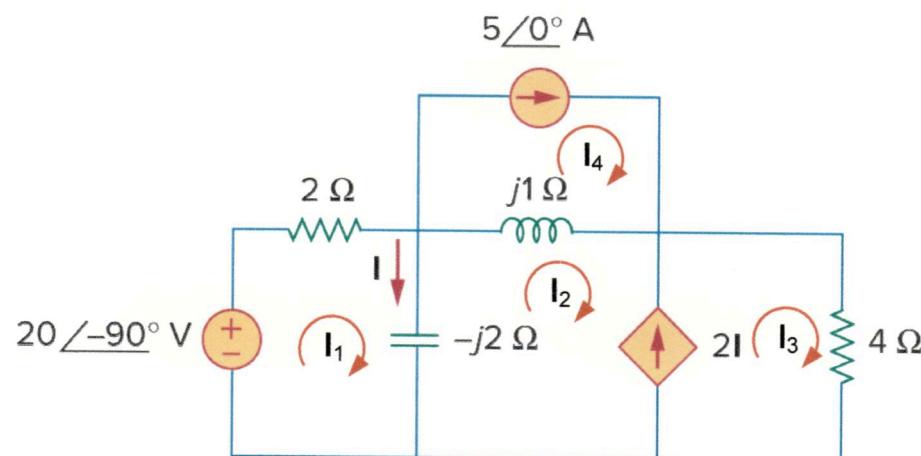


Fig. 1

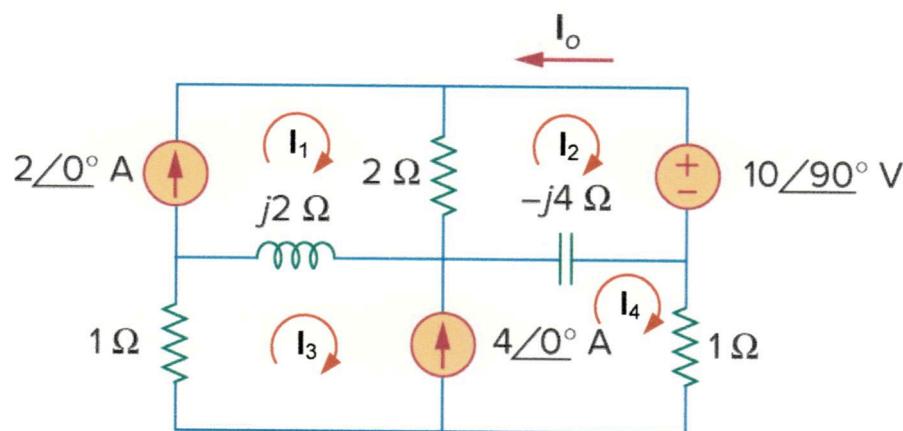


Fig. 2

Answer:

a) Fig. 1:
$$\begin{cases} (1-j)\mathbf{I}_1 + j\mathbf{I}_2 = -j10 \\ j2\mathbf{I}_1 - j\mathbf{I}_2 + 4\mathbf{I}_3 = j5 \\ 2\mathbf{I}_1 - \mathbf{I}_2 - \mathbf{I}_3 = 0 \\ \mathbf{I}_4 = 5 \end{cases}$$

b) Fig. 2:
$$\begin{cases} \mathbf{I}_1 = 2 \\ (1-j2)\mathbf{I}_2 + j2\mathbf{I}_4 = 2 - j5 \\ j4\mathbf{I}_2 + (1+j2)\mathbf{I}_3 + (1-j4)\mathbf{I}_4 = j4 \\ \mathbf{I}_3 - \mathbf{I}_4 = -4 \end{cases}$$

Solution: We have a supermesh between I_2 and I_3 :

$$I_4 = 5A$$

* KVL in mesh 1:

$$j20 + 2I_1 + (-j2)(I_1 - I_2) = 0$$

$$\xrightarrow{O.1} j10 + I_1 - jI_1 + jI_2 = 0$$

$$\Rightarrow (1-j1)I_1 + jI_2 = j10$$

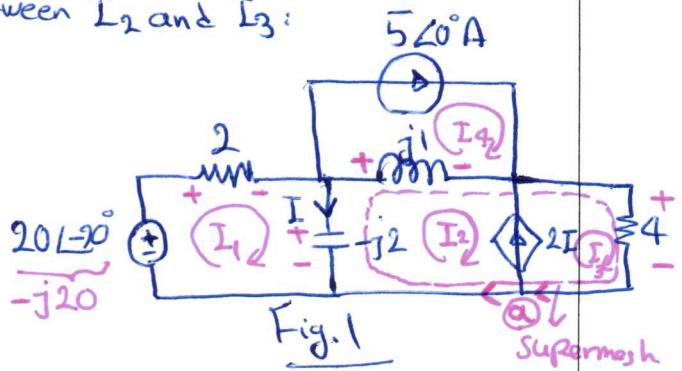


Fig. 1

Supermesh

* KVL in supermesh: $-(-j2)(I_1 - I_2) + j1(I_2 - I_4) + 4I_3 = 0$

$$\Rightarrow j2I_1 - j2I_2 + jI_2 - j5 + 4I_3 = 0$$

$$\Rightarrow j2I_1 - jI_2 + 4I_3 = j5$$

* KCL @ node @: $I_3 = 2I_1 + I_2 \xrightarrow{\substack{\text{Note that} \\ I = I_1 - I_2}} I_3 = 2I_1 - 2I_2 + I_2$

$$\Rightarrow 2I_1 - I_2 - I_3 = 0$$

Clearly in Fig. 2 $\rightarrow I_1 = 2A$

and we have supermesh again

* KVL in mesh 2:

$$j10 + (-j4)(I_2 - I_4) + 2(I_2 - I_1) = 0$$

$$-j4I_2 + j4I_4 + 2I_2 = 4 - j10 \xrightarrow{O.2}$$

$$\Rightarrow (1-j2)I_2 + j2I_4 = 2 - j5$$

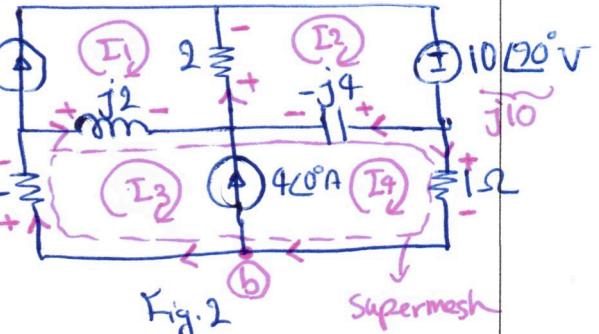


Fig. 2

Supermesh

* KVL in supermesh: $1I_3 + j2(I_3 - I_1) - (-j4)(I_2 - I_4) + 1I_4 = 0$

$$\Rightarrow I_3 + j2I_3 - j4 + j4I_2 - j4I_4 + I_4 = 0$$

$$\Rightarrow j4I_2 + (1+j2)I_3 + (1-j4)I_4 = j4$$

* KCL @ node b)

$$I_4 = 4 + I_3 \Rightarrow I_3 - I_4 = -4$$

3. Use superposition principle to find i_x and v_x in the following circuits

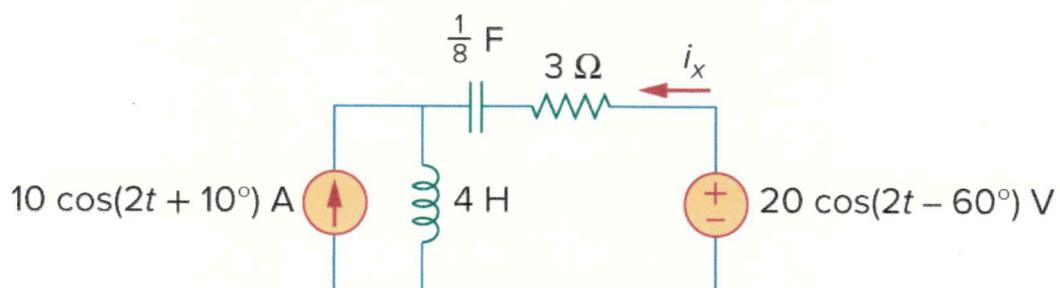


Fig. 1

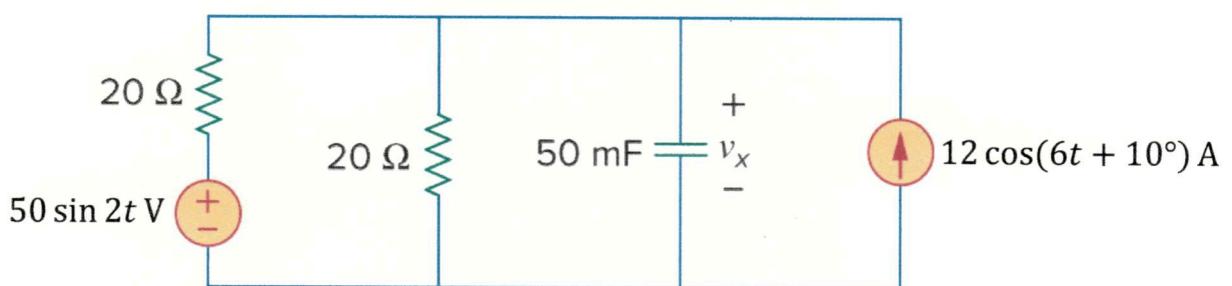


Fig. 2

Answer:

- Fig. 1: $i_x(t) = 19.804 \cos(2t - 129.17^\circ)$ A
- Fig. 2: $v_x(t) = [17.678 \cos(2t - 135^\circ) + 37.95 \cos(6t - 61.57^\circ)]$ V

Solution: For Fig. 1, transform it into phasor domain and Note that Frequencies are the same.

$$\omega = \frac{2\pi}{T} = \frac{2\pi}{1} = 2 \text{ rad/s}$$


$$10 \cos(2t + 10^\circ) \rightarrow 10 \angle 10^\circ \text{ A}$$

$$20 \cos(2t - 60^\circ) \rightarrow 20 \angle -60^\circ \text{ V}$$

$$4 \text{ H} \rightarrow j\omega L = j8 \text{ S} \Rightarrow I_x = I_{x1} + I_{x2}$$

$$\frac{1}{8} \text{ F} \rightarrow \frac{-j}{\omega C} = -j4 \text{ S} \quad \begin{cases} I_{x1}: \text{due to } 20 \angle -60^\circ \text{ V} \\ I_{x2}: \text{due to } 10 \angle 10^\circ \text{ A} \end{cases}$$

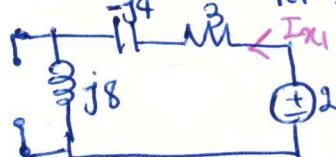
Draw the circuit for I_{x1} by setting $10 \angle 10^\circ \text{ A}$ to zero



All impedances are in series \rightarrow

$$\Rightarrow I_{x1} = \frac{20 \angle -60^\circ}{3 + j4} \text{ A}$$


$$I_{x1} = -1.57 - j3.67 \text{ A}$$

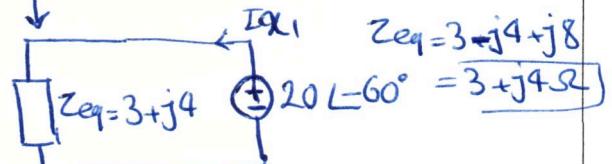

Keep it in rectangular form as it is going to be added to I_{x2} later.

→ Next Page

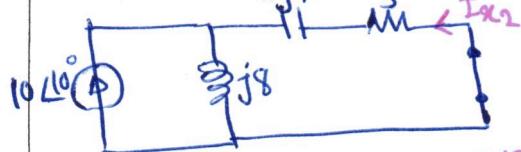Now draw the circuit for I_{X_2} by turning off $20 \angle -60^\circ V$



Note that we can use current division but I_{X_2} will be in opposite direction

$$\Rightarrow I_{X_2} = \frac{-j8 \angle 80^\circ}{3-j4+j8} \times 10 \angle 10^\circ = \frac{8 \angle -90^\circ \times 10 \angle 10^\circ}{3+j4} = \frac{80 \angle -80^\circ}{3+j4}$$

$$\Rightarrow I_{X_2} = -10.93 - j11.67 \text{ A}$$

$$\text{Thus } I_X = I_{X_1} + I_{X_2} = -12.51 - j15.35 = 19.8 \angle -129.17^\circ \text{ A}$$

Note that we are allowed to add I_{X_1} and I_{X_2} in phasor domain because they are due to sources with same frequency

$$\Rightarrow i_X(t) = 19.8 \cos(2t - 129.17^\circ) \text{ A}$$

For Fig. 2, Note that frequencies are NOT the same.

Thus $V_X = V_{X_1} + V_{X_2}$ but $V_X \neq V_{X_1} + V_{X_2}$ in phasor domain


V_{X_1} due to $50 \sin 2t \text{ V}$

V_{X_2} due to $12 \cos(6t + 10^\circ) \text{ A}$

* Draw the circuit in phasor domain for V_{X_1} $\rightarrow 50 \sin 2t = 50 \cos(2t - 90^\circ) \rightarrow 50 \angle -90^\circ$ by setting the current source to zero

$$\omega = 2 \text{ rad/s}$$
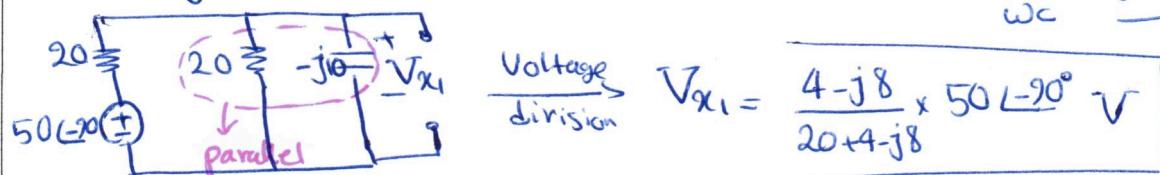
$$50 \text{ mF} \rightarrow -\frac{j}{\omega C} = -\frac{j}{2 \times 50} = -j10 \Omega$$




$$\text{Voltage division} \quad V_{X_1} = \frac{4-j8}{20+4-j8} \times 50 \angle -90^\circ \text{ V}$$

$$20(1-j10) = \frac{20 \times (-j10)}{20-j10} = 4-j8 \Omega$$


$$\Rightarrow V_{X_1} = 17.67 \angle -135^\circ \text{ V} \rightarrow V_{X_1} = 17.67 \cos(2t - 135^\circ) \text{ V}$$

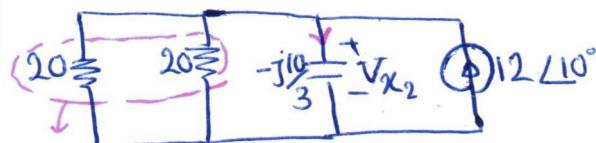* Draw the circuit in phasor domain for V_{X_2} $\rightarrow \omega = 6 \text{ rad/s}$



$$\text{Parallel } 20//20 = 10 \Omega$$
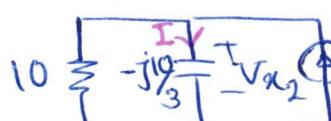
$$12 \cos(6t + 10^\circ) \rightarrow 12 \angle 10^\circ \\ 50 \text{ mF} \rightarrow -\frac{j}{\omega C} = -\frac{j}{6 \times 50} = -j10/3 \Omega$$




$$\text{Current division} \quad I = \frac{10}{10-j10} \times 12 \angle 10^\circ = 11.38 \angle 28.4^\circ \text{ A}$$

$$\rightarrow V_{X_2}(t) = 37.95 \cos(6t - 61.5^\circ) \text{ V}$$

$$V_{X_2} = -j10/3 \times I = 37.95 \angle -61.5^\circ$$


$$\Rightarrow V_X = V_{X_1} + V_{X_2} = [17.67 \cos(2t - 135^\circ) + 37.95 \cos(6t - 61.5^\circ)] \text{ V}$$

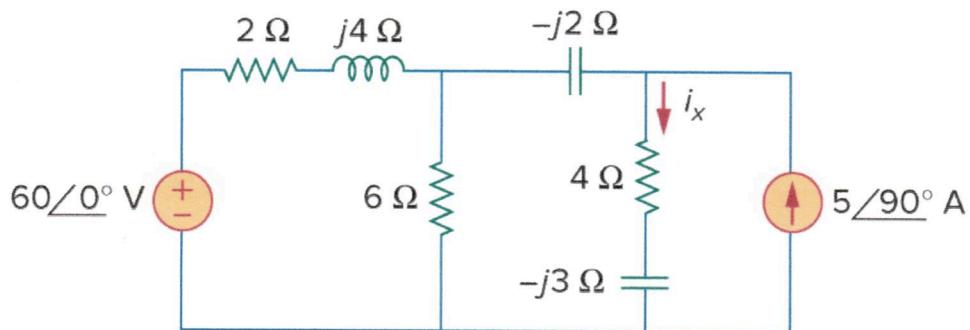4. Use source transformation to find I_x in the following circuit.



Answer: $I_x = 5.238 \angle 17.35^\circ \text{ A}$

Solution:

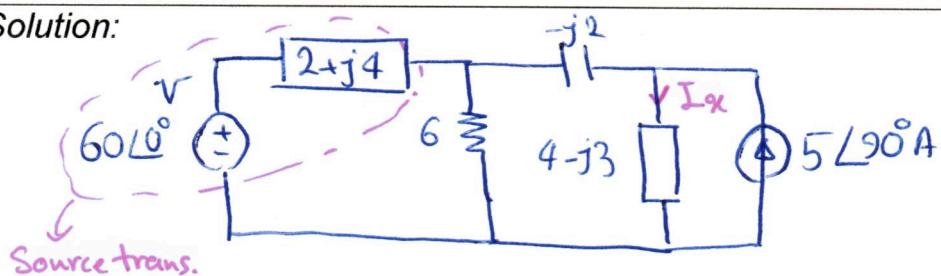

Source trans.

$$I_{S_1} = \frac{60 \angle 0^\circ}{2+j4} = 6-j12 = 13.41 \angle -63.43^\circ \text{ A}$$

Source trans.

parallel

$$(2+j4) \parallel 6 = \frac{6(2+j4)}{8+j4} = 2.4+j1.8$$


$$V_s = (2.4+j1.8) \times 13.41 \angle -63.43^\circ$$

$$= 40.25 \angle -26.56^\circ \text{ V}$$

Source trans.

$$I_{S_2} = \frac{40.25 \angle -26.56^\circ}{2.4-j0.2} = 16.71 \angle -21.8^\circ \text{ A}$$


→ next page

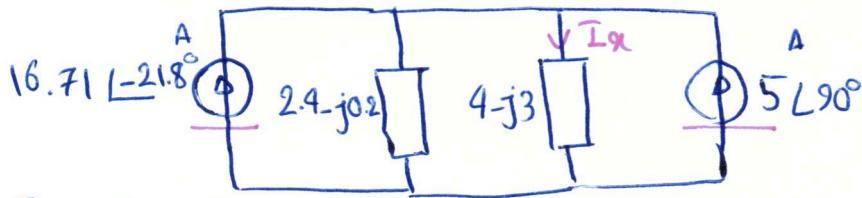

Current Sources have the same direction and connected to the same nodes
So add them

$$I_{S_3} = 16.71 \angle -21.8^\circ + 5 \angle 90^\circ = 15.56 \angle -4.44^\circ \text{ A}$$

use rectangular form

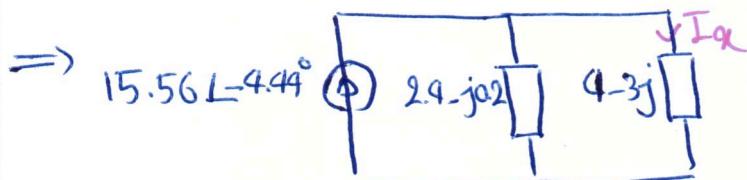


Using Current division:

$$I_x = \frac{2.4 - j0.2}{4 - j3 + 2.4 - j0.2} \times I_{S_3}$$

$$= 5.23 \angle 17.3^\circ \text{ A}$$

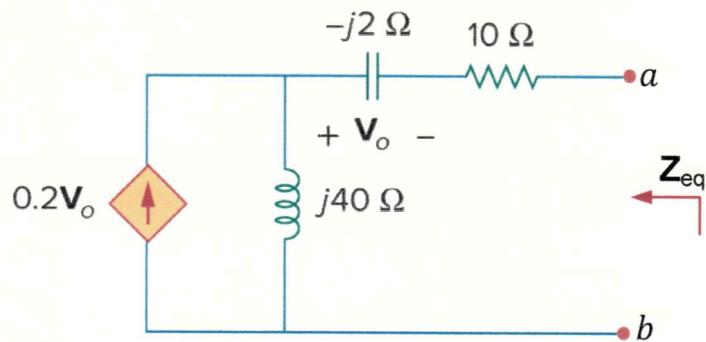
5. Calculate the equivalent impedance of the following circuit from the terminals a-b.



Answer: $Z_{eq} = -6 + j38 \Omega$.


Solution: Due to having one dependent current source and no independent source, we must connect an external source.

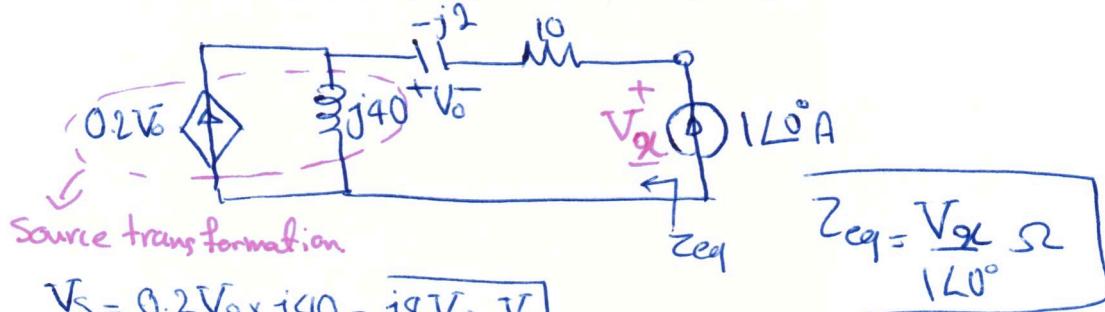Here we use a $1\angle 0^\circ A$ phasor current source



$$V_s = 0.2V_o \times j40 = j8V_o \text{ V}$$
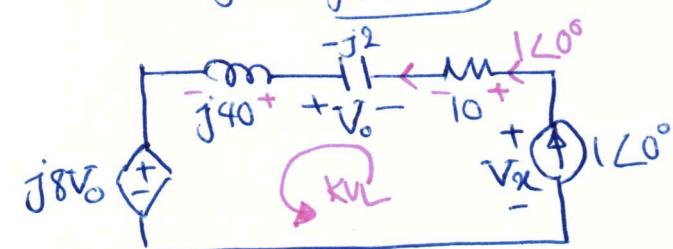
$$Z_{eq} = \frac{V_x}{1\angle 0^\circ A}$$




$$\star KVL: -V_m + 10 \times 1\angle 0^\circ - V_o + j40 \times 1\angle 0^\circ + j8V_o = 0$$

Note that $V_o = -(-j2) \times 1\angle 0^\circ = j2V$ (polarity and direction are opposite of passive sign convention.)

$$\Rightarrow V_x = 10 - j2 + j40 + j16$$


$$= -6 + j38 \text{ V} \Rightarrow Z_{eq} = \frac{-6 + j38}{1} = -6 + j38 \Omega$$

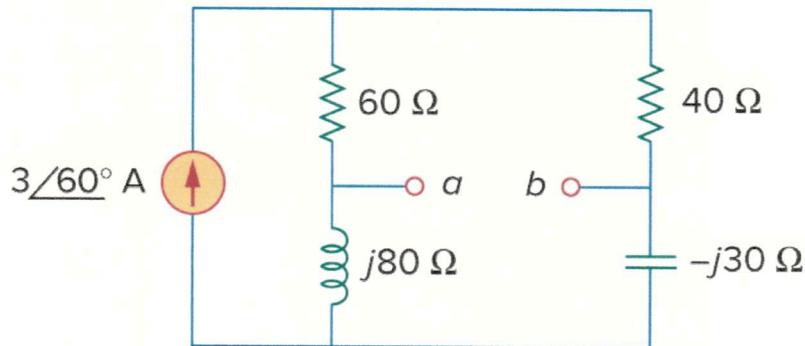6. For the following circuit, find the Thevenin and Norton equivalent circuits



Answer: $Z_{eq} = 20 + j40 \Omega = 44.72 \angle 63.43^\circ \Omega$, $V_{Th} = 134 \angle 123.4^\circ V$, $I_N = 3 \angle 60^\circ A$

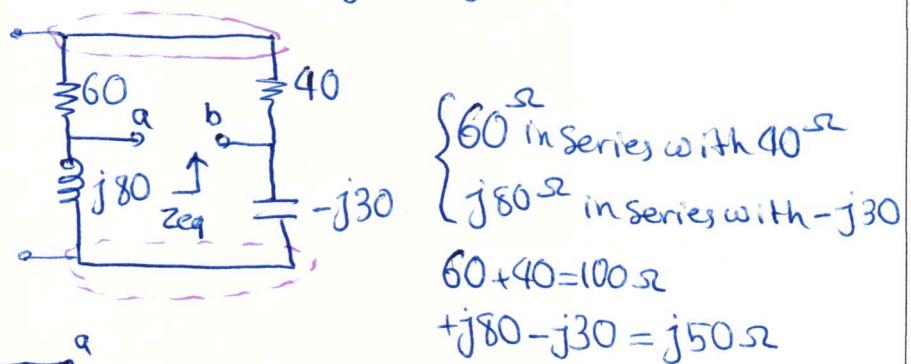Solution: First find $Z_{Th} = Z_{eq} = Z_N$ by setting all independent sources to zero:




\Rightarrow

acts like inductor $\left\{ \begin{array}{l} j50 \Omega \\ 100 \Omega \end{array} \right.$

$Z_{eq} \Rightarrow Z_{eq} = 100 \parallel j50 = \frac{100 \times j50}{100 + j50}$

$\Rightarrow Z_{eq} = 20 + j40 \Omega \stackrel{\approx}{=} 44.72 \angle 63.43^\circ \Omega = Z_{Th} = Z_N$

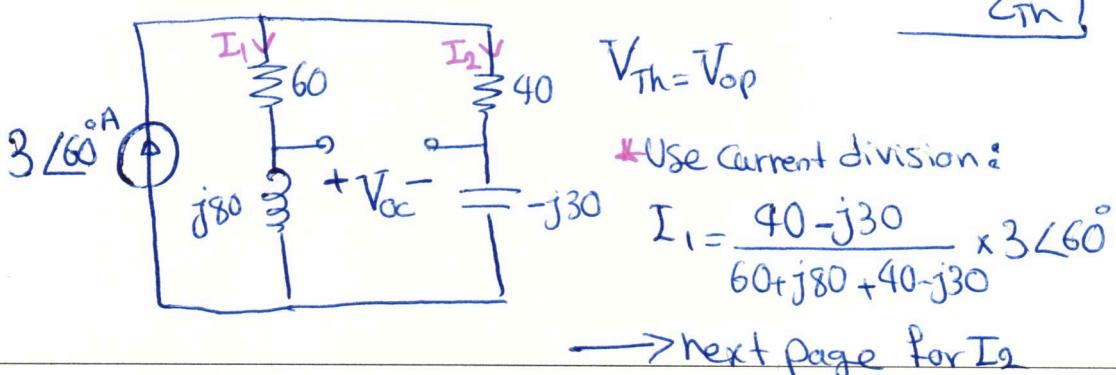In this circuit, it is easier to find V_{Th} and then $I_N = \frac{V_{Th}}{Z_{Th}}$



$$I_2 = \frac{60+j80}{40-j30+60+j80} \times 3 \angle 60^\circ$$

$$\Rightarrow \begin{cases} I_1 = \frac{40-j30}{100+j50} \times 3 \angle 60^\circ \\ I_2 = \frac{60+j80}{100+j50} \times 3 \angle 60^\circ \end{cases}$$


$$I_1 = 1.34 - j0.08 \text{ A}$$

$$= 1.34 \angle -3.43^\circ \text{ A}$$

$$I_2 = 0.16 + j2.67 \text{ A}$$

$$= 2.68 \angle 86.56^\circ \text{ A}$$

Now write KVL:

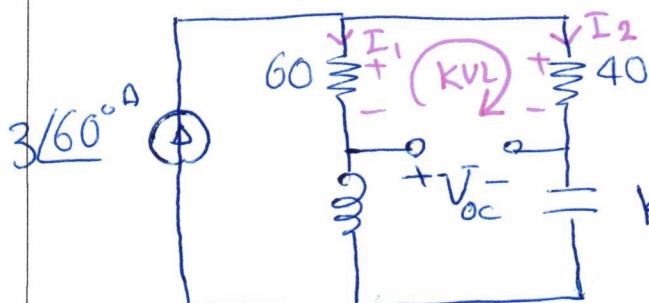

use rectangular form for I_1 and I_2
as in KVL they are being multiplied
by a real number and being added.



KVL:

$$-V_{oc} - 60I_1 + 40I_2 = 0$$


$$\Rightarrow V_{oc} = -60(1.34 - j0.08) + 40(0.16 + j2.67)$$

$$\Rightarrow V_{oc} = V_{Th} = -74 + j111.6 \text{ V} = 134 \angle 123.4^\circ$$
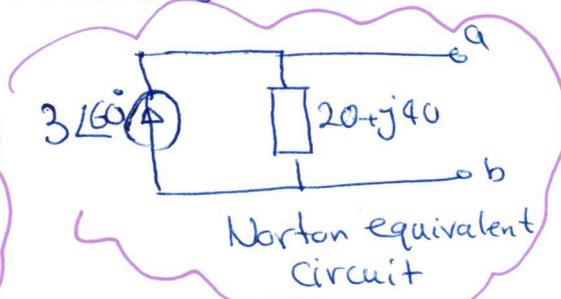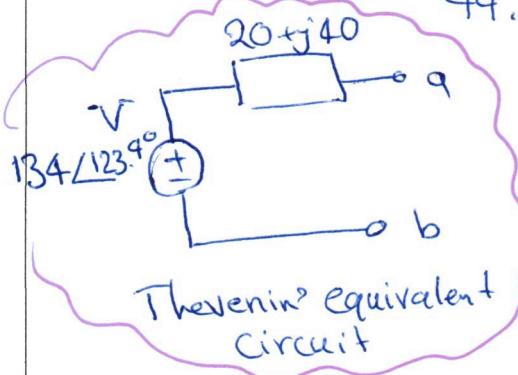
$$\text{Thus } I_N = \frac{V_{Th}}{Z_{Th}} = \frac{134 \angle 123.4^\circ}{44.72 \angle 63.43^\circ} \approx 3 \angle 60^\circ \text{ A}$$




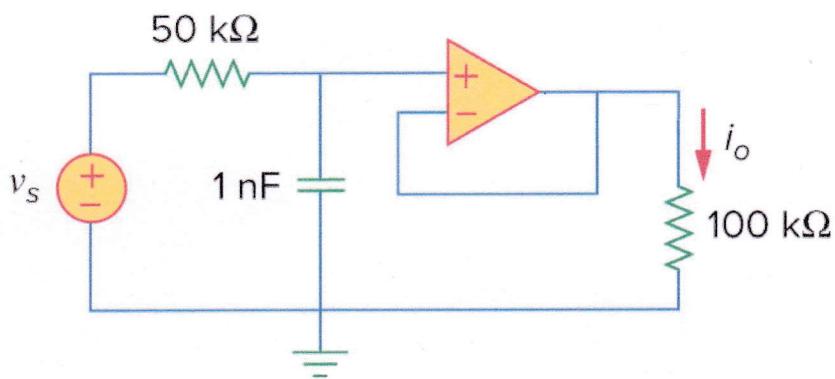7. Find $i_o(t)$ in the Op Amp circuit shown below if $v_s = 4 \cos(10^4 t) \text{ V}$



Answer: $i_o(t) = 35.78 \cos(10^4 t - 26.56^\circ) \mu\text{A}$

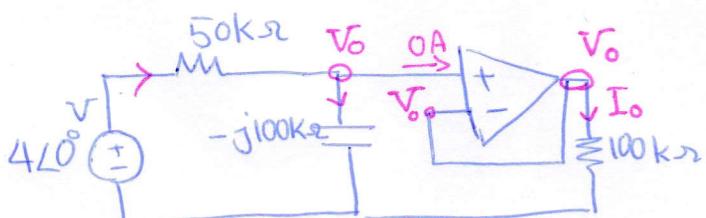Solution: Transform the circuit to phasor domain $v_s = 4 \cos(10^4 t) \rightarrow V_s = 4 \angle 0^\circ \text{ V}$



$$1 \text{ nF} \rightarrow -j \frac{1}{\omega C} \xrightarrow{\omega = 10^4 \text{ rad/s}} -j \frac{1}{10^4 \times 10^{-9}} = -j100 \text{ k}\Omega$$

\Rightarrow negative feedback and ideal opamp $\Rightarrow V^- = V^+ = V_o$


$$\text{KCL at non-inverting node: } \frac{4 - V_o}{50k} = \frac{jV_o}{100k} \xrightarrow{\times 100k} 8 - 2V_o = jV_o$$

$$\Rightarrow (2 + j) V_o = 8 \Rightarrow V_o = \frac{8}{2+j} = 3.578 \angle -26.56^\circ \text{ V}$$

$$\Rightarrow I_o = \frac{V_o}{100k} = 35.78 \angle -26.56^\circ \mu\text{A}$$


$$\Rightarrow i_o(t) = 35.78 \cos(10^4 t - 26.56^\circ) \mu\text{A}$$

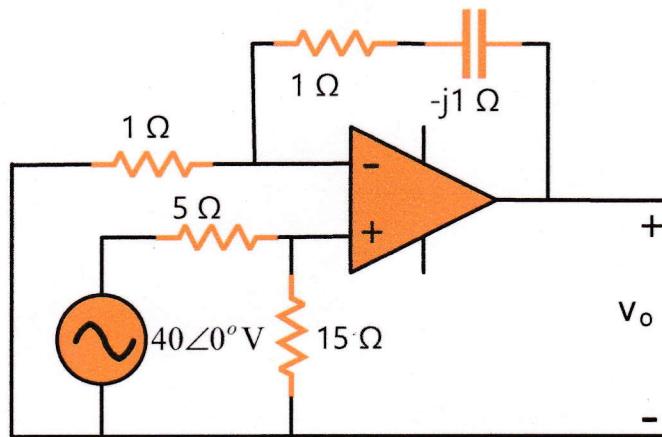8. (Final Exam – Summer, 2016-17) For the circuit shown in below, calculate the output voltage V_o .



Answer: $V_o = 67.08\angle(-26.56^\circ) V = 60 - j30 V$

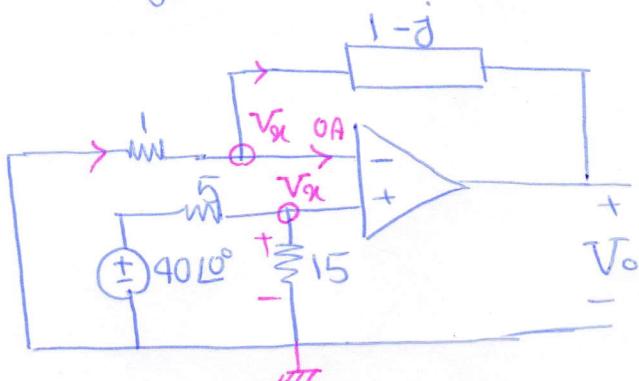
Solution: Negative feedback and ideal op amp $\rightarrow V^- = V^+$



Find \bar{V}_{x_1} using voltage division at non-inverting node:

$$\bar{V}_{x_1} = \frac{15}{5+15} \times 40\angle 0^\circ = 30\angle 0^\circ V$$

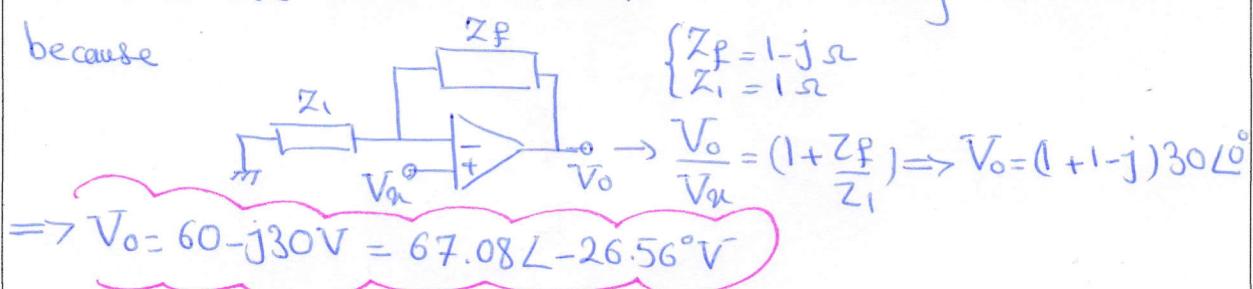Now we can use either Nodal analysis or non-inverting amplifier formula because




Using Nodal analysis by writing KCL at inverting node:

$$\frac{0 - \bar{V}_{x_1}}{1} = \frac{\bar{V}_{x_1} - \bar{V}_o}{1-j} \Rightarrow -(1-j)\bar{V}_{x_1} = \bar{V}_{x_1} - \bar{V}_o \Rightarrow \bar{V}_o = (1-j)\bar{V}_{x_1} + \bar{V}_{x_1}$$

$$\Rightarrow \bar{V}_o = (2-j)\bar{V}_{x_1} = (2-j)30\angle 0^\circ = 60 - j30 V = 67.08\angle(-26.56^\circ) V$$

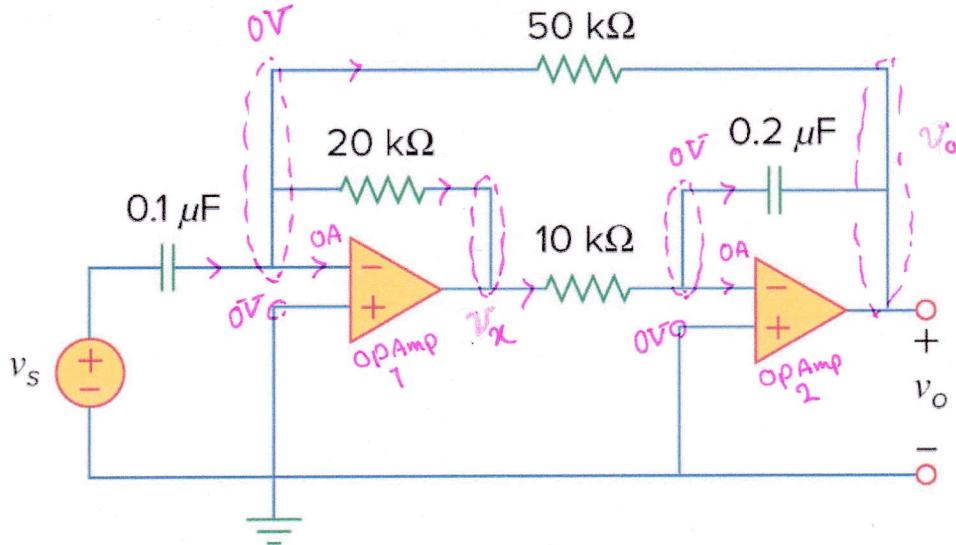9. Calculate $v_o(t)$ for the Op Amp circuit shown below if $v_s = 12 \cos(10^3 t - 60^\circ) \text{ V}$




Answer: $v_o(t) = 11.767 \cos(10^3 t - 71.31^\circ) \text{ V}$

Solution: Draw the circuit in phasor domain

$$v_s = 12 \cos(10^3 t - 60^\circ) \rightarrow \bar{V}_s = 12 \angle -60^\circ \text{ V}$$

$$\omega = 10^3 \text{ rad/s} \rightarrow 0.1 \mu\text{F} \rightarrow -j \frac{1}{\omega C} = -j 10 \text{ k}\Omega$$
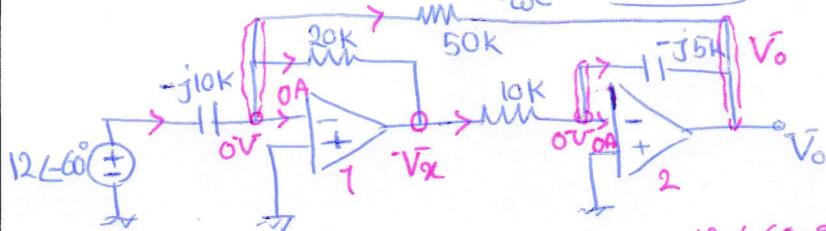
$$0.2 \mu\text{F} \rightarrow -j \frac{1}{\omega C} = -j 5 \text{ k}\Omega$$



* KCL at inverting node of Op Amp 1

$$j \left(\frac{12 \angle -60^\circ - 0}{-j 10} \right) = \frac{0 - \bar{V}_x}{20 \text{ k}} + \frac{0 - \bar{V}_o}{50 \text{ k}} \times 100 \text{ k}$$

$$120 \angle 30^\circ = -5 \bar{V}_x - 2 \bar{V}_o \Rightarrow \bar{V}_x = -24 \angle 30^\circ - 0.4 \bar{V}_o \quad (I)$$

* KCL at inverting node of Op Amp 2

$$\frac{\bar{V}_x - 0}{10 \text{ k}} = \frac{j(0 - \bar{V}_o)}{-j 5 \text{ k}} \times 10 \text{ k} \Rightarrow \bar{V}_x = -j 2 \bar{V}_o \quad (II)$$

Substitute

$$(II) \rightarrow (I) \Rightarrow -j 2 \bar{V}_o = -24 \angle 30^\circ - 0.4 \bar{V}_o \Rightarrow \bar{V}_o = \frac{-24 \angle 30^\circ}{0.4 - j 2} = \frac{24 \angle 30^\circ}{0.4 - j 2}$$

$$\Rightarrow \bar{V}_o = 11.767 \angle -71.31^\circ \text{ V} \Rightarrow V_o(+)=11.767 \cos(10^3 t - 71.31^\circ) \text{ V}$$