



School of Electrical Engineering &
Telecommunications

ELEC1111 Tutorial 1

Design of the rear lights of a vehicle

Conspicuity for the rear of a vehicle is provided by rear position lamps (also called tail lamps or tail lights). These are required to produce only red light and to be wired such that they are lit whenever the front position lamps are illuminated, including when the headlamps are on. Rear position lamps may be combined with the vehicle's stop lamps or separate from them. In combined-function installations (as the one you will explore today), the lamps produce brighter red light for the stop lamp function and dimmer red light for the rear position lamp function. Regulations worldwide stipulate minimum intensity ratios between the bright (stop) and dim (rear position) modes, so that a vehicle displaying rear position lamps will not be mistakenly interpreted as showing stop lamps, and vice versa.

Light Emitting Diodes (LEDs) are gradually coming to be preferred over filament bulbs as the light sources for vehicle rear lamps.

In this tutorial, you will be given a set of specifications, and an opportunity to design the rear lights of a hybrid vehicle.

Specifications:

The combined stop-rear lights circuit design is to conform to the following specifications:

1. Needs to illuminate 12 LEDs distributed in a grid pattern (i.e. X rows \times Y columns).
2. The intensity ratio between the bright (stop) and dim (rear position) modes is 100/30 (i.e. 100% intensity in stop mode, and 30% intensity in rear position mode).
3. All LEDs are to have equal current flowing through them (equal brightness).
4. Current through each LED is to be no greater than 75 mA.
5. The circuit is to be powered using a 12 V car battery.

Consider issues of cost, robustness, number of components and any other factors in making a good design.

Notes:

- LEDs used for our tail-lights (CP42B-RKS) drop about 2.5 V across terminals for currents around 70 mA.
- We will model the LED as a 2.5 V voltage source.
- You may use any number of switches.
- You may use any number of resistors. Resistors to be used are rated at 0.5 W. If possible, use standard resistor values (see list of standard resistor values on last page).

1. Hybrid vehicle battery analysis

A specific brand of a hybrid vehicle features a high voltage Hybrid Vehicle (HV) battery pack and a 12 V auxiliary battery. High voltage electricity powers the electric motor, generator, air conditioning, compressor, and inverter/converter. All other automotive electrical devices such as the rear lights, horn and radio are powered from a separate 12 V battery.

The HV battery pack is a Nickel Metal Hydride (NiMH) battery pack consisting of 34 low voltage (7.2 V) modules connected in series. The capacity of the battery is 6.5 Ah.

Q1. How much total energy is available from the HV battery pack? Express your answer in joules and KWh.


Answer: $w = 1.591 \text{ KWh}$ or $w = 5728320 \text{ J} = 5.728 \text{ MJ}$.

Q2. If the vehicle drives for 15 minutes as an all-electric vehicle using only the energy available in the fully charged HV battery pack, what is the average current used when driving? And the average power?

Answer: $i = 26 \text{ A}$, $p = 6364.8 \text{ W}$

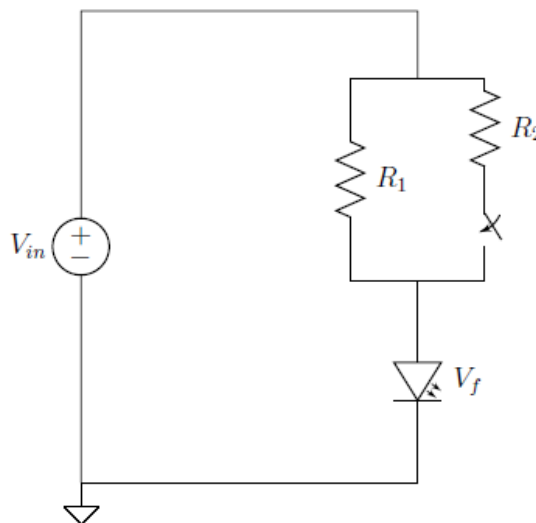2. Circuit to illuminate a single LED

To help you with the design task, you will start analysing a circuit that illuminates a single LED functioning as stop-rear light.



In the previous circuit, the stop mode occurs when the switch is closed, since the value of the resistance will decrease ($R_1 \parallel R_2 < R_1$) and the current and brightness of the LEDs will increase.

Q3. Calculate the current in stop mode (i_{stop}) and rear position mode (i_{rear}) if $V_{in} = 12\text{V}$, $R_1 = 442 \Omega$, $R_2 = 196 \Omega$, and $V_f = 2.5 \text{ V}$. Check whether these currents conform to the specifications.

Answer: $i_{stop} = 69.95 \text{ mA}$; $i_{rear} = 21.5 \text{ mA}$. They conform to the specifications.

Q4. Check whether the resistors meet the power specifications (resistors to be used are rated at 0.5 W).

Answer: $p_{R1} = 0.204 \text{ W}$; $p_{R2} = 0.46 \text{ W}$. They meet the power specifications.

3. Rear lights design

The values of R_1 and R_2 in the previous circuit were obtained according to the following design steps:

1. According to the specifications, the current through each LED is to be no greater than 75 mA. We can then choose:

$$i_{stop} = 70 \text{ mA}$$

$$i_{rear} = 70 \times 0.3 = 21 \text{ mA}$$

Note that the intensity ratio between the bright (stop) and dim (rear position) modes is 100/30.

2. If the car battery provides 12V and we assume ideal behaviour of the LED ($V_f = 2.5 \text{ V}$), R_1 can be then calculated as follows:

$$R_1 = \frac{12 - 2.5 \text{ V}}{0.021 \text{ A}} = 452.38 \Omega$$

We choose a standard resistor value as close as possible to 452 which meets the current limitation. E.g. $R_1 = 442 \Omega$ (from E48 series).

3. If $i_{stop} = 70 \text{ mA}$ and $i_{rear} = 21 \text{ mA}$, then $i_{R_2} = 70 - 21 = 49 \text{ mA}$. R_2 can be then calculated as follows:

$$R_2 = \frac{12 - 2.5 \text{ V}}{0.049 \text{ A}} = 193.88 \Omega$$

We choose a standard resistor value as close as possible to 194 which meets the current limitation. E.g. $R_2 = 196 \Omega$ (from E48 series).

- Q5.** Design the rear lights of a hybrid vehicle, conforming to the specifications listed in the first page. Use the single LED circuit functioning as stop-rear light as a starting point, and keep in mind the steps followed to design it.

Consider issues of cost, robustness, number of components and any other factors in making a good design.

Answer: There are many possible correct designs. If you have a design in mind and you want to know whether it is correct out of tutorial hours, you can simulate it using Falstad (<http://www.falstad.com/circuit/>) or any other simulator of electric circuits. Otherwise, please contact your lecturer to organise an appointment.

NOTE:

- CP42B-RKS price: \$0.28 per unit.
- Resistor price: \$0.75 per package of 5.
- Switch price (e.g. SP0720): \$1.45 per unit.

Note that these are illustrative prices. They might change a bit depending on the provider. Bulk pricing would be lower.

Standard EIA Decade Values Table (100 to 1,000 Decade)

E6	E12	E24	E48	E96	E192	E6	E12	E24	E48	E96	E192	E6	E12	E24	E48	E96	E192
100	100	100	100	100	100	220	220	220	215	215	215	470	470	470	464	464	464
				101	101					218	218					470	470
				102	102					221	221					475	475
				104	104					223	223					481	481
				105	105					226	226					487	487
				106	106					229	229					493	493
				107	107					232	232					499	499
				109	109					234	234					505	505
				110	110					237	237					511	511
				111	111					240	240					517	517
110	110	110	110	113	113	240	240	240	243	243	243	510	510	510	523	523	523
				114	114					246	246					530	530
				115	115					249	249					536	536
				117	117					252	252					542	542
				118	118					255	255					549	549
				120	120					258	258					556	556
				121	121					261	261					562	562
				123	123					264	264					569	569
				124	124					267	267					576	576
				126	126					271	271					583	583
120	120	120	120	127	127	270	270	270	274	274	274	560	560	560	590	590	590
				129	129					277	277					597	597
				130	130					280	280					604	604
				132	132					284	284					612	612
				133	133					287	287					619	619
				135	135					291	291					626	626
				137	137					294	294					634	634
				138	138					298	298					642	642
				140	140					301	301					649	649
				142	142					305	305					657	657
130	130	130	130	143	143	300	300	300	309	309	309	620	620	620	665	665	665
				145	145					312	312					673	673
				147	147					316	316					681	681
				149	149					320	320					690	690
				150	150					324	324					698	698
				152	152					328	328					706	706
				154	154					332	332					715	715
				156	156					336	336					723	723
				158	158					340	340					732	732
				160	160					344	344					741	741
150	150	150	150	162	162	330	330	330	348	348	348	680	680	680	750	750	750
				164	164					352	352					759	759
				165	165					357	357					768	768
				167	167					361	361					777	777
				169	169					365	365					787	787
				172	172					370	370					796	796
				174	174					374	374					806	806
				176	176					379	379					816	816
				178	178					383	383					825	825
				180	180					388	388					835	835
180	180	180	180	182	182	390	390	390	392	392	392	820	820	820	845	845	845
				184	184					397	397					856	856
				187	187					402	402					866	866
				189	189					407	407					876	876
				191	191					412	412					887	887
				193	193					417	417					898	898
				196	196					422	422					909	909
				198	198					427	427					920	920
				200	200					432	432					931	931
				203	203					437	437					942	942
200	200	200	200	205	205	430	430	430	442	442	442	910	910	910	953	953	953
				208	208					448	448					965	965
				210	210					453	453					976	976
				213	213					459	459					988	988