



Faculty of Engineering

School of Electrical Engineering and Telecommunications

ELEC 1111 – Topic 10

Digital Logic Circuits

Dr. Inmaculada (Inma) Tomeo-Reyes

Lecturer

School of Electrical Engineering and Telecommunications, UNSW

Topic 10 Content


This lecture covers:

- Binary numbers
 - Conversion from decimal to binary and vice versa
 - Simple binary arithmetic (addition and subtraction)
- Digital representations
- Digital logic
 - Truth table
- Digital gates
 - AND, OR, NOT
 - NAND, NOR,
 - XOR, XNOR
- Boolean algebra
 - DeMorgan's Theorem

This topic is not covered in the prescribed textbook for this course

Analog versus digital

- **Analog signal** is an electric signal whose value varies **continuously** with time.
 - A sinusoid voltage $v(t) = V_m \cos(\omega t)$ can take **any value** between $-V_m$ and V_m .
- **Digital signals** can take only a **finite** number of values. They are also called **discrete-time signals** as they vary between a finite set of **digits**.
 - Systems that **work** with **digital signals** are called **digital systems**.
 - To understand how digital systems work, we need to get familiar with **binary numbers** first.
 - The most common digital signals are **binary signals**.
 - A binary signal can take **only two** discrete values.
 - These two values are represented in **binary** format using **0** and **1** digits.

 

Decimal vs binary numbers

- **Decimal** numbers system is **base 10** or **radix 10**.

- In **decimal** system, there are **10 digits**, 0, 1, 2, ..., 9.
- A decimal number is represented by the **sum** of the **powers of 10**.

$$372.5 = (3 \times 10^2) + (7 \times 10^1) + (2 \times 10^0) + (5 \times 10^{-1})$$

- **Binary** number system is **base 2**.

- For any system that operates in **two states** (like on or off), **binary number system** is a natural choice.
- In **binary** system, there are **2 digits**, 0 and 1.
- A binary number is represented by the **sum** of the **powers of 2**.

$$10110 = (1 \times 2^4) + (0 \times 2^3) + (1 \times 2^2) + (1 \times 2^1) + (0 \times 2^0)$$


- We can use subscript to denote numbers in different **bases**.

$$(10110)_2 = 16 + 0 + 4 + 2 + 0 = (22)_{10} \quad \Rightarrow$$

To convert a **binary** number to **decimal**, just **expand** the binary number as the **sum** of the **powers of 2**.

Binary numbers

 - Binary digits are also called **bits**.
- The **rightmost bit** is called **least significant bit (LSB)**.
- The **leftmost bit** is called **most significant bit (MSB)**.



- Binary numbers require **large** number of bits to represent large numbers.
 - They are usually grouped in sets of 4, 8 or 16.
 - **Nibble**: group of **4/four** bits.
 - **Byte**: group of **8/eight** bits.
 - **Word**: group of **16/sixteen** bits.
 - $(11100110)_2$ is an **8-bit** number.

Conversion from decimal to binary

- Conversion from a decimal number to its binary equivalent is performed by **successive division** of the decimal number by **2/two** followed by the division of its quotients.
- The **remainders** constitute the binary number.
- This method is used to convert the **integer** part of decimal numbers **only**.

	Quotient	Remainder
$156 \div 2$	78	0 ← LSB
$78 \div 2$	39	0
$39 \div 2$	19	1
$19 \div 2$	9	1
$9 \div 2$	4	1
$4 \div 2$	2	0
$2 \div 2$	1	0
$1 \div 2$	0	1 ← MSB

↑

→ $(156)_{10} = (10011100)_2$

Addition

- To add binary numbers, the simple rule shown in the table is used:

Example:

$$15 + 20 = 35$$



$$\begin{array}{r} 1111 \\ +10100 \\ \hline 100011 \end{array}$$

	Q	R
$15 \div 2$	7	1
$7 \div 2$	3	1
$3 \div 2$	1	1
$1 \div 2$	0	1

$$(15)_{10} = (1111)_2$$

	Q	R
$20 \div 2$	10	0
$10 \div 2$	5	0
$5 \div 2$	2	1
$2 \div 2$	1	0
$1 \div 2$	0	1

$$(20)_{10} = (10100)_2$$

Addition Rule

$$0 + 0 = 0$$

$$0 + 1 = 1$$

$$1 + 0 = 1$$

$$1 + 1 = 0 \\ \text{(with a carry of 1)}$$

$$\begin{aligned} 100011 &= (1 \times 2^5) + 0 + 0 \\ &\quad + 0 + (1 \times 2^1) \\ &\quad + (1 \times 2^0) \\ &= 32 + 2 + 1 = 35 \end{aligned}$$

Subtraction

- For **subtraction**, $A - B$ is replaced with $A + (-B)$ so that only addition of a positive number to a negative one is applied.
- Three conventions** are used to represent a **negative number** in binary system:
 - Sign-magnitude:** Sign bit 1 means minus sign and Sign bit 0 means plus sign.
 - 1's complement:** Replacing 0's with 1's and vice versa (inverting) in a binary number.
 - 2's complement:** Adding 1 to the 1's complement in a binary number.

Sign-magnitude convention

Sign bit b_7	b_6	b_5	b_4	b_3	b_2	b_1	b_0
0 (+) 1 (-)	Actual binary number						

1's complement convention

Sign bit b_7	b_6	b_5	b_4	b_3	b_2	b_1	b_0
0 (+)	Actual binary number						
1 (-)	1's complement of binary number						

2's complement convention

Sign bit b_7	b_6	b_5	b_4	b_3	b_2	b_1	b_0
0 (+)	Actual binary number						
1 (-)	2's complement of binary number						

Subtraction

- **2's complement** is the most commonly used method in many digital computers for **subtraction**.
- In performing $A + (-B)$, $-B$ is the **2's complement** of B with **sign bit 1**, and we simply **add** the two numbers with their **sign bits** to obtain the **subtraction**.
- We need to know beforehand that how many bits are required to represent the largest number in the calculations.

Decimal (+)	4-bit 2's complement
1	0001
2	0010
3	0011
4	0100
5	0101
6	0110
7	0111

Sign bit

Decimal (-)	4-bit 2's complement
-1	1111
-2	1110
-3	1101
-4	1100
-5	1011
-6	1010
-7	1001

Note: To represent -8 using 2's complement, at least 5 bits are needed to accommodate sign bit.

Exercise

Perform the following subtraction in binary format:

$$(4)_{10} - (6)_{10} = (4)_{10} + (-6)_{10} = (-2)_{10}$$


Exercise

Perform the following subtraction in binary format:

$$(7)_{10} - (5)_{10} = (7)_{10} + (-5)_{10} = (2)_{10}$$

Digital systems

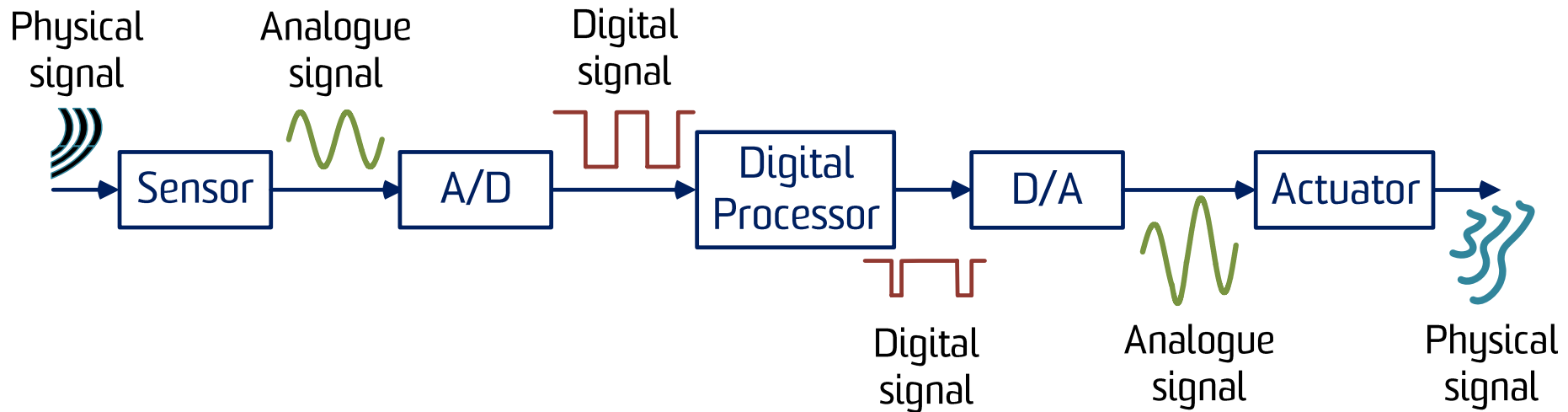A typical digital system would consist of the following parts:



Note:

A/D or ADC: Analog to Digital Converter.

D/A or DAC: Digital to Analog Converter.

Why use digital?


- Any physical quantity that is capable of switching between two values can be used to represent numerical quantities in the binary system.
- Numerical calculations can be used for manipulation of binary numbers.
- The benefits of using digital systems are numerous.
 - Benefits include: good noise rejection, high reliability, high accuracy, predictability, low power, ease of design.
 - There are some limitations too, such as noise generation and need for A/D & D/A interface.

Two-level logic for digital systems

- Binary digits can be represented with the use of a **voltage signal**:
 - **Presence of voltage** (“**high**”) denotes the **binary digit 1**.
 - **Absence of voltage** (“**low**”) denotes the **binary digit 0**.
- More specifically:
 - **5 V** represents **digit 1**.
 - **0 V** represents **digit 0**.


Two-level logic for digital systems

- In an “**ideal**” case:
 - The ‘sender’ of the digit outputs **exactly** either 5 V or 0 V as for 1 or 0.
 - The ‘receiver’ sees **exactly** the same voltages and translate 5 V to 1 and 0 V to 0.
- However, the world is not “ideal” or “perfect”:
 - Circuits **cannot** generate voltages with **high accuracy** (exactly 5 V).
 - There are **losses** in the circuits (voltage drops).
 - There is **noise**!
- One way to address this issue is the use of a **band of voltages** to define binary bits.
 - For instance, any voltage **between** 2.5 V and 5 V is interpreted as 1, and below this range as 0, as shown in the figure.
- However, the **noise** can affect the voltages around the **boundary** and it causes uncertainty in the accuracy of the received voltages.

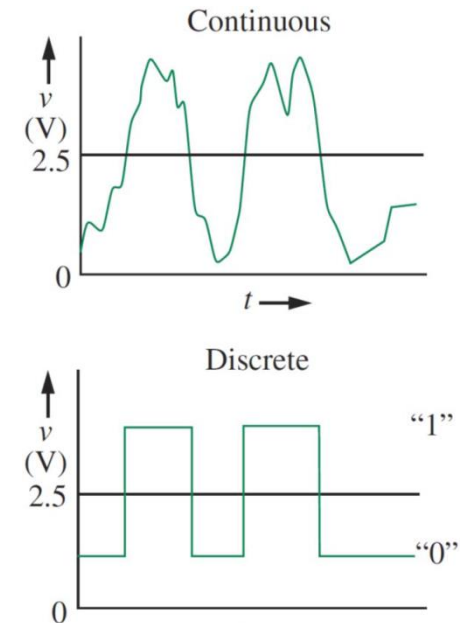

Two-level logic for digital systems



- To resolve the issue with the noise, a **clear zone** is introduced to **separate** the voltage range used for digit 1 and digit 0.
- This zone is called **forbidden region**.
- We have to introduce a tolerance on **how much noise** is acceptable to be present in a system.
- Based on the **technology** used in building a digital system (e.g. TTL or CMOS), different **standards** can be defined for the range of voltages to be used for digits 1 and 0.

 

In the **forbidden region**, the voltages received are considered as **undefined** or **noise-affected**.


Two-level logic for digital systems

 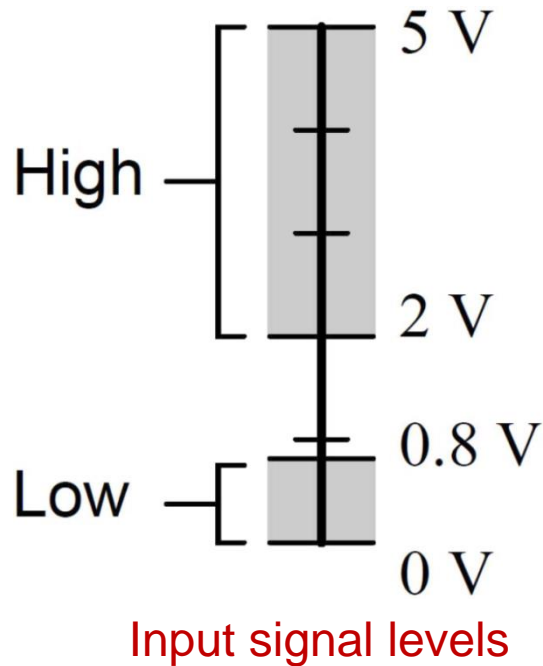- TTL (Transistor - Transistor Logic) uses the following voltages levels from 0 V to 5 V:





Two-level logic for digital systems

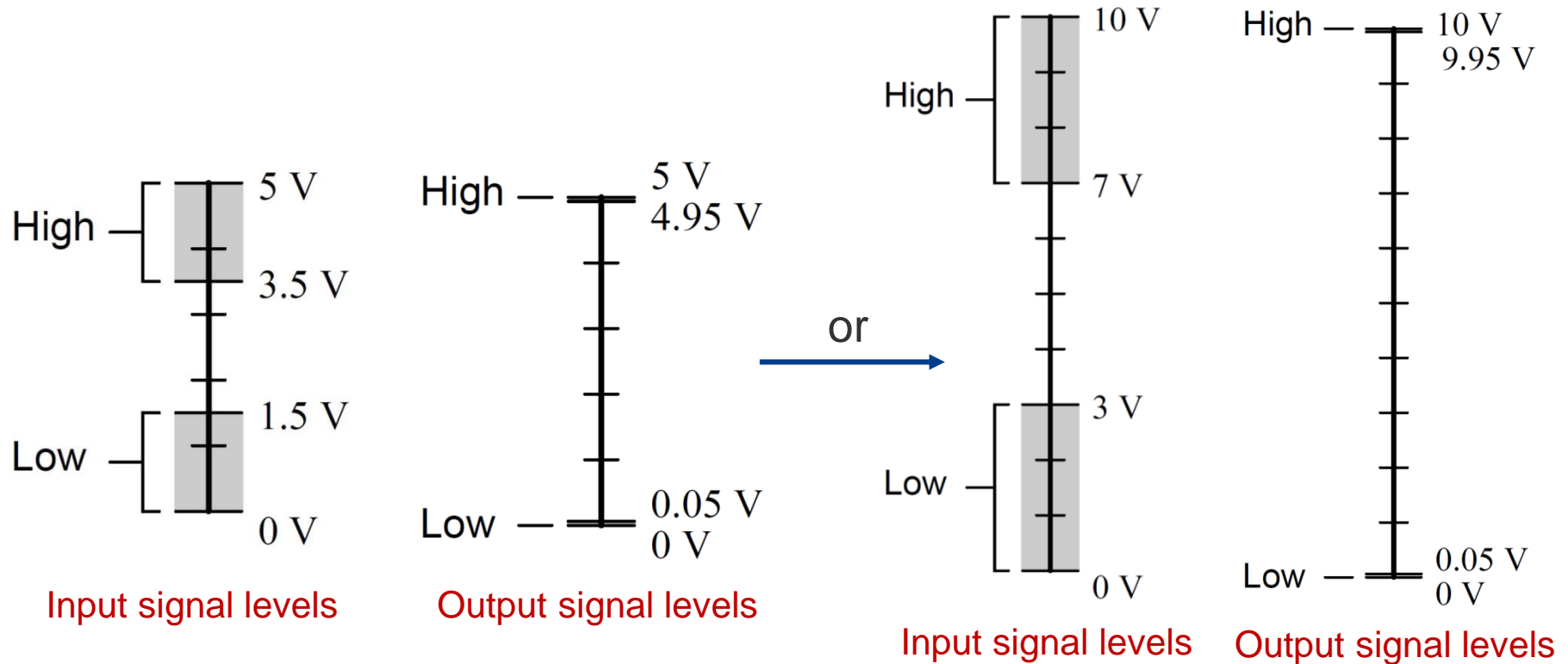- CMOS (Complementary Metal Oxide Semiconductor) can use higher voltage levels.



Logic circuits

  - Digital logic can be implemented in digital circuits. That's why they are also called **Digital Logic Circuits**.
- There are two types of logic circuits:
 1. **Combinational** logic.
 2. **Sequential** logic.



Combinational:

- **Output** depends **only** on the **current value** of the input.
- **No memory** is needed.

Sequential:

- Output depends on **both current and previous values** of the input.
- It **needs memory** to keep the previous values.

Truth table and logic variables

- **Truth table** is a method of tabulating and describing the output of a logic operation for all possible combinations of inputs.
- For example, the following logic statements can be tabulated as shown in the truth table:

Phone rings ($R = 1$) if the power is on ($P = 1$) and there is an incoming call ($C = 1$).

- In this example, R , P , and C are called **logic variables**.
- P and C are inputs and R is the output.
- They can be either **0** or **1**.
- There are $4 = 2^2$ combinations.

Truth Table

P	C	R
0	0	0
0	1	0
1	0	0
1	1	1

- In logic statements, assign a **logic variable** to **each precise statement**.
- If there are n inputs, there will be 2^n combinations.

Exercise

Create the truth table for the following example describing how David would make a purchase.


David buys if he wants an item **and** he has cash **or** if he needs the item **and** he has cash **or** EFTPOS card

Primitive logic gates

- A logic gate implements a combinational logic function.
- We can have 2^n possible functions of n variables.
- All these possible functions can be described using primitive gates:
 - AND
 - OR
 - NOT
 - NAND
 - NOR
 - XOR
 - XNOR

Logic AND gate

 - **AND** gate is the **binary multiplication**.
- It can have **multiple** inputs.
- For a **2-input AND** gate, the **truth table** is:



$$\begin{aligned}Z &= A \text{ and } B \\Z &= A \cdot B \\Z &= AB\end{aligned}$$


AND Truth Table

<i>A</i>	<i>B</i>	<i>Z</i>
0	0	0
0	1	0
1	0	0
1	1	1

$Z = 1$ if both A and B are 1

Logic AND gate

 - For a **3-input AND** gate, the **truth table** is:



$$Z = A.B.C$$


$Z = 1$ if all A and B and C are 1

AND Truth Table

<i>A</i>	<i>B</i>	<i>C</i>	<i>Z</i>
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

Logic OR gate

 - **OR** gate is the **binary addition**.
- It can have **multiple** inputs.
- For a **2-input OR** gate, the **truth table** is:



$$Z = A \text{ or } B$$
$$Z = A + B$$


OR Truth Table

<i>A</i>	<i>B</i>	<i>Z</i>
0	0	0
0	1	1
1	0	1
1	1	1

$Z = 1$ if either A or B is 1

Logic NOT gate

 - **NOT** gate is the **binary negation, complement or inversion**.
- **NOT** gate simply **inverts** 1 to 0 and vice versa (similar to an amplifier with a **negative unit gain**). It is known as an **inverter**.
- The **truth table** of **NOT** is:




$$\begin{aligned}Z &= \text{not } A \\Z &= \bar{A} \\Z &= A'\end{aligned}$$

NOT Truth Table

<i>A</i>	<i>Z</i>
0	1
1	0

Logic NAND gate (NOT AND)

 - **NAND** is the **inverted** of **AND** gate.
- It can have **multiple** inputs.
- For a **2-input NAND** gate, the **truth table** is:



$$Z = \overline{A \cdot B}$$
$$Z = \overline{AB}$$
$$Z = (AB)'$$


NAND Truth Table

<i>A</i>	<i>B</i>	<i>Z</i>
0	0	1
0	1	1
1	0	1
1	1	0

$Z = 1$ if either A or B is 0

Logic NOR gate (NOT OR)

 - **NOR** is the **inverted** of **OR** gate.
- It can have **multiple** inputs.
- For a **2-input NOR** gate, the **truth table**:



$$Z = \overline{A + B}$$
$$Z = (A + B)'$$


NOR Truth Table

<i>A</i>	<i>B</i>	<i>Z</i>
0	0	1
0	1	0
1	0	0
1	1	0

$Z = 1$ if both A and B are 0

Logic XOR (Exclusive OR)

 - **XOR** gate is a circuit whose output is 1 **only** if **one** of its inputs is 1 but **not both**.
- It can have **multiple** inputs.
- For a **2-input XOR** gate, the **truth table** is:



$$Z = A \text{ xor } B$$
$$Z = A \oplus B$$


XOR Truth Table

<i>A</i>	<i>B</i>	<i>Z</i>
0	0	0
0	1	1
1	0	1
1	1	0

$Z = 1$ if either A or B is 1 but **not both**

Logic XNOR (Exclusive NOR)

 - **XNOR** gate is the **inverted** of **XOR**.
- It can have **multiple** inputs.
- For a **2-input XNOR** gate, the **truth table** is:



$$Z = A \text{ xnor } B$$

$$Z = \overline{A \oplus B}$$

$$Z = (A \oplus B)'$$


XNOR Truth Table

<i>A</i>	<i>B</i>	<i>Z</i>
0	0	1
0	1	0
1	0	0
1	1	1


$Z = 1$ if A or B are the same

Logic gates with multiple inputs

 - As mentioned before, we can have gates with multiple inputs.
- The output still follows the same rule of the 2-input logical gate.




$$Z = A \cdot B \cdot C \cdot D$$

 








$$Z = \overline{A + B + C}$$

Drawing convention

 - For the sake of simplicity, sometimes the NOT gates at the inputs can be combined to with gate in the form of **small circle** representing inverted input.




Logical gates summary

       

Physical implementation on ICs

- Since logic gates are built using **transistors**, they can be easily implemented on **integrate circuits (ICs)** .
- For instance, **74LS00**, known as **Quad 2-input NAND gate**, contains **4 NAND** gates as seen below:

Connection Diagram

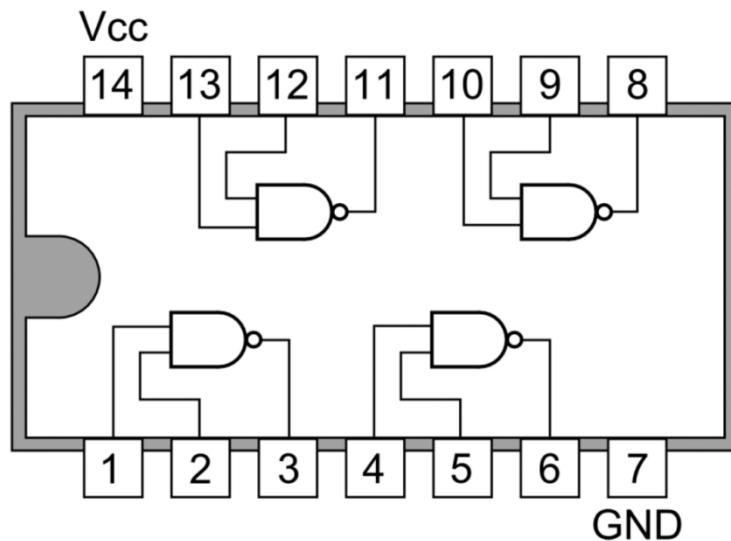


Function Table

$$Y = \overline{AB}$$


Inputs		Output
A	B	Y
L	L	H
L	H	H
H	L	H
H	H	L

H = HIGH Logic Level
L = LOW Logic Level

 


Physical implementation on ICs


4011
Quad NAND gate

 


4001
Quad NOR gate

 

4081
Quad AND gate

 


4071
Quad OR gate

 


Combining primitive gates

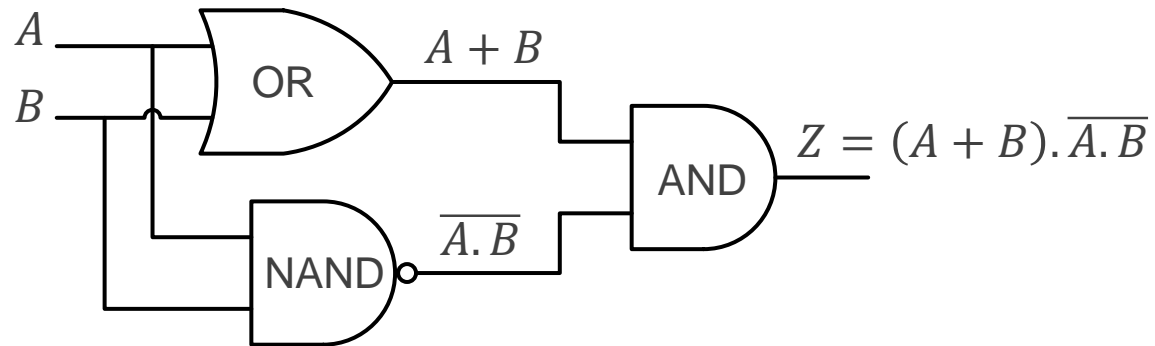- We can construct **truth table** for a digital circuit consisting of logical gates and find an **equivalent digital circuit** with **less** number of gates.
- Consider the following circuit:



Truth Table

A	B	$A + B$	$\overline{A.B}$	$(A + B).\overline{A.B}$	$A \oplus B$
0	0	0	1	0	0
0	1	1	1	1	1
1	0	1	1	1	1
1	1	1	0	0	0

 

Exercise

Using the logic given in the problem (and / or) write a logical expression describing the problem and draw the digital circuit.

David buys (B) if he wants an item (W) and he has cash (C) or if he needs the item (N) and he has cash (C) or EFTPOS card (E)

Truth Table
($2^4 = 16$ combinations)

N	W	C	E	B
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	1
0	1	1	1	1
1	0	0	0	0
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	0
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1


Exercise

For the following expression, draw the digital circuit using logical gates and construct the truth table.

$$Z = A + (B \cdot \bar{C})$$

Boolean algebra

- In practice, we deal with **switching circuits** where signals can have two states. These are known as **switching signals**.
- These switching circuits can be easily **implemented** using digital logic gates once the output is obtained as a function of inputs in the form of a **logic expression**.
- **Boolean algebra** is a **set of rules or laws** that enable us to **simplify** the **digital logic/Boolean expressions** and **reduce** the **number of gates** needed to perform a particular logic operation in switching circuits.

 

In this circuit, **four** switches control the operation of the bulb. The bulb is switched on if the switches **S1 and S2** are closed, **and S3 or S4** is also closed, otherwise the bulb will not be switched on.

Boolean algebra – Single value theorems

- **Variables** in Boolean algebra only have **two values**, 0 or 1.
- **Single value theorems** are a set of rules regarding different operations on a **single variable**. They are also known as **Boolean identities**.

AND operations

$$A \cdot 0 = 0$$

$$A \cdot 1 = A$$

$$A \cdot A = A$$

$$A \cdot \bar{A} = 0$$

OR operations

$$A + 0 = A$$

$$A + 1 = 1$$


$$A + A = A$$

$$A + \bar{A} = 1$$

NOT operations

$$\overline{(\bar{A})} = \bar{\bar{A}} = A$$

Double negation

 


Boolean algebra – Commutative laws

- **Commutative** laws state that **input order does not matter** in **AND/OR** operations.


AND operation

$$A \cdot B = B \cdot A$$

 

OR operation

$$A + B = B + A$$

 


Boolean algebra – Associative laws

- **Associative** laws state that there is **no precedence** in **multiple OR operations** and in **multiple AND operations**.


AND operation:

$$A.(B.C) = (A.B).C = A.B.C$$

 

OR operation:
 
$$A + (B + C) = (A + B) + C = A + B + C$$



Boolean algebra – Distributive laws

- According to distributive laws, **AND** operation can be **distributed** over **OR** and **vice versa**.

$$A.(B + C) = (A.B) + (A.C)$$

A	B	C	B + C	A.B	A.C	A.(B + C)	(A.B) + (A.C)
0	0	0	0	0	0	0	0
0	0	1	1	0	0	0	0
0	1	0	1	0	0	0	0
0	1	1	1	0	0	0	0
1	0	0	0	0	0	0	0
1	0	1	1	0	1	1	1
1	1	0	1	1	0	1	1
1	1	1	1	1	1	1	1

$$A + (B.C) = (A + B).(A + C)$$

A	B	C	B.C	A + B	A + C	A + (B.C)	(A + B).(A + C)
0	0	0	0	0	0	0	0
0	0	1	0	0	1	0	0
0	1	0	0	1	0	0	0
0	1	1	1	1	1	1	1
1	0	0	0	1	1	1	1
1	0	1	0	1	1	1	1
1	1	0	0	1	1	1	1
1	1	1	1	1	1	1	1

NOTE: AND operation has precedence over OR operation.

Boolean algebra – Absorption laws

- Using **single value theorems**, some expressions can be **reduced** to a single variable. This is known as **absorption laws**.

$$A + (A.B) = A$$



Proof: Use the identity $A = A.1$ and $B + 1 = 1$
 $A.1 + (A.B) = A(1 + B) = A.1 = A$

$$A.(A + B) = A$$



Proof: Use distribution and first absorption law
 $A.A + (A.B) = A + (A.B) = A$

$$A.B + A.\bar{B} = A$$



Proof: Factor out A and the identity $B + \bar{B} = 1$
 $A.(B + \bar{B}) = A.1 = A$

$$(A + B).(A + \bar{B}) = A$$



Proof: Use distribution, second absorption law, and the identities $B\bar{B} = 0$, and $1 + \bar{B} = 1$ and factoring out (For your practice!)

Exercise

Prove the equivalency of the following expressions:

1. $(A + B) \cdot (A + C) = A + B \cdot C$

2. $A + (\bar{A} \cdot B) = A + B$

Exercise


Write a logical expression for the output Z given the following truth table.

<i>A</i>	<i>B</i>	<i>Z</i>
0	0	0
0	1	1
1	0	1
1	1	1


Boolean algebra – DeMorgan's Theorems

- The **two** famous DeMorgan's Theorems state the relationship in converting **NAND** operation into **OR of negated** inputs, and **NOR** operation into **AND of negated** inputs.
 
$$\overline{A + B} = \bar{A} \cdot \bar{B}$$


 
$$\overline{\bar{A} \cdot \bar{B}} = \bar{\bar{A}} + \bar{\bar{B}}$$



Boolean algebra – DeMorgan's Theorems

$$\overline{A + B} = \bar{A} \cdot \bar{B}$$



Truth Table

A	B	$\overline{A + B}$	$\bar{A} \cdot \bar{B}$
0	0	1	1
0	1	0	0
1	0	0	0
1	1	0	0

$$\overline{\bar{A} \cdot \bar{B}} = A + B$$



Truth Table

A	B	$\overline{\bar{A} \cdot \bar{B}}$	$A + B$
0	0	1	1
0	1	1	1
1	0	1	1
1	1	0	0

Boolean algebra – DeMorgan's Theorems

- DeMorgan's Theorems describe the equivalent relationship between gates with **inverted inputs** and gates with **inverted outputs**.
- When “**breaking**” a **complementation bar** in a Boolean expression, the operation directly underneath the break (addition or multiplication) **reverses**, and the broken bar pieces remain over the respective terms.
 - A **NAND** gate is equivalent to a “**Negative Input**”-OR gate.
 - A **NOR** gate is equivalent to a “**Negative Input**”-AND gate.
- Other important points include:
 - It is often easier to approach a problem by **breaking the longest (uppermost) bar** before breaking any bars under it
 - **Never** attempt to break **two bars** in **one** step!
 - Complementation bars function as **grouping** symbols.
 - When a bar is broken, the terms **underneath** it must remain **grouped**.
 - **Parentheses** may be placed around these grouped terms as a help to **avoid** changing precedence.

Exercise

Prove the equivalency of the following expressions:

1. $\overline{A + \overline{BC}}$

2. $\overline{\overline{AB} + \overline{A + BC}}$

Questions?

