
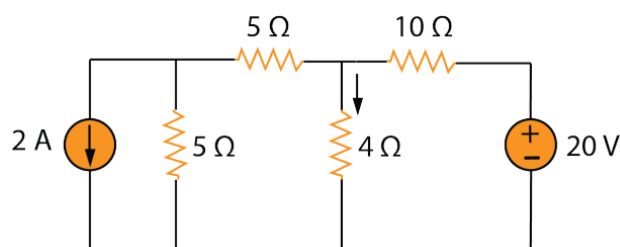


Topic 3: Circuit Theorems

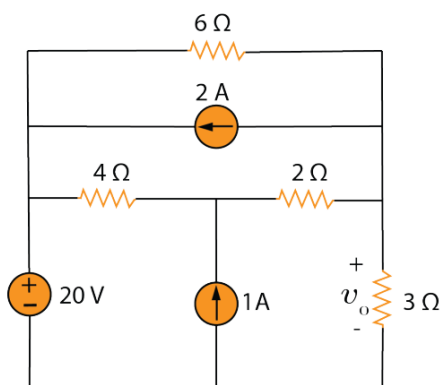
1. Using *source transformation*, find the current of the $4\ \Omega$ resistor of the following circuit.



2. Find the voltage across the $3\ \Omega$ resistor using the *superposition theorem* of the following circuit.




3. Consider the following circuit.

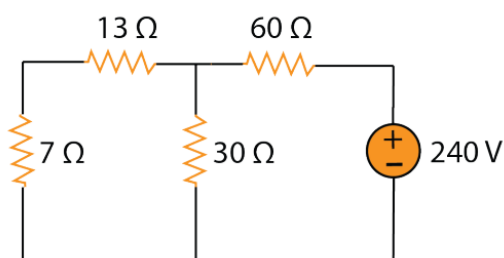


- (a) Determine the Thevenin equivalent as seen by the $7\ \Omega$ resistor.

(b) Calculate the current through the $7\ \Omega$ resistor.

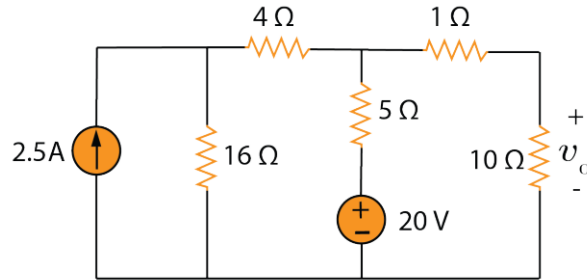4. Calculate the voltage v_o in the following circuit using *Thevenin's Theorem*.



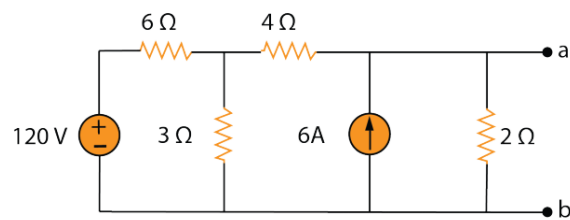5. Calculate the Norton equivalent as seen by terminals a-b.



6. Find the *maximum power* that can be delivered to the resistor R of the following circuit.

