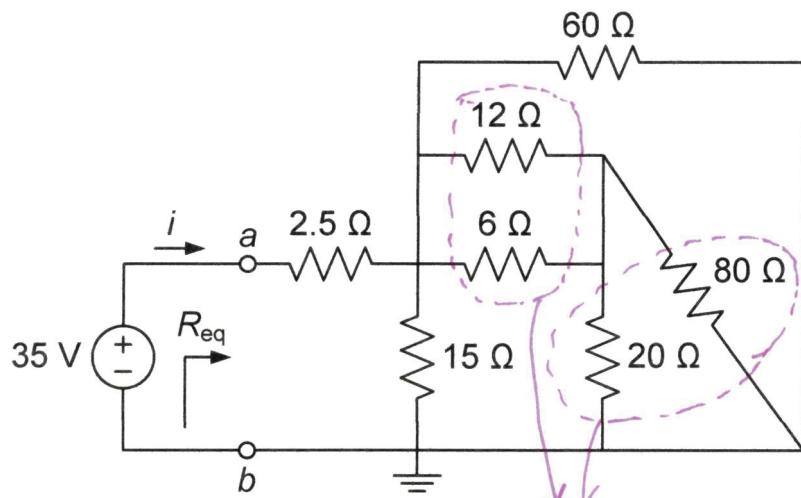


QUESTION 1 [20 marks]

(i) For the circuit shown in Figure 1,

- Calculate the equivalent resistance R_{eq} as seen from terminals a-b.
- Find the current i through the network using the result of part (a).




a)


$$20 \parallel 80 = \frac{20 \times 80}{100} = \frac{160}{10} = 16\Omega$$

Figure 1
Parallel


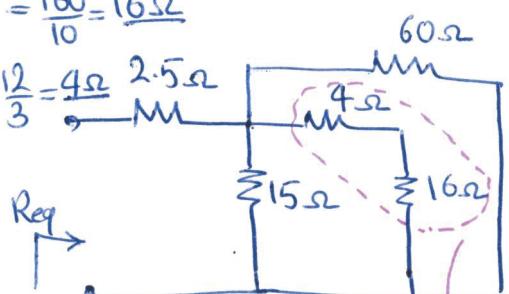
$$6 \parallel 12 = \frac{6 \times 12}{18} = \frac{12}{3} = 4\Omega$$



$$4 + 16 = 20\Omega$$

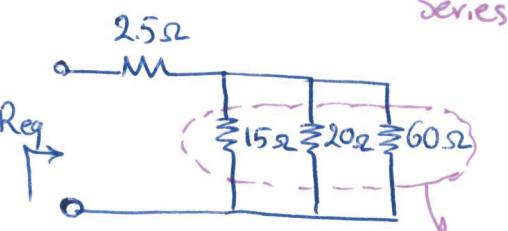
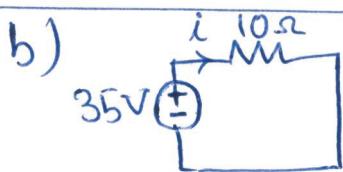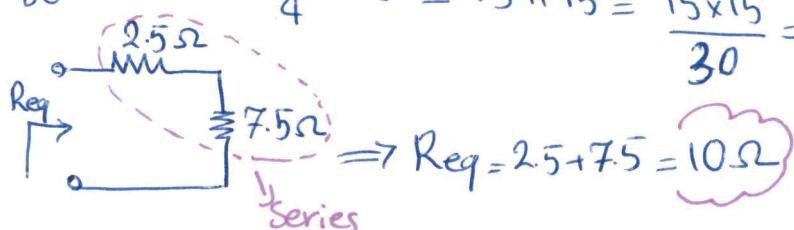
$$60 \parallel 20 \parallel 15 = \left(\frac{60 \times 20}{80} \right) \parallel 15 = \frac{60}{4} \parallel 15 = 15 \parallel 15 = \frac{15 \times 15}{30} = \frac{15}{2} = 7.5\Omega$$



$$i = \frac{V}{R} = \frac{35}{10} = 3.5\text{ A}$$

Ohm's Law

QUESTION 2 [40 marks]

(i) [24 marks] For the circuit shown in Figure 2,

- [10 marks] Apply nodal analysis to obtain the node voltage at nodes v_1 and v_2 , and show that $v_1 = 20 \text{ V}$ and $v_2 = 12 \text{ V}$
- [12 marks] Calculate all the powers absorbed/supplied by resistors and sources and specify which element supplies power and which element absorbs power.
- [2 marks] Verify the law of conservation of energy for this circuit.

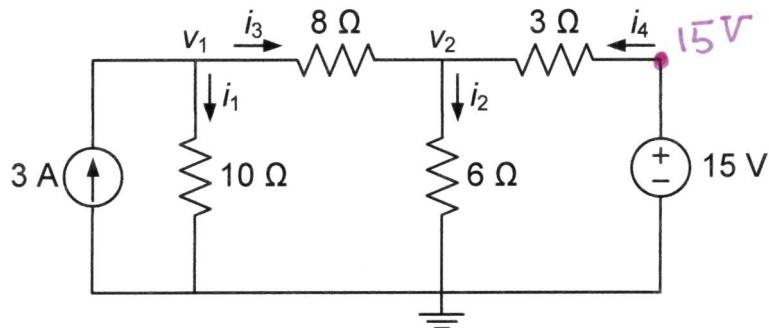


Figure 2

a)

$$\text{KCL at } v_1: 3 = \frac{v_1}{10} + \frac{v_1 - v_2}{8} \quad (\text{based on directions of } i_1 \text{ and } i_3)$$

$$\xrightarrow{\times 40} 120 = 4v_1 + 5v_1 - 5v_2 \rightarrow 9v_1 - 5v_2 = 120$$

$$\text{KCL at } v_2: \frac{v_1 - v_2}{8} + \frac{15 - v_2}{3} = \frac{v_2}{6} \quad (\text{based on directions of } i_2, i_3, i_4)$$

$$\xrightarrow{\times 24} 3v_1 - 3v_2 + 8 \times 15 - 8v_2 = 4v_2 \rightarrow 3v_1 - 15v_2 = -120 \xrightarrow{\times \frac{1}{3}}$$

$$\rightarrow v_1 - 5v_2 = -40$$

$$\textcircled{I} \rightarrow v_1 = 5v_2 - 40$$

\textcircled{II}

$$\rightarrow 9(5v_2 - 40) - 5v_2 = 120$$

$$\rightarrow 40v_2 = 480 \rightarrow v_2 = \frac{480}{40} \rightarrow v_2 = 12 \text{ V}$$

$$\begin{cases} \textcircled{I} & 9v_1 - 5v_2 = 120 \\ \textcircled{II} & v_1 - 5v_2 = -40 \end{cases}$$

$$\rightarrow 45v_2 - 360 - 5v_2 = 120 \rightarrow v_1 = 5 \times 12 - 40 = 60 - 40 = 20 \text{ V}$$

$$\rightarrow v_1 = 20 \text{ V}$$

b)

$$P = \frac{V^2}{R} \rightarrow 10 \Omega \rightarrow P_{10} = \frac{v_1^2}{10} = \frac{20^2}{10} = 40 \text{ W absorbed}$$

$$8 \Omega \rightarrow P_8 = \frac{(v_1 - v_2)^2}{8} = \frac{(20 - 12)^2}{8} = \frac{8^2}{8} = 8 \text{ W absorbed}$$

$$6 \Omega \rightarrow P_6 = \frac{v_2^2}{6} = \frac{12^2}{6} = 24 \text{ W absorbed}$$

$$3 \Omega \rightarrow P_3 = \frac{(15 - v_2)^2}{3} = \frac{(15 - 12)^2}{3} = \frac{3^2}{3} = 3 \text{ W absorbed}$$

$$3 \text{-A Source: } P_{3A} = v_1 \times 3 = 20 \times 3 = 60 \text{ W Supplied (or -60W)}$$

$$15 \text{-V Source: } P_{15V} = 15 \times i_4 = 15 \times (15 - v_2) = 15 \times \left(\frac{15 - 12}{3}\right) = 15 \text{ W Supplied (or -15W)}$$

c) Conservation of energy $\sum P = 0$

$$P_{10} + P_8 + P_6 + P_3 = P_{3A} + P_{15V}$$

$$40 + 8 + 24 + 3 = 60 + 15$$


$$75 \text{ W} = 75 \text{ W}$$

Absorbed Supplied

QUESTION 2

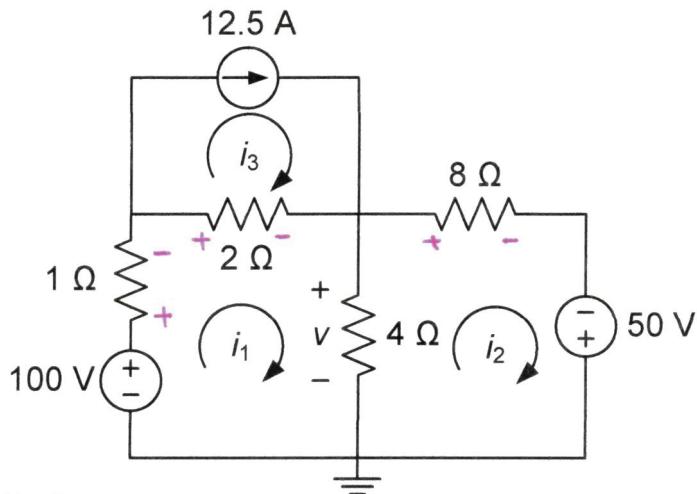(ii) [16 marks] For the circuit shown in Figure 3,

- (10 marks) Apply mesh analysis to obtain the mesh currents i_1 , i_2 and i_3 , and show that $i_1 = 25 \text{ A}$ and $i_2 = 12.5 \text{ A}$
- (2 marks) Find the voltage v across 4Ω resistor.
- (4 marks) Calculate the power of the 50-V voltage source and explain whether it supplies or absorbs power.



a) mesh 3: $i_3 = 12.5 \text{ A}$ ①

Figure 3

$\xrightarrow{\text{KVL in mesh 1}} -100 + 1i_1 + 2(i_1 - i_3) + 4(i_1 - i_2) = 0$
 $\xrightarrow{\text{②}} i_1 + 2i_1 - \underline{2 \times 12.5} + 4i_1 - 4i_2 = 100 \rightarrow \underline{7i_1 - 4i_2 = 125}$

$\xrightarrow{\text{KVL in mesh 2}} -50 - 4(i_1 - i_2) + 8i_2 = 0 \rightarrow -4i_1 + 4i_2 + \underline{8i_2 = 50}$
 $\rightarrow -4i_1 + 12i_2 = 50 \xrightarrow{\times -\frac{1}{2}} \underline{2i_1 - 6i_2 = -25}$

$\xrightarrow{\text{④}} i_1 = \frac{1}{2}(6i_2 - 25) = 3i_2 - 12.5 \xrightarrow{\text{①}} 7(3i_2 - 12.5) - 4i_2 = 125 \rightarrow 21i_2 - 87.5 - 4i_2 = 125$
 $\rightarrow 17i_2 = 212.5 \rightarrow i_2 = \frac{212.5}{17} \rightarrow i_2 = 12.5 \text{ A}$ ②
 $i_1 = \frac{50}{2} \rightarrow i_1 = 25 \text{ A}$


b) $v = 4(i_1 - i_2) = 4(25 - 12.5) = 4 \times 12.5 \Rightarrow v = 50 \text{ V}$

c) $P = v \cdot i = 50 \times i_2 = 50 \times 12.5 = 625 \text{ W supplied}$
 (or -625W)


QUESTION 3 [20 marks]

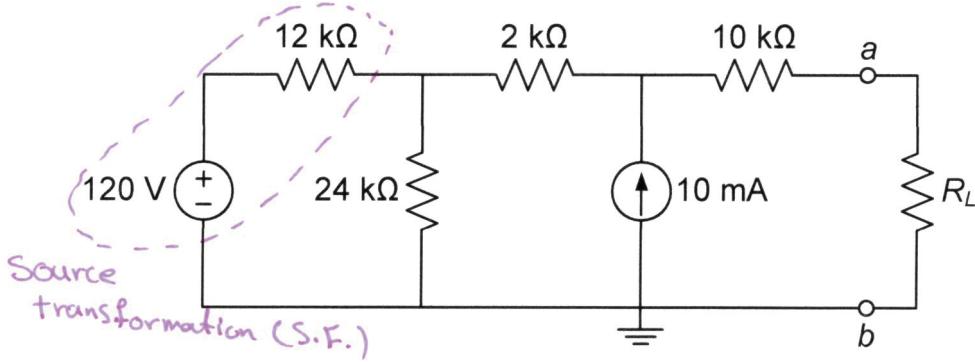(i) [10 marks] For the circuit shown in Figure 4,

- (6 marks)** Use source transformation to obtain Thevenin equivalent circuit from terminals $a-b$ and draw the Thevenin equivalent circuit.
 - (4 marks)** Determine the value of load resistance R_L for maximum power transfer, and then calculate the maximum power that can be delivered to R_L .


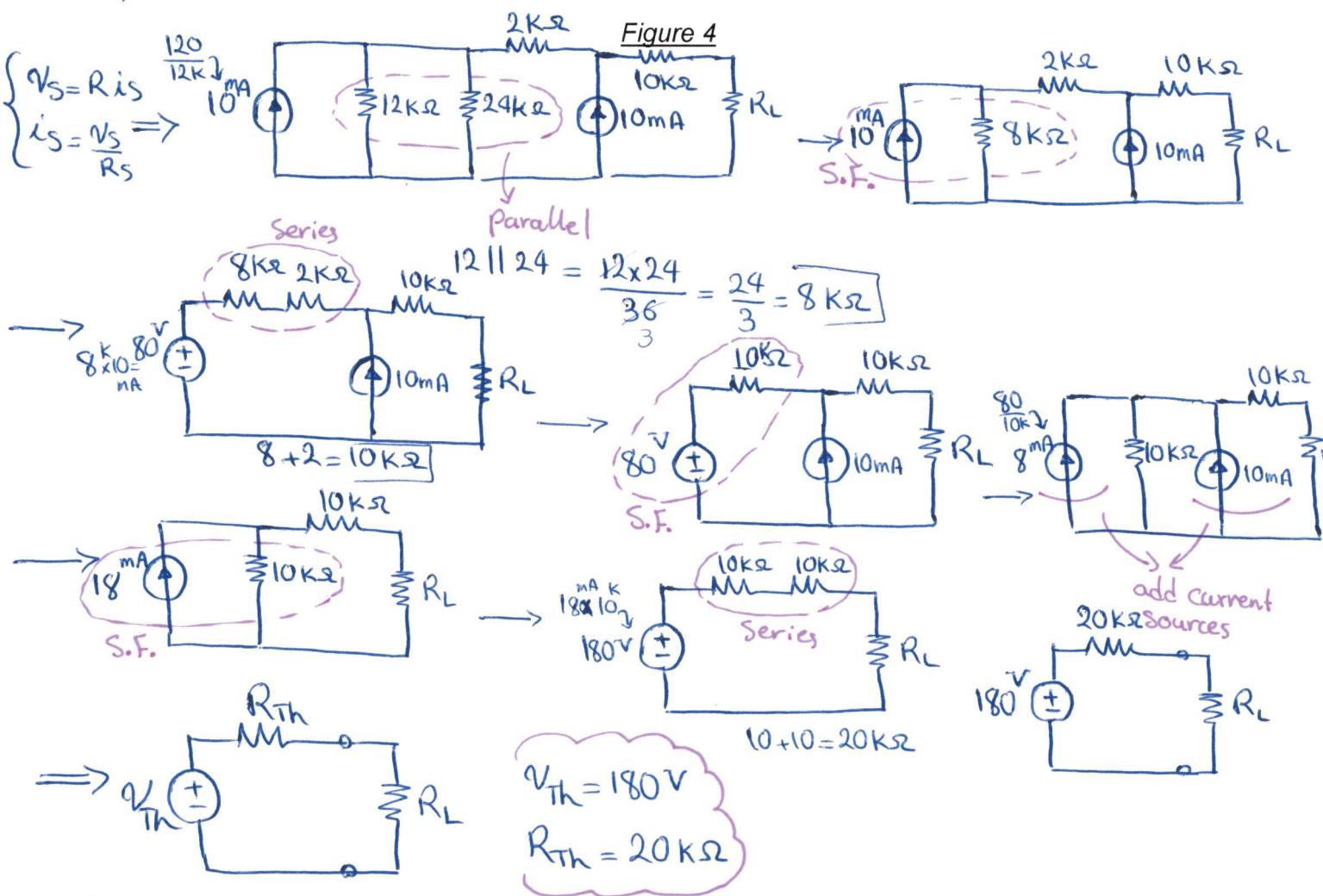
$$\left\{ \begin{array}{l} V_S = R_i S \\ i_S = \frac{V_S}{R_S} \Rightarrow \end{array} \right.$$




b) For power transfer $\rightarrow R_L = R_{Th}$ $\Rightarrow R_L = 20\text{ k}\Omega$

$$P_{\max} = \frac{V_{Th}^2}{4R_{Th}} = \frac{(180)^2}{4 \times 20 \times 10^3} = 405 \text{ mW}$$

QUESTION 3

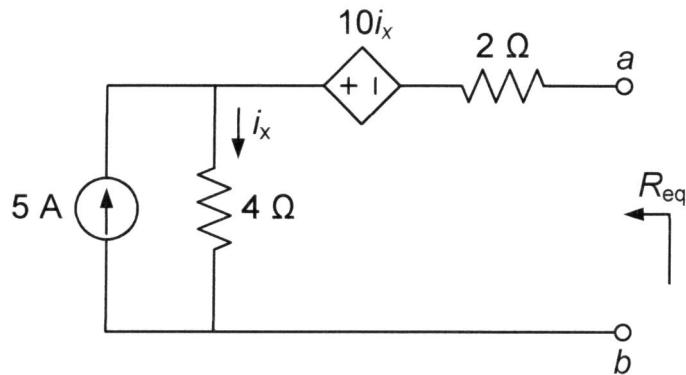
(ii) [10 marks] Find the equivalent resistance R_{eq} in the circuit given in Figure 5.



Dependent source → Connect an external Figure 5
Voltage or current source

First approach: 1-V

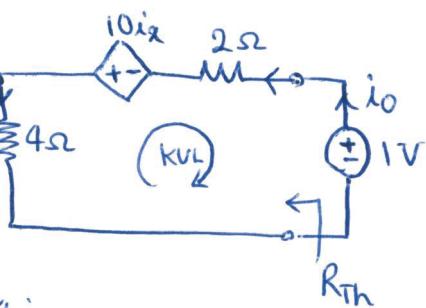* Connect a Voltage Source $V_0 = 1V$
disconnect 5-A source



$$R_{Th} = \frac{V_o}{i_o} = \frac{1}{i_o}$$


$$\begin{aligned} i_x &= i_o \\ \Rightarrow \text{KVL: } -4i_x + 10i_x - 2i_x + 1 &= 0 \rightarrow 4i_x + 1 = 0 \\ \rightarrow 4i_x &= -1 \rightarrow i_x = -\frac{1}{4} \text{ A} \end{aligned}$$

$$i_o = i_x = -\frac{1}{4} \text{ A} \quad \Rightarrow R_{Th} = \frac{1}{-\frac{1}{4}} = -4 \Omega$$

Second approach:

* Connect a 1-A Current Source

$i_o = 1A$
disconnect 5-A source

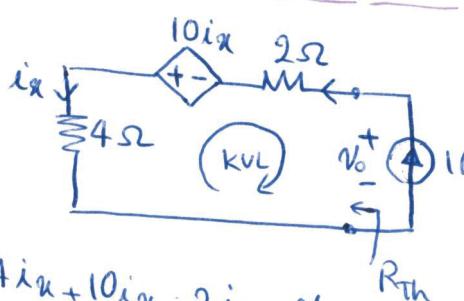


$$R_{Th} = \frac{V_o}{i_o} = \frac{V_o}{1}$$

$$\begin{aligned} i_x &= 1A \\ \Rightarrow \text{KVL: } -4i_x + 10i_x - 2i_x + V_o &= 0 \rightarrow 4i_x + V_o = 0 \\ \rightarrow 4 + V_o &= 0 \rightarrow V_o = -4V \end{aligned}$$

$$R_{Th} = \frac{-4}{1} = -4 \Omega$$

QUESTION 4 [20 marks]

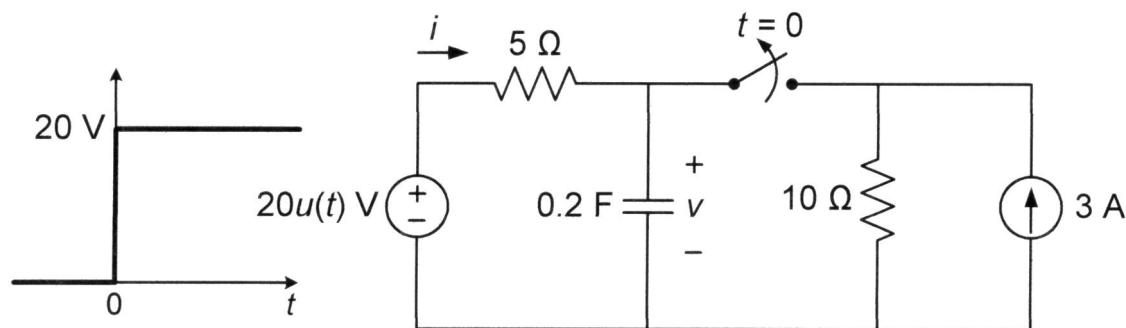- (i) In the circuit shown in Figure 6, the switch has been closed for a long time before it is opened at $t = 0$. The voltage source is given a step function.
- Find the initial voltage $v(0^-)$ across the capacitor under steady-state condition.
 - Calculate the initial energy $w_c(0)$ stored in the capacitor.
 - Find the final voltage $v(\infty)$ across the capacitor under steady-state condition.
 - Derive an expression for the voltage of the capacitor $v(t)$ for all time (i.e., for both $t < 0$ and $t > 0$).
 - Sketch the obtained voltage $v(t)$ in part (d) as a function of time.
 - Derive an expression for the current $i(t)$ through the 5Ω resistor for all time (i.e., for both $t < 0$ and $t > 0$).




$$a) \quad 20u(t) = \begin{cases} 0 & t < 0 \\ 20 & t > 0 \end{cases}$$

Step input Voltage

Figure 6

$t < 0$ Circuit before the change

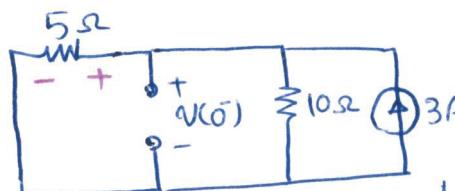

$$V(0^-) = V_{5\Omega} \text{ (parallel)}$$

Circuit is in steady-state
Capacitor \rightarrow open circuit


$$\text{S.T. } 5\Omega \parallel 10\Omega \Rightarrow V(0^-) = 3 \times 10 = 30V$$

$$\text{Voltage division} \quad V(0^-) = \frac{5}{5+10} \times 30 = 10V$$

$$b) \quad w_c(0) = \frac{1}{2} C V^2(0) \rightarrow V(0) = V(0^-) \Rightarrow w_c(0) = \frac{1}{2} \times 0.2 \times 10^2 = 10J$$

c) $t > 0$ Circuit after the change

No sudden change in Capacitor Voltage

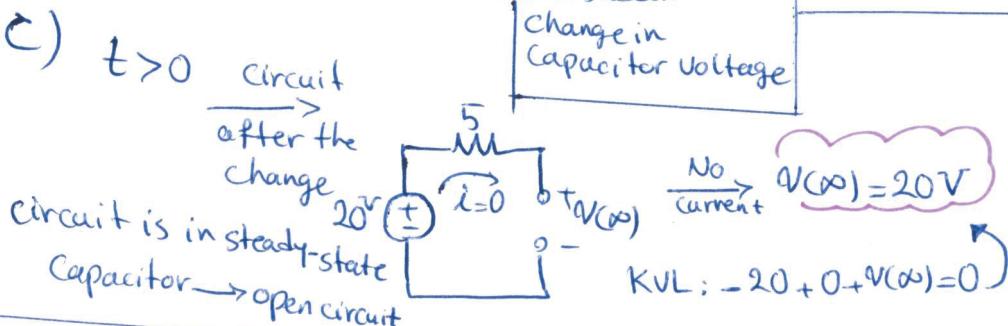

$$V(\infty) = 20V$$

$$d) \quad V(t) = \begin{cases} V(0^-) & t < 0 \\ V(\infty) + (V(0^+) - V(\infty)) e^{-\frac{t}{RC}} & t > 0 \end{cases}$$

for all time

$$V(0^+) = V(0) = V(0^-) = 10V$$


no sudden change after change



$$T = R_{Th,\infty} \cdot C$$

Q4

Continued

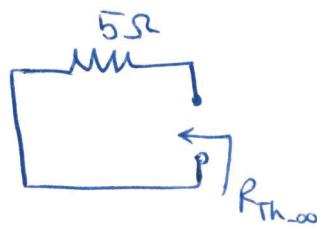


$R_{Th,\infty}$: Thevenin equivalent resistance

in the circuit from capacitor terminals
after changes.

$$R_{Th,\infty} = 5\Omega \rightarrow T = 5 \times 0.2 = 1s$$

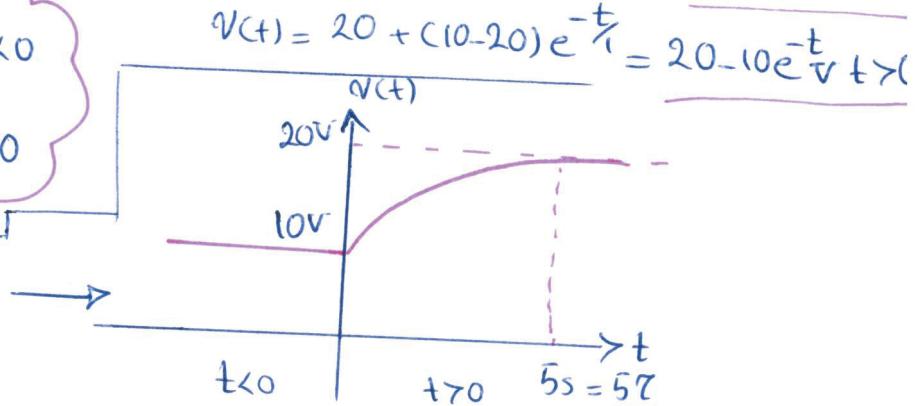
$$\Rightarrow V(t) = \begin{cases} 10V & t < 0 \\ 20 - 10e^{-t}V & t > 0 \end{cases}$$



e)

f) $t < 0$


Circuit
before the
change (Steady
state)

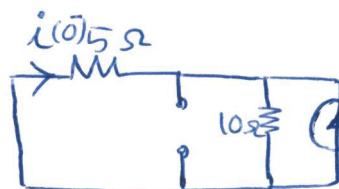

$$i(0) = -\frac{10}{5+10} \times 3 = -\frac{10}{5} = -2A$$

$t > 0$

Circuit
after the
change

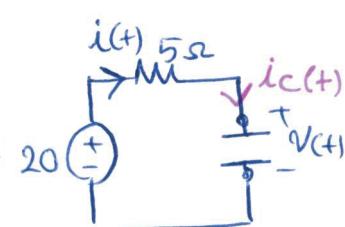

Current
division


$$i(t) = i_c(t) = C \frac{dV(t)}{dt} = 0.2 \times (-10)(-1)e^{-t}$$

* First approach:

$$i(t) = \begin{cases} -2A & t < 0 \\ 2e^{-t}A & t > 0 \end{cases}$$

$$\rightarrow i(t) = 2e^{-t}A$$

* Second approach:

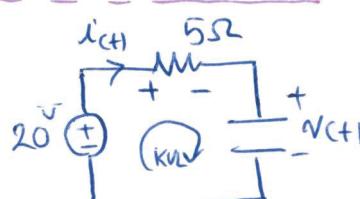

$$KVL: -20 + 5i(t) + V(t) = 0 \quad t > 0$$

$$\Rightarrow i(t) = \frac{20 - V(t)}{5} \quad t > 0$$

$$\Rightarrow i(t) = \begin{cases} -2A & t < 0 \\ 2e^{-t}A & t > 0 \end{cases}$$

$$\Rightarrow i(t) = \frac{20 - 20 + 10e^{-t}}{5} = \frac{2e^{-t}A}{5} \quad t > 0$$