

Faculty of Engineering

School of Electrical Engineering and Telecommunications

# ELEC 1111 – Topic 2

## Kirchhoff's Laws, Nodal & Mesh Analysis

**Dr. Inmaculada (Inma) Tomeo-Reyes**

Lecturer

School of Electrical Engineering and Telecommunications, UNSW

# Topic 2 Content

## **This lecture covers:**


- Nodes, Branches and Loops/Meshes
- Kirchhoff's Laws
- Series and Parallel Connection of Circuit Elements
- Voltage and Current Division
- Nodal Analysis
- Mesh Analysis

**Corresponds to Chapters 2  
and 3 of your textbook**
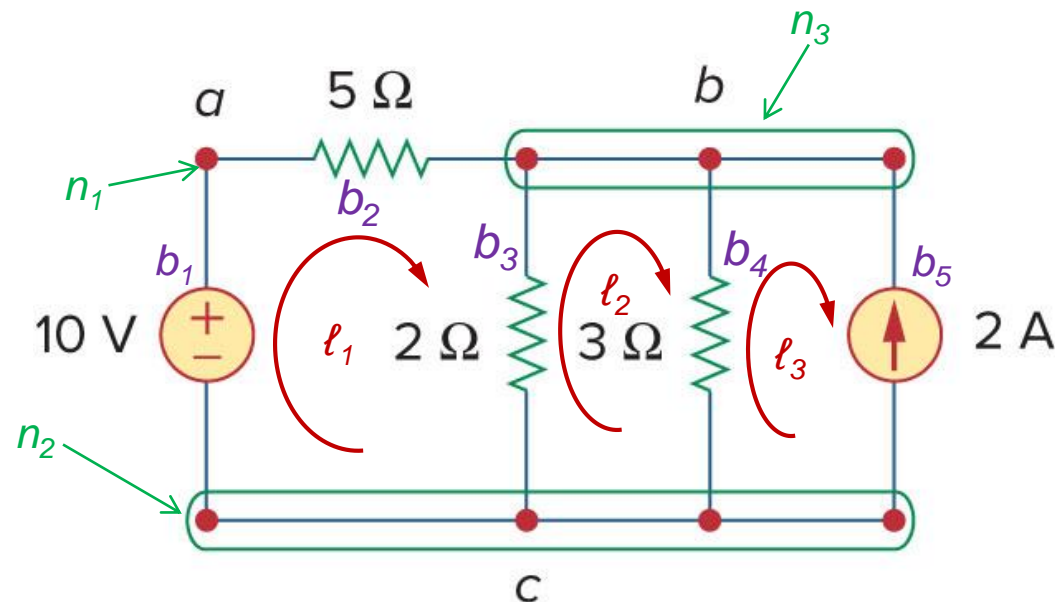
# Nodes, branches and loops/meshes

- Circuit elements can be interconnected in multiple ways.
- To understand this, we need to be familiar with some network topology concepts:
  - A **branch** represents a **single element** such as a voltage source or a resistor.
  - A **node** is the **point of connection** between two or more branches.
  - A **loop** is any **closed path** in a circuit.
  - A **mesh** is a loop that contains **no** other loop.

$n_k = \text{node } k$   
 $b_k = \text{branch } k$   
 $\ell_k = \text{loop/mesh } k$





# Series and parallel

- Two or more elements are in **series** if they **exclusively share a single node** and consequently carry the **same current**.
- Two or more elements are in **parallel** if they are connected to the **same two nodes** and consequently have the **same voltage** across them.


In the following example:

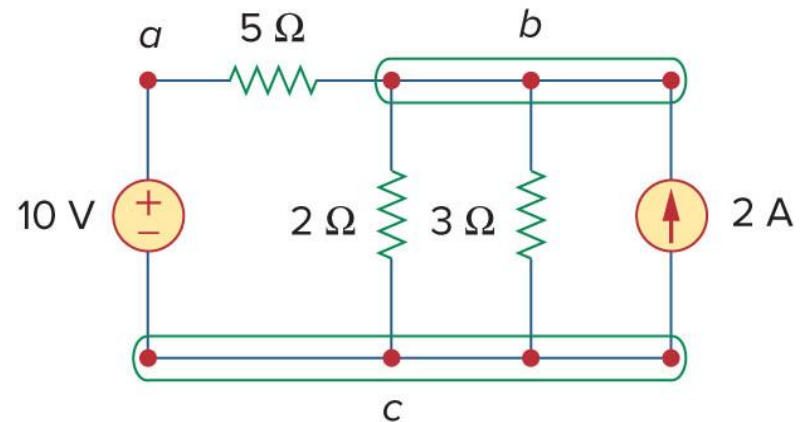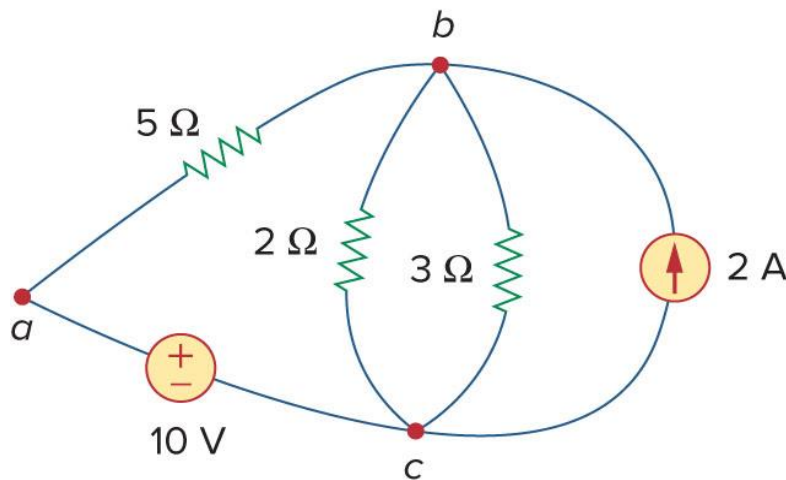- Series:  $5\ \Omega$  resistor and  $10\text{ V}$  source.
- Parallel:  $2\text{ A}$  source and  $3\ \Omega$  and  $2\ \Omega$  resistors.


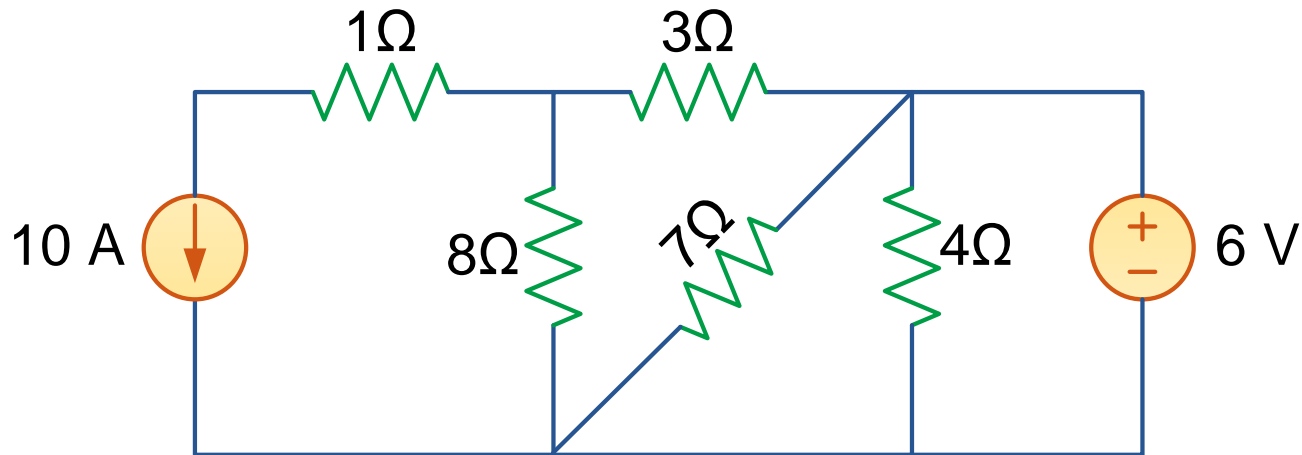
# Exercise

- Count the number of branches, nodes, and meshes.
- Identify series and parallel elements.





# Kirchhoff's Current Law (KCL)

- The **algebraic sum of all currents entering a node is zero.**

$$\sum_{n=1}^N i_n = 0$$


$N$  is the number of branches connected to the node

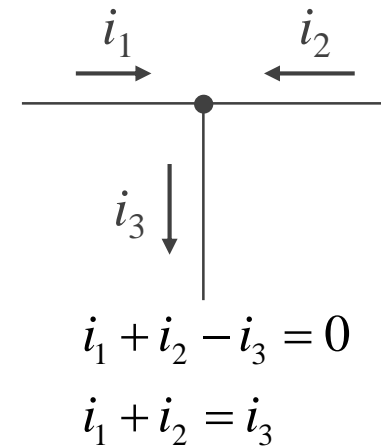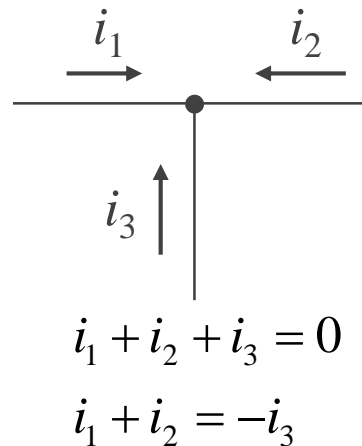- You may consider the currents **entering the node** to be **positive** and those **leaving the node** to be **negative** or vice versa.
- You may also consider that the **sum of currents entering the node is equal** to the **sum of currents leaving the node**.



# Exercise

Given the following circuit:

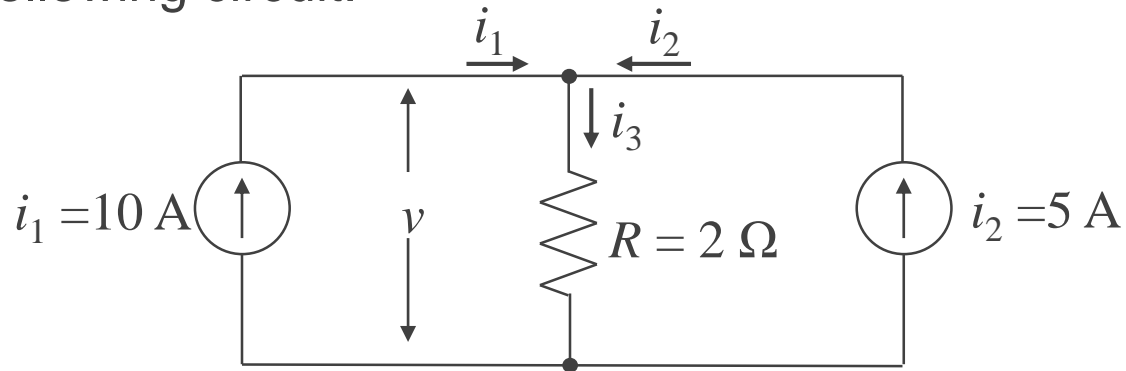

- How much current flows through the resistor?
- What is the voltage across the resistor?



# Kirchhoff's Voltage Law (KVL)


- The **algebraic sum of all voltage drops around a closed path** (or a loop) is **zero**.

$$\sum_{m=1}^M v_m = 0$$

$M$  is the number of voltage drops in the loop


- You may **start from any node** in the loop and go around the loop **clockwise (CW)** or **counterclockwise (CCW)**.
- Use the **sign** of the terminal that you **first encounter** as you go around the loop.

$$-v_1 + v_2 + v_3 - v_4 + v_5 = 0$$

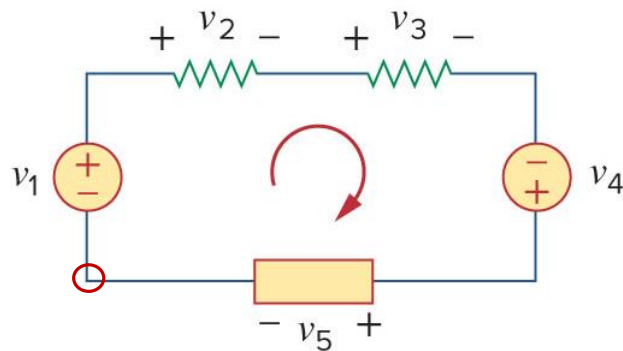

or


$$v_4 - v_3 - v_2 + v_1 - v_5 = 0$$

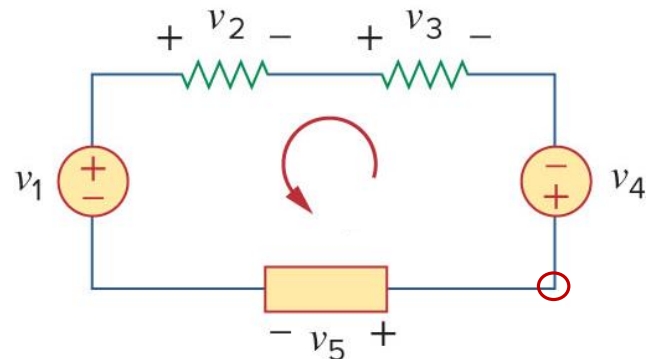




# Exercise

Given the following circuit:

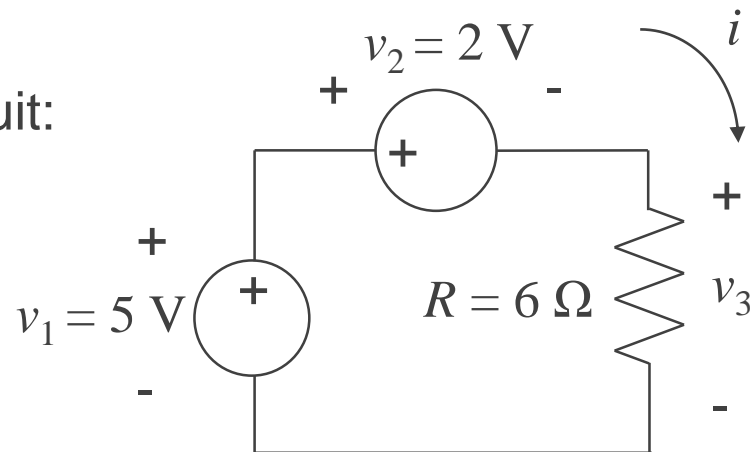

- What is the voltage across the resistor?
- What is the current in the loop?

# Voltage sources in series

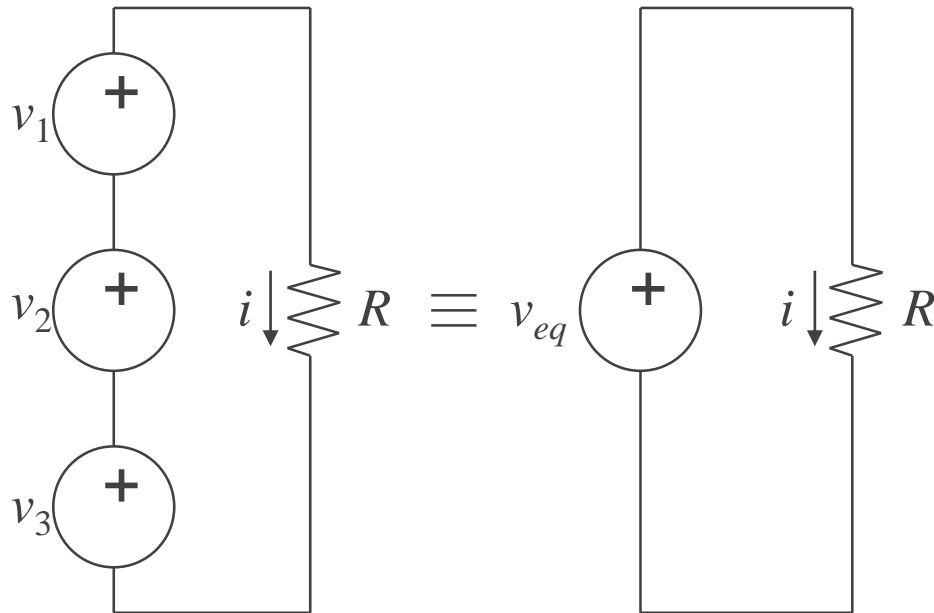

- Kirchoff's Voltage Law (KVL) gives:

$$-v_1 - v_2 - v_3 + iR = 0$$

$$(v_1 + v_2 + v_3) = iR$$


- Equivalent voltage:

$$v_{eq} = iR$$

$$v_{eq} = v_1 + v_2 + v_3$$

- Voltage sources in series are summed.

# Resistors in series

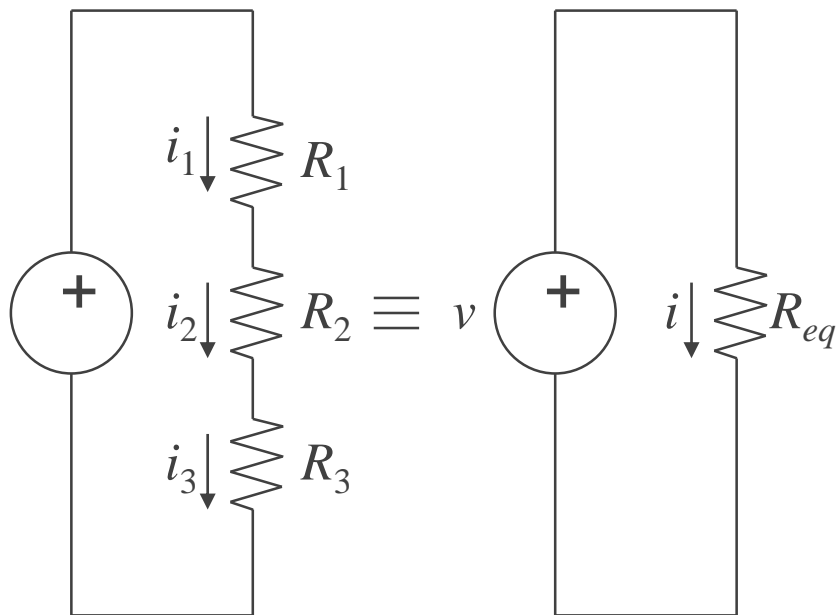

- Current is the same in all resistors:

$$i_1 = i_2 = i_3 = i$$

- KVL gives:

$$-v + iR_1 + iR_2 + iR_3 = 0$$

$$v = i(R_1 + R_2 + R_3)$$

- Equivalent resistance:


$$v = iR_{eq}$$

$$R_{eq} = R_1 + R_2 + R_3$$

- Resistors in series are summed.

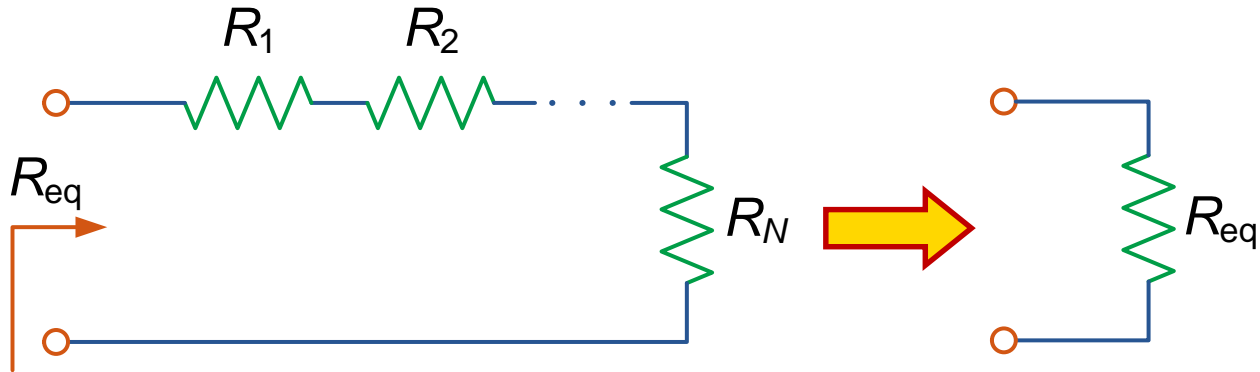
# Resistors in series

- The **equivalent resistance** of any number of **series resistors** is the **sum** of the **individual resistances**.




$$R_{eq} = R_1 + R_2 + \cdots + R_N = \sum_{n=1}^N R_n$$

# Current sources in parallel

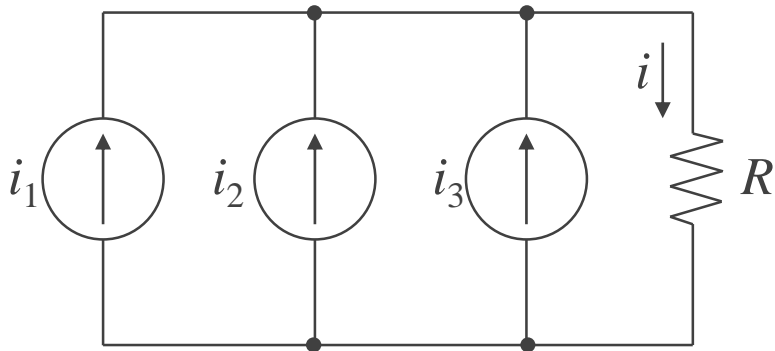

|||

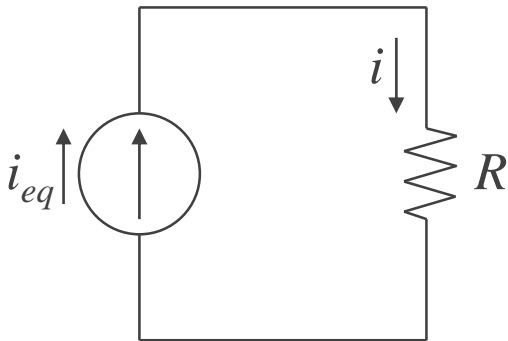

- We can find the current in the resistor by KCL:


$$i_1 + i_2 + i_3 = i$$

- The equivalent current source would put the same current through the resistor, so:


$$i_{eq} = i_1 + i_2 + i_3$$

- Current sources in parallel are summed.

# Resistors in parallel

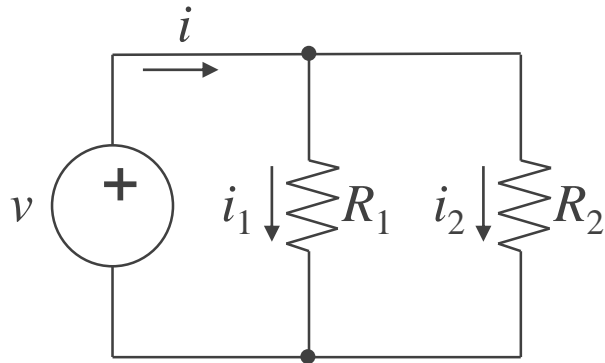

|||

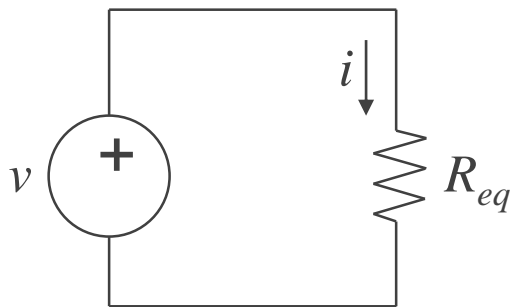

- Voltages across the resistors are the same:

$$v = i_1 R_1 = i_2 R_2$$

Therefore:

$$i_1 = \frac{v}{R_1}; i_2 = \frac{v}{R_2}$$

- Using KCL:


$$i = i_1 + i_2 = v \left( \frac{1}{R_1} + \frac{1}{R_2} \right)$$

$$\frac{i}{v} = \frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$R_{eq} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}} = \frac{R_1 R_2}{R_1 + R_2}$$
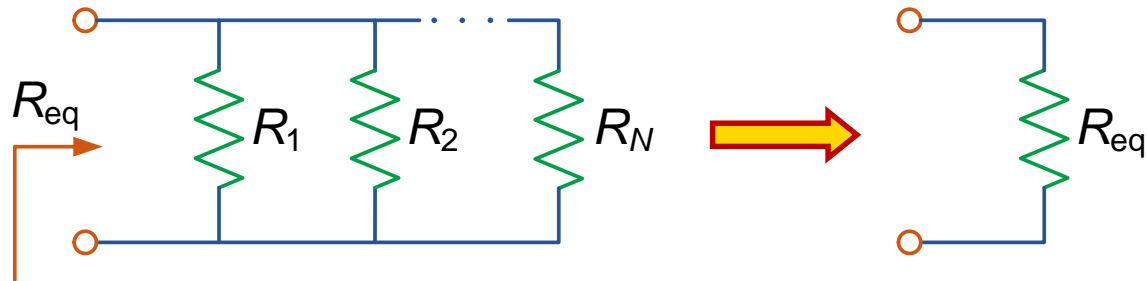
# Resistors in parallel

- The **reciprocal** of the **equivalent resistance** of any number of **parallel resistors** is the **sum** of the **individual reciprocal resistances**.



$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_N}$$

or

$$G_{eq} = G_1 + G_2 + \dots + G_N$$


or

$$R_{eq} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_N}}$$



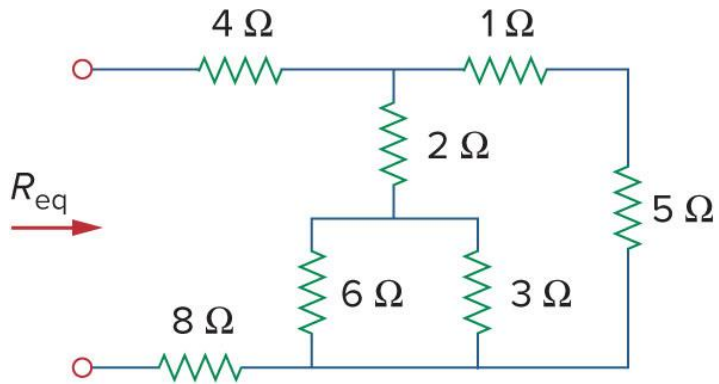
# Exercise

Find the equivalent resistance  $R_{eq}$ .


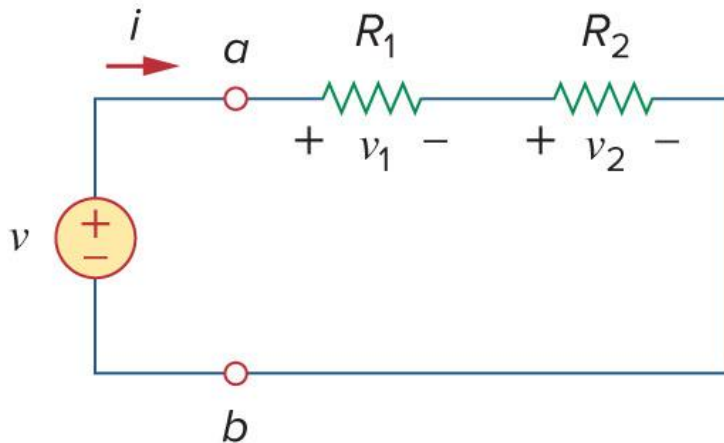
# Voltage divider

- A voltage divider is a simple circuit that divides a voltage **in proportion** to the **series resistances** (the higher the resistance, the higher the voltage).



- The current through the resistors is:

$$i = \frac{v}{R_1 + R_2}$$


- The voltage across the resistors:

$$v_1 = iR_1; v_2 = iR_2$$

$$v_1 = v \frac{R_1}{R_1 + R_2}; v_2 = v \frac{R_2}{R_1 + R_2}$$
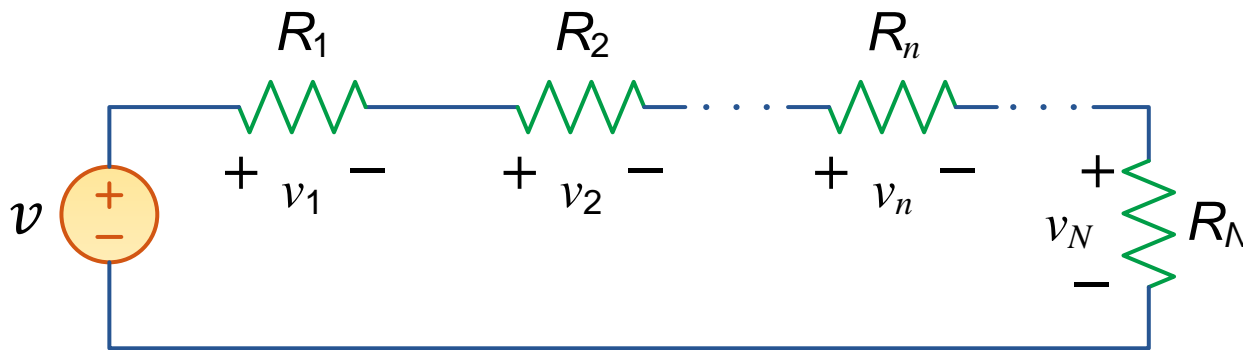
# Voltage divider

- In general, the **voltage drop** across the  $n^{\text{th}}$  resistor in a **voltage divider** with  $N$  **series resistors** is obtained as follows:




$$v_n = v \frac{R_n}{R_1 + R_2 \cdots + R_N} = v \frac{R_n}{R_{eq}}$$

**Remark:** As long as we know the input voltage to be divided, this voltage can be provided by any element or circuit, not necessarily a voltage source.
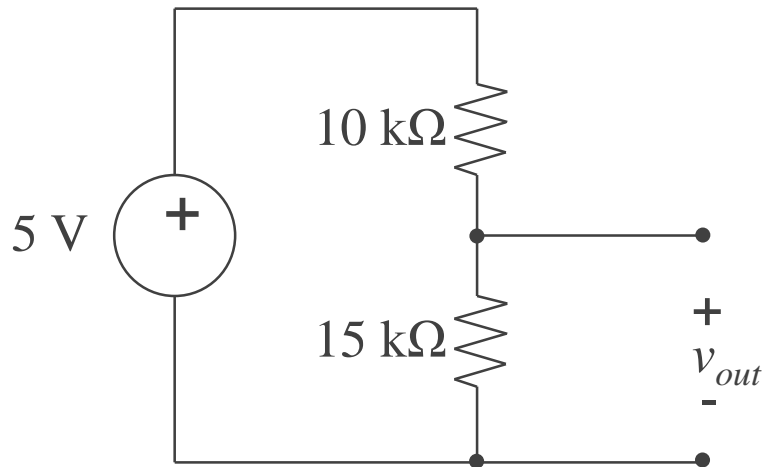
# Exercise


- Find the voltage across the 15 k $\Omega$  resistor.



$$v_n = v \frac{R_n}{R_{eq}}$$
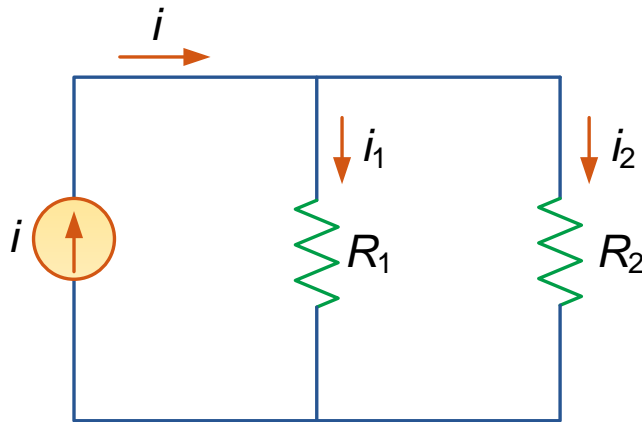
# Current divider

- A current divider is a simple circuit that divides the current among **parallel resistors** in **inverse proportion** to their **resistance** (the higher the resistance, the lower the current).



- The voltage across the resistors is:

$$v = i(R_1 \parallel R_2)$$


- The current through each resistor:

$$i_1 = \frac{v}{R_1} = i \frac{(R_1 \parallel R_2)}{R_1}$$

$$i_2 = \frac{v}{R_2} = i \frac{(R_1 \parallel R_2)}{R_2}$$
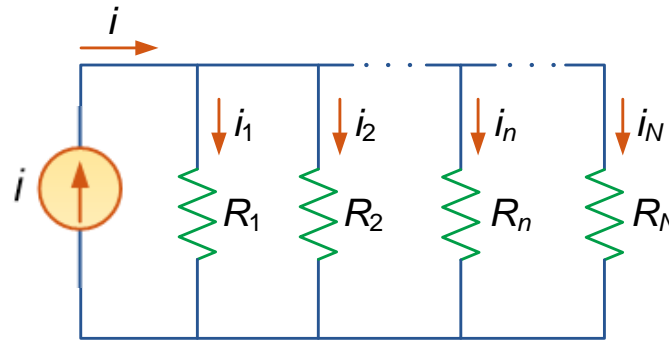
# Current divider

- In general, the **current** through the  $n^{\text{th}}$  resistor in a **current divider** with  $N$  **parallel resistors** is obtained as follows:



$$i_n = i \frac{R_1 \parallel R_2 \parallel \dots \parallel R_N}{R_n} = i \frac{R_{eq}}{R_n}$$


- If conductances are used instead of resistances, then:

$$i_n = i \frac{G_n}{G_1 + G_2 + \dots + G_N}, \text{ where } G_n = \frac{1}{R_n}$$

**Remark:** As long as we know the input current to be divided, this current can be provided by any element or circuit, not necessarily a current source.
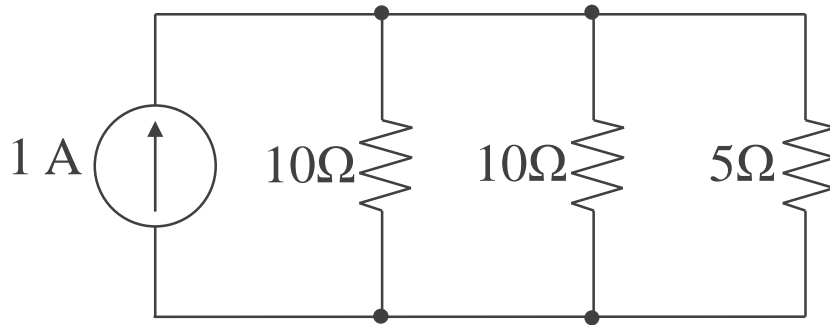
# Exercise

- Find the current in the  $5\ \Omega$  resistor.



$$i_n = i \frac{R_{eq}}{R_n}$$




# Current divider

## Specific cases


- **Short circuit:** The entire current  $i$  flows through the **smallest resistance** (short circuit), effectively bypassing  $R_1$ .

$$R_{eq} = 0$$

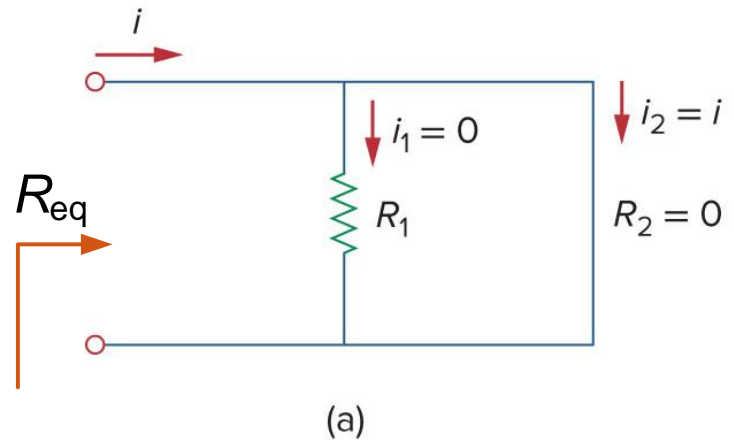


- **Open circuit:** The entire current  $i$  flows through the **smallest resistance** ( $R_1$ ).

$$R_{eq} = R_1$$

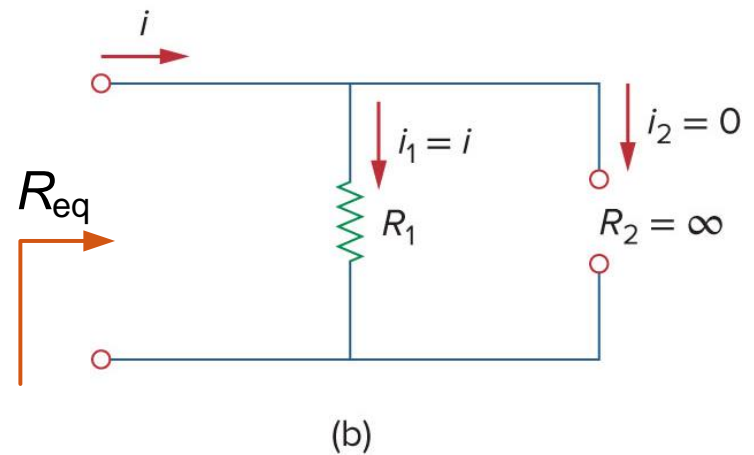

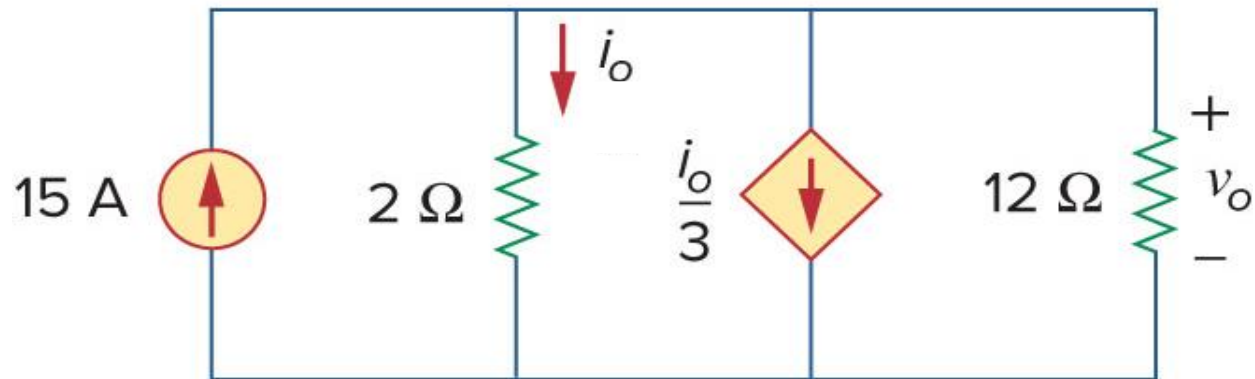
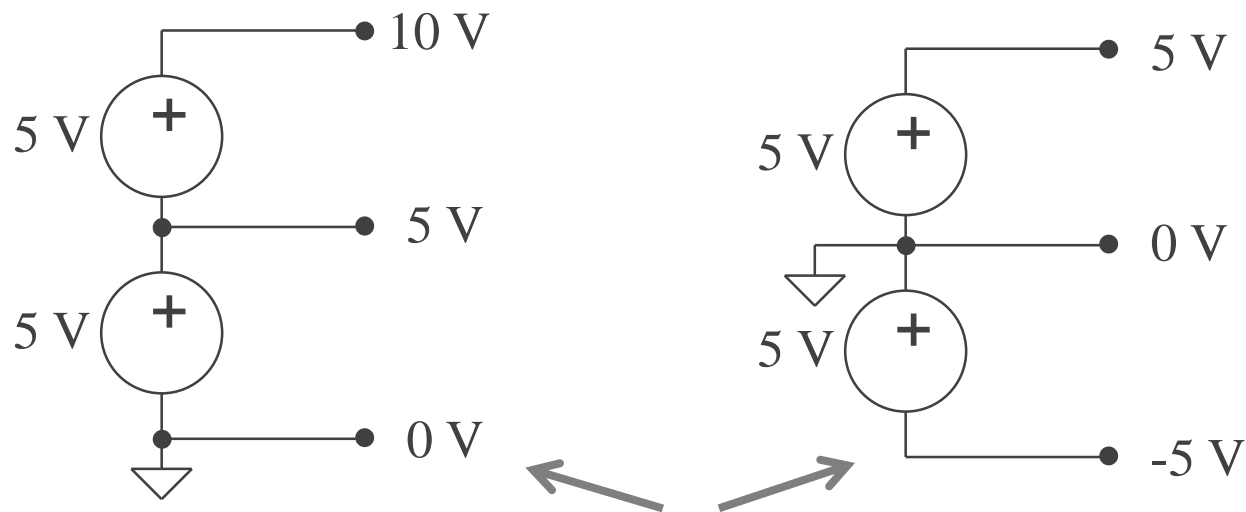
# Exercise

Find  $v_o$  and  $i_o$  in the circuit below.



# Circuit ground

- Voltage is a differential quantity, so we need a reference node, usually at zero volts.
- Any node in a circuit can be defined as zero volts.
- The **zero volt** point is referred to as the **circuit ground**.
- Symbol: 



Different choice of circuit ground leads to different voltages with respect to ground.

# Earth

- An earthed ground is literally a connection to the earth, which provides an important role in electrical safety.
- Symbol:  $\perp$



# Circuit analysis


- Using Kirchhoff's laws and Ohm's law we can analyse any circuit to determine the currents and voltages; however, this might result in many simultaneous equations.
- The challenge of formal circuit analysis is to derive the **smallest set of simultaneous equations** that completely define the operating characteristics of a circuit (voltages and currents).
- Nodal and mesh analysis are two very useful methods for analysing any circuit.
  - They are based on the systematic application of Kirchhoff's laws.

# Nodal analysis
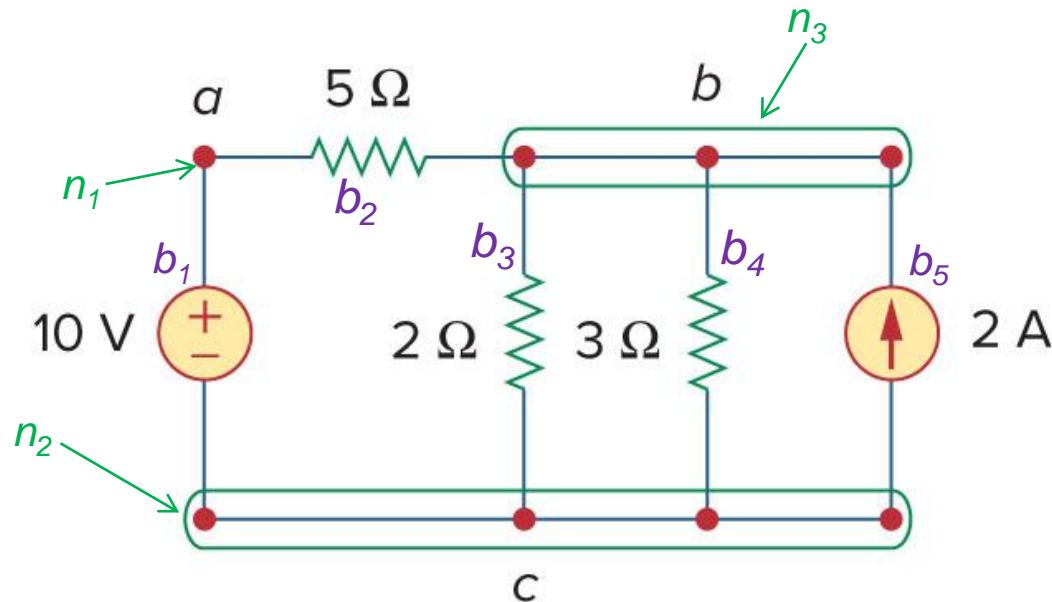
## Nodes

- A branch represents a single element such as a voltage source or a resistor.
- A node is the point of connection between two or more branches.

$n_k = \text{node } k$   
 $b_k = \text{branch } k$



# Nodal analysis

- It is based on KCL.
- We use **node voltages** (potential of each node) as the **main circuit variables**.
  - Voltages are relative to a reference node.
- Objective: To solve for these node voltages.
  - In general, an  $N$ -node circuit will need  $N-1$  voltages and  $N-1$  equations.
  - It will also require the solution of a  $N-1$  system of equations.
  - KCL will be applied at each node except for one – the *reference node*.



# Nodal analysis

## Reference node

Any node can be chosen as the reference node.

Most common choices are:

- the ground node,
- top or bottom node, or
- node connected to the highest number of branches.

# Nodal analysis

- Given a circuit with  $n$  nodes, the nodal analysis is accomplished via the following steps:

1. Select a node as the **reference node**.
2. Assign voltages  $v_1, v_2, \dots, v_n$  to the remaining  $n - 1$  nodes. These voltages are relative to the reference node.
3. Apply **KCL** to each of the  $n - 1$  non-reference nodes.
  - For resistors, use Ohm's law to express the currents in terms of node voltages. Keep in mind the passive sign convention.
4. Solve the resulting  $n - 1$  simultaneous equations to obtain the unknown node voltages.

NOTE: Always simplify the circuit before you start doing the analysis.

# Nodal analysis


Before starting, **simplify** the circuit (if possible) and identify all the nodes.

1. Choose **ground** as **reference node** ( $v_0 = 0$  V).
2. Assign voltages  $v_1$  and  $v_2$  to nodes 1 and 2.
  - Recall that:

$$v_{R_1} = v_1 - 0$$

$$v_{R_2} = v_1 - v_2$$

$$v_{R_3} = v_2 - 0$$

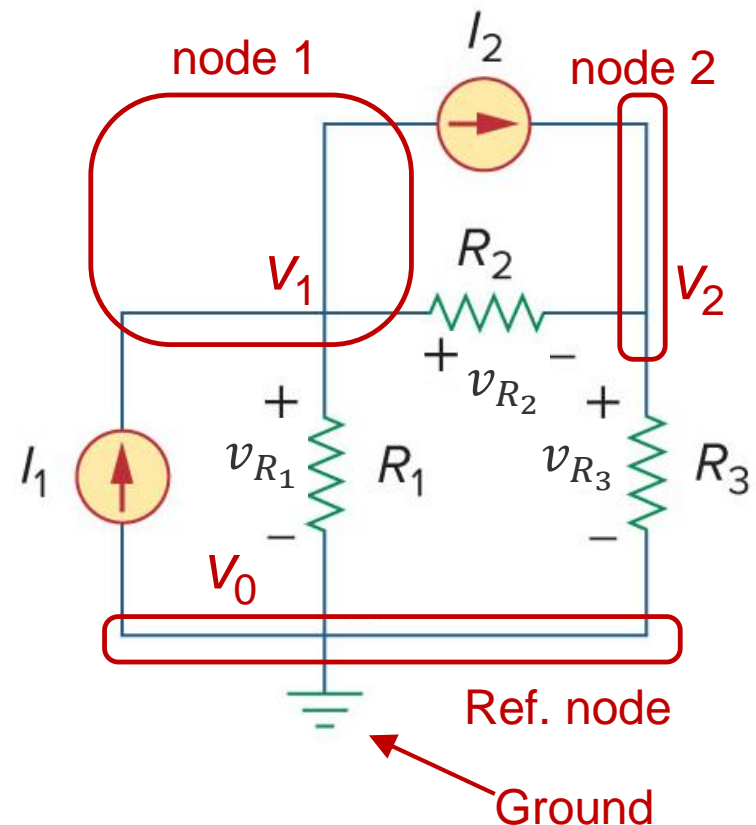

# Nodal analysis

## 3. Apply KCL to nodes 1 and 2.

node 1:  $I_1 = I_2 + i_1 + i_2$

node 2:  $I_2 + i_2 = i_3$

- For resistors, use Ohm's law to express the branch currents in terms of node voltages. Keep in mind the passive sign convention.

$$i_n = \frac{v_{R_n}}{R_n} = \frac{v_{\text{higher}} - v_{\text{lower}}}{R_n}$$


$$i_1 = \frac{v_{R_1}}{R_1} = \frac{v_1 - 0}{R_1}$$

$$i_2 = \frac{v_{R_2}}{R_2} = \frac{v_1 - v_2}{R_2}$$

$$i_3 = \frac{v_{R_3}}{R_3} = \frac{v_2 - 0}{R_3}$$

- Substitute back  $i_1$ ,  $i_2$ , and  $i_3$  into the node equations

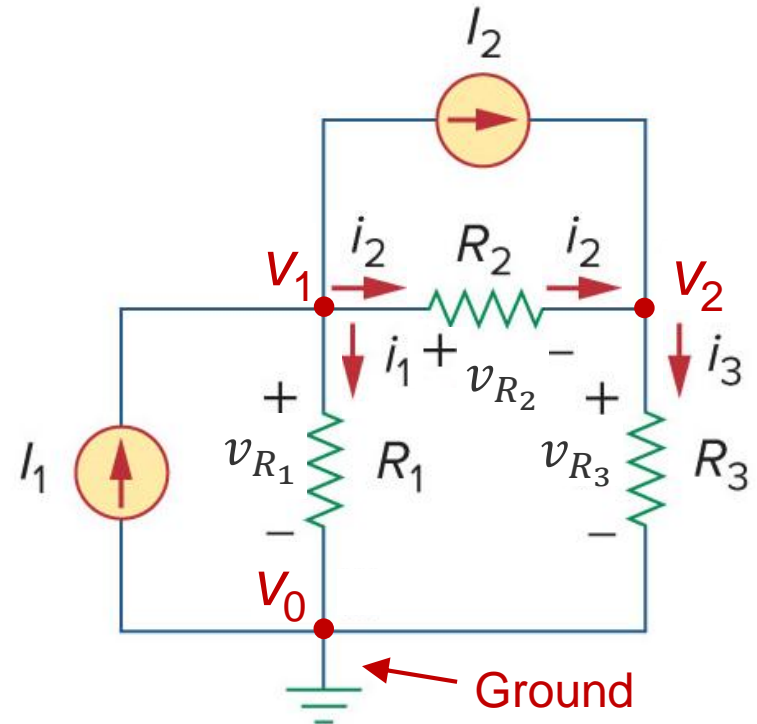
## 4. Solve simultaneous equations (for $v_1$ and $v_2$ ).



$$\begin{cases} I_1 = I_2 + \frac{v_1}{R_1} + \frac{v_1 - v_2}{R_2} \\ I_2 + \frac{v_1 - v_2}{R_2} = \frac{v_2}{R_3} \end{cases}$$
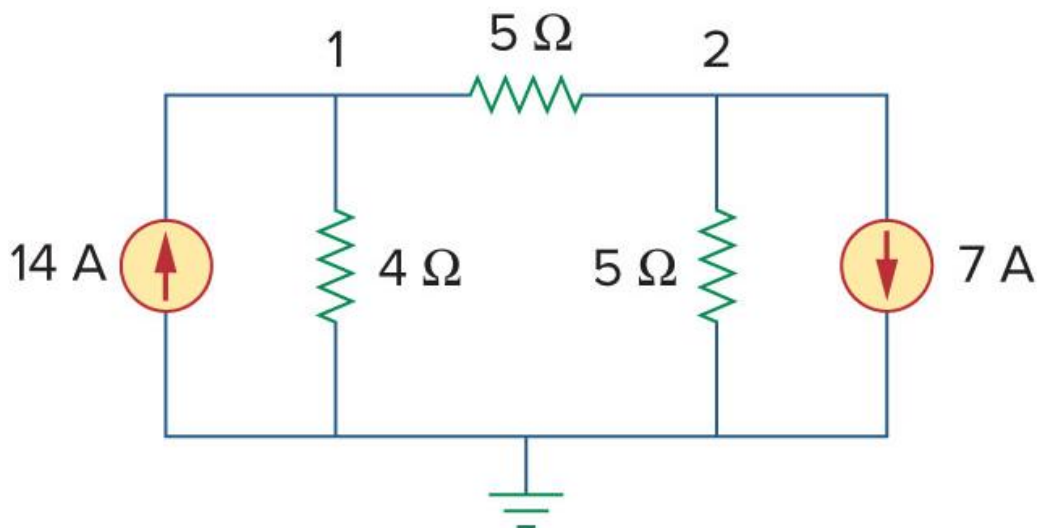
# Exercise


Obtain the node voltages in the circuit below and find the power dissipated in the  $4\Omega$  resistor.



# Nodal analysis with voltage sources

- Voltage sources generate or dissipate power at a specified voltage with whatever current is required.
  - The voltage is known at the terminals, but the current is not (and Ohm's law does not apply).
- There are 2 cases for nodal analysis with (independent or dependent) voltage sources.
  - **Case 1:** Voltage source is between the reference node and a non-reference node.
    - Set the voltage at the non-reference node to the voltage of the source.

$$v_1 = 10 \text{ V}$$

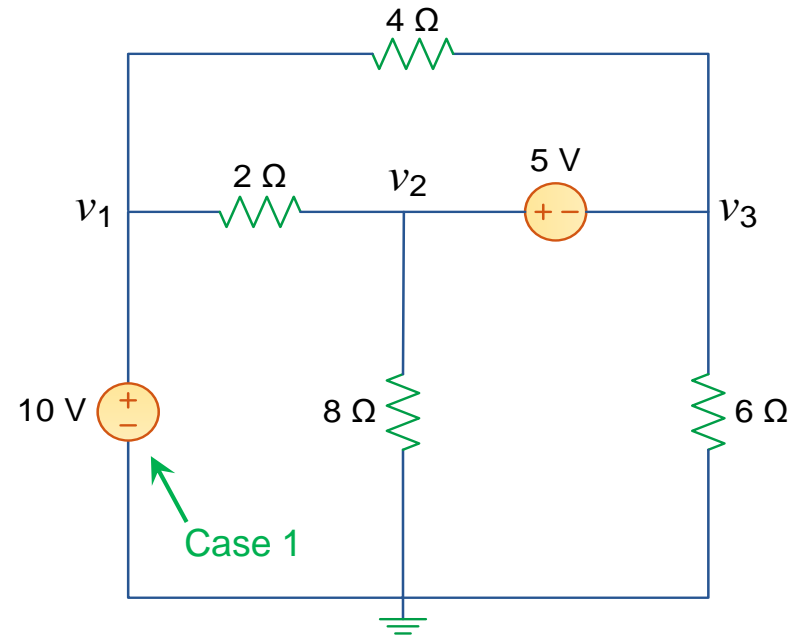


# Nodal analysis with voltage sources

- **Case 2:** Voltage source is between two non-reference nodes.
  - The two nodes form a **supernode**.
  - The voltage across the voltage source can be expressed in terms of node voltages (KVL in bottom-right mesh).

$$v_2 - v_3 = 5 \text{ V}$$

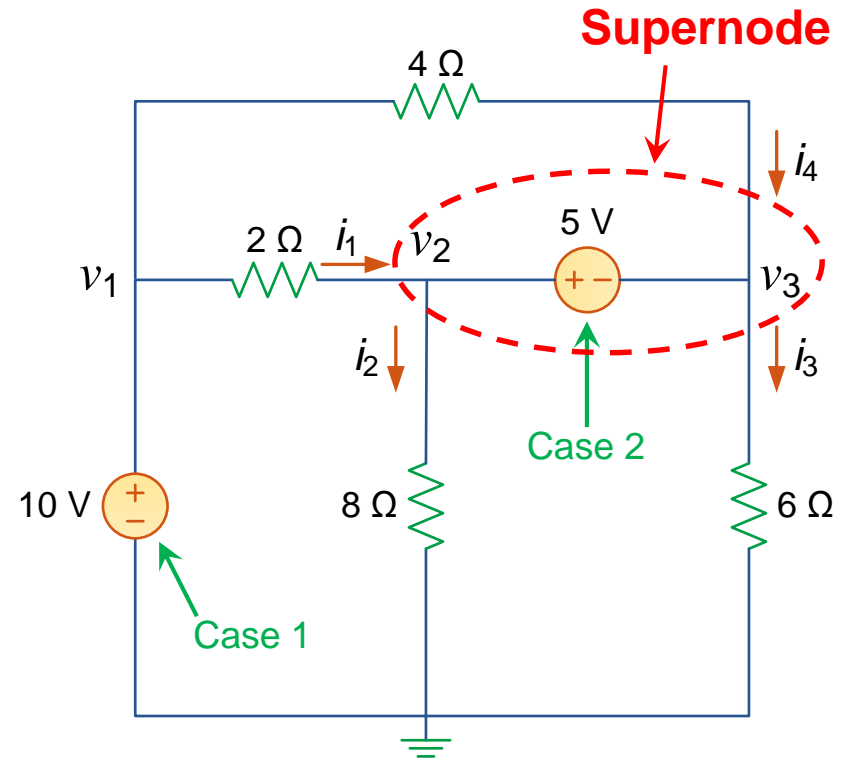A **supernode** is formed by **enclosing a voltage source** connected between **two non-reference** nodes and **any element** connected **in parallel** with it.




## Supernode properties

1. The voltage source inside the supernode provides a **constraint equation** needed to solve node voltages.
2. A supernode has **no voltage** of its own.
3. A supernode requires the application of **both KCL** and **KVL**.


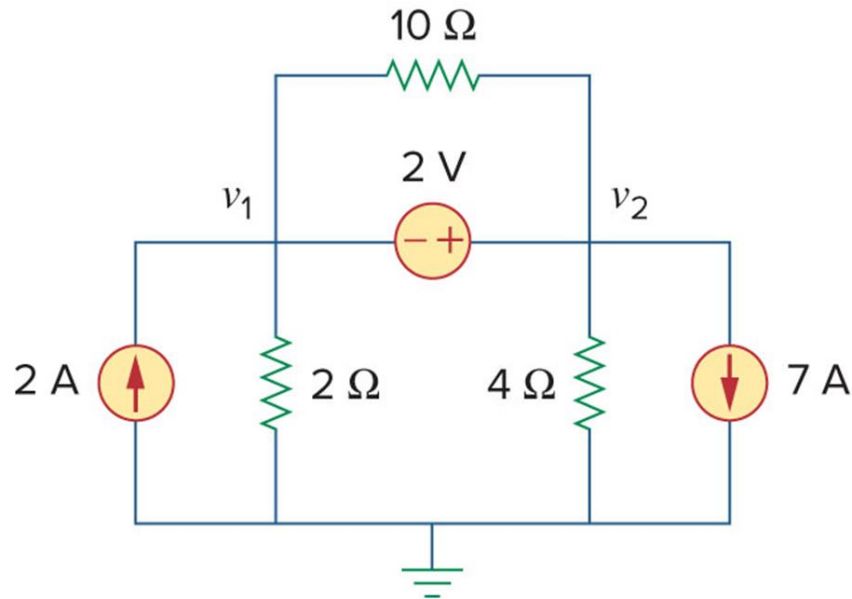
# Exercise


Find the node voltages in the circuit below.



# Mesh analysis
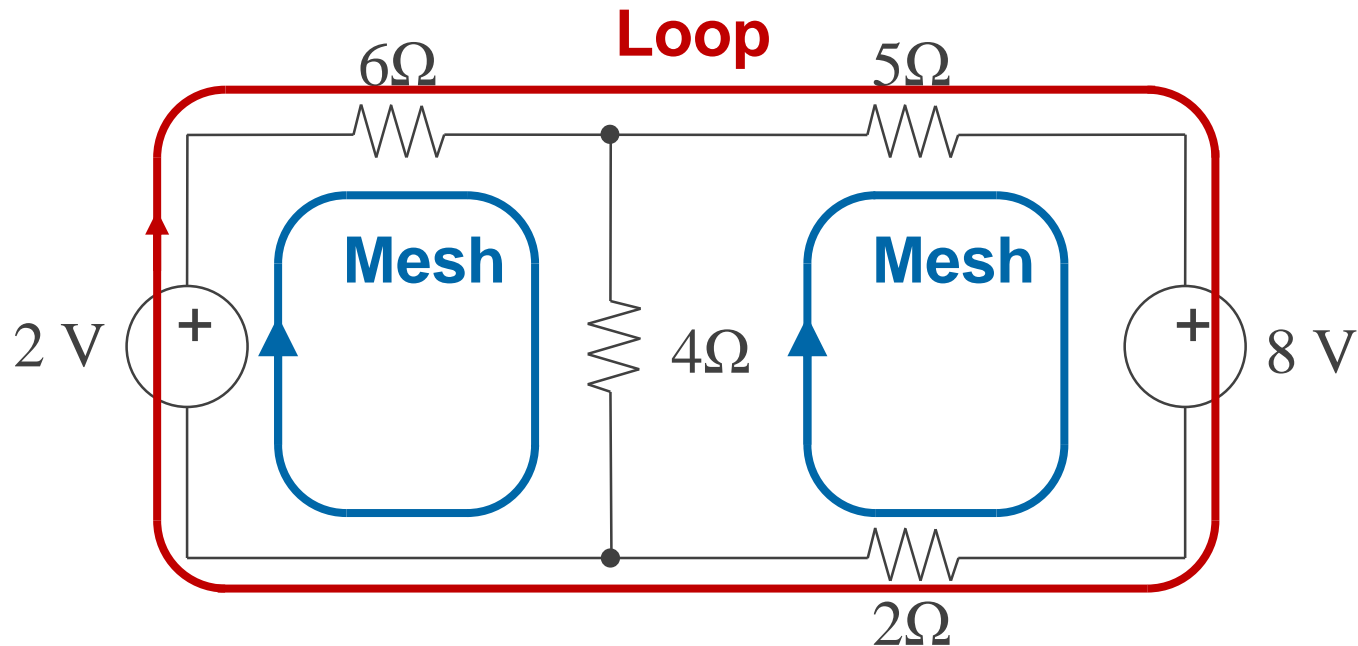
## Meshes


- A loop is any closed path in a circuit.
- A mesh is a loop that contains no other loop.



# Mesh analysis

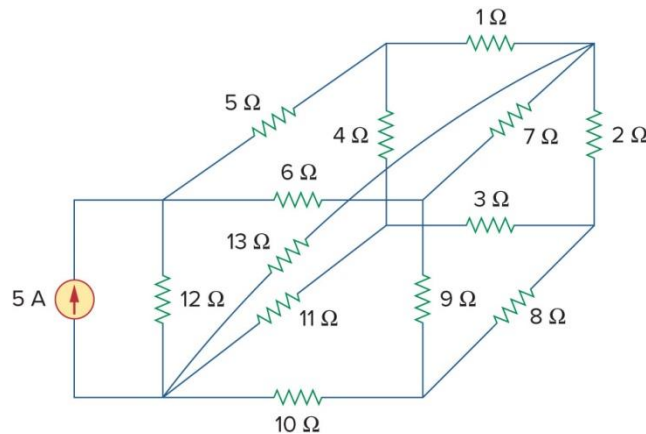
## Planar vs non-planar circuits

- A planar circuit is a circuit that can be drawn in a plane with **no crossing branches**.
- Mesh analysis is only applicable to planar circuits.
  - Nodal analysis can be applied to both.




Non-planar circuit.

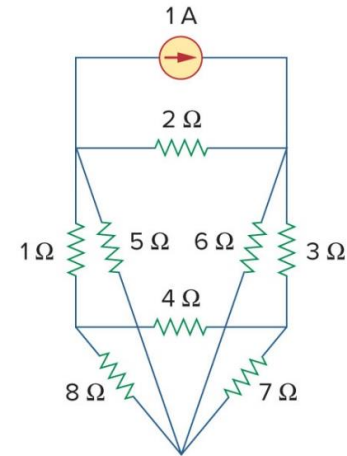The branch with the  $13\Omega$  resistor prevents the circuit from being drawn without crossing branches.



(a)

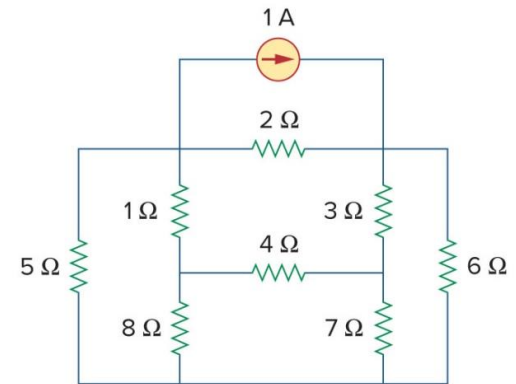

(b)

Planar circuit.

(a) Original, (b) Redrawn circuit.

# Mesh analysis

- It is based on KVL.
- We use **mesh currents** instead of element currents as the **main circuit variables**.
  - It reduces the number of equations that must be solved simultaneously.
- Objective: To solve for these mesh currents.
  - In general, an N-mesh circuit will need N currents and N equations.
  - It will also require the solution of a N system of equations.
  - KVL will be applied at each mesh.

# Mesh analysis

- Given a circuit with  $n$  meshes, the mesh analysis is accomplished via the following steps:

1. Assign mesh currents  $i_1, i_2, \dots, i_n$  to the  $n$  meshes with a direction (generally clockwise).
2. Apply **KVL** to each of the  $n$  meshes (following the same direction as mesh currents).
  - For resistors, use Ohm's law to express the voltages in terms of mesh currents.
4. Solve the resulting  $n$  simultaneous equations to obtain the unknown mesh currents.

NOTE: Always simplify the circuit before you start doing the analysis.

# Mesh analysis


Before starting, **simplify** the circuit (if possible) and identify all the meshes.

1. Assign currents  $i_1$  and  $i_2$  to meshes 1 and 2.
  - Current for each branch is:

$$I_1 = i_1$$

$$I_2 = i_2$$

$$I_3 = i_1 - i_2$$

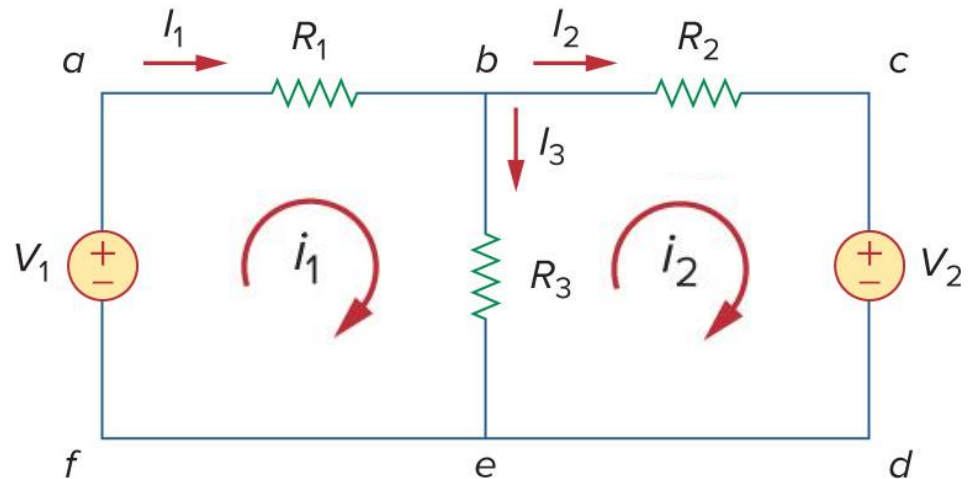

The current in the **common branch** between two meshes is the **difference** of the **two mesh currents** according to the current **direction** assigned to that branch.

NOTE: You can use  $I$  for **current branch** and  $i$  for **mesh current** or the other way round to distinguish between two types of currents, although most of the time we work directly with the mesh currents.

# Mesh analysis

3. Apply KVL to meshes 1 and 2.

$$\text{mesh 1: } -V_1 + v_{R_1} + v_{R_3} = 0$$

$$\text{mesh 2: } -v_{R_3} + v_{R_2} + V_2 = 0$$

- For resistors, use Ohm's law to express the voltages in terms of mesh currents.

$$v_{R_1} = R_1 I_1 = R_1 i_1$$

$$v_{R_2} = R_2 I_2 = R_2 i_2$$


$$v_{R_3} = R_3 I_3 = R_3(i_1 - i_2)$$

- Substitute back  $v_{R_1}$ ,  $v_{R_2}$ , and  $v_{R_3}$  into the mesh equations.




$$\begin{cases} -V_1 + R_1 i_1 + R_3(i_1 - i_2) = 0 \\ -R_3(i_1 - i_2) + R_2 i_2 + V_2 = 0 \end{cases}$$

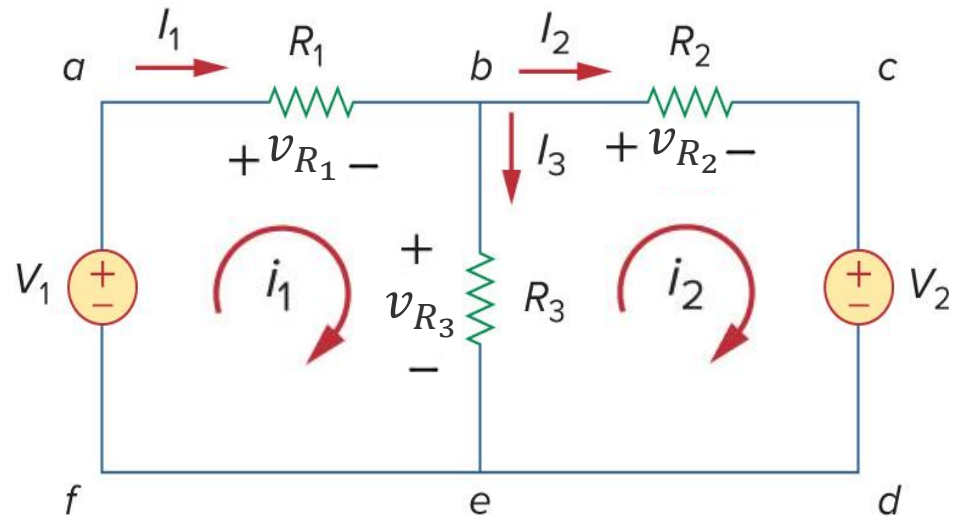4. Solve simultaneous equations (for  $i_1$  and  $i_2$ ).


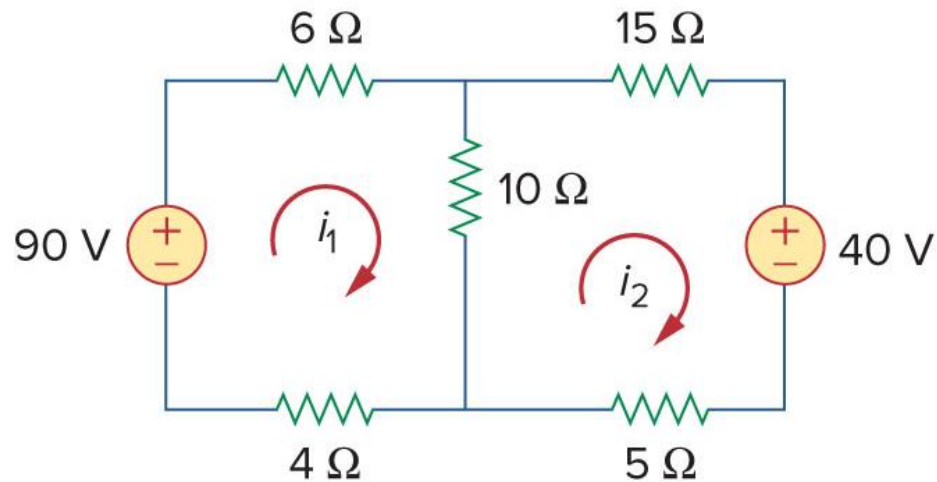
# Exercise

Calculate the mesh currents  $i_1$  and  $i_2$  in the circuit below, and find the power in the 40 V voltage source.






# Mesh analysis with current sources

- Current sources generate or dissipate power at a specified current with whatever voltage is required.
  - The current is known at the terminals, but the voltage is not (and Ohm's law does not apply).
- There are 2 cases for mesh analysis with (independent or dependent) current sources.
- **Case 1:** Current source exists only in one mesh.
  - Set the mesh current to the current of the source.

$$i_2 = 10 \text{ A}$$

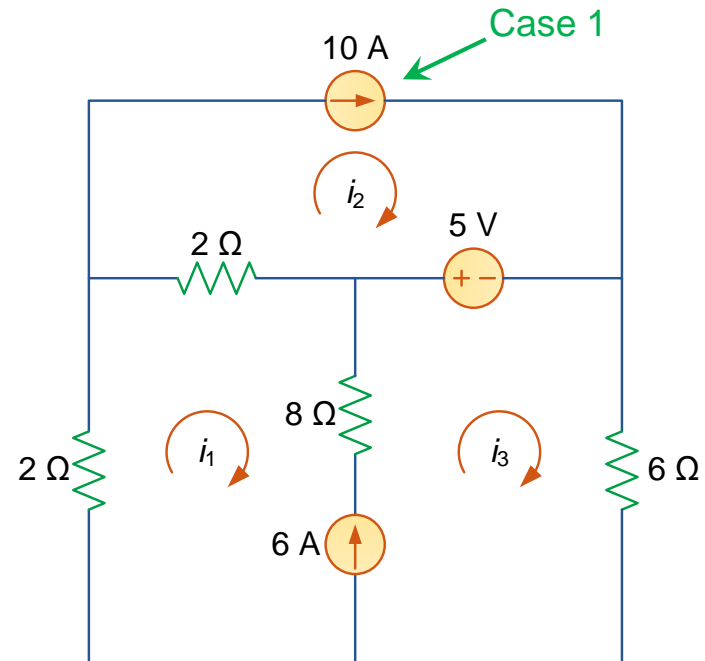


# Mesh analysis with current sources

- **Case 2:** Current source is between two meshes.
  - The two meshes form a **supermesh** by excluding the branch with current source.
  - The current through the current source can be expressed in terms of mesh currents (KCL in bottom node).

$$i_3 = i_1 + 6 \text{ A}$$

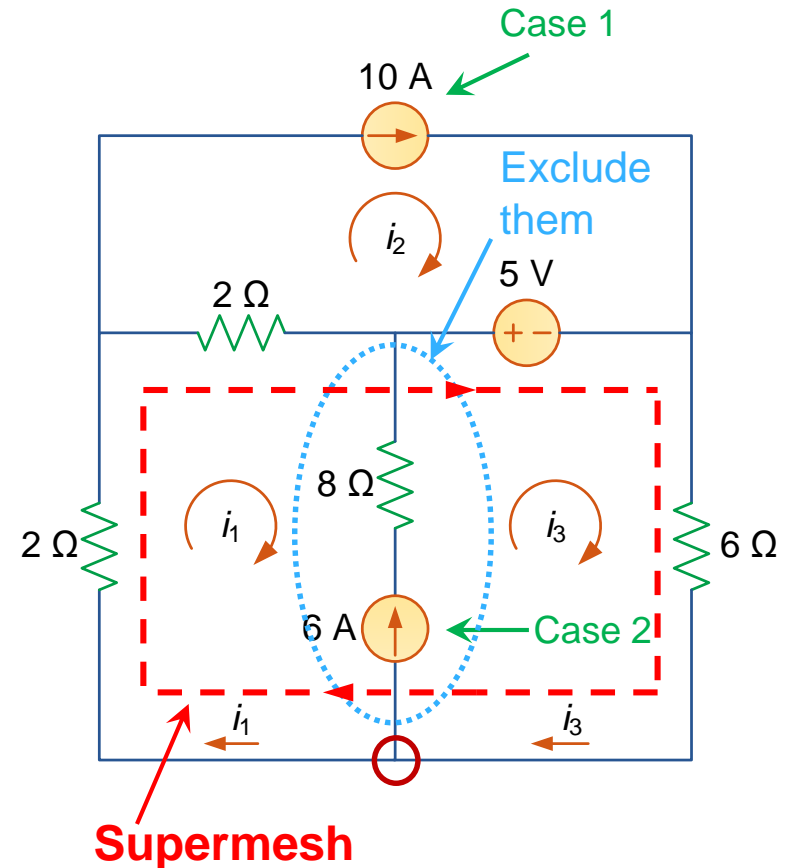
A **supermesh** is formed by **merging** two meshes and **excluding** the shared **current source** and **any element** connected **in series** with it.



# Mesh analysis with current sources


## Supermesh properties

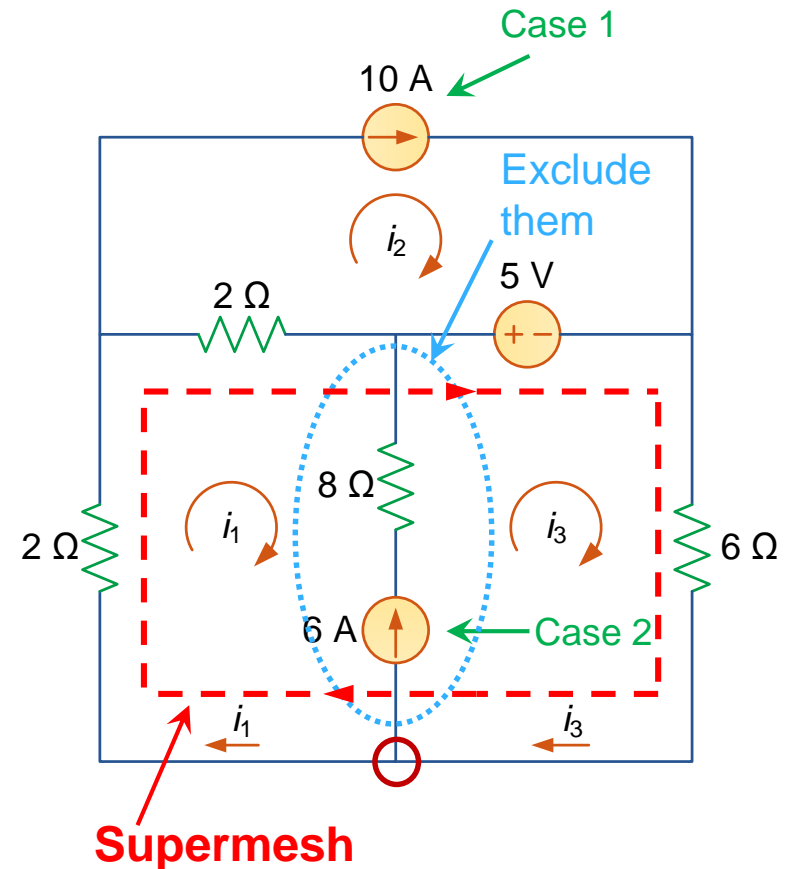1. The current source inside the supermesh provides a **constraint equation** needed to solve mesh currents.
2. A supermesh has **no current** of its own.
3. A supermesh requires the application of **both KVL** and **KCL**.
4. **Intersecting** supermeshes in a circuit must be combined to form a **larger** supermesh.


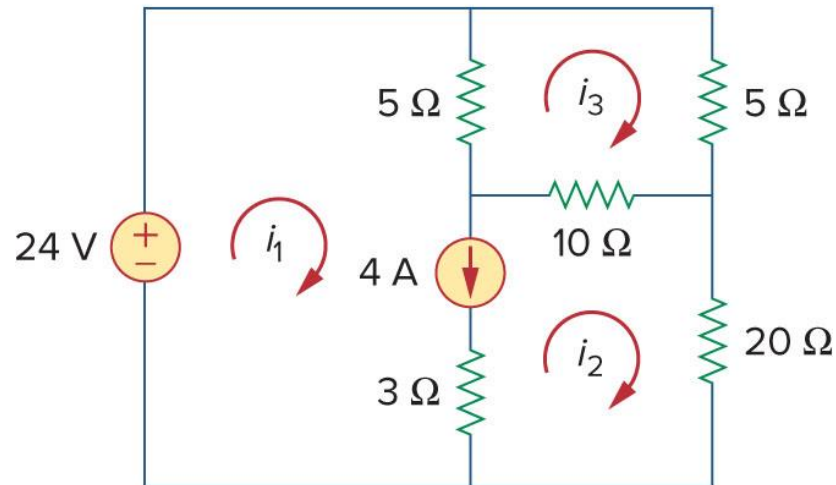
# Exercise

In the circuit below, use mesh analysis to determine  $i_1$ ,  $i_2$ , and  $i_3$ .



# Nodal analysis vs mesh analysis

- We aim to select the method that results in the smaller number of equations.
  - We prefer **nodal analysis** for circuits with **fewer nodes** than meshes.
  - We prefer **mesh analysis** for circuits with **fewer meshes** than nodes.

$$\begin{aligned}
 & (x-2)^2(y-2x+2)^2(y+2x-10)^2(x-4)^2(y-2x+8)^2(y+2x-16)^2\left(y-3-3\left\lfloor\frac{x-11}{2}\right\rfloor\right)^2(x-8)^2 \\
 & \cdot\left(y-2-3\left\lfloor\frac{x-8}{2}\right\rfloor\right)^2(x-11)^2\left(y-\frac{1}{2}x+\frac{5}{2}-3\left\lfloor\frac{x-11}{2}\right\rfloor\right)^2\left(y+\frac{1}{2}x-\frac{17}{2}-3\left\lfloor\frac{x-11}{2}\right\rfloor\right)^2(x-15)^2 \\
 & \cdot\left(y-4-3\left\lfloor\frac{x-14}{2}\right\rfloor\right)^2(y-2x+52)^2(x-17)^2(y+x-21)^2(x-19)^2(y-x+17-3\lfloor x-20\rfloor)^2 \\
 & \cdot\left(y+x-23-3\lfloor x-20\rfloor\right)^2(y-x+19-3\lfloor x-21\rfloor)^2(y-3-3\lfloor x-21\rfloor)^2(x-25)^2\left(y+\frac{1}{4}x-\frac{41}{4}-3\left\lfloor\frac{x-25}{2}\right\rfloor\right)^2 \\
 & \cdot\left(y-\frac{1}{8}x-\frac{1}{8}-3\left\lfloor\frac{x-25}{2}\right\rfloor\right)^2\left(y+\frac{5}{8}x-\frac{151}{8}-3\left\lfloor\frac{x-25}{2}\right\rfloor\right)^2(y-2x+54)^2(y+2x-62)^2\left(y-3-3\left\lfloor\frac{x-57}{2}\right\rfloor\right)^2 \\
 & \cdot(x-31)^2(y+x-35)^2(x-33)^2(x-34)^2\left(y+\frac{1}{2}x-21-3\left\lfloor\frac{x-34}{2}\right\rfloor\right)^2\left(y-\frac{1}{2}x+15-3\left\lfloor\frac{x-34}{2}\right\rfloor\right)^2 \\
 & \cdot((x-38)^2+(y-3)^2-1)^2(x-40)^2(y+2x-84)^2(y-2x+80)^2(x-42)^2(x-43)^2\left(y-2-3\left\lfloor\frac{x-43}{2}\right\rfloor\right)^2 \\
 & \cdot(y-3-|x-47|)^2((x-47)^2+(y-3+\sqrt{y^2-6y+9})^2+(y^2-6y+8+\sqrt{y^4-12y^3+52y^2-96y+64})^2=0
 \end{aligned}$$

# Questions?

