

2016 Semester I Final Exam

Question 1

a)

$$i) V = V_1 - V_2$$

KCL at node 1:

$$\frac{1}{2} = \frac{V_1}{4} + \frac{V_1 - V_2}{4}$$

$$4 = 2V_1 + V_1 - V_2$$

$$3V_1 - V_2 = 4 \quad (1)$$

KCL at node 2:

$$\frac{V_2 - V_1}{4} + \frac{V_2}{1} + \frac{V_2 - V_3}{3} = 0$$

$$3V_2 - 3V_1 + 12V_2 + 4V_2 - 4V_3 = 0$$

$$-3V_1 + 19V_2 - 4V_3 = 0 \quad (2)$$

Supernode:

$$V_3 - V_4 = 1$$

$$\text{But } V_4 = 2(V_1 - V_2)$$

$$-2V_1 + 2V_2 + V_3 = 1 \quad (3)$$

Voltage source:

$$V_4 = 2(V_1 - V_2)$$

$$= 2V_1 - 2V_2$$

$$2V_1 - 2V_2 - V_4 = 0 \quad (4)$$

ii) Solve for V_1, V_2, V_3 first then substitute for V_4 to make it easier

$$\begin{array}{ccc|c} V_1 & V_2 & V_3 \\ \hline 3 & -1 & 0 & 4 \\ -3 & 19 & -4 & 0 \\ -2 & 2 & 1 & 1 \end{array}$$

$$R_2 = R_2 + R_1$$

$$R_3 = 3R_3 + 2R_1$$

$$\begin{array}{ccc|c} 3 & -1 & 0 & 4 \\ 0 & 18 & -4 & 4 \\ 0 & 4 & 3 & 11 \end{array}$$

$$R_3 = 9R_3 - 2R_2$$

Final answers:

$$V_1 = 1.6V$$

$$V_2 = 0.8V$$

$$V_3 = 2.6V$$

$$V_4 = 1.6V$$

$$\begin{array}{ccc|c} 3 & -1 & 0 & 4 \\ 0 & 18 & -4 & 4 \\ 0 & 0 & 35 & 91 \end{array}$$


$$\therefore V_3 = \frac{91}{35} = 2.6V$$

$$V_2 = \frac{4 + 4(2.6)}{18} = 0.8V \therefore V_4 = 2(1.6 - 0.8) = 1.6V$$

$$V_1 = \frac{4 + 0.8}{3} = 1.6V$$

b)

i) $i = (i_1 - i_2)$

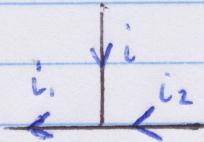

KVL at mesh 1:

$$-4 + 5(i_1 - i_3) + 6(i_1 - i_2) = 0$$

$$11i_1 - 6i_2 - 5i_3 = 4 \quad \textcircled{1}$$

KVL at mesh 2:

$$6(i_2 - i_1) + 2(i_2 - i_3) + 12(i_1 - i_2) = 0$$

$$6i_1 - 4i_2 - 2i_3 = 0$$

$$3i_1 - 2i_2 - i_3 = 0 \quad \textcircled{2}$$

KVL at mesh 3:

$$4i_3 + 2(i_3 - i_2) + 5(i_3 - i_1) = 0$$

$$-5i_1 - 2i_2 + 11i_3 = 0 \quad \textcircled{3}$$

Final answers:

$$i_1 = 6A$$

$$i_2 = 7A$$

$$i_3 = 4A$$

$$\left(\begin{array}{ccc|c} i_1 & i_2 & i_3 & \\ 11 & -6 & -5 & 4 \\ 3 & -2 & -1 & 0 \\ -5 & -2 & 11 & 0 \end{array} \right)$$

$$R_2 = 11R_2 - 3R_1$$

$$R_3 = 11R_3 + 5R_1$$

$$\left(\begin{array}{ccc|c} 11 & -6 & -5 & 4 \\ 0 & -4 & 4 & -12 \\ 0 & -52 & 96 & 20 \end{array} \right)$$

$$R_2 = R_3 - 13R_2$$


$$\left(\begin{array}{ccc|c} 11 & -6 & -5 & 4 \\ 0 & -4 & 4 & -12 \\ 0 & 0 & 44 & 176 \end{array} \right)$$

$$\therefore i_3 = 4A$$

$$i_2 = \frac{-12 - 16}{-4} = 7A$$

$$i_1 = \frac{4 + 6(7) + 5(4)}{11} = 6A$$

ii) Finding R_{eq}

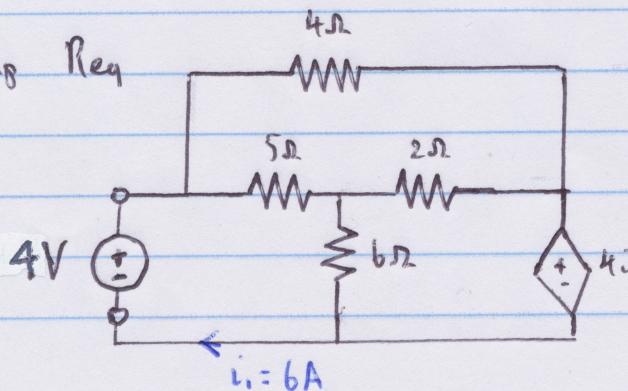


Attaching a 4V source at the terminals, we can use Thevenin's theorem to calculate R_{eq} :


$$R_{eq} = \frac{4}{6} = \frac{2}{3} \Omega$$

Question 2

a)

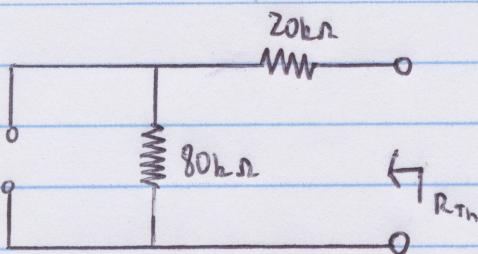


$$R_{Th} = 100 \text{ k}\Omega$$

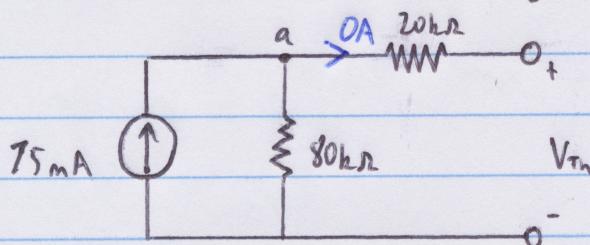

KCL at node a:


$$\frac{V_a}{80 \times 10^3} = 75 \times 10^{-3}$$
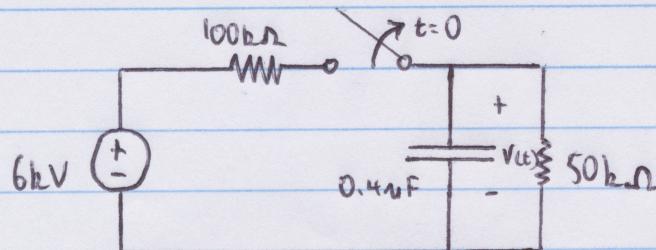
$$V_a = 6 \text{ kV} = V_{Th} \quad \text{since } \frac{V_a - V_m}{20 \text{ k}\Omega} = 0$$



(Thermin equivalent circuit)

b) At $t = 0^-$

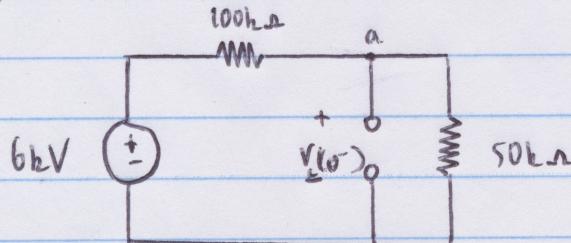

KCL at node a:

$$\frac{V_c(0^-) - 6 \times 10^3}{100 \times 10^3} + \frac{V_L(0^-)}{50 \times 10^3} = 0$$

$$3V_c(0^-) = 6 \times 10^3$$

$$V_c(0^-) = 2 \text{ kV}$$

c) $R_{Th} = 50 \times 10^3 \Omega$ after switch has opened

$$T = R_{Th} C = 50 \times 10^3 \times 0.4 \times 10^{-6}$$

$$= 20 \times 10^{-3} \text{ s}$$

d) $V_{oo} = 0 \text{ V}$ (No source to supply voltage so capacitor discharges)

$$V_c(t) = 0 + (2 \times 10^3 - 0) e^{-\frac{t}{50 \times 10^3}} \text{ V for } t > 1$$

$$= (2 \times 10^3) e^{-50t} \text{ V}$$

$$e) i(t) = C \frac{dv}{dt}$$

$$= (0.4 \times 10^{-6}) \times (-50) \times (2 \times 10^3) e^{-50t} \text{ A}$$

$$= -0.04 e^{-50t} \text{ A}$$

$$f) W = \frac{1}{2} C V_c (0)^2$$

$$= \frac{1}{2} \times 0.4 \times 10^{-6} \times (2 \times 10^3)^2$$

$$= 0.8 \text{ J}$$


Question 3

a)

$$i) 6\sin 2t \Rightarrow 6\cos(2t-90^\circ)$$

$$\nu = 2 \text{ rad/s}$$
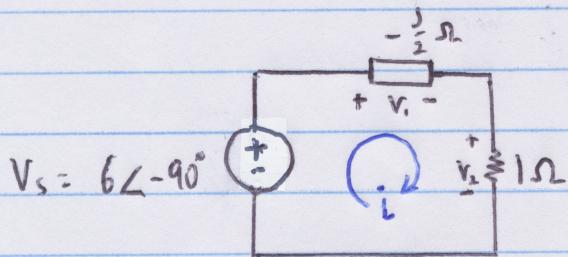
$$Z_{eq}(\text{LF}) = -\frac{j}{\omega L} = -\frac{j}{2} \Omega$$





$$\text{KVL: } i = \frac{6\angle-90^\circ}{1 + \frac{j}{2}} = 5.367\angle-63.43^\circ \text{ A}$$

$$\therefore V_1 = \left(-\frac{j}{2}\right) \times i = 2.683\angle-153.43^\circ \text{ V}$$

$$V_2 = 1 \times i = 5.367\angle-63.43^\circ \text{ V}$$

ii)

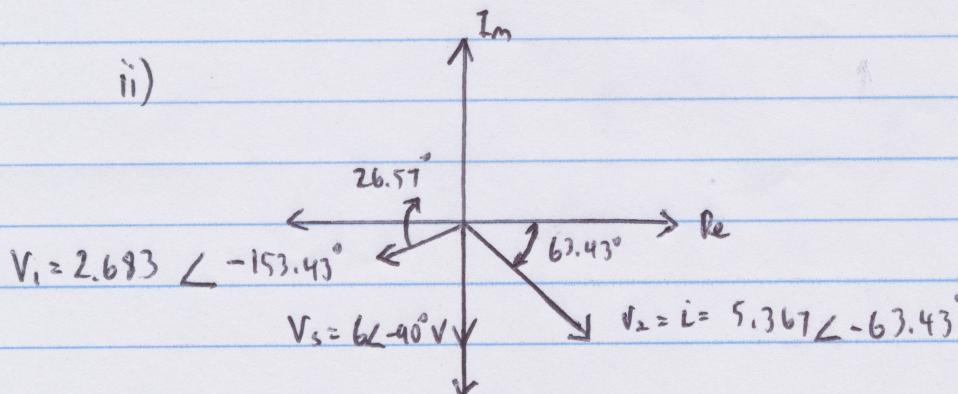

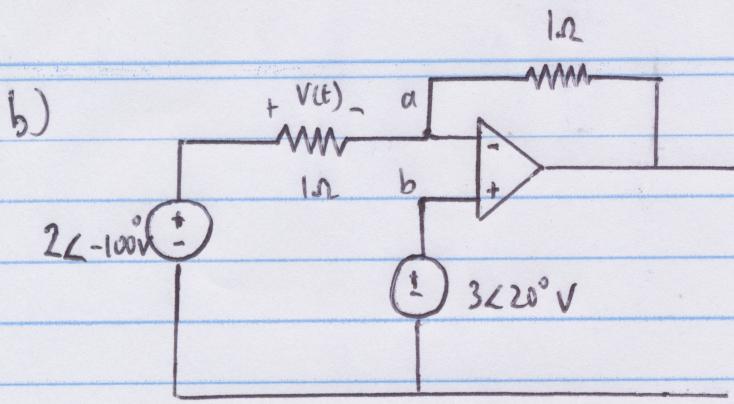

$$2 \sin(2t - 10^\circ) \Rightarrow 2 \sin(2t - 100^\circ) = 2L - 100^\circ$$

$V_b = V_a = 3 \angle 20^\circ$ (Principle of Op amp.)

$$\begin{aligned} v(t) &= 2L - 100^\circ - 3 \angle 20^\circ \\ &= 4.359 \angle -136.59^\circ \end{aligned}$$

$= 4.359 \cos(2t - 136.59^\circ) V \leftarrow$ Must be this form when asked for $v(t)$ as they are asking for voltage as a function of time.

c) $Z_{eq} = (R + j\omega L) \parallel \left(-\frac{j}{\omega C}\right)$

$$= \frac{(R + j\omega L)\left(-\frac{j}{\omega C}\right)}{R + j\left(\omega L - \frac{1}{\omega C}\right)} = \frac{\frac{R}{C} - j\left(\frac{R}{\omega C}\right)}{R + j\left(\omega L - \frac{1}{\omega C}\right)} = \frac{R_1 L \theta_1}{R_2 \angle \theta_2} = \frac{R_1}{R_2} \angle \theta_1 - \theta_2$$

If $\theta_1 - \theta_2 = 0$, then Z_{eq} will be purely resistive $\Rightarrow \theta_1 = \theta_2$

$$\theta_1 = \tan^{-1}\left(\frac{-R}{\omega C} \div \frac{L}{C}\right) = \tan^{-1}\left(\frac{-R}{\omega L}\right)$$

$$\theta_2 = \tan^{-1}\left(\frac{\omega L - \frac{1}{\omega C}}{R}\right) = \tan^{-1}\left(\frac{\omega^2 CL - 1}{\omega LR}\right)$$

$$\therefore \frac{-R}{\omega L} = \frac{\omega^2 CL - 1}{\omega CR}$$

$$-\omega CR^2 = \omega^3 CL^2 - \omega L$$


$$\omega (\omega^2 CL^2 - L + R^2 C) = 0 \Rightarrow \omega \neq 0$$

$$\omega^2 CL^2 - L + R^2 C = 0$$

$$\omega = \sqrt{\frac{L - R^2 C}{L^2 C}} = 1.278 \times 10^3 \text{ rad/s}$$

Question 4

a) At $t=0^-$

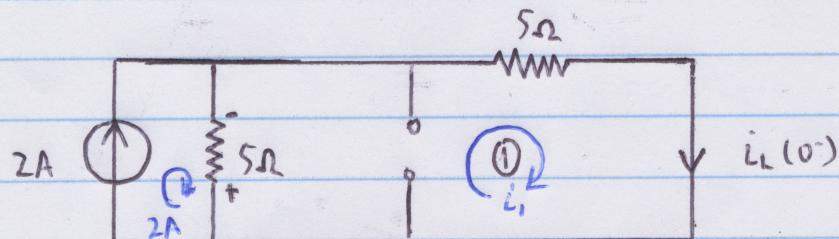

Note: $i_L = i_L(0^-)$


KVL in mesh ①:

$$5(i_L - 2) + 5i_L = 0$$

$$10i_L = 10$$

$$i_L = 1 \text{ A} = i_L(0^-)$$

At $t=0^+$

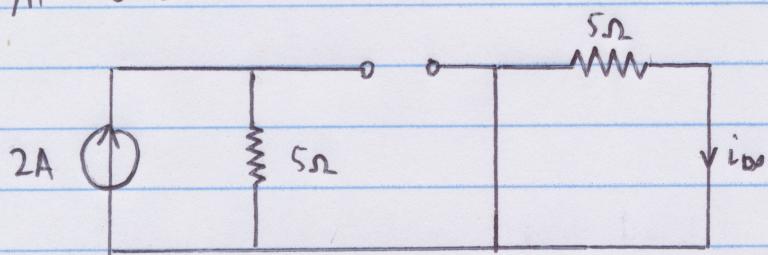

$$i_{\infty} = 0 \text{ A}$$


$$R_{Th} = 5 \Omega$$

$$T = \frac{L}{R} = \frac{100 \times 10^{-3}}{5} = 20 \times 10^{-3}$$

$$i_L(t) = i_{\infty} + (i_L(0) - i_{\infty}) e^{-\frac{t}{T}}$$

$$= 1 e^{-50t} \text{ A for } t > 0$$

b)

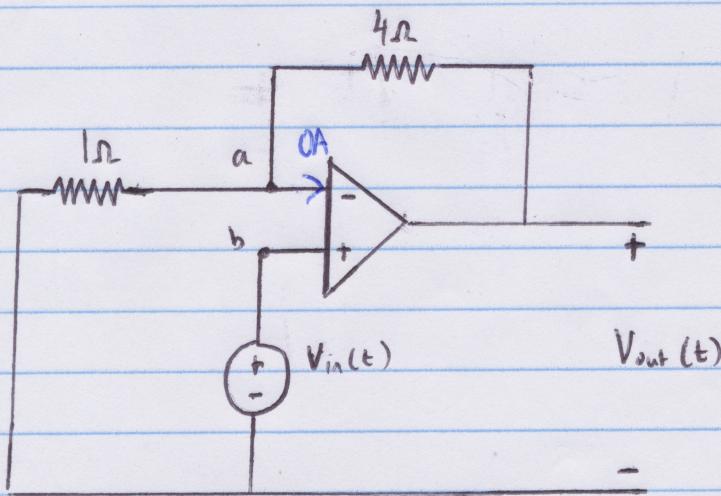

$$V_a = V_b = V_{in}(t)$$

KCL at node a:

$$\frac{V_a}{1} + \frac{V_a - V_{out}}{4} = 0$$


$$4V_a + V_{out} = V_{out}$$

$$5V_a = V_{out}(t)$$

$$\therefore 5V_{in}(t) = V_{out}(t)$$

Negative feedback is desirable so that ideal op amp principles can be used ($V_b = V_a$)

c) Finding R_{Th}

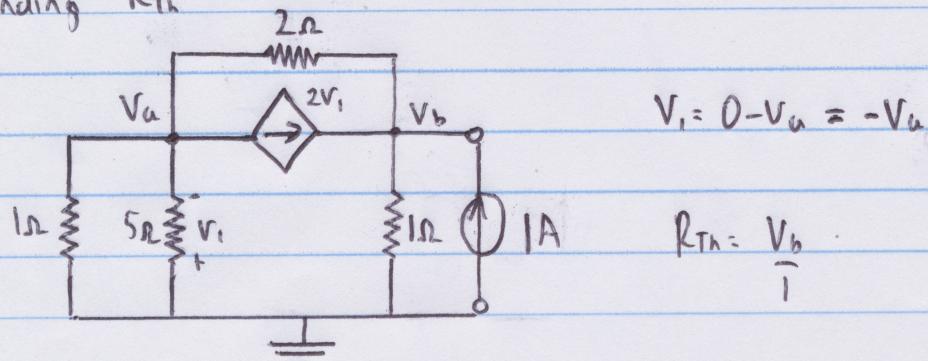

KCL at node a:

$$\frac{V_a}{1} + \frac{V_a}{5} + \frac{V_a - V_b}{2} - 2V_a = 0 \Rightarrow 10V_a + 2V_a + 5V_a - 5V_b - 20V_a = 0$$

$$-3V_a - 5V_b = 0 \quad (1)$$

KCL at node b:

$$\frac{V_b - V_a}{2} + \frac{V_b}{1} = -2V_a + 1 \Rightarrow V_b - V_a + 2V_b = -4V_a + 2$$

$$3V_a + 3V_b = 2 \quad (2)$$


(1) + (2)

$$-2V_b = 2$$

$$\therefore V_b = -1$$

$$\therefore R_{Th} = -1\Omega$$

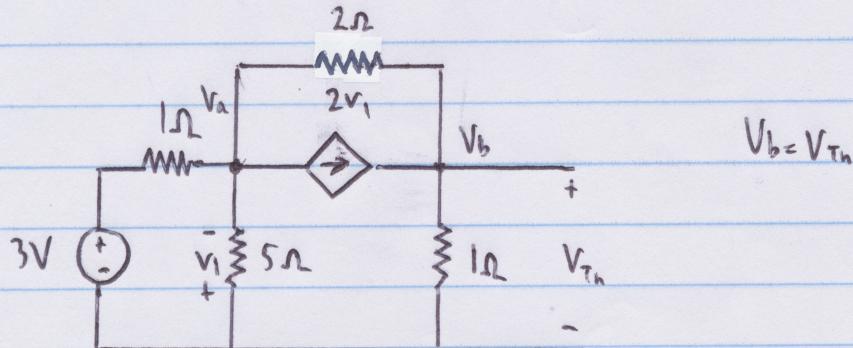Finding V_{Th} (There are less nodes than there is meshes)



KCL at node a:

$$\frac{V_a - 3}{1} + \frac{V_a - V_b}{2} - 2V_a + \frac{V_a}{5} = 0$$
$$-3V_a - 5V_b = 30 \quad (1)$$

KCL at node b:


$$\frac{V_b - V_a}{2} + \frac{V_b}{1} = -2V_a$$
$$3V_a + 3V_b = 0 \quad (2)$$

$$(1) + (2)$$

$$-2V_b = 30$$


$$V_b = -15V = V_{Th}$$

$$\therefore I_N = \frac{V_{Th}}{R_{Th}} = 15A$$

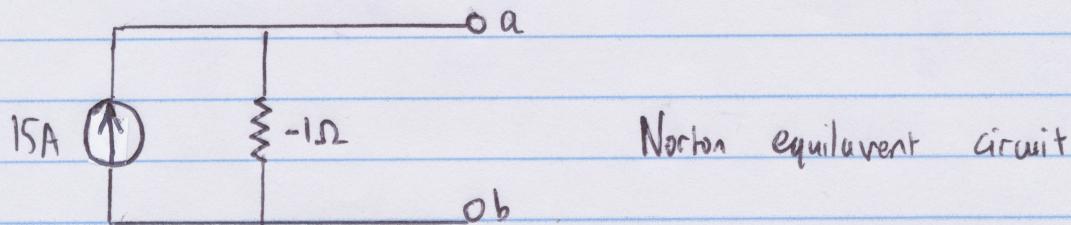

Question 5

a)

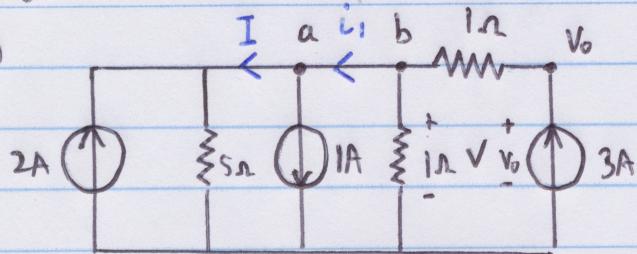

KCL at node a:

$$\frac{V}{1} + \frac{V}{5} + 1 = 2 + 3$$

$$5V + V + 5 = 20$$

$$\therefore V = \frac{10}{3} V$$

KCL at node b:

$$\begin{aligned} i_1 &= -\frac{10}{3} A \\ i_1 + \frac{10}{3} &= 3 \\ i_1 &= -\frac{1}{3} A \end{aligned}$$

KCL at node ai:

$$\begin{aligned} I &= -\frac{1}{3} A \\ I + 1 &= -\frac{4}{3} A \\ \therefore I &= -\frac{4}{3} A \end{aligned}$$

b) Voltage across 1Ω resistor

$$\frac{V_o - V_b}{1} = 3$$

$$V_o = 3 + \frac{10}{3} = \frac{19}{3} V$$

$$P_{2A} = -\left(\frac{10}{3} \times 2\right) = -\frac{20}{3} W = \frac{20}{3} W \text{ supplied}$$

$$P_{1A} = \frac{10}{3} \times 1 = \frac{10}{3} W \text{ absorbed}$$

$$P_{3A} = -\left(\frac{10}{3} \times 3\right) = -19 W = 19 W \text{ supplied}$$

c)

$$f(A, B, C) = \overline{\overline{A} \cdot \overline{B}} \cdot \overline{\overline{A} \cdot \overline{C}} \Rightarrow \text{Remove two lines}$$

$$= \overline{A} \cdot \overline{B} \cdot \overline{B} \cdot \overline{C} \Rightarrow \text{Demorgan's theorem}$$

$$= \overline{A} \cdot \overline{B} + \overline{B} \cdot \overline{C} + \overline{A} \cdot \overline{C} \Rightarrow \text{Remove two lines}$$

$$= A \cdot B + B \cdot C + A \cdot C$$

d)	A	B	C	A, B	B, C	A, C	$f(A, B, C)$
	0	0	0	0	0	0	0
	0	0	1	0	0	0	0
	0	1	0	0	0	0	0
	0	1	1	0	1	0	1
	1	0	0	0	0	0	0
	1	0	1	0	0	1	1
	1	1	0	1	0	0	1
	1	1	1	1	1	1	1

e)

