



Faculty of Engineering

School of Electrical Engineering and Telecommunications

ELEC 1111 – Topic 9

AC Power

Dr. Inmaculada (Inma) Tomeo-Reyes

Lecturer

School of Electrical Engineering and Telecommunications, UNSW

Topic 9 Content

This lecture covers:

- AC power.
 - Instantaneous power.
 - Average power.
 - Maximum average power transfer.
- Effective or RMS value.

**Corresponds to the first part of Chapter 11
of your textbook**

AC power

- **Power analysis** is quite important as all electrical, electronic, and communications systems rely on transmission of power (either in AC or DC form) from one point to another.
- The **most common** form of power is **AC power** due to its low cost and convenience in transmission of high-voltage power from the generator to the consumer.
- There are **multiple concepts** for AC power depending on the application of power and how it is being measured.
- In this lecture just **two main concepts** of AC power are introduced:
 - **Instantaneous** power.
 - **Average** power.




https://en.wikipedia.org/wiki/Transmission_tower

Instantaneous power

- **Instantaneous power** (in watts) is the power at **any instance** of time.
- Instantaneous power $p(t)$ absorbed by an element (or network) is the **product** of the **instantaneous voltage** $v(t)$ across the element (or network) and the **instantaneous current** $i(t)$ through it, assuming **passive sign convention**.

$$p(t) = v(t)i(t)$$

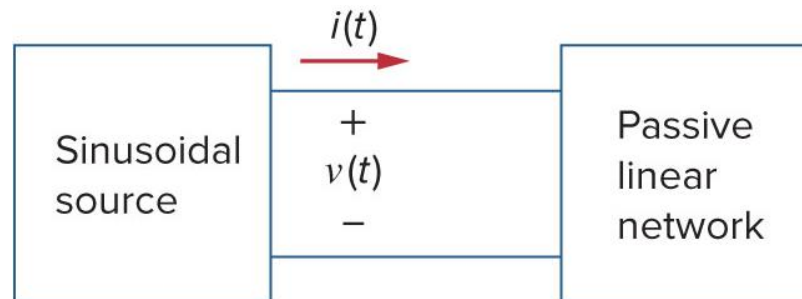

- Instantaneous power is the **rate** at which an element absorbs **energy**.


$$w = \int_0^t p(\tau) d\tau \quad \rightarrow \quad p(t) = \frac{dw}{dt}$$

Instantaneous power

- Consider the general case where the voltage and current at the terminals of a circuit with passive elements under sinusoidal excitation are as follows:

$$v(t) = V_m \cos(\omega t + \theta_v)$$

$$i(t) = I_m \cos(\omega t + \theta_i)$$

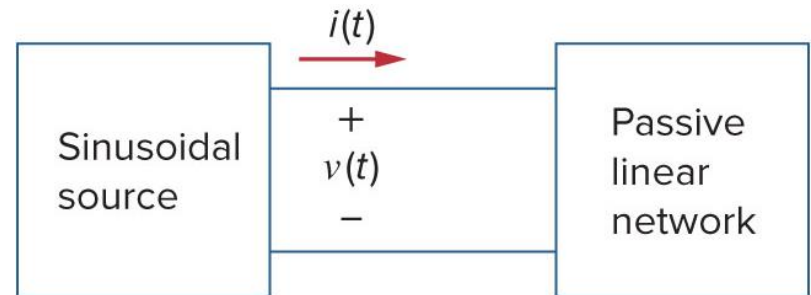

- The instantaneous power absorbed by the circuit is as follows:

$$p(t) = v(t)i(t) = V_m I_m \cos(\omega t + \theta_v) \cos(\omega t + \theta_i)$$

Apply the trigonometric identity: $\cos A \cos B = \frac{1}{2} [\cos(A - B) + \cos(A + B)]$

$$p(t) = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) + \frac{1}{2} V_m I_m \cos(2\omega t + \theta_v + \theta_i)$$


Instantaneous power

- Instantaneous power has two parts:

$$p(t) = \underbrace{\frac{1}{2} V_m I_m \cos(\theta_v - \theta_i)}_{\text{Constant term depending only on phase difference between voltage and current}} + \underbrace{\frac{1}{2} V_m I_m \cos(2\omega t + \theta_v + \theta_i)}_{\text{Sinusoidal term with twice the frequency of voltage or current } T_0 = \frac{T}{2}}$$

Constant term depending **only** on **phase difference** between **voltage** and **current**

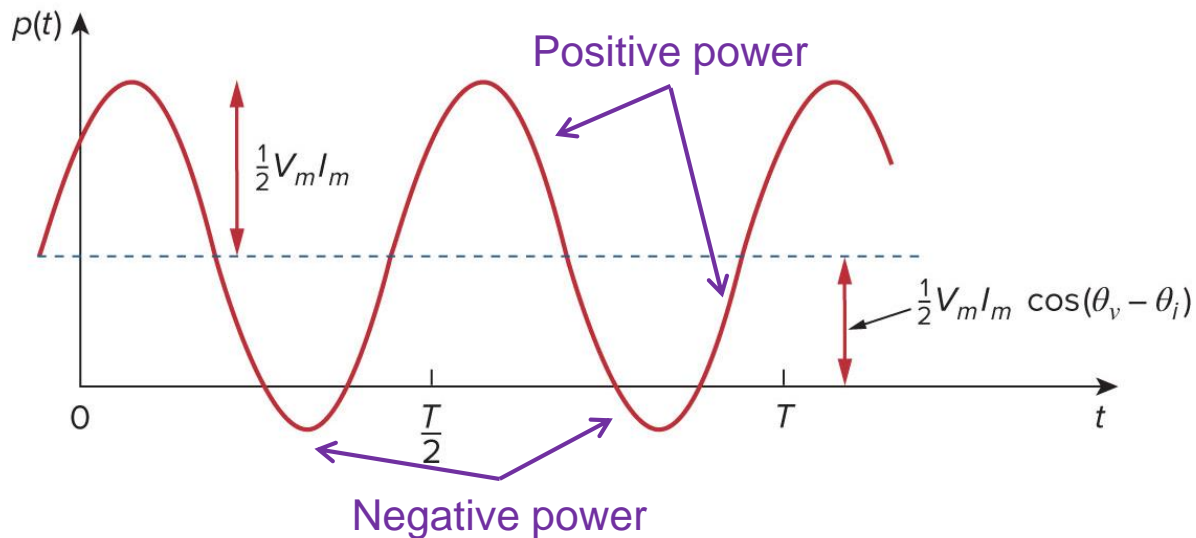Sinusoidal term with **twice** the **frequency** of voltage or current $T_0 = \frac{T}{2}$



- When $p(t)$ is **positive**, power is **absorbed** by the **circuit** (or supplied by the source).
- When $p(t)$ is **negative**, power is **absorbed** by the **source** (or transferred from the circuit to the source).

Note: This is possible due to storage elements (**capacitors** and **inductors**).

Average power

- **Average power** (in watts) is the **average** of the **instantaneous** power over **one period**.
 - Instantaneous power is difficult to measure as it changes with time.
 - The **average power** is more convenient to measure.
 - **Wattmeter**, an instrument for measuring power, provides the **average power**.

$$P = \frac{1}{T} \int_0^T p(t) dt$$

$$P = \frac{1}{T} \int_0^T p(t) dt = \frac{1}{T} \int_0^T \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) dt + \frac{1}{T} \int_0^T \frac{1}{2} V_m I_m \cos(2\omega t + \theta_v + \theta_i) dt$$

$$P = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) \underbrace{\frac{1}{T} \int_0^T dt}_1$$

$$P = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i)$$

Integrating a sinusoid over an integer multiple of its period is **zero**, $T = 2T_0 = 2 \times \frac{2\pi}{2\omega} = \frac{2\pi}{\omega}$.

The positive area under the sinusoid cancels the negative area

Average power

- **Average power** $P = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i)$ depends on **amplitudes** and **phases** of current and voltage only.
- **Phasor voltage** $\mathbf{V} = V_m \angle \theta_v$ and **phasor current** $\mathbf{I} = I_m \angle \theta_i$ can be used to calculate the average power as follows:

$$\frac{1}{2} \mathbf{V} \mathbf{I}^* = \frac{1}{2} V_m \angle \theta_v \times I_m \angle (-\theta_i) = \frac{1}{2} V_m I_m \angle (\theta_v - \theta_i),$$

where \mathbf{I}^* is the **complex conjugate** of phasor current \mathbf{I} .

Transform to rectangular form:


$$\frac{1}{2} \mathbf{V} \mathbf{I}^* = \underbrace{\frac{1}{2} V_m I_m \cos(\theta_v - \theta_i)}_{\text{average power}} + j \frac{1}{2} V_m I_m \sin(\theta_v - \theta_i)$$



$$P = \frac{1}{2} \text{Re}[\mathbf{V} \mathbf{I}^*] = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i)$$

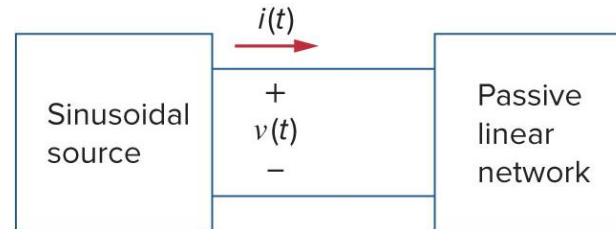Exercise

Given $v(t) = 120 \cos(377t + 45^\circ)$ V and $i(t) = 10 \cos(377t - 10^\circ)$ A, find the instantaneous and average power absorbed by the passive linear network shown below.



Average power

- A **resistive load** $\mathbf{Z} = R$ absorbs **average power** at all times in AC circuits.
- When $\theta_v = \theta_i$, the voltage and current are **in phase**. This implies a **purely resistive** circuit or **resistive load**, $\mathbf{V} = R\mathbf{I}$, thus:

$$P = \frac{1}{2} \operatorname{Re}[\mathbf{V}\mathbf{I}^*] = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i)$$

$$P = \frac{1}{2} V_m I_m$$

$$P = \frac{1}{2} R I_m^2 = \frac{1}{2} R |\mathbf{I}|^2$$

$$P = \frac{1}{2} \frac{V_m^2}{R} = \frac{1}{2} \frac{|\mathbf{V}|^2}{R}$$

Proof of the last two:

$$P = \frac{1}{2} \operatorname{Re}[\mathbf{V}\mathbf{I}^*] = \frac{1}{2} \operatorname{Re}[R\mathbf{I} \times \mathbf{I}^*] = \frac{1}{2} R |\mathbf{I}|^2 = \frac{1}{2} R I_m^2$$

$$P = \frac{1}{2} \operatorname{Re}[\mathbf{V}\mathbf{I}^*] = \frac{1}{2} \operatorname{Re}\left[\mathbf{V} \times \frac{\mathbf{V}^*}{R}\right] = \frac{1}{2} \frac{|\mathbf{V}|^2}{R} = \frac{1}{2} \frac{V_m^2}{R}$$

Average power


- A **reactive load** $\mathbf{Z} = j\omega L$ or $\mathbf{Z} = 1/j\omega C$ absorbs **zero average power** in AC circuits.
 - Inductor L and capacitor C absorb zero average power in AC circuits because they **charge and discharge the power** during a full period of the voltage and current.
- When $\theta_v - \theta_i = \pm 90^\circ$, it implies a **purely reactive** circuit or **reactive load**, so:

$$P = \frac{1}{2} \operatorname{Re}[\mathbf{VI}^*] = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i)$$

$$P = \frac{1}{2} V_m I_m \cos 90^\circ = 0$$

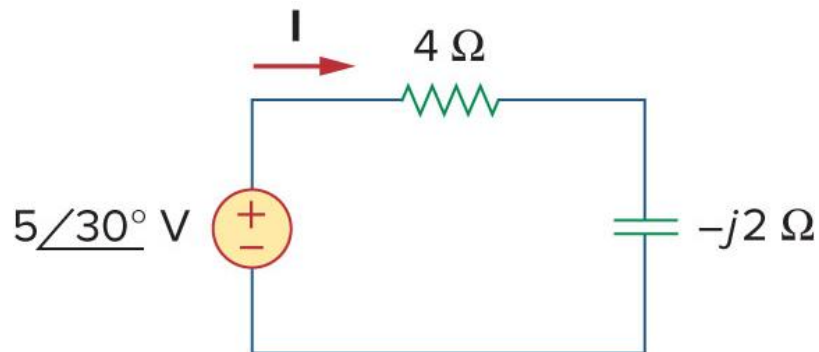Exercise


For the circuit below, find the average power supplied by the source and the average power absorbed by the resistor.



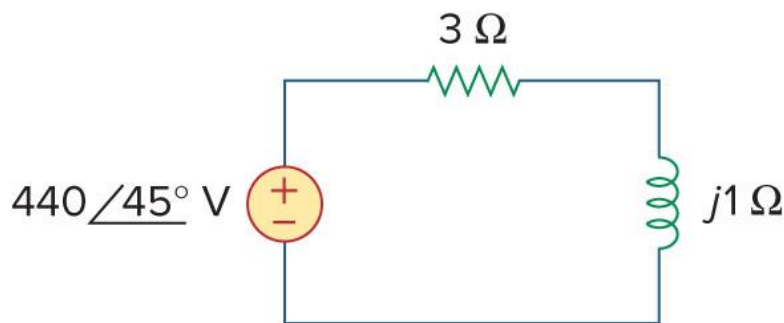Exercise


For the circuit below, find the average power supplied by the source and the average power absorbed by the resistor and inductor.

- For practice!
- Answer: 29.04 kW supplied by the source.
29.04 kW absorbed by the resistor.
0 kW absorbed by the inductor.



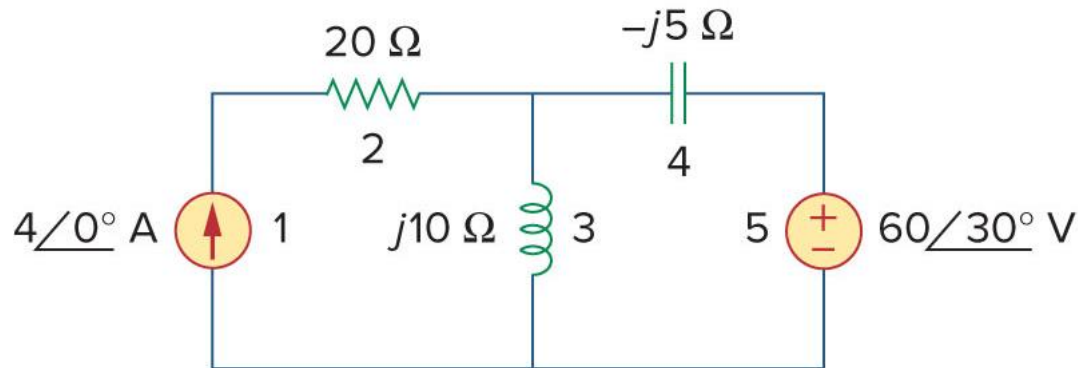Exercise


Determine the average power generated by each source and the average power absorbed by passive elements in the circuit below.



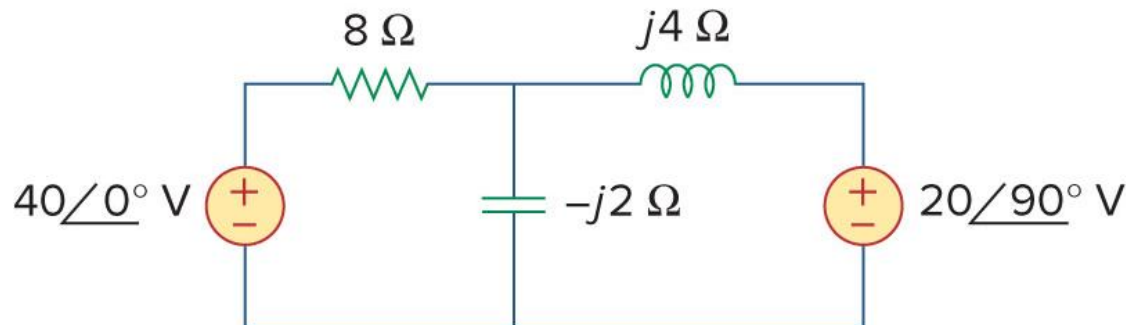Exercise

Calculate the average power absorbed/supplied by each of the five elements in the circuit below

- For practice!
- Answer: $P_{40V} = 60 \text{ W}$ supplied
 $P_{j20V} = 40 \text{ W}$ supplied
 $P_{8\Omega} = 100 \text{ W}$ absorbed
 $P_{j4\Omega} = P_{-j2\Omega} = 0 \text{ W}$ absorbed



Maximum average power transfer

- Recall that a DC circuit with resistive elements represented by its **Thevenin equivalent circuit** can transfer **maximum power** if and only if $R_L = R_{Th}$.
- The results can be extended to AC circuits in a similar fashion

Consider the Thevenin equivalent circuit shown in Fig. (b) with rectangular form for impedances:


$$\mathbf{Z}_{Th} = R_{Th} + jX_{Th} \quad \text{and} \quad \mathbf{Z}_L = R_L + jX_L$$

The current through the load is:


$$\mathbf{I} = \frac{\mathbf{V}_{Th}}{\mathbf{Z}_{Th} + \mathbf{Z}_L} = \frac{\mathbf{V}_{Th}}{(R_{Th} + jX_{Th}) + (R_L + jX_L)}$$

The average power delivered to the load is:

$$P = \frac{1}{2} R_L |\mathbf{I}|^2 = \frac{\frac{R_L |\mathbf{V}_{Th}|^2}{2}}{(R_{Th} + R_L)^2 + (X_{Th} + X_L)^2}$$

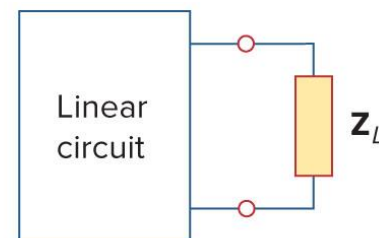

(a)

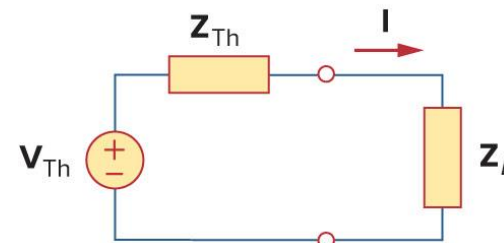

(b)

Maximum average power transfer

- To **maximize the average power** in terms of R_L and X_L , set the **partial derivatives** of P with respect to R_L and X_L to **zero** solve them for R_L and X_L :

$$P = \frac{1}{2} R_L |\mathbf{I}|^2 = \frac{\frac{R_L |\mathbf{V}_{Th}|^2}{2}}{(R_{Th} + R_L)^2 + (X_{Th} + X_L)^2}$$

$$\frac{\partial P}{\partial X_L} = \frac{-|\mathbf{V}_{Th}|^2 R_L (X_{Th} + X_L)}{[(R_{Th} + R_L)^2 + (X_{Th} + X_L)^2]^2}$$

$$\frac{\partial P}{\partial R_L} = \frac{|\mathbf{V}_{Th}|^2 [(R_{Th} + R_L)^2 + (X_{Th} + X_L)^2 - 2R_L(R_{Th} + R_L)]}{2[(R_{Th} + R_L)^2 + (X_{Th} + X_L)^2]^2}$$

Setting $\frac{\partial P}{\partial X_L}$ and $\frac{\partial P}{\partial R_L}$ to zero results in:

$$X_L = -X_{Th}$$

and

$$R_L = \sqrt{R_{Th}^2 + (X_{Th} + X_L)^2}$$

Combining the results:

$$\mathbf{Z}_L = R_L + jX_L = R_{Th} - jX_{Th} = \mathbf{Z}_{Th}^*$$




$$\begin{cases} R_L = R_{Th} \\ X_L = -X_{Th} \end{cases}$$

Maximum average power transfer


- Setting $R_L = R_{Th}$ and $X_L = -X_{Th}$ in the **average power** equation leads to:

$$\boxed{\mathbf{Z}_L = \mathbf{Z}_{Th}^*} \quad \Rightarrow \quad \boxed{P_{\max} = \frac{|\mathbf{V}_{Th}|^2}{8R_{Th}}}$$

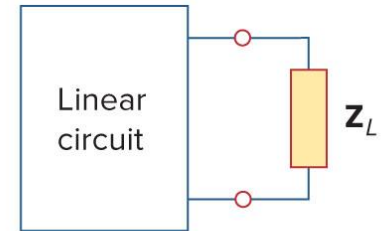Maximum power is transferred to the load when the **load impedance \mathbf{Z}_L** is **equal** to the **complex conjugate** of the **Thevenin impedance \mathbf{Z}_{Th}^*** as seen from the load terminals.



(a)

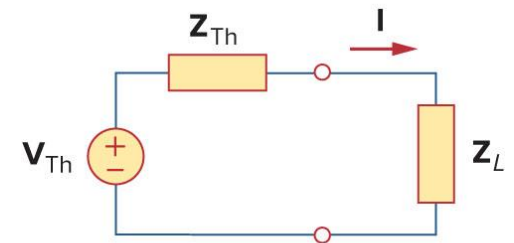

(b)


Maximum average power transfer

- For a **pure resistive load** $\mathbf{Z}_L = R_L$, **maximum average power transfer condition** is given by setting $X_L = 0$ in $R_L = \sqrt{R_{Th}^2 + (X_{Th} + X_L)^2}$, as follows:

$$R_L = \sqrt{R_{Th}^2 + X_{Th}^2} = |\mathbf{Z}_{Th}|$$




$$P_{\max} = \frac{1}{2} R_L |\mathbf{I}_L|^2 = \frac{1}{2} \frac{|\mathbf{V}_L|^2}{R_L}$$

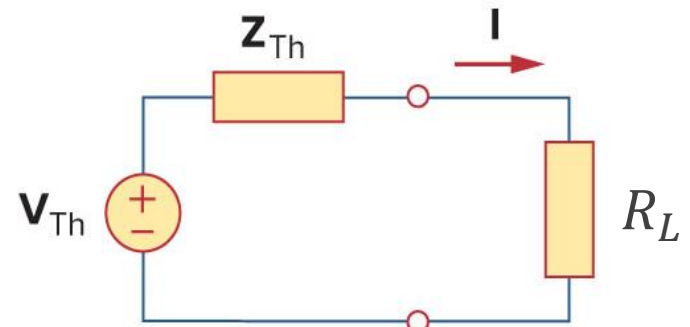

Maximum average power transferred to a **pure resistive load** ($\mathbf{Z}_L = R_L$) can be calculated in an AC circuit using **direct** calculation of **average power** absorbed by a **load resistor**.

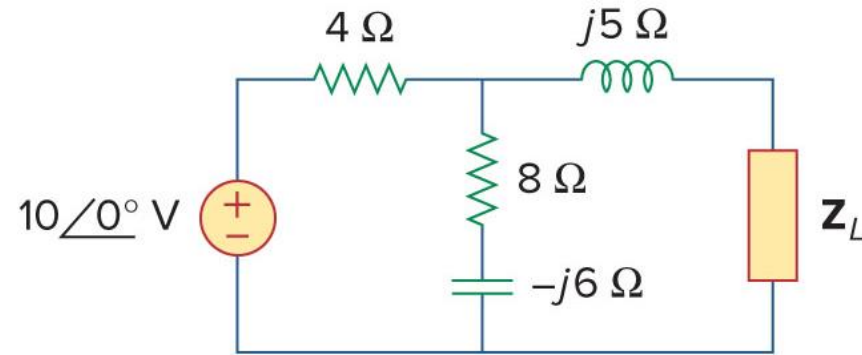Exercise


Determine the load impedance \mathbf{Z}_L that maximizes the average power drawn from the circuit below, and then find the maximum average power.



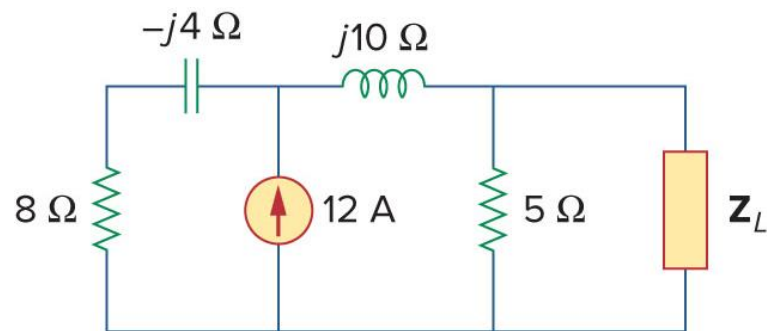Exercise


For the circuit shown below, find the load impedance \mathbf{Z}_L that absorbs maximum average power. Calculate the maximum average power.

- For practice!
- Answer: $\mathbf{Z}_L = \mathbf{Z}_{Th}^* = 3.415 - j0.731 \Omega$ and $P_{max} = 51.47 \text{ W}$ absorbed



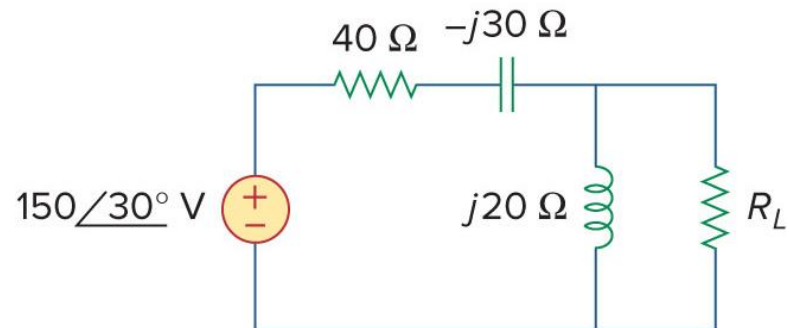Exercise


In the circuit below, find the value of R_L that will absorb the maximum average power, and then calculate that power.



Exercise

For the circuit shown below, find the load resistance R_L such that it absorbs maximum average power, and then calculate the maximum average power transferred to it.

- For practice!
- Answer: $R_L = |\mathbf{Z}_{Th}|^2 = 30 \Omega$ and $P_{max} = 23.06 \text{ W}$ absorbed

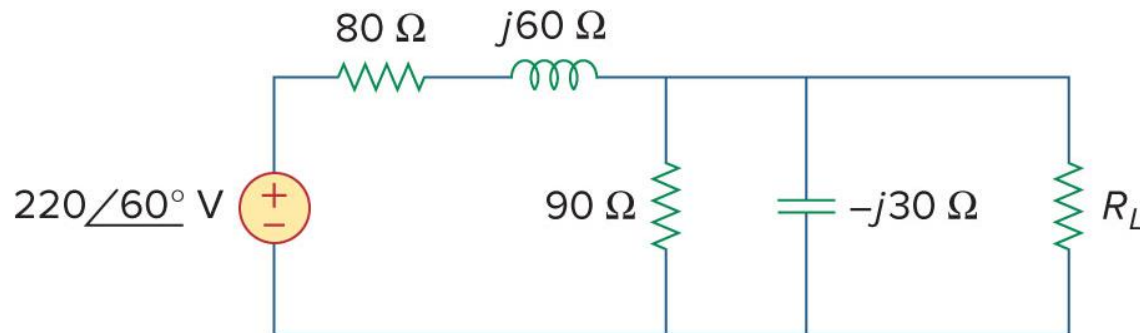

Effective or RMS value

- When a time-varying source is delivering power to a resistive load, we often want to know the effectiveness of that source on delivering power.
- The **effective value** of a **periodic** current is a **DC** current that can deliver **the same average power** to a **resistor** as the periodic current.

Consider the circuit in Fig. (a). The average power is given by:


$$P = \frac{1}{T} \int_0^T p(t) dt = \frac{1}{T} \int_0^T Ri(t)^2 dt = \frac{R}{T} \int_0^T i(t)^2 dt$$

The power absorbed in the DC circuit in Fig. (b) is:


$$P = RI_{\text{eff}}^2$$

The objective is to find I_{eff} such that it delivers the same average power as the AC circuit. Thus:
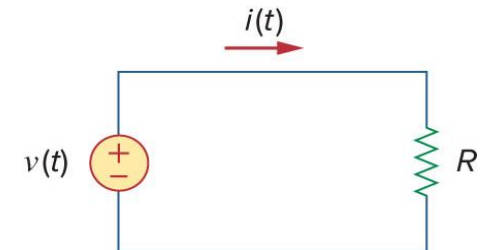
$$P = RI_{\text{eff}}^2 = \frac{R}{T} \int_0^T i(t)^2 dt \quad \Rightarrow \quad I_{\text{eff}} = \sqrt{\frac{1}{T} \int_0^T i(t)^2 dt}$$



(a)

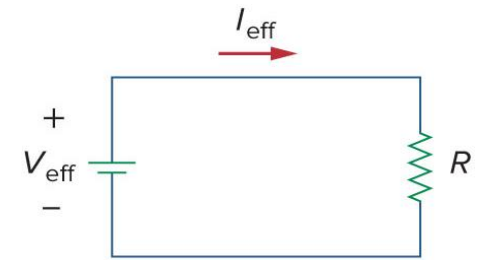

(b)

Effective or RMS value

- The effective value of the AC voltage is obtained in the same way as the effective current:

$$V_{\text{eff}} = \sqrt{\frac{1}{T} \int_0^T v(t)^2 dt}$$

- The effective values for both current and voltage take the form of the **square root** of the **average (mean)** of the **square** of the periodic signal. This is referred to as the **root mean square**, or **RMS value** for short.

$$I_{\text{rms}} = I_{\text{eff}} \quad \text{and} \quad V_{\text{rms}} = V_{\text{eff}}$$

For any periodic signal $x(t)$ in general, the RMS value is given by:

$$X_{\text{eff}} = X_{\text{rms}} = \sqrt{\frac{1}{T} \int_0^T x(t)^2 dt}$$

Effective or RMS value

- The RMS value of the **constant signal** (DC signal) is the **constant itself**.
- For a sinusoid $i(t) = I_m \cos(\omega t + \phi)$ the RMS value is obtained as follows:

Using the trigonometric identity
 $\cos^2(a) = \frac{1 + \cos(2a)}{2}$

$$I_{\text{rms}} = \sqrt{\frac{1}{T} \int_0^T I_m^2 \cos^2(\omega t + \phi) dt} = \sqrt{\frac{I_m^2}{T} \underbrace{\int_0^T \frac{1}{2} dt}_{= \frac{1}{2}T} + \underbrace{\int_0^T \cos(2\omega t + 2\phi) dt}_{= 0, \text{ Integration over an integer multiple of period}}}$$

$\Rightarrow I_{\text{rms}} = \frac{I_m}{\sqrt{2}}$

- Similarly, for $v(t) = v_m \cos(\omega t + \phi) \Rightarrow V_{\text{rms}} = \frac{V_m}{\sqrt{2}}$

Note: These RMS values are only valid for sinusoidal currents and voltages, or sinusoidal signals in general.

Note: An example of RMS value is the **household appliances** working with RMS voltage $V_{\text{rms}} = 220 \text{ V}$, which is:

$$v(t) = 220\sqrt{2} \cos(2\pi 50t) \text{ V}$$

RMS value and average power

- The **average power** can be determined in terms of RMS values:

$$P = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) = \frac{1}{\sqrt{2} \times \sqrt{2}} V_m I_m \cos(\theta_v - \theta_i) = \frac{V_m}{\sqrt{2}} \frac{I_m}{\sqrt{2}} \cos(\theta_v - \theta_i)$$

$$P = V_{\text{rms}} I_{\text{rms}} \cos(\theta_v - \theta_i)$$

- Similarly, the **average power** absorbed by a **resistor** R is given by:

$$P = V_{\text{rms}} I_{\text{rms}}$$

$$P = R I_{\text{rms}}^2$$

$$P = \frac{V_{\text{rms}}^2}{R}$$

Questions?

