

Topic 6 recap

- Operational Amplifiers (Op Amps) are **active** elements.
 - They can be modelled as a **voltage-controlled voltage source**.
 - Op Amp circuits are designed to perform **mathematical operations** on input signals. They are manufactured in the form of Integrated circuits (ICs).
- From the 8 pins of the Op Amp IC, we are only interested in 5 of them.
 - Inverting input v_1 (pin 2).
 - Non-inverting input v_2 (pin 3).
 - Output v_o (pin 6).
 - Positive power supply V^+ (pin 7).
 - Negative power supply V^- (pin 4).
- The output of the Op Amp in open-loop is proportional to the differential input voltage.
$$v_o = Av_d = (v_2 - v_1), \text{ where } A \text{ is the open-loop gain (in the range of } 10^5 \text{ to } 10^8).$$
- Op Amp circuits should be operated in the **linear region** to avoid **saturation** of the output (output should not exceed the voltage of power supply $|V_{cc}|$).

$$-V_{cc} \leq v_o \leq V_{cc}$$

Topic 6 recap

- An **Ideal Op Amp** has the following properties:
 - **Open-loop gain** close to **infinity**, $A \simeq \infty$.
 - **Input** resistance close to, **infinity** $R_i \simeq \infty \Omega$ (open circuit).
 - **Output** resistance close to **zero**, $R_o \simeq 0 \Omega$ (short circuit).
 - The **currents** into both terminals are **zero**.


$$i_1 = i_2 = 0$$

- The **voltage** across the input terminals is **zero** (if there is negative feedback).

$$v_d = v_2 - v_1 = 0 \quad \text{or} \quad v_1 = v_2$$


- Use **Nodal analysis** to solve and analyse Op Amp circuits.
 - KCL at input nodes to calculate v_0 .
 - Once output voltage v_0 is found, use KCL at output node to find output current i_0 (if needed).
 - Gain of the circuit = ratio of output to the input (v_0 / v_i).
- Op Amp circuits are mostly used in **negative feedback** configuration.
 - The output is fed back to the inverting input via feedback resistor R_f .
 - The inverting input and non-inverting input are connected to either ground or a source via input resistor R_1 .

Topic 6 recap

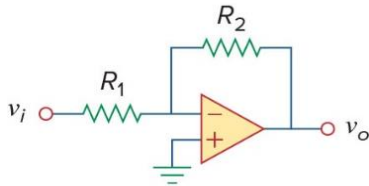


Inverting amplifier

$$v_o = -\frac{R_2}{R_1}v_i$$

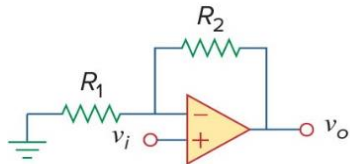


Noninverting amplifier
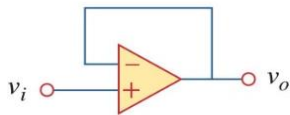
$$v_o = \left(1 + \frac{R_2}{R_1}\right)v_i$$




Voltage follower

$$v_o = v_i$$

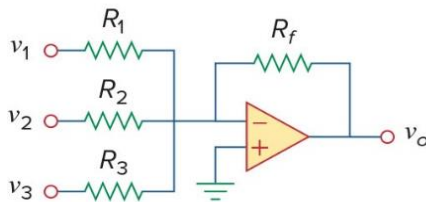


Summer
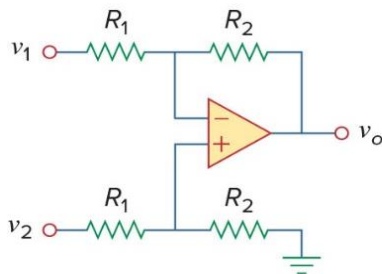
$$v_o = -\left(\frac{R_f}{R_1}v_1 + \frac{R_f}{R_2}v_2 + \frac{R_f}{R_3}v_3\right)$$




Difference amplifier

$$v_o = \frac{R_2}{R_1}(v_2 - v_1)$$

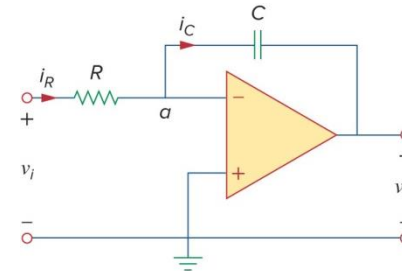

Integrator
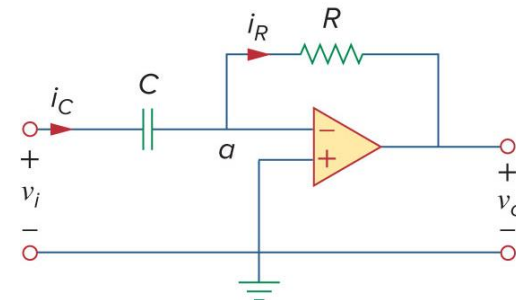
$$v_o(t) = -\frac{1}{RC} \int_0^t v_i(\tau) d\tau$$



Differentiator

$$v_o(t) = -RC \frac{dv_i}{dt}$$