

Topic 8: AC Circuits I

- For the following pairs of sinusoids, find the phasors corresponding to each pair and then determine which one leads and by how much. Also, sketch each pair in phasor diagram using rectangular form of the phasors.
 - $v(t) = 50 \cos(4t - 60^\circ)$ V and $i(t) = 17 \sin(4t + 50^\circ)$ A
 - $v_1(t) = 4 \cos(314t + 10^\circ)$ V and $v_2(t) = -20 \cos(314t)$ V
 - $i_1(t) = 13 \cos(2t) + 5 \sin(2t)$ A and $i_2(t) = 15 \cos(2t - 11.8^\circ)$ A
 - $v(t) = 50 \cos(20t + 70^\circ)$ V and $i(t) = 40 \cos(25t + 20^\circ)$ V

Answer:

- $V = 50 \angle(-60^\circ)$ V, $I = 17 \angle(-40^\circ)$ A. i leads v by 20°
- $V_1 = 4 \angle(10^\circ)$ V, $V_2 = 20 \angle(\pm 180^\circ)$ V. v_2 leads v_1 by 170° or v_1 leads v_2 by 190°
- $I_1 = 13.92 \angle(-21.03^\circ)$ A, $I_2 = 15 \angle(-11.8^\circ)$ A. i_2 leads i_1 by 9.23°
- Not comparable! Why?


Solution: Transform all sinusoids to Cosine form first

a) $v(t) = 50 \cos(4t - 60^\circ)$ V $\rightarrow V = 50 \angle -60^\circ$ \rightarrow transform to rectangular

for phasor diagram: $V = 50 \cos(-60^\circ) + j 50 \sin(-60^\circ) = 25 - j 43.3$ V

$i(t) = 17 \sin(4t + 50^\circ)$ A $= 17 \cos(4t + 50^\circ - 90^\circ) = 17 \cos(4t - 40^\circ)$ A

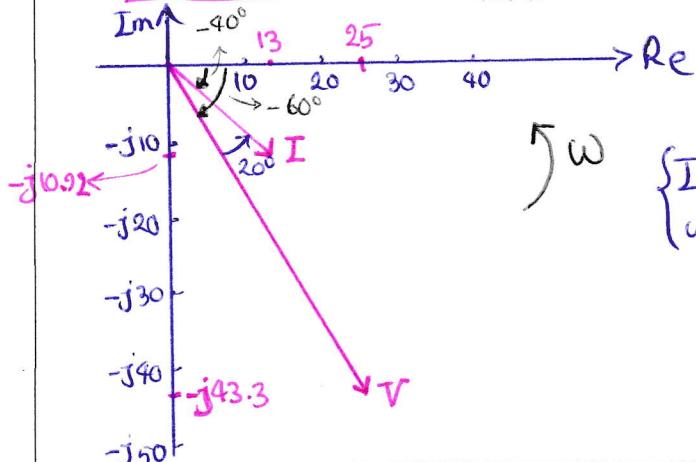$\Rightarrow I = 17 \angle -40^\circ$ A $\xrightarrow{\text{rectangular form}} I = 17 \cos(-40^\circ) + j 17 \sin(-40^\circ) = 13.02 - j 10.92$ A




$\left\{ \begin{array}{l} I \text{ leads } V \text{ by } 20^\circ \text{ thus } i \text{ leads } v \\ \text{with the same phase } (20^\circ) \end{array} \right.$

$$b) V_1 = 4 \cos(314t + 10^\circ) V \rightarrow V_1 = 4 \angle 10^\circ \text{ rectangular form}$$

$$= 3.94 + j0.69 V$$

$$V_2 = -20 \cos(314t) V = 20 \cos(314t \pm 180^\circ) \text{ both are correct!}$$
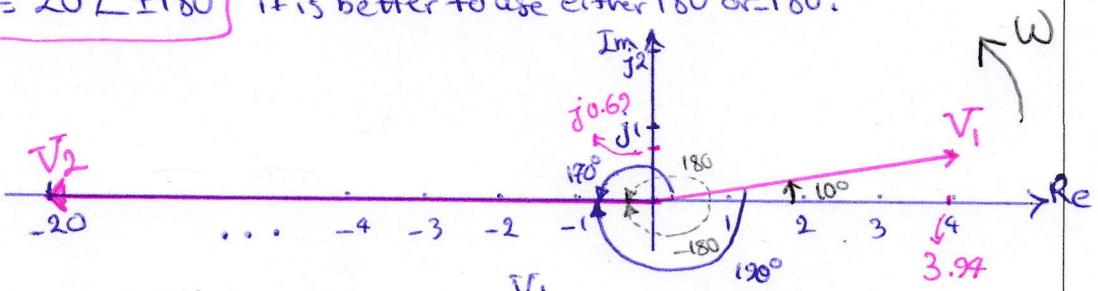
$$\rightarrow V_2 = 20 \angle \pm 180^\circ \text{ it is better to use either } 180^\circ \text{ or } -180^\circ.$$



{if we use $+180^\circ$ for $V_2 \rightarrow V_2$ leads by 170° (preferable)
 {if we use -180° for $V_2 \rightarrow V_1$ leads V_2 by 190°

$$C) i_1 = 13 \cos 2t + 5 \sin 2t A = 13 \cos 2t + 5 \cos(2t - 90^\circ)$$

$$\rightarrow I_1 = 13 \angle 0^\circ + 5 \angle -90^\circ = 13 + 5 \cos(-90^\circ) + j5 \sin(-90^\circ)$$

$$\text{Note: } 13 \angle 0^\circ = 13$$


$$= 13 - 5j A$$

$$\text{Note: } 5 \angle -90^\circ = -j5$$

$$\text{Transfer to polar form} \rightarrow I_1 = \sqrt{13^2 + 5^2} \angle \tan^{-1}\left(\frac{-5}{13}\right) = 13.92 \angle -21.03^\circ A$$

$$I_2 = 15 \cos(2t - 11.8^\circ) A \rightarrow I_2 = 15 \angle -11.8^\circ A$$
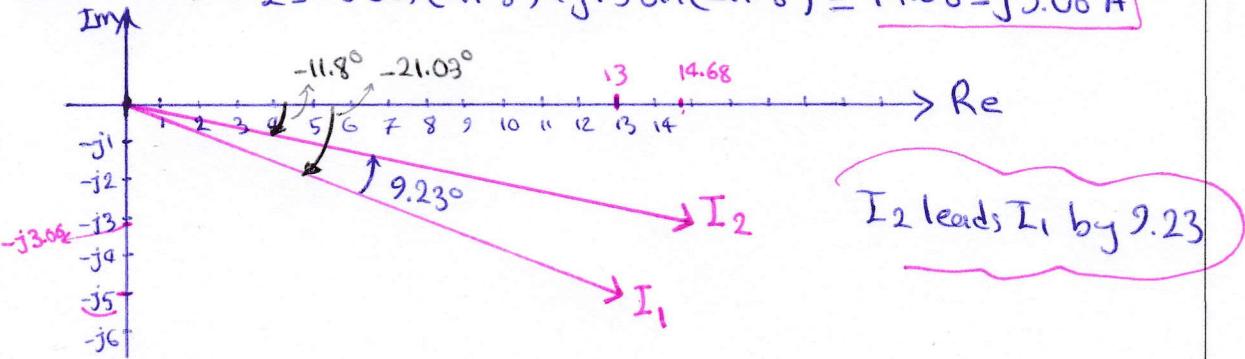
$$\text{rectangular} \rightarrow I_2 = 15 \cos(-11.8^\circ) + j15 \sin(-11.8^\circ) = 14.68 - j3.06 A$$



d) They cannot be compared in phasor domain since they have different frequencies $\rightarrow 50 \cos(20t + 70^\circ) \quad 40 \cos(25t + 20^\circ)$

$$\omega_v = 20 \text{ rad/s} \neq \omega_i = 25 \text{ rad/s}$$

2. Evaluate the following complex numbers and express your results in both polar and rectangular forms.

a) $\frac{(5\angle 10^\circ)(10\angle(-40^\circ))}{(4\angle(-80^\circ))(-6\angle 50^\circ)}$

b) $\frac{2+j3}{1-j6} + \frac{7-j8}{-5+j11}$

c) $\begin{vmatrix} 2+j3 & -j2 \\ 2e^{-j\pi/2} & 8-j5 \end{vmatrix}$

d) $\frac{60e^{j45^\circ}}{7.5-j10} + j2$

Answer:

a) Polar form: $2.083\angle 180^\circ$, rectangular forms: -2.083

b) Polar form: $1.284\angle 173.2^\circ$, rectangular forms: $-1.275 + j0.152$

c) Polar form: $37.696\angle 21.8^\circ$, rectangular forms: $35 + j14$

d) Polar form: $6.786\angle 95.741^\circ$, rectangular forms: $-0.678 + j6.752$

Solution:

$$\text{a) } \frac{(5\angle 10^\circ)(10\angle(-40^\circ))}{4\angle(-80^\circ)(-6\angle 50^\circ)} = \frac{5 \times 10 \angle(10^\circ - 40^\circ)}{4 \times (-6) \angle(-80^\circ + 50^\circ)} = \frac{50 \angle -30^\circ}{-24 \angle -30^\circ}$$

$$= -\frac{50}{24} \angle 0 = \underline{-2.083} \quad \text{polar} \quad \underline{2.083 \angle \pm 180^\circ}$$

either 180° or -180°
one is enough!

b) $\frac{2+j3}{1-j6} + \frac{7-j8}{-5+j11}$

method ①
 using Complex Conjugate for division $z\bar{z}^* = |z|^2$
 $i \neq z = x+jy \rightarrow \bar{z} = x-jy$ also $j^2 = -1$

$$\Rightarrow \frac{(2+j3)(1+j6)}{1+6^2} + \frac{(7-j8)(-5-j11)}{5^2+11^2} = \frac{2(j12+j3)+j^218}{37} + \frac{-35-j77+j40+j88}{146}$$

$$= \frac{2-18+j(12+3)}{37} + \frac{-35-88+j(40-77)}{146} = \frac{-16+j15}{37} + \frac{-123-j37}{146}$$

$$= \frac{-16}{37} + \frac{j15}{37} - \frac{123}{146} - \frac{j37}{146} = \underline{-1.275 + j0.152}$$

to polar form $\sqrt{(-1.275)^2 + (0.152)^2} / \tan^{-1}\left(\frac{0.152}{-1.275}\right) = \underline{1.284 \angle 173.2^\circ}$

Method ② using polar form transformation first

$2+j3 \cong 3.6 \angle 56.3^\circ$

$1-j6 \cong 6.08 \angle -80.53^\circ$

$7-j8 = 10.63 \angle -48.81^\circ$

$-5+j11 = 12.08 \angle 114.49^\circ$

$$\Rightarrow \frac{3.6 \angle 56.3^\circ}{6.08 \angle -80.59^\circ} + \frac{10.63 \angle -48.81^\circ}{12.08 \angle 14.94^\circ} = 0.592 \angle 136.83^\circ + 0.88 \angle -163.25^\circ$$

back to rectangular form $-0.432 + j0.405 + (-0.842 - j0.253) = -1.275 + j0.152$

C1 Determinant: $(2+j3)(8-j5) - (-j2)(2e^{-j\pi/2})$

Note: $e^{j\pi/2} = e^{j90^\circ}$
 $= 1 \angle 90^\circ$
 $= -j$

$$\Rightarrow 16 - j10 + j24 - j^2(15 - j^24) = 16 + 15 + 4 + j(24 - 10)$$

$$= 35 + j14$$

polar form: $\sqrt{35^2 + 14^2} \angle \tan^{-1}\left(\frac{14}{35}\right) = 37.69 \angle 21.8^\circ$

d) $\frac{60 \angle 45^\circ}{\sqrt{7.5^2 + 10^2} \angle \tan^{-1}\left(\frac{-10}{7.5}\right)} + j2$

Polar form $\frac{60 \angle 45^\circ}{12.5 \angle -53.13^\circ} + j2 = \frac{60}{12.5} \angle (45^\circ + 53.13^\circ) + 2j$

$$= 4.8 \angle 98.13^\circ + 2j \xrightarrow{\text{rectangular form}} 4.8 \cos(98.13^\circ) + j4.8 \sin(98.13^\circ) + 2j$$

$$= -0.678 + j4.752 + j2 = -0.678 + j6.752$$

Polar form $\sqrt{(-0.678)^2 + (6.752)^2} \angle \tan^{-1}\frac{6.752}{-0.678} = 6.786 \angle 95.74^\circ$

3. Obtain the sinusoids corresponding to each of the following phasors.

a) $V_1 = 60 \angle 15^\circ V, \omega = 1 \text{ rad/s}$

b) $V_2 = 6 + j8 V, \omega = 40 \text{ rad/s}$

c) $I_1 = 2.8e^{-j\pi/3} A, f = 50 \text{ Hz}$

Answer:

a) $v_1(t) = 60 \cos(t + 15^\circ) V$

b) $v_2(t) = 10 \cos(40t + 53.13^\circ) V$

c) $i_1(t) = 2.8 \cos(314.16t - 60^\circ) A$

Solution: pick the magnitude as amplitude with the given frequency in rad/s and the phase as the phase of the sinusoid. \star Assumption from phasor to sinusoid is always Cosine form

a) $V_1(t) = 60 \cos(t + 15^\circ)$

b) $V_2 = \sqrt{6^2 + 8^2} \angle \tan^{-1}\left(\frac{8}{6}\right) = 10 \angle 53.13^\circ \Rightarrow v_2(t) = 10 \cos(40t + 53.13^\circ)$

c) $I_1 = 2.8 \angle -60^\circ \text{ but } \omega = 2\pi f = 2 \times 3.1416 \times 50 = 314.16 \text{ rad/s}$

$\Rightarrow i_1(t) = 2.8 \cos(314.16t - 60^\circ)$

4. Find $v(t)$ and $i(t)$ in the following integrodifferential equations using phasor approach.

a) $v(t) + \int v(t) dt = 10 \cos(t)$

b) $10 \int i(t) dt + \frac{di(t)}{dt} + 6i(t) = 5 \cos(5t + 22^\circ)$

Answer:

a) $v(t) = 7.071 \cos(t + 45^\circ)$ V

b) $i(t) = 745 \cos(5t - 4.56^\circ)$ mA

Hint: use the properties of differentiation and integration in time domain and their equivalents in phasor domain ,i.e., $\frac{dv(t)}{dt} \Leftrightarrow j\omega V$ and $\int v(t) dt \Leftrightarrow \frac{V}{j\omega}$, then solve the equations for the phasor of the main variables by writing the equations in phasor domain assuming that V is the phasor of $v(t)$ and I is the phasor of $i(t)$.

Solution: "phasor domain can be used to solve differential equations"

a) phasor domain $V + \frac{V}{j\omega} = 10 \angle 0^\circ \xrightarrow{\omega=1 \text{ rad/s}} V - jV = 10$

$$\rightarrow V(1-j) = 10 \rightarrow V = \frac{10}{1-j} = \frac{10(1+j)}{1^2 + 1^2} = \underline{\underline{5+j5 \text{ V}}}$$

Polar form $\sqrt{5^2 + 5^2} \angle \tan^{-1}\left(\frac{5}{5}\right) = \sqrt{50} \angle 45^\circ = \underline{\underline{7.071 \angle 45^\circ \text{ V}}}$

Thus $\underline{\underline{v(t) = 7.071 \cos(t + 45^\circ) \text{ V}}}$

the solution to the equation

b) phasor domain $\frac{10I}{j\omega} + j\omega L + 6I = 5 \angle 22^\circ \xrightarrow{\omega=5 \text{ rad/s}}$

$$\Rightarrow -j\frac{10}{5}I + j5I + 6I = 5 \angle 22^\circ \rightarrow I(6+j3) = 5 \angle 22^\circ$$


$$\Rightarrow I = \frac{5 \angle 22^\circ}{6+j3} = \frac{5 \angle 22^\circ}{\sqrt{6^2+3^2} \angle \tan^{-1}\left(\frac{3}{6}\right)} = \frac{5 \angle 22^\circ}{6.708 \angle 26.58^\circ}$$

$$\Rightarrow I = \frac{5}{6.708} \angle (22 - 26.58) = \underline{\underline{0.745 \angle -4.56^\circ \text{ A}}}$$

Thus $\underline{\underline{i(t) = 745 \cos(5t - 4.56^\circ) \text{ mA}}}$

* Steady-state Solution of a differential equation to a sinusoidal input is always a sinusoid with the same frequency. *

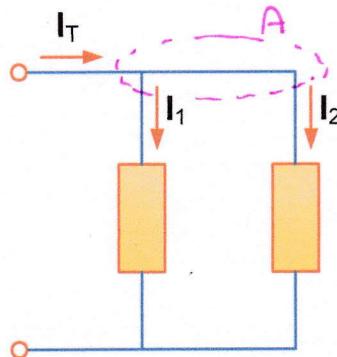5. (Final Exam – S1, 2015) In the following figure, $i_1 = 100 \sin(50t + 100^\circ)$ A and $i_T = 50 \sin(50t - 40^\circ)$ A. Determine phasors \mathbf{I}_1 , \mathbf{I}_2 and \mathbf{I}_T and draw the phasor diagram showing \mathbf{I}_1 , \mathbf{I}_2 and \mathbf{I}_T . Also, determine which one lags and by how much.



Answer: $\mathbf{I}_1 = 100 \angle 10^\circ$ A, $\mathbf{I}_2 = 141.98 \angle (-156.92^\circ)$ A and $\mathbf{I}_T = 50 \angle (-130^\circ)$ A.
 \mathbf{I}_2 lags \mathbf{I}_T by 26.92° and lags \mathbf{I}_1 by 166.92° , also \mathbf{I}_T lags \mathbf{I}_1 by 140° .

Solution:

$$i_1 = 100 \cos(50t + 100^\circ - 90^\circ) = 100 \cos(50t + 10^\circ) \rightarrow \mathbf{I}_1 = 100 \angle 10^\circ$$

$$i_T = 50 \cos(50t - 40^\circ - 90^\circ) = 50 \cos(50t - 130^\circ) \rightarrow \mathbf{I}_T = 50 \angle -130^\circ$$

rectangular form $\mathbf{I}_1 = 100 \cos(10^\circ) + j100 \sin(10^\circ) = 98.48 + j17.36$ A


$$\mathbf{I}_T = 50 \cos(-130^\circ) + j50 \sin(-130^\circ) = -32.14 - j38.3$$
 A

KCL: $\mathbf{I}_T = \mathbf{I}_1 + \mathbf{I}_2 \rightarrow \mathbf{I}_2 = \mathbf{I}_T - \mathbf{I}_1 = -32.14 - j38.3 - (98.48 + j17.36)$
@ node A

$$\Rightarrow \mathbf{I}_2 = -130.62 - j55.66$$
 A


Polar form $\sqrt{130.62^2 + 55.66^2} \angle \tan^{-1}\left(\frac{55.66}{-130.62}\right)$
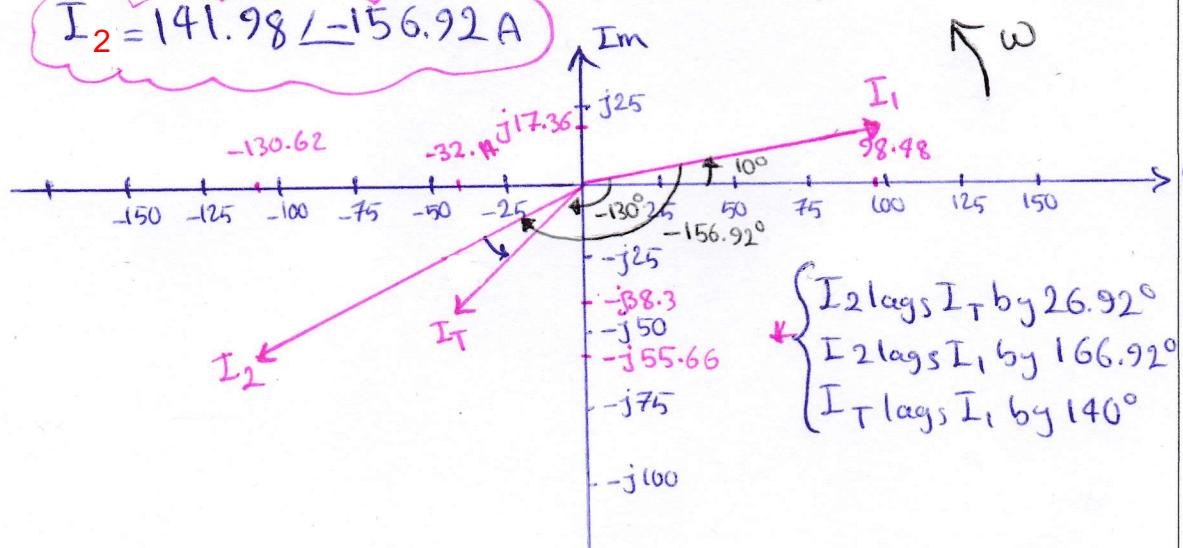
$$\mathbf{I}_2 = 141.98 \angle -156.92^\circ$$



6. For the following circuit,

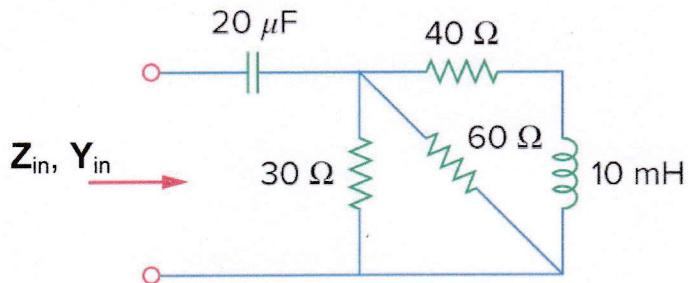- a) Find the input impedance Z_{in} and input admittance Y_{in} with their corresponding resistance, reactance, conductance and susceptance if $\omega = 10^3 \text{ rad/s}$.
- b) Is the circuit *inductive or capacitive?*



Answer:

a) $\begin{cases} Z_{in} = R + jX = 13.51 - j48.92 \Omega = 50.75 \angle (-74.56^\circ) \Omega \\ Y_{in} = \frac{1}{Z_{in}} = G + jB = 5.24 + j18.99 \text{ mS} = 19.704 \angle 74.56^\circ \text{ mS} \end{cases}$


b) Capacitive.

Solution: First find all the individual impedances:

$$20 \mu\text{F} \rightarrow \frac{1}{j\omega C} = \frac{-j}{10^3 \times 20 \times 10^{-6}} = \frac{-j}{2 \times 10^{-2}} = -j \frac{100}{2} = -j50 \Omega$$

$$10 \text{ mH} \rightarrow j\omega L = j \times 10^3 \times 10 \times 10^{-3} = j10 \Omega$$

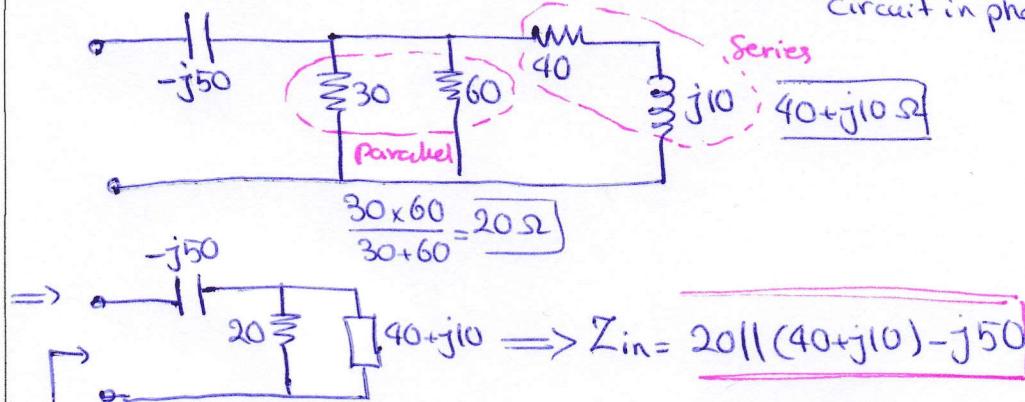Then, redraw the circuit in phasor domain: (It is important to draw the circuit in phasor domain in exam)



$$Z_{in} = \frac{20 \times (40+j10)}{20+40+j10} - j50 = \frac{800+j200}{60+j10} - j50 = \frac{(80+j20)(6-j)}{6^2+1^2} - j50$$

$$= 13.51 + j1.08 - j50 = 13.51 - j48.92 \Omega$$

$$Y_{in} = \frac{1}{Z_{in}} = \frac{1}{13.51 - j48.92}$$

$R = 13.51$
 $X = -48.92 \rightarrow$ negative reactance
 \Rightarrow Capacitive circuit

polar form $= \frac{1}{\sqrt{13.51^2 + 48.92^2} / \tan(\frac{-48.92}{13.51})} = \frac{1}{50.75 \angle -74.56^\circ} = 19.704 \angle 74.56^\circ \text{ mS}$

rectangular form $Y_{in} = 19.704 \cos(74.56^\circ) + j19.704 \sin(74.56^\circ) = \frac{G}{G} + j \frac{B}{B} \text{ mS}$

$$\{ G = 5.24 \}$$

$$\{ B = 18.99 \}$$

7. Calculate I_o in Fig. 1 and $v_o(t)$ in Fig. 2.

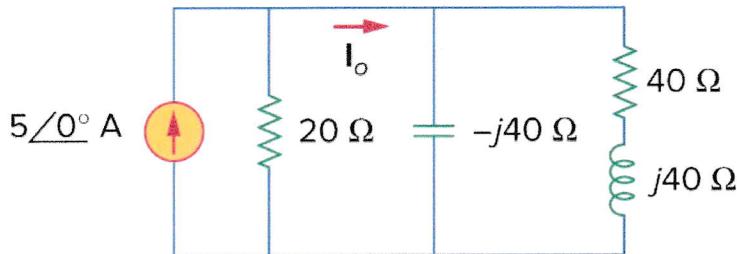


Fig. 1

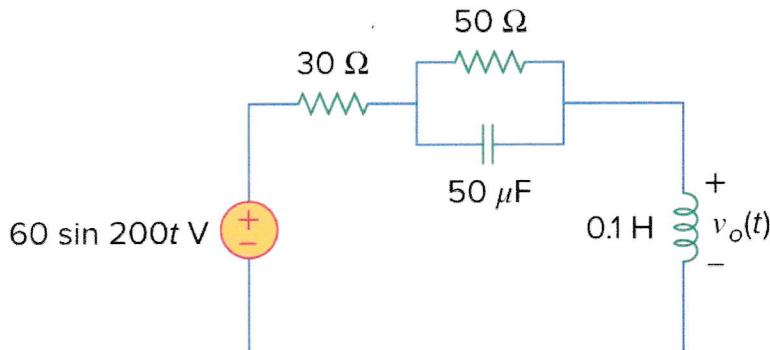


Fig. 2

Answer: Fig. 1: $I_o = 1.386 \angle 33.69^\circ$ A, and Fig. 2: $v_o(t) = 17.14 \cos(200t)$ V

Solution:

Fig 1: The circuit is already in phasor domain

Simplify:

$$\begin{aligned}
 & \text{Original circuit: } \\
 & \text{Simplified circuit: } \\
 & (40 + j40) \parallel (-j40) = 40 - j40 \\
 & \rightarrow (40 + j40) \parallel (-j40) = \frac{(40 + j40) \times (-j40)}{40 + j40 - j40} = \frac{-j1600 - j^2 1600}{40} = \\
 & = \underline{\underline{40 - j40 \Omega}}
 \end{aligned}$$

Thus: I_o is obtained via current division:

$$\begin{aligned}
 I_o &= \frac{20}{20 + 40 - j40} \times 5 \angle 0^\circ = \frac{10 \angle 0^\circ}{6 - j4} = \frac{10 \angle 0^\circ}{\sqrt{6^2 + 4^2} \angle \tan^{-1} \frac{4}{6}} = \frac{10 \angle 0^\circ}{7.21 \angle -33.69^\circ} \\
 \Rightarrow I_o &= \frac{10}{7.21} \angle +33.69^\circ = 1.38 \angle 33.69^\circ \text{ A}
 \end{aligned}$$

→ Next page for Fig 2 →


Fig 2: Find all impedances and phasors first:

$$60 \sin 200t = 60 \cos(200t - 90^\circ) \rightarrow 60 \angle -90^\circ \quad \omega = 200 \text{ rad/s}$$

$$50 \mu F \rightarrow \frac{1}{j\omega C} = \frac{-j}{200 \times 50 \times 10^{-6}} = -j100 \Omega$$

$$0.1 \text{ H} \rightarrow j\omega L = j200 \times 0.1 = j20 \Omega$$


Redraw the circuit in phasor domain:

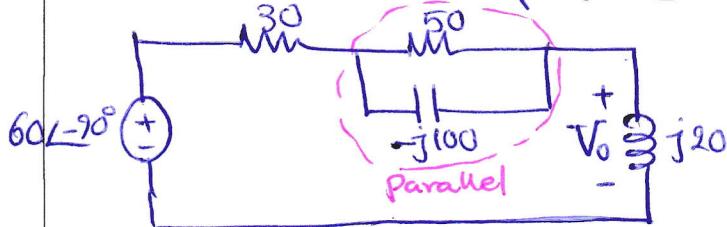

Find V_o which is the phasor of $v_o(t)$

$$50 \parallel (-j100) = \frac{50 \times (-j100)}{50 - j100} = \frac{-j100}{1 - j2} = \frac{-j100(1 + j2)}{1 + 4} = \frac{1+4}{5}$$
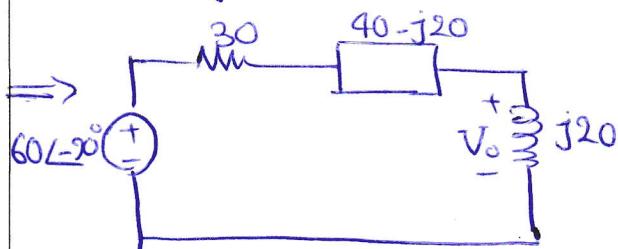
$$= \frac{-j20(1 + j2)}{-j20 - j^240} = \frac{40 - j20}{40 - j^240} \Omega$$




V_o is obtained via Voltage division

$$V_o = \frac{j20}{30 + 40 - j20 + j20} \times 60 \angle -90^\circ \frac{j20}{70} \times 60 \angle -90^\circ = 0.285 \angle 90^\circ \times 60 \angle -90^\circ$$

$$= 17.14 \angle 0^\circ \text{ V}$$

$$\text{Thus: } v_o(t) = 17.14 \cos(200t) \text{ V}$$

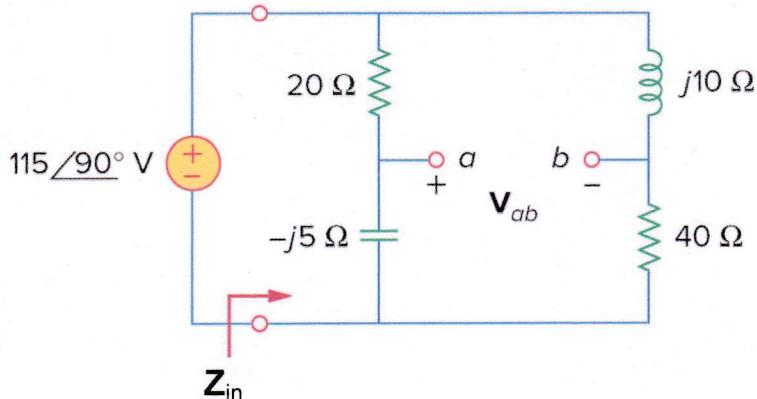
8. For the circuit given below, calculate input impedance Z_{in} and V_{ab} .



Answer: $Z_{in} = 14.069 - j1.172 \Omega = 14.117 \angle(-4.76^\circ) \Omega$, and $V_{ab} = 101.4 \angle(-90^\circ) V \equiv 101.4 \angle 270^\circ V$

Solution: The circuit is already in phasor domain


for Z_{in} :

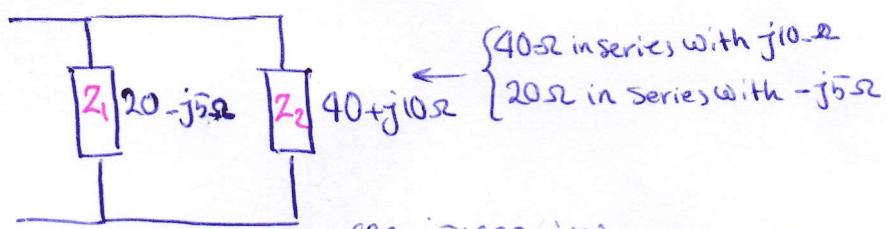

$$\Rightarrow Z_{in} = (20-j5) \parallel (40+j10) = \frac{(20-j5)(40+j10)}{20-j5+4+j10} = \frac{800-j200+j200-j50}{60+j5} \\ = \frac{850}{60+j5} = \frac{170}{12+j} = 14.069 - j1.172 \Omega$$

in polar form: $Z_{in} = \sqrt{14.069^2 + 1.172^2} \angle \tan^{-1}\left(\frac{-1.172}{14.069}\right) = 14.117 \angle -4.76^\circ \Omega$

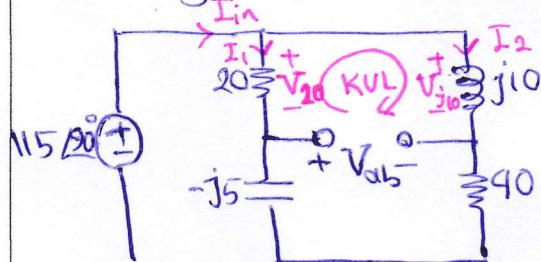* Finding V_{ab} : We can use two approaches: long method and quick method



First we need to write KVL either in the upper mesh or lower mesh

$$\text{KVL: } -V_{ab} - V_{20} + V_{j10} = 0 \\ \Rightarrow V_{ab} = V_{j10} - V_{20}$$

Now to find V_{j10} and V_{20} we can use two approaches:


First $\rightarrow V_{20} = 20I_1$ and $V_{j10} = j10I_2 \rightarrow I_1 + I_2 = I_{in}$

long method ↑ So we need to find I_{in} to calculate I_1 and I_2 using current division

To find I_{in} , we can use Z_{in} :

that we calculated $115 \angle 90^\circ$ before $Z_{in} \rightarrow$ next page
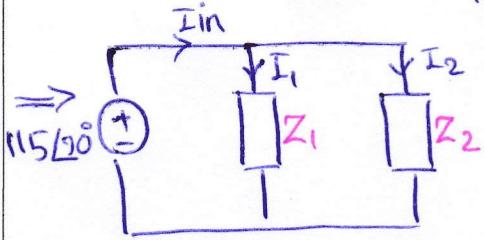
$$\rightarrow I_{in} = \frac{115 \angle 90^\circ}{Z_{in}} = \frac{115 \angle 90^\circ}{14.117 \angle -4.76^\circ} = 8.145 \angle 94.76^\circ A \quad (I)$$



$$Z_1 = 20 - j5 \Omega$$

$$Z_2 = 40 + j10 \Omega$$


$$\Rightarrow I_1 = \frac{40 + j10}{60 + j5} \times I_{in}$$

$$I_2 = \frac{20 - j5}{60 + j5} \times I_{in}$$

Simplify $I_1 = \frac{8+j2}{12+j} I_{in}$

$I_2 = \frac{4-j}{12+j} I_{in}$

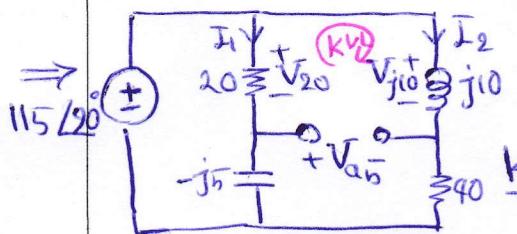No need to find their numerical values as you will see in KVL equation



factor out I_{in}

$$\Rightarrow V_{ab} = \left[\frac{j40 - j^2 10 - 160 - j40}{12+j} \right] I_{in} = \frac{-150}{12+j} I_{in}$$

use (I), $V_{ab} = 101.4 \angle -90^\circ$ or $101.4 \angle 270^\circ V$

Second approach is to use voltage division to directly find V_{j10} and V_{20} (This one is suggested by a student in a tutorial class)

Note that the 20Ω and $-j5\Omega$ branch is in parallel with the source as well as parallel with $j10\Omega$ and 40Ω

\Rightarrow Find V_{20} using voltage division between 20Ω , $-j5\Omega$ and $115 \angle 90^\circ V$

quick method Find V_{j10} using voltage division between $j10\Omega$, 40Ω and $115 \angle 90^\circ V$

$$V_{20} = \frac{20}{20 - j5} \times 115 \angle 90^\circ$$

$$V_{j10} = \frac{j10}{40 + j10} \times 115 \angle 90^\circ$$

simplify $V_{20} = \frac{4}{4-j} \times 115 \angle 90^\circ$

$$V_{j10} = \frac{j}{4+j} \times 115 \angle 90^\circ$$


$$\Rightarrow V_{ab} = V_{j10} - V_{20} = \left(\frac{j}{4+j} - \frac{4}{4-j} \right) \times 115 \angle 90^\circ$$

$$= \frac{j(4-j) - 4(j+4)}{(4+j)(4-j)} \times 115 \angle 90^\circ$$

$$= -\frac{15}{17} \times 115 \angle 90^\circ = 101.4 \angle -90^\circ V$$

Challenging Problem

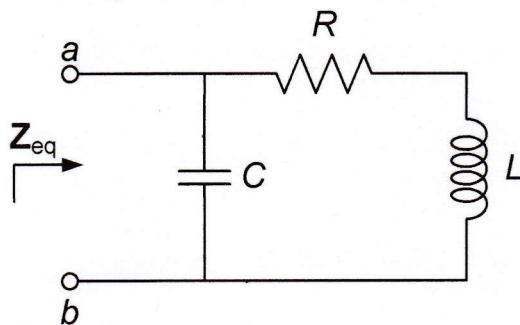
9. (Final Exam – S1, 2016) Consider the circuit shown in the figure below, where $L = 27 \text{ mH}$, $C = 22 \mu\text{F}$ and $R = 6 \Omega$. Find the angular frequency ω for which the impedance Z_{eq} between terminals a-b is purely resistive.



Answer: $\omega = 1.278 \times 10^3 \text{ rad/s}$

Hint: The reactance of Z_{eq} is a function of ω and it should be zero for pure resistive impedance, or the phase of Z_{eq} should be zero for pure resistive impedance.

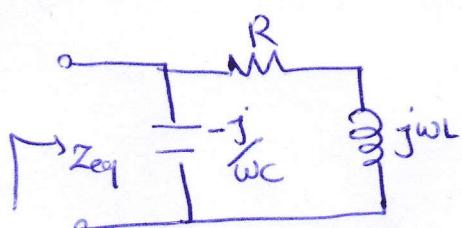Solution: Redraw the circuit in phasor domain without substituting numerical values:



$$Z_{eq} = R(\omega) + jX(\omega) \rightarrow X(\omega) = 0 \\ = |Z_{eq}| / Z_{eq} \rightarrow \angle Z_{eq} = 0$$

Both methods result in Z_{eq} being a real number meaning pure resistive impedance.

* Let's first try to find $X(\omega)$ (hard and long method) and set it to zero to find the corresponding frequency at which Z_{eq} becomes pure resistive.

$$Z_{eq} = -\frac{j}{\omega_C} \parallel (R + j\omega L) = \frac{-j\omega_C \cdot (R + j\omega L)}{-j\omega_C + R + j\omega L} = \frac{-j(R + j\omega L)}{-j + RC\omega + j\omega^2 LC}$$

$$Z_{eq} = \frac{\omega L - jR}{RC\omega + j(\omega^2 LC - 1)}$$

(I) multiply by the conjugate of denominator

$$= \frac{(\omega L - jR)(RC\omega - j(\omega^2 LC - 1))}{[RC\omega + j(\omega^2 LC - 1)][RC\omega - j(\omega^2 LC - 1)]}$$

$$Z_{eq} = \frac{RLC\omega^2 - j\omega L(\omega^2 LC - 1) - jR^2 CW + jR(\omega^2 LC - 1)}{(RC\omega)^2 + (\omega^2 LC - 1)^2}$$

→ next page

$$Z_{eq} = \underbrace{\frac{RL\omega^2 - R(\omega^2 LC - 1)}{(RC\omega)^2 + (\omega^2 LC - 1)^2}}_{R(\omega)} + j \underbrace{\frac{-WL(\omega^2 LC - 1) - R^2 C\omega}{(RC\omega)^2 + (\omega^2 LC - 1)^2}}_{X(\omega)}$$

\Rightarrow To have $Z_{eq} = R(\omega) \rightarrow X(\omega) = 0 \rightarrow$ numerator only needs to be zero

$$\Rightarrow \cancel{\frac{-WL(\omega^2 LC - 1) - R^2 C\omega}{(RC\omega)^2 + (\omega^2 LC - 1)^2}} = 0 \rightarrow \omega(\omega^2 L^2 C - L + R^2 C) = 0$$

$$\Rightarrow \begin{cases} \omega = 0 \rightarrow \text{obvious answer} \\ \text{or} \\ \omega^2 L^2 C - L + R^2 C = 0 \Rightarrow \omega^2 L^2 C = L - R^2 C \end{cases}$$

$$\omega = \sqrt{\frac{L - R^2 C}{L^2 C}}$$

if the frequency of the input source is chosen in this way, the total impedance from the terminal becomes pure resistive

* This time, we try to find the phase of Z_{eq} and set it to zero.
(easy and quick method)

$$\text{Recall I, } Z_{eq} = \frac{\omega L - jR}{RC\omega + j(\omega^2 LC - 1)} \Rightarrow Z_{eq} = \frac{r_1 L \varphi_1}{r_2 L \varphi_2} = \frac{r_1}{r_2} \frac{\varphi_1 - \varphi_2}{Z_{eq}}$$

where $r_1 = \sqrt{(\omega L)^2 + R^2}, r_2 = \sqrt{(RC\omega)^2 + (\omega^2 LC - 1)^2}$

$$\text{to have } \varphi_1 = \tan^{-1} \frac{-R}{\omega L}, \quad \varphi_2 = \tan^{-1} \left(\frac{\omega^2 LC - 1}{RC\omega} \right)$$

$$\Rightarrow Z_{eq} = |Z_{eq}| \rightarrow \angle Z_{eq} = 0 \Rightarrow \varphi_1 - \varphi_2 = 0 \quad \text{we only need this part}$$

$$\Rightarrow \tan^{-1} \left(\frac{-R}{\omega L} \right) = \tan^{-1} \left(\frac{\omega^2 LC - 1}{RC\omega} \right) \xrightarrow[\text{must be the same}]{\text{arguments}} \frac{-R}{\omega L} = \frac{\omega^2 LC - 1}{RC\omega}$$

$$\Rightarrow -R^2 C\omega = \omega L(\omega^2 LC - 1) \rightarrow \omega L(\omega^2 LC - 1) + R^2 C\omega = 0$$

$$\Rightarrow \omega(\omega^2 L^2 C - L + R^2 C) = 0 \rightarrow \begin{cases} \omega = 0 \\ \omega^2 L^2 C - L + R^2 C = 0 \end{cases}$$

$$\text{Now } R = 6\Omega$$

$$L = 27 \text{ mH}$$

$$C = 22 \mu\text{F}$$

$$\Rightarrow \omega = \sqrt{\frac{27 \times 10^{-3} - 36 \times 22 \times 10^{-6}}{27^2 \times 10^{-6} \times 22 \times 10^{-6}}} = 1.278 \times 10^3 \text{ rad/s}$$