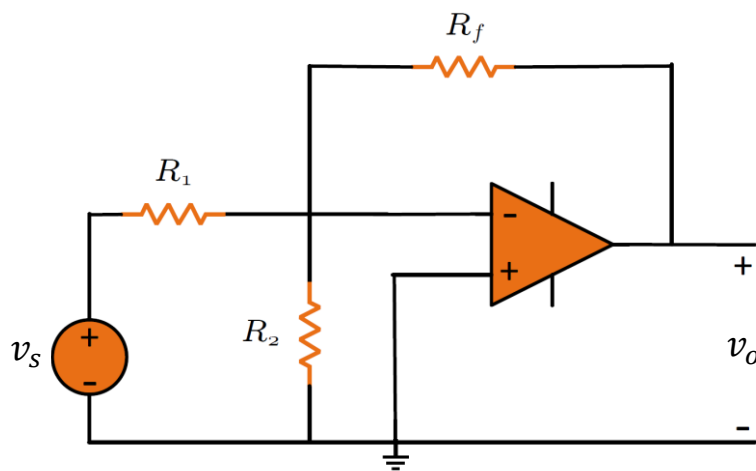



## Topic 6: Operational Amplifiers

1. Find the voltage gain  $\frac{v_o}{v_s}$  in the following operational amplifier circuit.





**Answer:**  $\frac{v_o}{v_s} = -\frac{R_f}{R_1}$

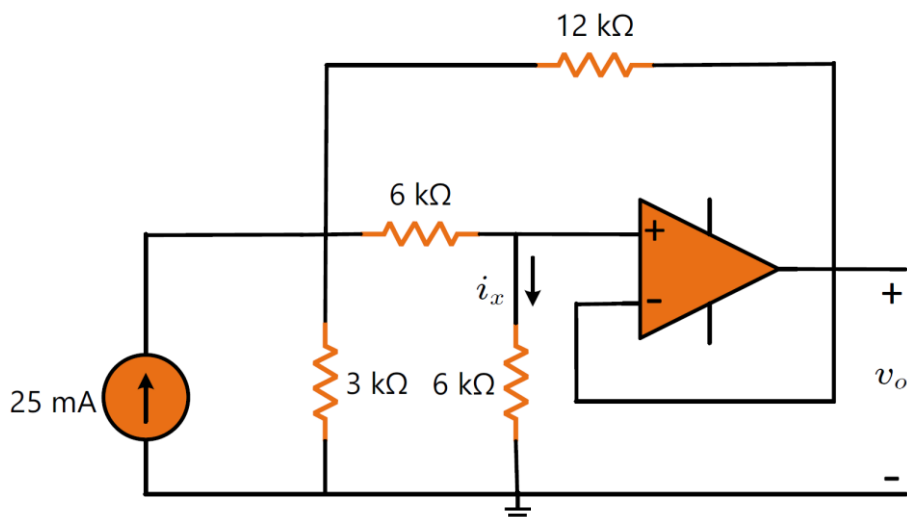2. Find the current  $i_x$  in the following operational amplifier circuit.



**Answer:**  $i_x = 4.545 \text{ mA}$ ,

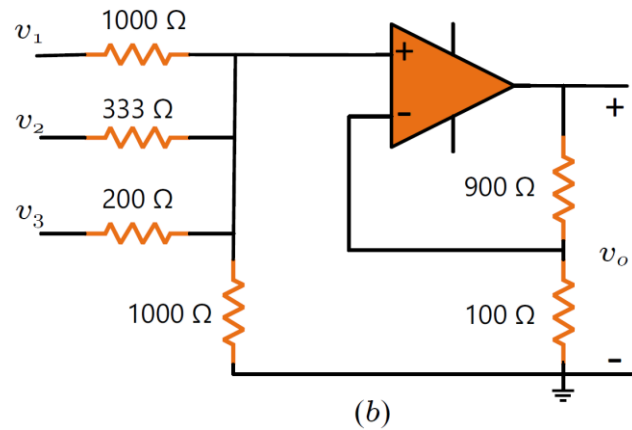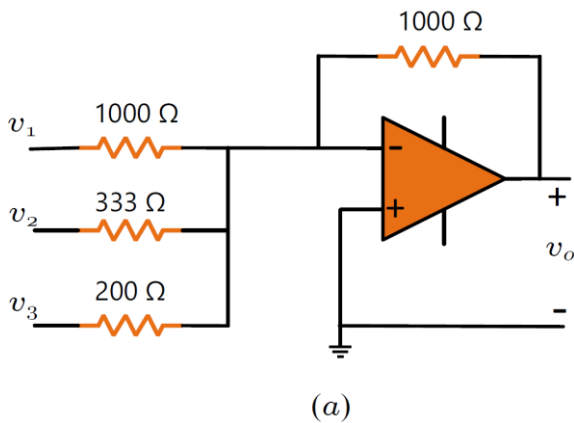3. Calculate  $v_o$  in the following two Op Amp circuits in terms of three input voltages  $v_1$ ,  $v_2$ , and  $v_3$ .




**Answer:**

a)  $v_o = -(v_1 + 3v_2 + 5v_3)$

b)  $v_o = v_1 + 3v_2 + 5v_3$

4. In the following circuit,

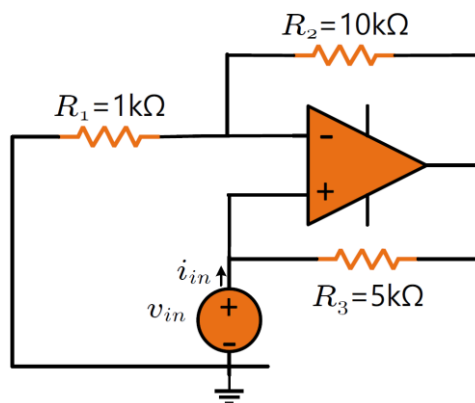- a) Calculate the ratio  $\frac{v_{in}}{i_{in}}$  in terms of  $R_1$ ,  $R_2$ , and  $R_3$ , and then use the numerical values of resistances given in the circuit to determine the ratio. What does this ratio represent?
- b) If  $R_1 = R_2 = R$ , determine the value of  $R_3$  for the Op Amp circuit such that  $\frac{v_{in}}{i_{in}} = -33 \text{ k}\Omega$




**Answer:**

a)  $\frac{v_{in}}{i_{in}} = -\frac{R_1 R_3}{R_2}$

b)  $R_3 = 33 \text{ k}\Omega$

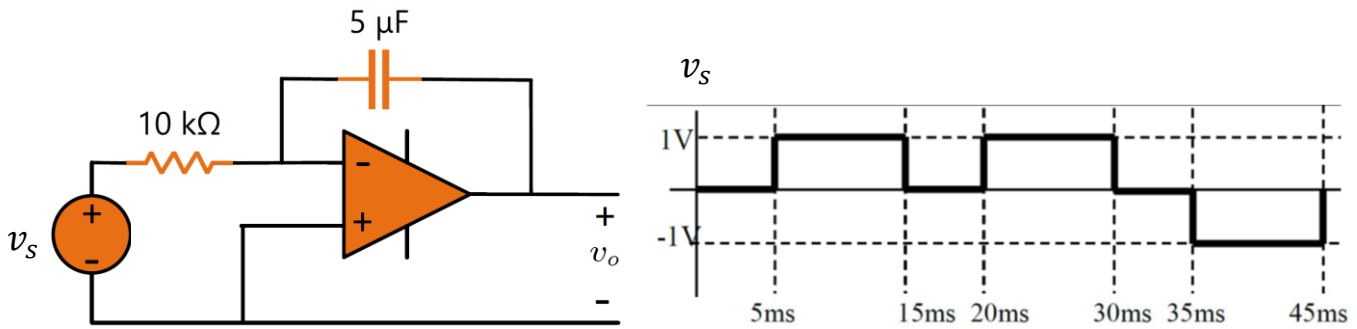
5. Calculate and draw the output voltage  $v_o$  in the following circuit for input voltage signal  $v_s$  given in the graph from  $0 \leq t \leq 45$  ms .



**Answer:**  $v_o(t) = -20 \int_0^t v_s(\tau) d\tau$ , You must complete the output graph sketch.

6. (Final Exam – S1, 2014) Consider the Op Amp circuit below with input  $v_{in}$  and output  $v_o$ .

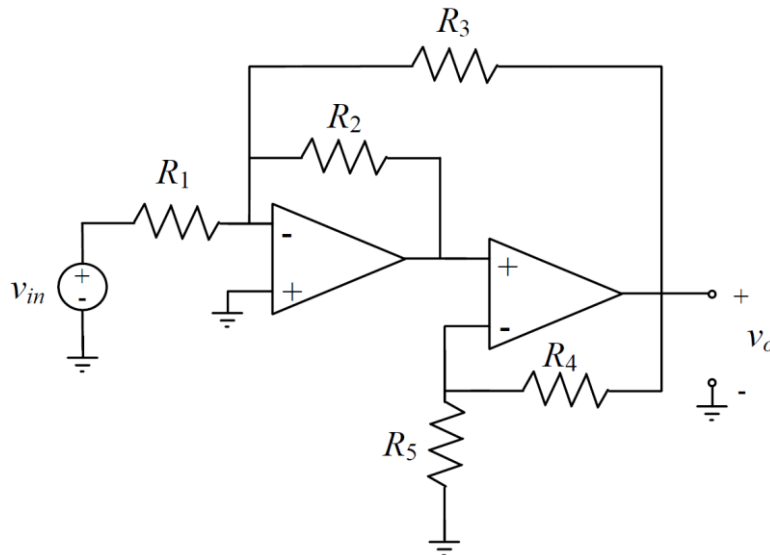- a) Derive an expression for the voltage gain  $\frac{v_o}{v_{in}}$  in terms of the resistor values  $R_1, R_2, R_3, R_4$ , and  $R_5$ .
- b) If  $R_1 = 1\text{ k}\Omega$ ,  $R_2 = 2\text{ k}\Omega$ ,  $R_3 = 3\text{ k}\Omega$ , and  $R_5 = 4\text{ k}\Omega$ , determine the value of  $R_4$  such that the voltage gain  $\frac{v_o}{v_{in}} = -1.8$ .



**Answer:**

- a)  $\frac{v_o}{v_{in}} = -\frac{R_2 R_3 (R_4 + R_5)}{R_1 R_3 R_5 + R_1 R_2 (R_4 + R_5)}$
- b)  $R_4 = 5\text{ k}\Omega$

7. Design a circuit with operational amplifiers that can generate the following output

$$v_o = 9v_1 - 6v_2$$

considering that the range of inputs are  $1\text{ V} \leq v_1 \leq 2\text{ V}$  and  $2\text{ V} \leq v_2 \leq 3\text{ V}$ . The operational amplifiers have a supply voltage of  $\pm 12\text{ V}$ .

**Hint:** Consider the impact that the supply voltage of the operational amplifier has on the output of the device and how you can design around this limitation. This means that you have to break the design in two steps:

**Step1:** Design an Op Amp circuit for  $v_{o1} = 3v_1 - 2v_2$  as first Op amp stage,

**Step2:** Cascade the Op Amp circuit in Step 1 to another Op Amp stage for  $v_o = 3v_{o1}$ .