

# "Final Exam, S2 2017 Solutions"


## QUESTION 1 [20 marks]

(i) [10 marks] For the circuit shown in Figure 1,

a. (8 marks) Apply mesh analysis and show that the mesh equations are given as below,

$$\begin{cases} i_1 + 3i_2 - 2i_3 = 8 \\ i_1 + i_2 - 4i_3 = -1 \\ i_1 - i_2 = -4 \end{cases}$$

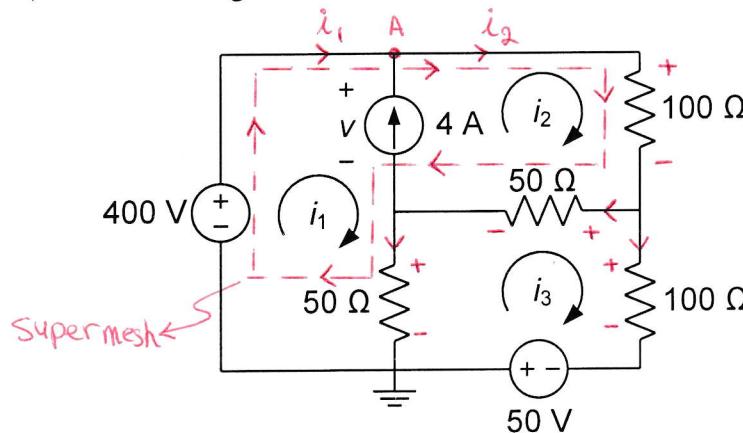b. (2 marks) Given the values of mesh currents as  $i_1 = -0.5$  A,  $i_2 = 3.5$  A, and  $i_3 = 1$  A, find the voltage  $v$  across 4-A current source.



(i)-a:

Figure 1

\* KVL in supermesh:

$$-400 + 100i_2 + 50(i_2 - i_3) + 50(i_1 - i_3) = 0 \xrightarrow{\times 50}$$

$$\rightarrow -8 + 2\underline{i_2} + \underline{i_2} - \underline{i_3} + \underline{i_1} - \underline{i_3} = 0 \Rightarrow \underbrace{i_1 + 3i_2 - 2i_3 = 8}$$

\* KVL in mesh 3:

$$-50 - 50(i_1 - i_3) - 50(i_2 - i_3) + 100i_3 = 0 \xrightarrow{\times 50}$$

$$\rightarrow -1 - \underline{i_1} + \underline{i_3} - \underline{i_2} + \underline{i_3} + 2\underline{i_3} = 0 \Rightarrow \underbrace{i_1 + i_2 - 4i_3 = -1}$$

\* KCL at node A:

$$i_1 + 4 = i_2 \Rightarrow \underbrace{i_1 - i_2 = -4}$$

(i)-b:

\* KVL in mesh 1:

$$V + 50(i_1 - i_3) - 400 = 0 \xrightarrow{\substack{i_1 = -0.5 \text{ A} \\ i_3 = 1 \text{ A}}} V = 50(i_3 - i_1) + 400$$

$$\Rightarrow V = 50(1 + 0.5) + 400 = 475 \text{ V}$$


Question 1 continued

(ii) [10 marks] For the circuit shown in Figure 2,

a. (8 marks) Apply nodal analysis and show that the nodal equations are given as below,

$$\begin{cases} 11v_1 - 6v_2 = 108 \\ 4v_1 - 3v_2 = -54 \end{cases}$$

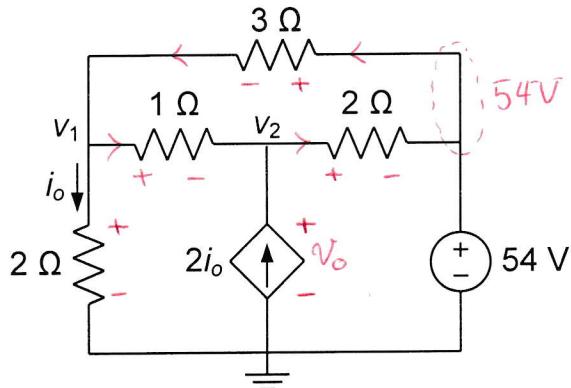b. (2 marks) Given the values of node voltages as  $v_1 = 72$  V and  $v_2 = 114$  V, Calculate the power of the dependent current source.



(ii)-a:

Figure 2

\* KCL at node 1:

$$\frac{54-v_1}{3} = \frac{v_1-0}{2} + \frac{v_1-v_2}{1} \times 6 \rightarrow 108 - 2v_1 = 3v_1 + 6v_1 - 6v_2$$

$$\Rightarrow \underbrace{11v_1 - 6v_2 = 108}$$

\* KCL at node 2:

$$\frac{v_1-v_2}{1} + 2i_o = \frac{v_2-54}{2} \quad \boxed{i_o = \frac{v_1}{2}} \quad v_1 - v_2 + v_1 = \frac{v_2 - 54}{2} \times 2$$

$$\Rightarrow 4v_1 - 2v_2 = v_2 - 54 \Rightarrow \underbrace{4v_1 - 3v_2 = -54}$$

(ii)-b:

$$P_o = 2i_o \times v_o \rightarrow \text{Passive sign convention for sources (Active element)}$$

$$2i_o = 2 \times \frac{v_1}{2} = v_1 = 72 \text{ A}$$

$$v_o = v_2 = 114 \text{ V}$$

$$\Rightarrow P_o = 72 \times 114 = 8208 \text{ W} = 8.208 \text{ kW}$$

Supplied

## QUESTION 2 [20 marks]

(i) [10 marks] For the circuit shown in Figure 3,

- (4 marks) Calculate the open-circuit voltage  $v_{oc}$  and short-circuit current  $i_{sc}$  at the terminals a-b.
- (4 marks) Obtain the Norton equivalent circuit with respect to the terminals a-b and draw the equivalent circuit.
- (2 marks) Determine the value of the load resistance  $R_L$  for maximum power transfer, and then calculate the maximum power that can be delivered to  $R_L$ .


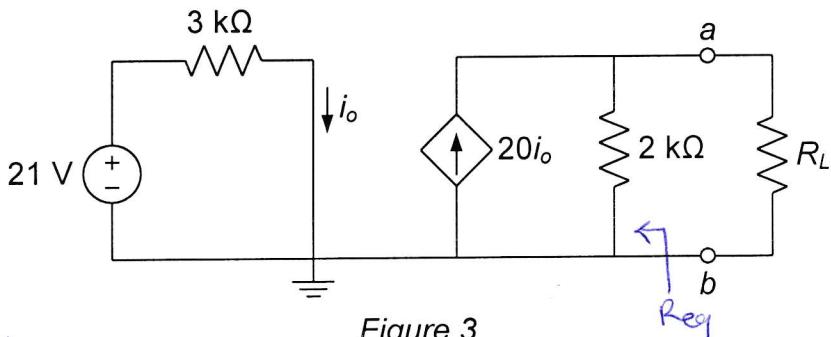


Figure 3

(i)-a:

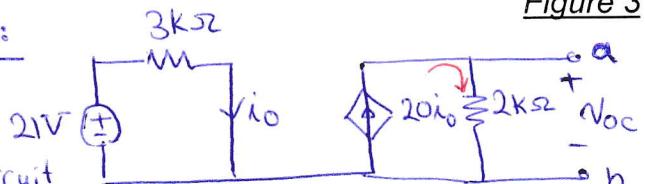


$$i_0 = \frac{21V}{3k\Omega} = 7mA \quad (I)$$

$$v_{oc} = V_{2k\Omega} = 2k\Omega \times 20i_0 = 280V$$

\* Open-circuit voltage  $v_{oc}$ :


\* Short-circuit current  $i_{sc}$ :

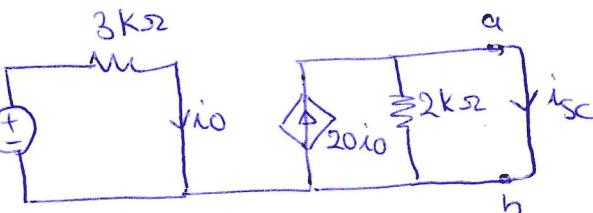

$$i_{sc} = 20i_0 \quad (I) \rightarrow i_{sc} = 140mA$$

(i)-b:

The equivalent circuit  
Norton

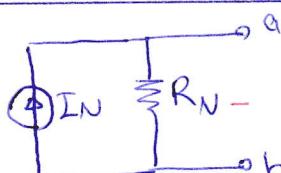

$$\begin{cases} R_N = R_{eq} \\ I_N = i_{sc} \end{cases}$$


Since there exists a dependent source:

$$R_{eq} = \frac{v_{oc}}{i_{sc}} = \frac{280V}{140mA} = 2k\Omega = R_N$$

$$I_N = i_{sc} = 140mA$$

(i)-c:

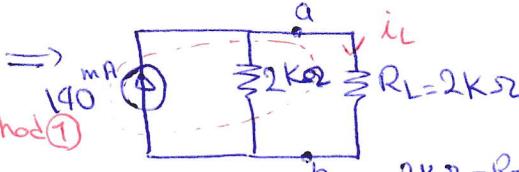
for maximum power transfer  $R_L = R_{Th} = R_N = 2k\Omega$



$$i_L = \frac{2k\Omega}{2k\Omega + 2k\Omega} \times 140mA = 70mA$$

$$P_{max} = R_L i_L^2 = 2k\Omega \times 70mA^2 = 9800mW = 9.8W$$

Page 4 of 11

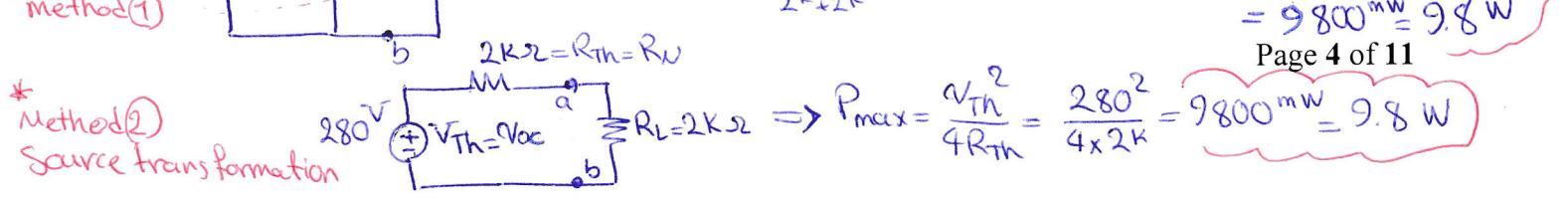


$$P_{max} = \frac{V_{Th}^2}{4R_{Th}} = \frac{280^2}{4 \times 2k\Omega} = 9800mW = 9.8W$$

Question 2 continued

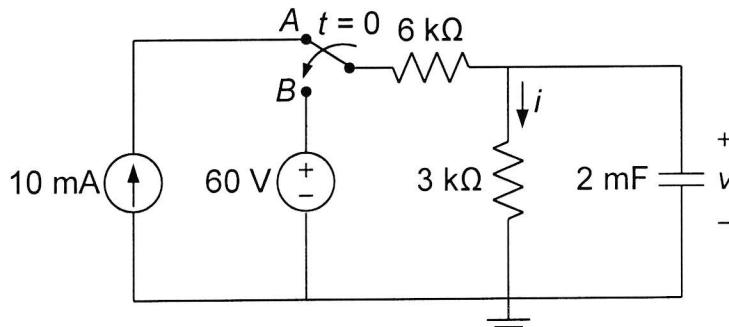- (ii) [10 marks] In circuit shown in Figure 4, the switch has been in position A for a long time. At  $t = 0$ , the switch moves to position B.

- (4 marks) Find the voltage  $v(t)$  across the capacitor immediately after the switch changes to position B,  $v(0^+)$ , and its final voltage when  $t \rightarrow \infty$ ,  $v(\infty)$ .
- (4 marks) Derive an expression for the capacitor voltage  $v(t)$  for all time (i.e., for both  $t < 0$  and  $t > 0$ ).
- (2 marks) Find the current  $i(t)$  through  $3\text{-k}\Omega$  resistor for  $t > 0$ .




(ii)-a:


Figure 4

$$V(0^+) = V(0^-) \text{ No sudden change in capacitor voltage}$$

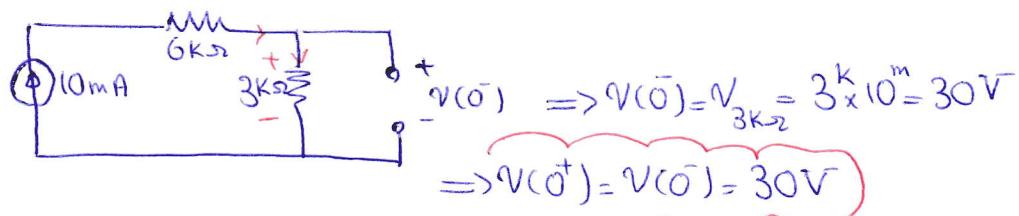\* Circuit when  $t < 0$   
Switch is at A




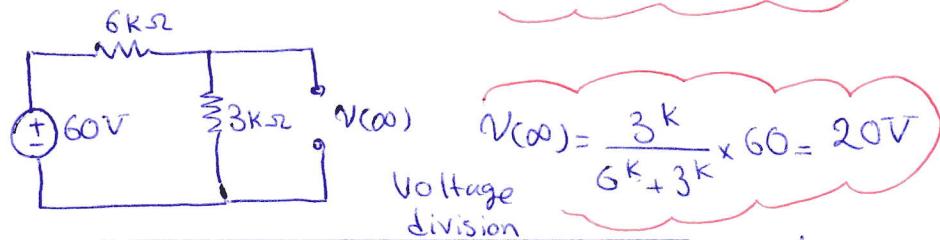\* Circuit when  $t > 0$   
and  $t \rightarrow \infty$   
Switch is at B



$$(ii)-b: \text{ After switch changes to B} \rightarrow V(t) = V(\infty) + (V(0^+) - V(\infty)) e^{-\frac{t}{R_{Th}C}}$$

$$T = R_{Th}C \rightarrow$$

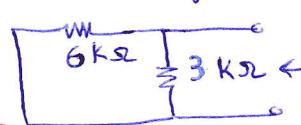

$$\Rightarrow V(t) = \begin{cases} 30 \text{ V} & t \leq 0 \\ 20 + 10e^{-\frac{t}{4}} \text{ V} & t > 0 \end{cases}$$

$$R_{Th} = 3 \parallel 6 = \frac{3 \times 6}{3+6} = \frac{18}{9} = 2 \text{ k}\Omega \Rightarrow T = 2 \times 2 = 4 \text{ s}$$

$$\Rightarrow V(t) = 20 + (30 - 20) e^{-\frac{t}{4}} = 20 + 10e^{-\frac{t}{4}} \text{ V}$$

(ii)-c:

$$i(t) = \frac{V_{3\text{k}\Omega}}{3\text{k}\Omega} = \frac{V(t)}{3\text{k}\Omega}$$

$3\text{k}\Omega$  is in parallel with Capacitor

$$t \leq 0 \rightarrow i(t) = \frac{30}{3\text{k}\Omega} = 10 \text{ mA}$$

$$t > 0 \rightarrow i(t) = \frac{20}{3} + 10e^{-\frac{t}{4}} \text{ mA}$$


$$i(t) = \begin{cases} 10 \text{ mA} & t \geq 0 \\ \frac{20}{3} + 10e^{-\frac{t}{4}} \text{ mA} & t < 0 \end{cases}$$

### QUESTION 3 [20 marks]

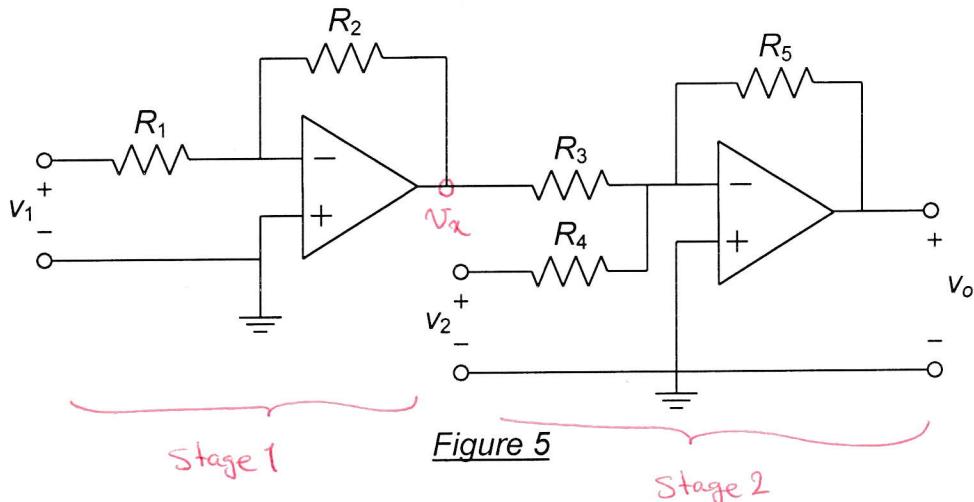- (i) [8 marks] For the Op Amp circuit shown in Figure 5 show that the output  $v_0$  can be given by the following equation,

$$v_0 = a_1 v_1 - a_2 v_2$$

and determine the parameters  $a_1$  and  $a_2$  in terms of resistors  $R_1$  to  $R_5$ .



(i):

\* Stage 1: Inverting amplifier:

$$\frac{v_x}{v_1} = -\frac{R_2}{R_1} \quad (I)$$

\* Stage 2: Summing amplifier:


$$v_0 = -\left(\frac{R_5}{R_3} v_x + \frac{R_5}{R_4} v_2\right) \xrightarrow{(I)} v_0 = -\left(\frac{R_5}{R_3} \frac{-R_2}{R_1} v_1 + \frac{R_5}{R_4} v_2\right)$$

$$\Rightarrow v_0 = \frac{R_5 R_2}{R_3 R_1} v_1 - \frac{R_5}{R_4} v_2$$

$$\Rightarrow v_0 = a_1 v_1 - a_2 v_2$$

choose
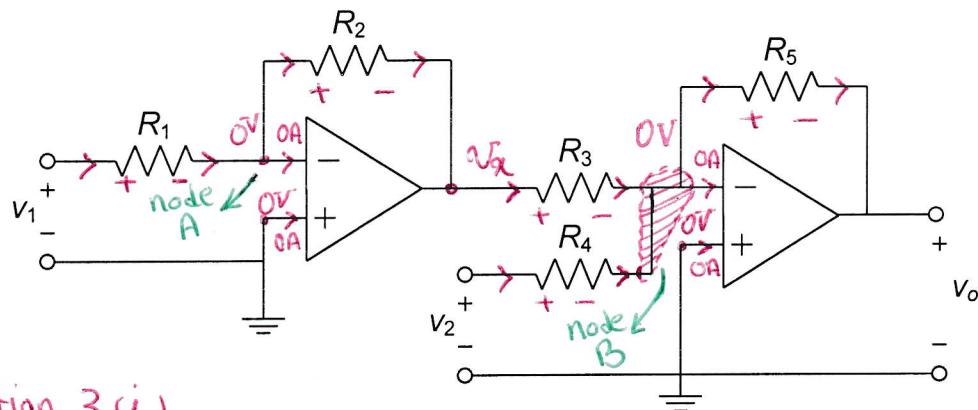
$$\begin{cases} a_1 = \frac{R_5 R_2}{R_3 R_1} \\ a_2 = \frac{R_5}{R_4} \end{cases}$$



Question 3(i)

Figure 5

Nodal analysis approach:

$$* \text{KCL at node A: } \frac{V_1 - 0}{R_1} = \frac{0 - V_x}{R_2} \xrightarrow{x - R_2} V_x = -\frac{R_2}{R_1} V_1 \quad (I)$$

$$* \text{KCL at node B: } \frac{V_x - 0}{R_3} + \frac{V_2 - 0}{R_4} = \frac{0 - V_o}{R_5} \xrightarrow{x - R_5} V_o = -\frac{R_5}{R_3} V_x - \frac{R_5}{R_4} V_2 \quad (II)$$

$(I) \rightarrow (II)$   
Substitute  $V_x$

$$V_o = + \frac{R_5 R_2 V_1}{R_3 R_1} - \frac{R_5}{R_4} V_2$$

choose


$$\begin{aligned} a_1 &= \frac{R_5 R_2}{R_3 R_1} \\ a_2 &= \frac{R_5}{R_4} \end{aligned}$$

$$\Rightarrow V_o = a_1 V_1 - a_2 V_2$$

Question 3 continued

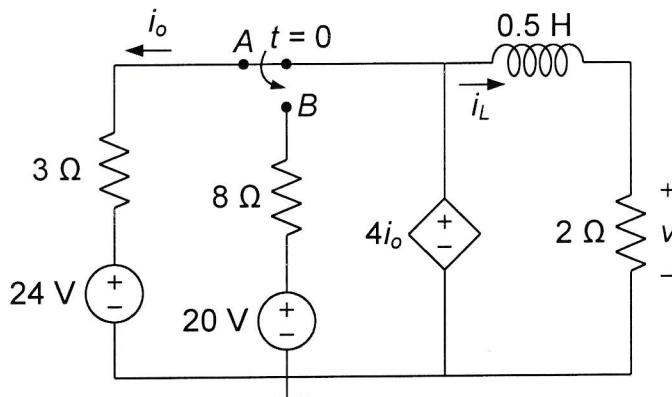(ii) [12 marks] In the circuit of Figure 6, the switch has been in position A for a long time before changing its position to B at  $t = 0$ .

- [10 marks] Derive an expression for the inductor current  $i_L(t)$  for all time (i.e., for both  $t < 0$  and  $t > 0$ ) and sketch  $i_L(t)$  as a function of time showing all critical points in the sketch.
- [2 marks] Find the voltage  $v(t)$  across the  $2\Omega$  resistor for  $t > 0$ .



(ii)-a:

Circuit at  $t < 0$

Switch is at A

\* KVL in big loop  
to find  $i_0$

$$-24 - 3i_0 + 4i_0 = 0 \rightarrow i_0 = 24A$$

Using (I)  $i_L(0^-) = 2i_0 = 48A$  t<sub>0</sub>

Circuit at  $t > 0$

and  $t \rightarrow \infty$

switch is at B


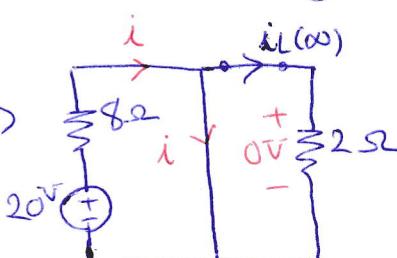


Figure 6

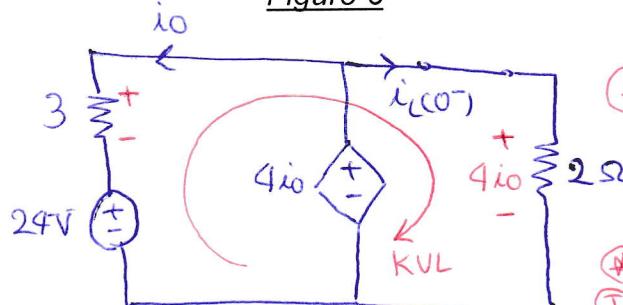


\* 2-Ω resistor is in parallel with dependent voltage source thus  $V_{2\Omega} = 4i_0$  (I)

\* Also  $V_{2\Omega} = 2i_L(0^-)$

Thus  $4i_0 = 2i_L(0^-)$
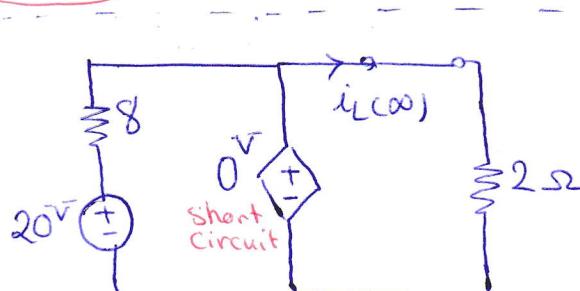
$$\Rightarrow i_L(0^-) = 2i_0 \quad (II)$$



when switch changes to B,  $i_0 = 0A$  which means any dependent source relying on  $i_0$  will be zero.


$$i_L(t) = i_L(\infty) + [i_L(0^+) - i_L(\infty)] e^{-\frac{t}{T}} , T = \frac{L}{R_{Th}}$$

$$i_L(0^+) = i_L(0^-) = 48A$$

→ next page

Q3 part (ii)-a Continued

Finding  $R_{Th}$ :

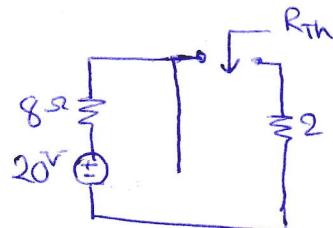


$$R_{Th} = 2\Omega \Rightarrow \tau = \frac{L}{R_{Th}} = \frac{0.5}{2} = \frac{1}{4} \text{ s}$$

$$\Rightarrow i_L(t) = 0 + [48 - 0] e^{-\frac{t}{\tau}} = 48 e^{-4t} \text{ A } t \geq 0$$

Thus:
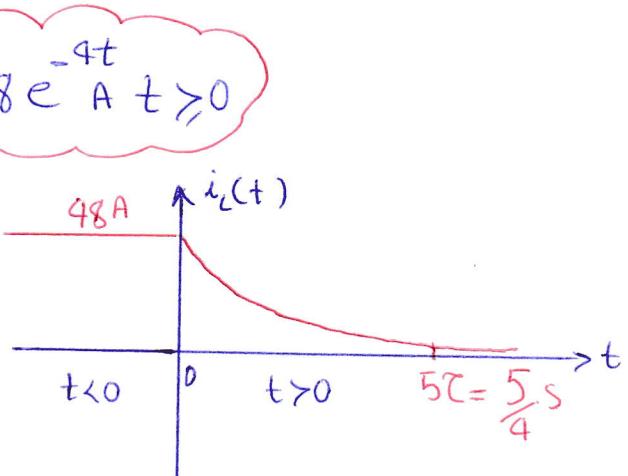
$$i_L(t) = \begin{cases} 48 \text{ A} & t \leq 0 \\ 48 e^{-4t} \text{ A} & t > 0 \end{cases}$$



(ii)-b:  $V(t) = 2i_L(t)$  for all time

$$\Rightarrow V(t) = 2 \times 48 = 96 \text{ V } t \leq 0$$


$$V(t) = \frac{2 \times 48}{96} e^{\frac{4t}{\tau}} \text{ V } t > 0$$

$$\Rightarrow V(t) = \begin{cases} 96 \text{ V} & t \leq 0 \\ 96 e^{\frac{-4t}{\tau}} \text{ V} & t > 0 \end{cases}$$

## QUESTION 4 [20 marks]

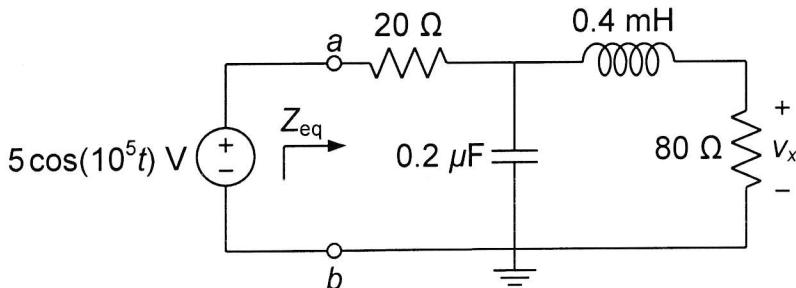(i) [10 marks] For the circuit shown in Figure 7,

- [4 marks] Find the equivalent impedance  $Z_{eq}$  seen from terminals a-b
- [6 marks] Apply phasor analysis and source transformation to calculate the voltage  $v_x$  across the  $80\Omega$  resistor.



(i)-a:

Figure 7


\* Draw the circuit in phasor domain

$$5 \cos(10^5 t) \rightarrow 5 \angle 0^\circ$$

$$\omega = 10^5 \text{ rad/s} \Rightarrow 0.4 \text{ mH} \rightarrow j\omega L = j(10^5 \times 0.4 \times 10^{-3}) = j40 \Omega$$

$$0.2 \mu\text{F} \rightarrow -j \frac{1}{\omega C} = -j \frac{1}{10^5 \times 0.2 \times 10^{-6}} = -j50 \Omega$$

=>


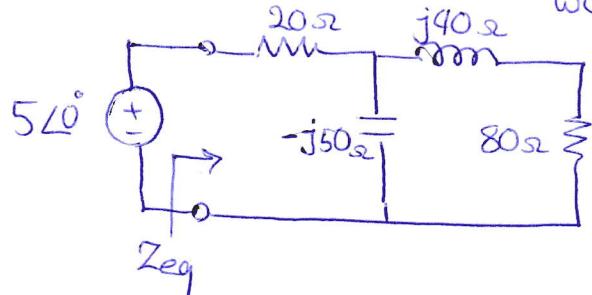


$$Z_{eq} = (80 + j40) \parallel (-j50) + 20$$

$$\Rightarrow Z_{eq} = \frac{(80 + j40) \times (-j50)}{80 + j40 - j50} + 20 = 50.769 - j46.153 \Omega = 68.61 \angle -42.27^\circ \Omega$$

Source transformation  $V_s = Z I_s$  or  $I_s = \frac{V_s}{Z}$

(i)-b:

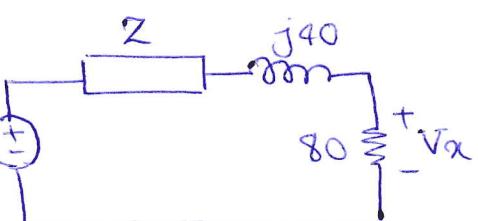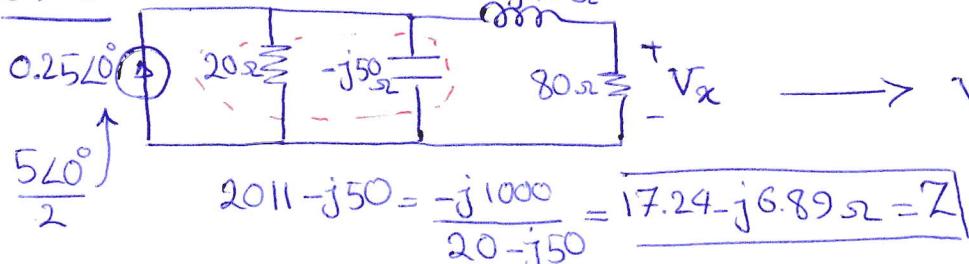

$$V_s = Z \times 0.25 \angle 0^\circ = 4.642 \angle -21.8^\circ \text{ V}$$

Voltage division


$$\Rightarrow V_x = \frac{80}{Z + j40 + 80} \times V_s = 3.615 \angle -40.6^\circ \text{ V}$$

$$\Rightarrow V_x(t) = 3.615 \cos(10^5 t - 40.6^\circ) \text{ V}$$

Question 4 continued

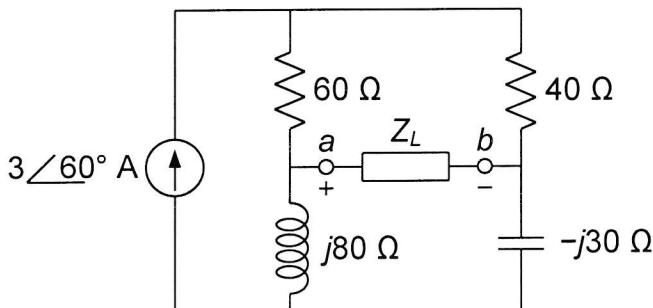(ii) [10 marks] For the circuit shown in Figure 8,


- (6 marks) Find the Thevenin equivalent circuit as seen from the terminals a-b, and draw the equivalent circuit.
- (2 marks) Determine the value of the load impedance  $Z_L$  for maximum average power transfer.
- (2 marks) Calculate the maximum average power that can be delivered to the load  $Z_L$  from this circuit.



(ii)-a:


Figure 8

\* Find  $Z_{Th}$ :

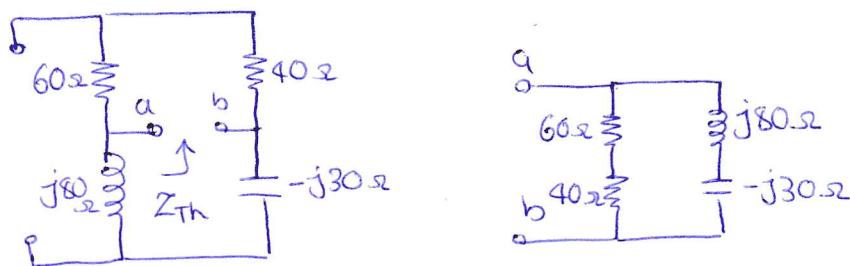

$$\Rightarrow Z_{Th} = (60+40) \parallel (j80-j30) = \frac{100 \times j50}{100+j50} = 20+j40 \Omega = 44.72 \angle 63.43^\circ \Omega$$

\* Find  $V_{Th}$ :

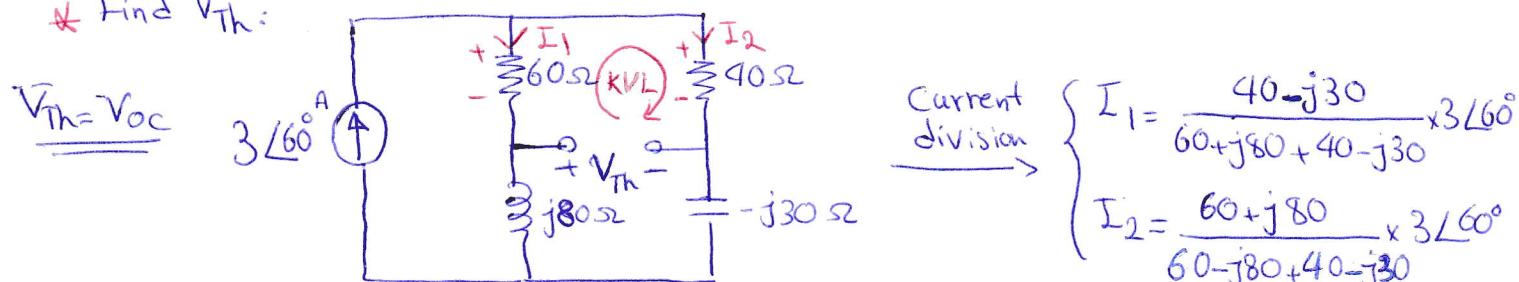

$$\Rightarrow I_1 = 1.34 - j0.08 A = 1.34 \angle -3.43^\circ A$$

$$I_2 = 0.16 + j2.67 A = 2.68 \angle 86.56^\circ A$$


\* KVL in upper-right mesh:

$$-V_{Th} - 60I_1 + 40I_2 = 0$$

$$134 \angle 123.4^\circ - V_{Th} = 0$$

$$\Rightarrow V_{Th} = -60 \times (1.34 - j0.08) + 40 \times (0.16 + j2.67)$$
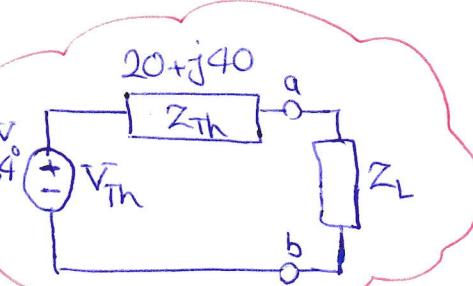
$$V_{Th} = -74 + j111.6 V = 134 \angle 123.4^\circ V$$



Q4 part (ii) Continued

(ii)-b:

For maximum average power transfer  $Z_L = Z_{Th}^*$

$$\text{Thus } Z_L = 20 - j40 \Omega = 44.72 \angle -63.43^\circ \Omega$$

(ii)-c:

$$P_{max} = \frac{|V_{Th}|^2}{8R_{Th}} = \frac{(134)^2}{8 \times 20} = 112.225 \text{ W}$$


$$Z_{Th} = 20 + j40 \Omega$$

$$\Rightarrow R_{Th} = \boxed{20 \Omega}$$

## QUESTION 5 [20 marks]

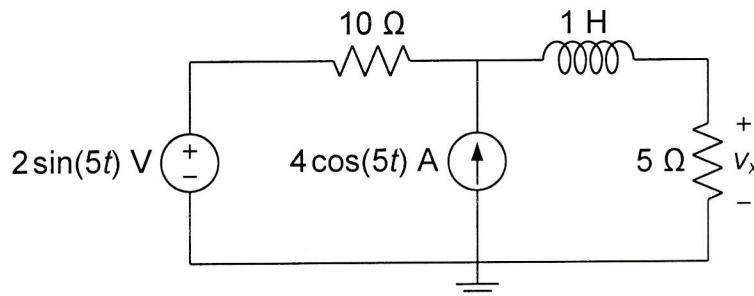(i) [10 marks] For the circuit shown in Figure 9,

- [6 marks] Find the output voltage  $v_x$  using phasor analysis and superposition principle.
- [4 marks] Sketch the phasors of voltage source  $V$  and current source  $I$  along with phasor of voltage  $V_x$  on a phasor diagram.



(i)-a:

Figure 9

Both Sources have the same frequency

$$V = 2\sin(5t) = \underline{2\cos(5t - 90^\circ)} = \underline{2 \angle -90^\circ V} = \underline{-2j}$$


$$I = 4\cos(5t) = \underline{4 \angle 0^\circ A}$$

$$\omega = 5 \rightarrow 1H \rightarrow j\omega L = \underline{j5 \Omega}$$


$$V_x = V_{x1} + V_{x2} \quad \left\{ \begin{array}{l} V_{x1} \text{ is due to Voltage source} \\ V_{x2} \text{ is due to Current source} \end{array} \right.$$

same frequency

$$\rightarrow V_x = V_{x1} + V_{x2}$$

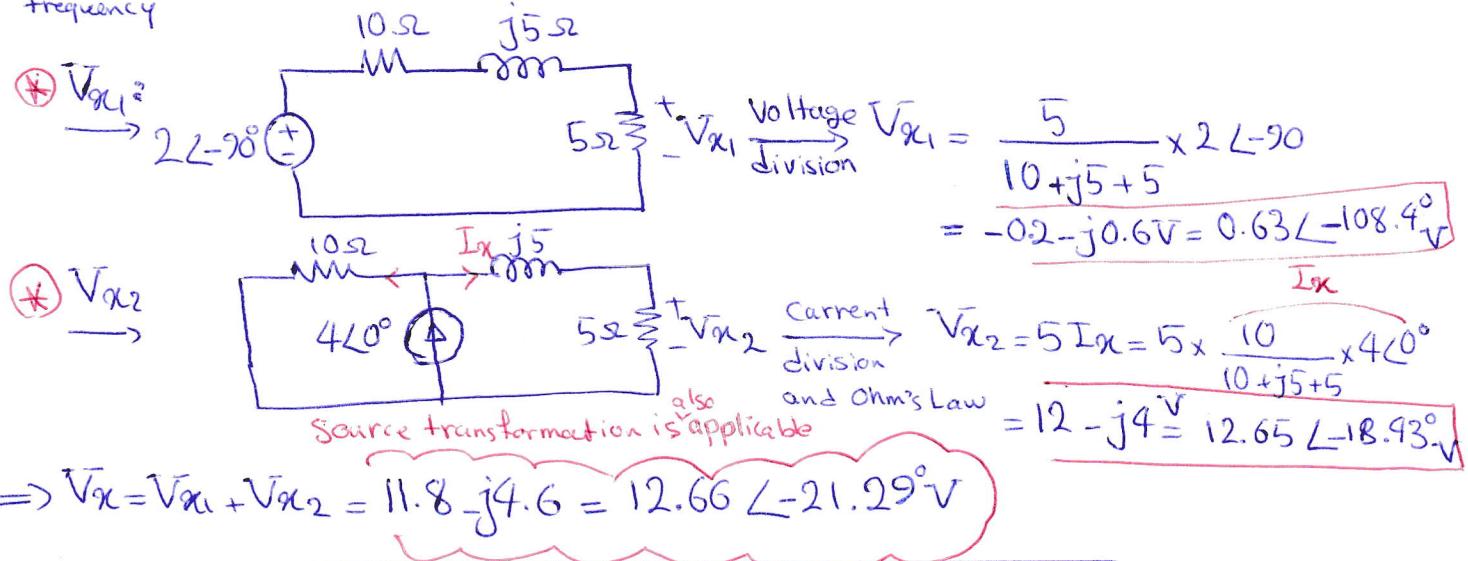

(i)-b:

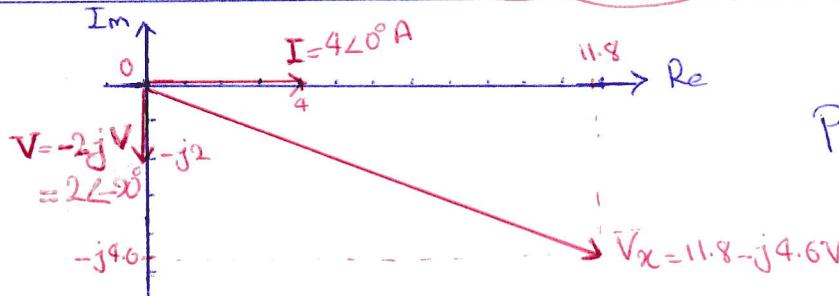


Phasor diagram

Question 5 continued

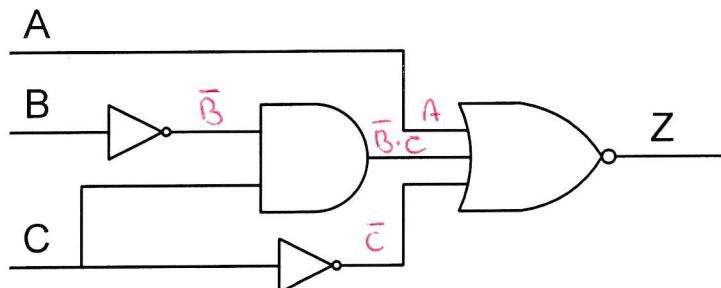(ii) [10 marks] Consider the following logical diagram shown in Figure 10.

- (4 marks) Derive and simplify the logical expression for Z.
- (4 marks) Construct the truth table relating Z to inputs A, B, and C.
- (2 marks) Using part a. and/or part b., show that Z can be realised using exactly one 3-input AND gate and one 1-input NOT gate showing all working.



(ii)-a:

$$Z = \overline{A + \bar{B} \cdot C + \bar{C}}$$

Figure 10


$$\begin{aligned} \text{DeMorgan's Theorem} \rightarrow Z &= \overline{\overline{A} \cdot \overline{\bar{B} \cdot C} \cdot \overline{\bar{C}}} = \overline{\overline{A}} \cdot (\overline{\bar{B} + \bar{C}}) \cdot \overline{C} = \overline{\overline{A}} \cdot (\overline{B \cdot C} + \overline{\bar{C} \cdot C}) \\ &= \overline{\overline{A}} \cdot (\overline{B \cdot C} + 0) \end{aligned}$$

(ii)-b:

	A	B	C	$\bar{A}$	$\bar{B}$	$\bar{C}$	$\bar{B} \cdot C$	$A + \bar{B} \cdot C + \bar{C}$	$\overline{A + \bar{B} \cdot C + \bar{C}}$	$\bar{A} \cdot B \cdot C$
Truth Table:	0	0	0	1	1	1	0	1	0	0
	0	0	1	1	1	0	1	1	0	0
	0	1	0	1	0	1	0	1	0	0
	0	1	1	1	0	0	0	0	1	1
	1	0	0	0	1	1	0	1	0	0
	1	0	1	0	1	0	1	1	0	0
	1	1	0	0	0	1	0	1	0	0
	1	1	1	0	0	0	0	1	0	0

(ii)-c:
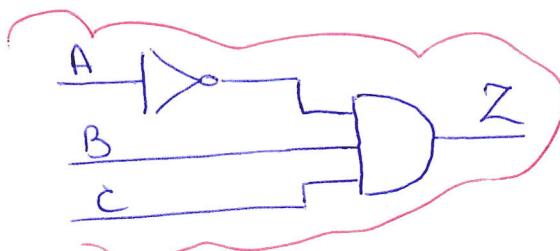
$$Z = \bar{A} \cdot B \cdot C \Rightarrow$$



END OF PAPER