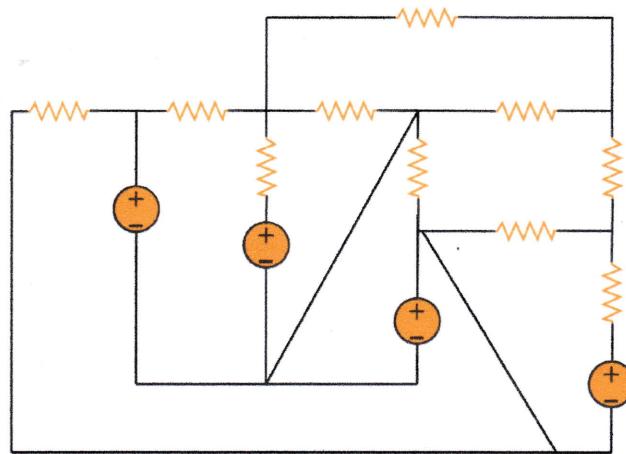



Topic 2: Kirchhoff's Laws, Nodal & Mesh Analysis

- Identify all the nodes, branches, and meshes in the following figure.




Solution:

{ 4 branches
 8 nodes
 7 meshes

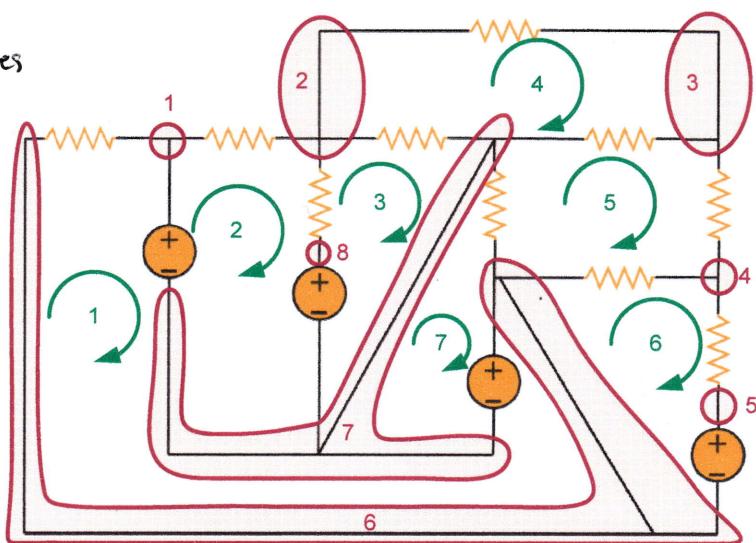

- In the following circuit (Question 3 of the Online Tutorial 1) the total sum of powers being consumed and generated is not equal to zero, violating the conservation of energy law.

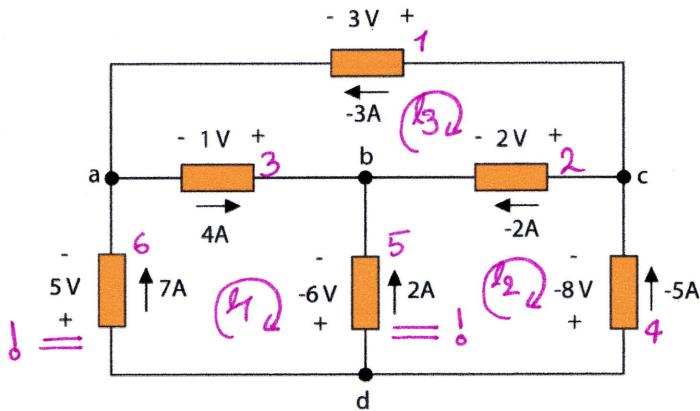- Identify the error in the circuit using Kirchhoff's Current and Voltage Laws.
- Confirm your answer by calculating the powers and their total sum.



Solution: First check KCLs and KVLs

$$\text{KCL: } @ \text{node } a: 7 - 3 - 4 = 0 \checkmark$$

$$@ \text{node } b: 4 + 2 - 2 = 4 \neq 0 \times \text{ error}$$

$$@ \text{node } c: -5 + 2 + 3 = 0 \checkmark$$

$$@ \text{node } d: 7 + 2 - 5 = 4 \neq 0 \times \text{ error}$$

This suggests branch 5 has the wrong direction: $\downarrow 2A \checkmark$ or $\uparrow -2A$

$$\text{KVL: in } l_1: +5 - 1 - (-6) = 10 \neq 0 \times \text{ error}$$

$$\text{in } l_2: +(-6) - 2 - (-8) = 0 \checkmark$$

$$\text{in } l_3: +(-3) + 2 + 1 = 0 \checkmark$$

This suggests branch 6 has the wrong polarity: $+\underline{\underline{5V}}$ or $-\underline{\underline{-5V}}$

Summation of powers with corrected direction and polarity:


$$P_1 = -9W \quad P_4 = 40W$$

$$P_2 = -4W \quad P_5 = 12W \quad \Rightarrow \sum_{n=1}^6 P_n = 40 + 12 - 35 - 4 - 4 - 9 = 0 \checkmark$$

$$P_3 = -4W \quad P_6 = -35W$$

Confirmed

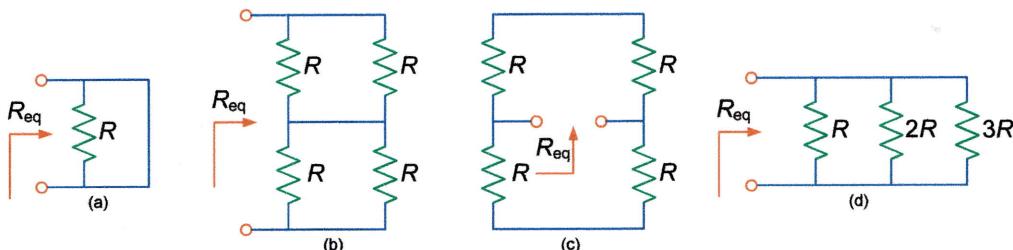3. Find the equivalent resistance of the following networks.



Solution: a) Extreme case of short circuit being parallel with R $\Rightarrow R_{eq} = 0\Omega$


$$\text{b) } R \parallel R = \frac{R}{2} \quad (R \parallel R) + (R \parallel R) \Rightarrow R_{eq} = \frac{R^2}{2R} + \frac{R^2}{2R} = R$$

$$\text{c) } \begin{array}{c} \text{---} \\ | \\ \text{---} \\ 2R \\ | \\ \text{---} \\ 2R \end{array} \rightarrow \begin{array}{c} \text{---} \\ | \\ \text{---} \\ 2R \parallel 2R \\ | \\ \text{---} \\ 4R \end{array} \Rightarrow R_{eq} = \frac{2R \times 2R}{4R} = R$$


$$\text{d) } R_{eq} = R \parallel 2R \parallel 3R \Rightarrow \frac{1}{R_{eq}} = \frac{1}{R} + \frac{1}{2R} + \frac{1}{3R} = \frac{6R^2 + 3R^2 + 2R^2}{6R^3} = \frac{11R^2}{6R^3}$$

$$\Rightarrow R_{eq} = \frac{6}{11} R$$

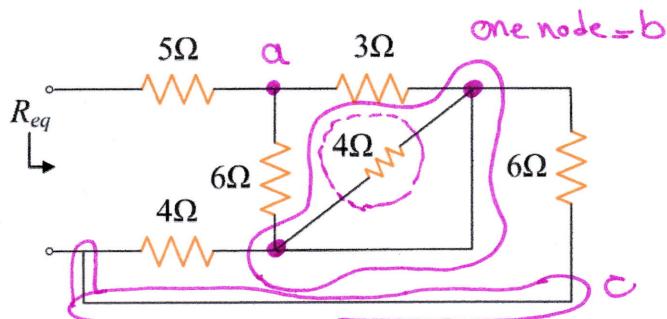4. (Midterm Exam - S1, 2016) For the circuit below, calculate the equivalent resistance R_{eq} of the network as seen from the terminals.




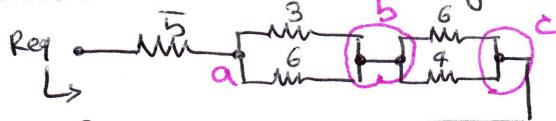Solution: Note that 4Ω is being short circuited.



$$R_{eq} = 5 + \frac{3}{6} + \frac{6}{4} = 5 + \frac{3 \times 6}{3+6} + \frac{6 \times 4}{6+4} = 5 + 2 + 2.4 = 9.4 \Omega$$

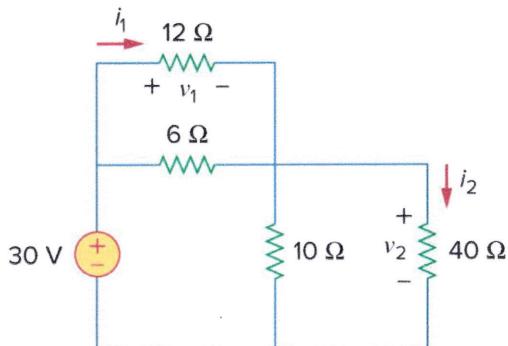
5. Find v_1 and v_2 in the circuit shown below. Also the currents i_1 and i_2 .



Solution: Note that $12\Omega \parallel 6\Omega$ with equal voltage V_1
and $10\Omega \parallel 40\Omega$ with equal voltage V_2


$$R_1 = \frac{12 \times 6}{12+6} = 4\Omega, R_2 = \frac{10 \times 40}{10+40} = 8\Omega$$
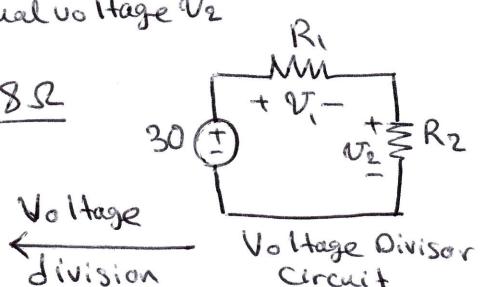
$$\begin{cases} V_1 = \frac{R_1}{R_1+R_2} \times 30 = \frac{4}{4+8} \times 30 = 10V \\ V_2 = \frac{R_2}{R_1+R_2} \times 30 = \frac{8}{4+8} \times 30 = 20V \end{cases}$$



$$\text{Ohm's Law: } i_1 = \frac{V_1}{12\Omega} = \frac{10}{12} = \frac{5}{6} \approx 833.3 \text{ mA}, i_2 = \frac{V_2}{40\Omega} = \frac{20}{40} = 0.5 \text{ A} = 500 \text{ mA}$$

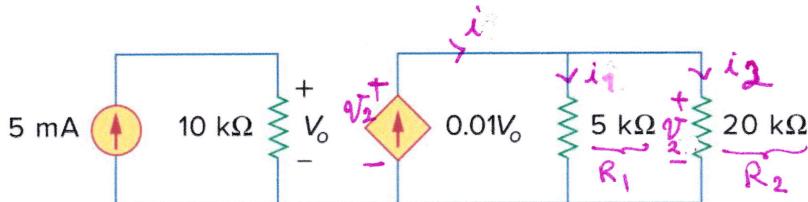6. In the following circuit, calculate the current and voltage of the $20\text{ k}\Omega$ resistor. What is the power generated/supplied by the dependent current source?



Solution: Note that 5 mA only flows through 10 kΩ

$$\rightarrow V_o = 10 \text{ k} \times 5 \text{ mA} = 50 \text{ V}$$

Voltage-Controlled Current Source $\rightarrow i = 0.01V_o = 0.01 \times 50 = 0.5 \text{ A}$

Current divisor circuit


$$i = \frac{V_1}{R_1 + R_2} \rightarrow i_2 = \frac{R_1}{R_1 + R_2} \times i = \frac{5 \text{ k}}{5 \text{ k} + 20 \text{ k}} \times 0.5 = 0.1 \text{ A}$$

$$V_2 = 20 \text{ k} \times i_2 = 20 \text{ k} \cdot 0.1 \text{ A} = 2 \text{ KV} = 2000 \text{ V}$$


VCCS has the same voltage as $V_2 \rightarrow P_{VCCS} = V_2 \times i = 2 \text{ KV} \times 0.5 \text{ A} = 1 \text{ KW}$

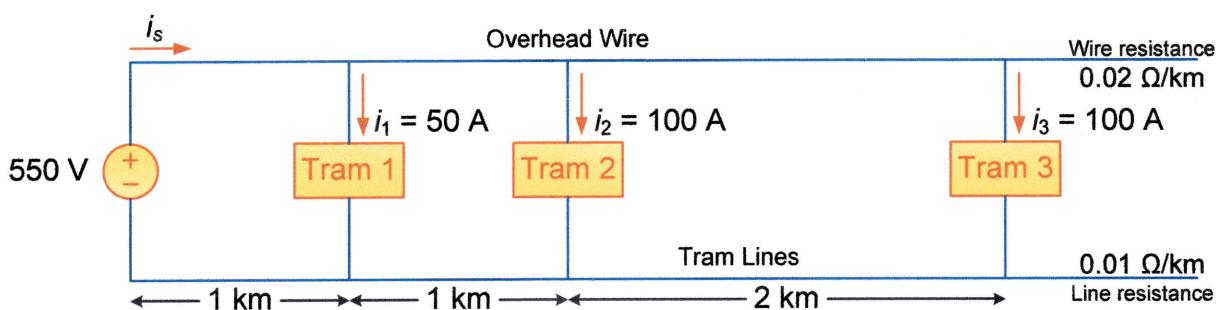7. The DC traction power supply system (TPSS) of a light rail network, as shown in the following figure, consists of a DC Voltage source, overhead wires and an earth return. At a given moment, three trams travel within one section post and absorb 50 A, 100 A, and 100 A, respectively. Considering the overhead wires electric resistance given in units of Ω/km , calculate the power that is absorbed by each trams. What is the overall efficiency of this TPSS?

Efficiency η is defined as the ratio of the total useful power consumed by a system (to perform a task) to the total power supplied to it. Efficiency is an indication of how much of the supplied power is being lost like the heat dissipation by wires resistances.



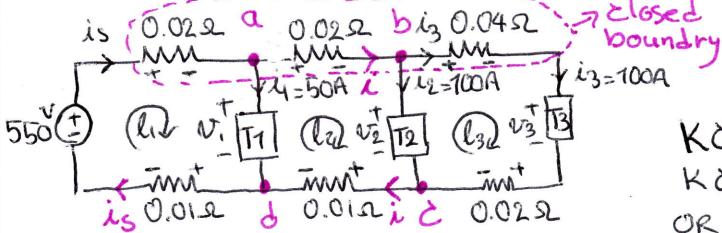Solution: Draw the equivalent Circuit. Note that wires and lines can be modelled with their equivalent resistance according to their length in the circuit diagram.



$$\text{KCL at } b: i = i_2 + i_3 = 200 \text{ A} \triangleq @c$$

$$\text{KCL at } a: i_s = i + i_1 = 250 \text{ A} \triangleq @d$$

OR you can consider a closed boundary with resistors inside

Continue on next page →

$$\text{KVL in } l_1: -550 + 0.02i_s + V_1 + 0.01i_s = 0 \Rightarrow V_1 = 550 - 0.03 \times 250 = 542.5 \text{ V}$$

$$\text{KVL in } l_2: -V_1 + 0.02i_s + V_2 + 0.01i_s = 0 \Rightarrow V_2 = 542.5 - 0.03 \times 200 = 536.5 \text{ V}$$

$$\text{KVL in } l_3: -V_2 + 0.04i_3 + V_3 + 0.02i_3 = 0 \Rightarrow V_3 = 536.5 - 0.06 \times 100 = 530.5 \text{ V}$$

$$P_1 = V_1 i_1 = 542.5 \times 50 = 27.125 \text{ kW}$$

$$P_2 = V_2 i_2 = 536.5 \times 100 = 53.65 \text{ kW}$$

$$P_3 = V_3 i_3 = 530.5 \times 100 = 53.05 \text{ kW}$$


$$\Rightarrow \eta = \frac{P_1 + P_2 + P_3}{P_S} = \frac{133.825}{137.5 \text{ kW}} = 0.973 = 97.3\%$$

8. An industrial heating application can be modelled by using a connection of resistive elements as shown in the figure below. The two requirements for this industrial heating application are stated as below,

1) The total power consumed is equal to 3500 W.

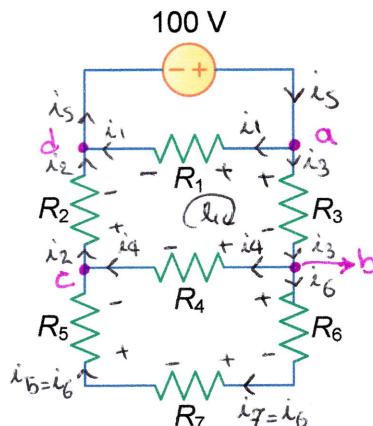2) The elements generate heat uniformly (this means that they dissipate equal power).

Based on the above requirements, calculate the value of resistances R_1 to R_7 .



Solution: Since each resistor consumes the same amount of power, thus the power of each resistor is $\frac{3500}{7} = 500 \text{ W} = P_{R1} = P_{R2} = P_{R3} = P_{R4} = P_{R5} = P_{R6} = P_{R7} = P$

$$R_1 \text{ is in parallel with } 100 \text{ V} \Rightarrow V_{R1} = 100 \text{ V} \Rightarrow P = \frac{V_{R1}^2}{R_1} \Rightarrow R_1 = \frac{V_{R1}^2}{P} = \frac{10000}{500} = 20 \Omega$$

$$\text{Also } i_1 = \frac{V_{R1}}{R_1} = \frac{100}{20} = 5 \text{ A}$$

Note that Total power absorbed = total power supplied. Thus the 100V source supplies 3500W
 $\Rightarrow i_s = \frac{3500}{100} = 35 \text{ A}$

KCL @ b & c: $\begin{cases} i_3 = i_4 + i_6 \\ i_2 = i_4 + i_6 \end{cases} \Rightarrow i_2 = i_3$. Also $R_5 = R_6 = R_7$ since they have the same current and consume the same power
 $\Rightarrow R_2 = R_3$ as they also consume the same power

$$\text{KCL@ a: } i_s = i_1 + i_3 \Rightarrow i_3 = 35 - 5 = 30 \text{ A} \quad i_2 = 30 \text{ A} \quad P = R_2 i_2^2 \Rightarrow R_2 = \frac{500}{900} = \frac{5}{9} = 0.555 \Omega$$

$$\text{Now } V_{R3} = V_{R2} \text{ since } R_2 = R_3 \text{ and } i_2 = i_3 \Rightarrow V_{R2} = \frac{5}{9} \times 30 = \frac{50}{3} \text{ V} = V_{R3}$$


$$\text{KVL } l_1: -V_{R1} + V_{R2} + V_{R4} + V_{R3} = 0 \Rightarrow V_{R4} = 100 - 2 \times \frac{50}{3} = \frac{200}{3} \text{ V}$$

$$\text{I: } i_6 = i_3 - i_4 = 30 - \frac{200}{3} = 30 - \frac{400}{45} = 30 - \frac{15}{2} = \frac{45}{2} \text{ A}$$

$$P = R_6 i_6^2 \Rightarrow R_6 = \frac{500}{(\frac{45}{2})^2} = \frac{2000}{2025} = 0.987 \Omega = R_5 = R_7$$

$$R_4 = \frac{(200)^2}{500} = \frac{400}{45}$$

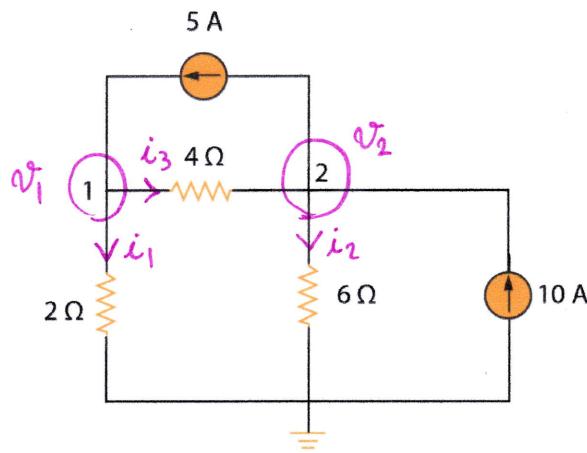9. Find the node voltages in the circuit given below.




$$\text{Answer: } v_1 = \frac{40}{3} = 13.333 \text{ V and } v_2 = 20 \text{ V.}$$

Solution: Assign v_1 and v_2 to nodes 1 and 2 and choose arbitrary direction for currents.

$$\begin{aligned} \text{KCL @ n1: } 5 &= \frac{v_1}{2} + \frac{v_1 - v_2}{4} \xrightarrow{\times 4} 20 = 3v_1 - v_2 \\ \text{KCL @ n2: } 10 + \frac{v_1 - v_2}{4} &= 5 + \frac{v_2}{6} \xrightarrow{\times 12} 60 = 5v_2 - 3v_1 \Rightarrow \begin{cases} 3v_1 - v_2 = 20 \\ 3v_1 - 5v_2 = -60 \end{cases} \\ \Rightarrow v_1 &= \frac{40}{3} = 13.333 \text{ V} \\ v_2 &= 20 \text{ V} \end{aligned}$$

Note that in the case of $i_3 = \frac{v_1 - v_2}{4} = -1.66 \text{ A}$ showing that the actual direction of current is opposite.

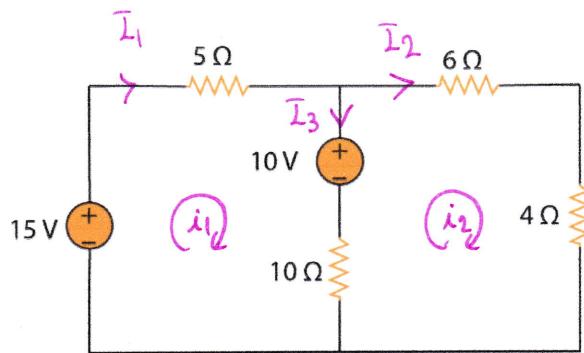10. In the following circuit, find all the branch currents using mesh analysis. (Assign mesh currents and branch currents individually)



Answer: $I_1 = 1 \text{ A}$ (current in 15-V voltage source and 5-Ω resistor), $I_2 = 1 \text{ A}$ (current in 6-Ω and 4-Ω resistors), and $I_3 = 0 \text{ A}$ (current in 10-V voltage source and 10-Ω resistor).

$$\text{Solution: KVL in m1: } -15 + 5i_1 + 10 + 10(i_1 - i_2) = 0$$


$$\text{KVL in m2: } 6i_2 + 4i_2 - 10(i_1 - i_2) - 10 = 0$$

$$\Rightarrow \begin{cases} 15i_1 - 10i_2 = 5 \\ -10i_1 + 20i_2 = 10 \end{cases} \xrightarrow{\begin{matrix} \times 5 \\ \times 10 \end{matrix}} \begin{cases} 3i_1 - 2i_2 = 1 \\ i_1 - 2i_2 = -1 \end{cases} \Rightarrow \begin{cases} i_1 = 1 \text{ A} \\ i_2 = 1 \text{ A} \end{cases}$$

$$\text{Thus: } \begin{cases} I_1 = i_1 = 1 \text{ A} \\ I_2 = i_2 = 1 \text{ A} \\ I_3 = i_1 - i_2 = 0 \text{ A} \end{cases}$$

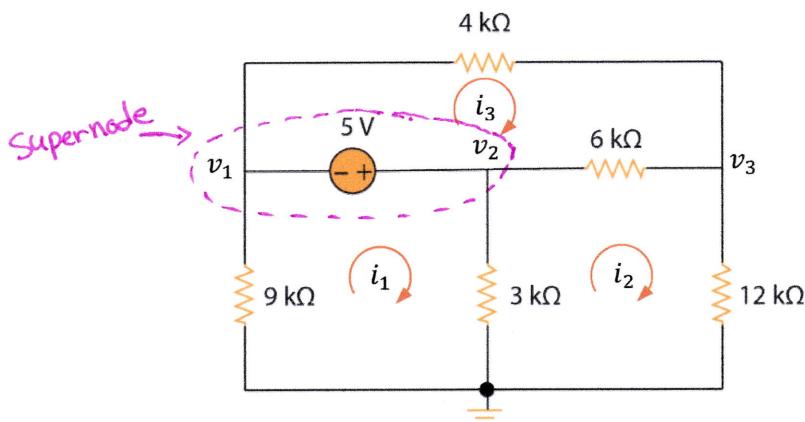11. For the circuit below,

- Write nodal equations using nodal analysis
- Write mesh equations using mesh analysis




Answer:

- $\begin{cases} v_1 - v_2 = -5 \\ 13v_1 + 18v_2 - 15v_3 = 0 \\ 3v_1 + 2v_2 - 6v_3 = 0 \end{cases}$
- $\begin{cases} 12i_1 - 3i_2 = 5 \\ 3i_1 - 21i_2 + 6i_3 = 0 \\ 6i_2 - 10i_3 = 5 \end{cases}$

Solution: Nodal analysis	Mesh analysis
*KCL@ supernode: $\frac{V_1}{3} + \frac{V_2}{6} + \frac{V_2 - V_3}{6} + \frac{V_1 - V_3}{4} = 0$	*KVL in m1: $9i_1 - 5 + 3(i_1 - i_2) = 0 \rightarrow 12i_1 - 3i_2 = 5$
*36 $\rightarrow 13V_1 + 18V_2 - 15V_3 = 0$	*KVL in m2: $12i_2 - 3(i_1 - i_2) + 6(i_2 - i_3) = 0 \rightarrow -3i_1 + 21i_2 - 6i_3 = 0 \xrightarrow{x-1}$
*KCL@ n3: $\frac{V_3}{12} = \frac{V_2 - V_3}{6} + \frac{V_1 - V_3}{4}$	*KVL in m3: $4i_3 - 6(i_2 - i_3) + 5 = 0 \rightarrow 10i_3 - 6i_2 = -5 \xrightarrow{x-1}$
*Supernode Constraint (KVL) $V_2 - V_1 = 5$	$\Rightarrow \begin{cases} 12i_1 - 3i_2 = 5 \\ 3i_1 - 21i_2 - 6i_3 = 0 \\ 6i_2 - 10i_3 = 5 \end{cases}$ Mesh equation
$\Rightarrow \begin{cases} V_1 - V_2 = -5 \\ 13V_1 + 18V_2 - 15V_3 = 0 \\ 3V_1 + 2V_2 - 6V_3 = 0 \end{cases}$ Nodal equation	

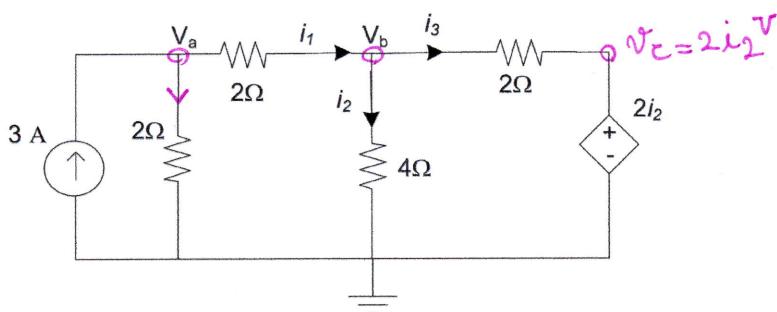12. (Mid-session Exam – S2, 2016) For the circuit below,

- Apply nodal analysis to write down the node voltage equations at nodes V_a and V_b .
- Solve the voltage equations in part (a) to find the voltages V_a and V_b .
- Find the currents i_1 , i_2 and i_3 based on your results in part (b)



Answer:

- $\begin{cases} 2V_a - V_b = 6 \\ 2V_a - 4V_b = 0 \end{cases}$
- $V_a = 4 \text{ V}$ and $V_b = 2 \text{ V}$.
- $i_1 = 1 \text{ A}$, $i_2 = 0.5 \text{ A}$ and $i_3 = 0.5 \text{ A}$

Solution: Note that V_c is directly connected to dependent voltage source	
a) *KCL@ V_a : $3 = \frac{V_a}{2} + \frac{V_a - V_b}{2} \xrightarrow{x2} 2V_a - V_b = 6$	(I)
*KCL@ V_b : $\frac{V_a - V_b}{2} = \frac{V_b}{4} + \frac{V_b - V_c}{2}$ Also $V_c = 2i_2$ and $i_2 = \frac{V_b}{4} \Rightarrow V_c = \frac{V_b}{2}$	
*4 & (I) $\rightarrow 2(V_a - V_b) = V_b + 2(V_b - \frac{V_b}{2}) \rightarrow 2V_a - 4V_b = 0$	
\Rightarrow Nodal equation $\begin{cases} 2V_a - V_b = 6 \\ 2V_a - 4V_b = 0 \end{cases}$	
b) Solve the equations $\rightarrow V_a = 4 \text{ V}$ and $V_b = 2 \text{ V}$	


$$i_1 = \frac{V_a - V_b}{2} = \frac{4 - 2}{2} = 1 \text{ A}$$

$$i_2 = \frac{V_b}{4} = \frac{2}{4} = 0.5 \text{ A}$$

$$i_3 = \frac{V_b - V_c}{2} \stackrel{(I)}{=} \frac{V_b - \frac{V_b}{2}}{2} = \frac{V_b}{4} = \frac{2}{4} = 0.5 \text{ A}$$

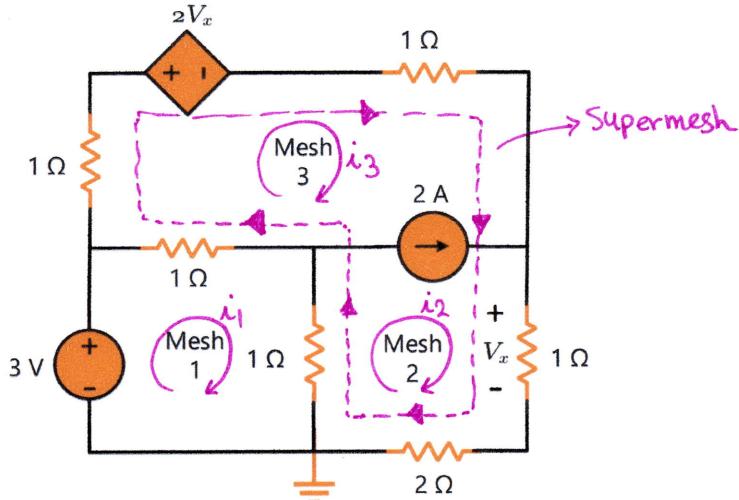13. (Mid-session Exam – Summer, 2017) For the circuit below,

- Apply mesh analysis to write down the mesh current equations in Mesh 1, Mesh 2, and Mesh 3 (this part was only given in the actual exam).
- Solve the current equations in part (a) to find the mesh current.
- Find the power generated by the dependent voltage source based on your results in part (b).



Answer:

$$\text{a) } \begin{cases} 2i_1 - i_2 - i_3 = 3 \\ 2i_1 - 6i_2 - 3i_3 = 0 \\ i_2 - i_3 = 2 \end{cases}$$

$$\text{b) } i_1 = 1.5 \text{ A}, i_2 = 1 \text{ A} \text{ and } i_3 = -1 \text{ A}$$

$$\text{c) } P = 2 \text{ W supplied}$$

Solution: Note that 2-A current source is a common branch between Mesh 2 and Mesh 3.

$$\text{a) *KVL in m1: } -3 + 1(i_1 - i_3) + 1(i_1 - i_2) = 0 \rightarrow 2i_1 - i_2 - i_3 = 3$$

$$\text{*KVL in Supermesh: } 1i_3 + 2V_x + 1i_3 + 1i_2 - 1(i_1 - i_2) - 1(i_1 - i_3) = 0$$

$$\rightarrow 2V_x - 2i_1 + 4i_2 + 3i_3 = 0 \quad \text{Also } V_x = 1i_2 \quad \text{Note the polarity of } V_x \text{ and direction of } i_2$$

$$\Rightarrow -2i_1 + 6i_2 + 3i_3 = 0$$

$$\text{* Supermesh Constraint (KCL): } i_2 - i_3 = 2$$


$$\text{Thus: } \begin{cases} 2i_1 - i_2 - i_3 = 3 \\ 2i_1 - 6i_2 - 3i_3 = 0 \\ i_2 - i_3 = 2 \end{cases}$$

$$\text{b) Solve the equations } \rightarrow \begin{cases} i_1 = 1.5 \text{ A} \\ i_2 = 1 \text{ A} \\ i_3 = -1 \text{ A} \end{cases}$$

$$\text{c) } P = -(-1) \times 2V_x = 1 \times 2 \times 1 = 2 \text{ W supplied or } -2 \text{ W absorbed}$$

Note that i_2 enters the positive terminal of the dependent voltage source.

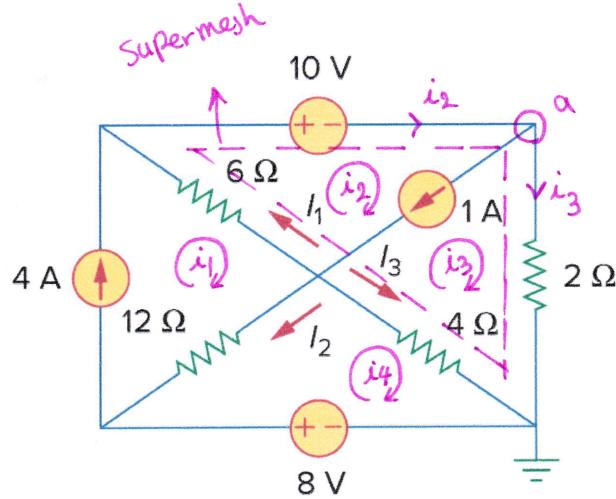14. In the circuit below, find the branch currents I_1 , I_2 , and I_3 .



Answer: $I_1 = -1 \text{ A}$, $I_2 = 0 \text{ A}$, and $I_3 = 2 \text{ A}$

Solution: Note that 1A current source is a common branch between mesh 2 and mesh 3.

Also, it is clear that $i_1 = 4 \text{ A}$ (I) in mesh 1

* KVL in m4: $-8 - 12(i_1 - i_4) + 4(i_4 - i_3) = 0 \xrightarrow{* -\frac{1}{4}} 3i_1 + i_3 - 4i_4 = -2$

* KVL in Supermesh: $10 + 2i_3 - 4(i_4 - i_3) + 6(i_2 - i_1) = 0$

x -\frac{1}{2} $\rightarrow -3i_1 + 3i_2 + 3i_3 - 2i_4 = -5$

* Supermesh Constraint (KCL @ node a): $i_2 = i_3 + 1$

$$\xrightarrow{(I)} \begin{cases} i_3 - 4i_4 = -14 \\ 3i_2 + 3i_3 - 2i_4 = 7 \\ i_2 - i_3 = 1 \end{cases} \xrightarrow{\text{Solve}} \begin{cases} i_2 = 3 \text{ A} \\ i_3 = 2 \text{ A} \\ i_4 = 4 \text{ A} \end{cases} \xrightarrow{\text{Thus}} \begin{cases} I_1 = i_2 - i_1 = -1 \text{ A} \\ I_2 = i_1 - i_4 = 0 \text{ A} \\ I_3 = i_1 - i_3 = 2 \text{ A} \end{cases}$$