



Family Name

Given Name

Student No.

Signature

THE UNIVERSITY OF NEW SOUTH WALES

School of Electrical Engineering & Telecommunications

MID-SEMESTER EXAMINATION

Semester 2, 2018

ELEC1111

Electrical and Telecommunications Engineering

TIME ALLOWED: 75 min

TOTAL MARKS: 100

TOTAL NUMBER OF QUESTIONS: 5

THIS EXAM CONTRIBUTES 25% TO THE TOTAL COURSE ASSESSMENT

Reading Time: 5 minutes.

This paper contains 4 pages.

Candidates must **ATTEMPT ALL** questions.

Answer each question in a **separate answer booklet**.

Marks for each question are indicated beside the question.

This paper **MAY NOT** be retained by the candidate.

Print your name, student ID and question number on the front page of each answer book.

Authorised examination materials:

Candidates should use their own UNSW-approved electronic calculators.

This is a closed book examination.

Assumptions made in answering the questions should be stated explicitly.

All answers must be written in ink. Except where they are expressly required, pencils **may only be used** for drawing, sketching or graphical work.

QUESTION 1 [15 marks]

For the circuit shown in Figure 1,

- (6 marks)** Calculate the equivalent resistance R_{eq} as seen from terminals $a-b$.
- (3 marks)** Find voltage v using the result of part (a).
- (6 marks)** Use voltage division to find voltage v_1 from voltage v .

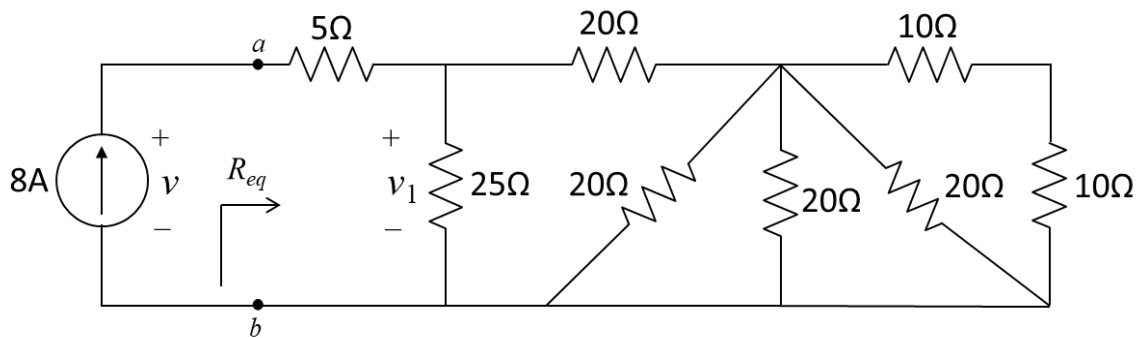


Figure 1

QUESTION 2 [20 marks]

Use nodal analysis to calculate the power supplied/absorbed by the dependent voltage source in the circuit shown in Figure 2.

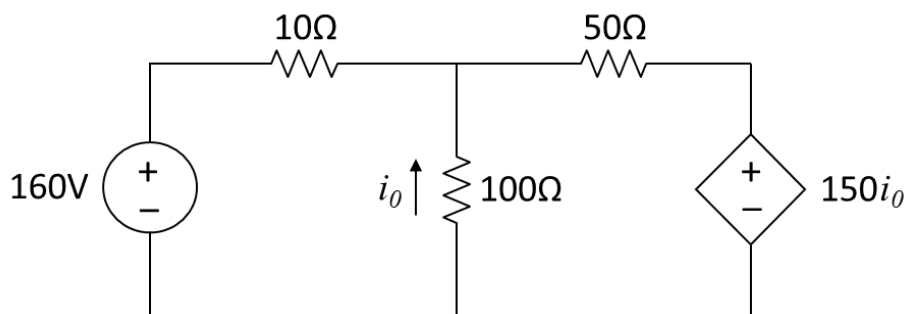


Figure 2

QUESTION 3 [15 marks]

Use a series of source transformations to find i_0 in the circuit shown in Figure 3.

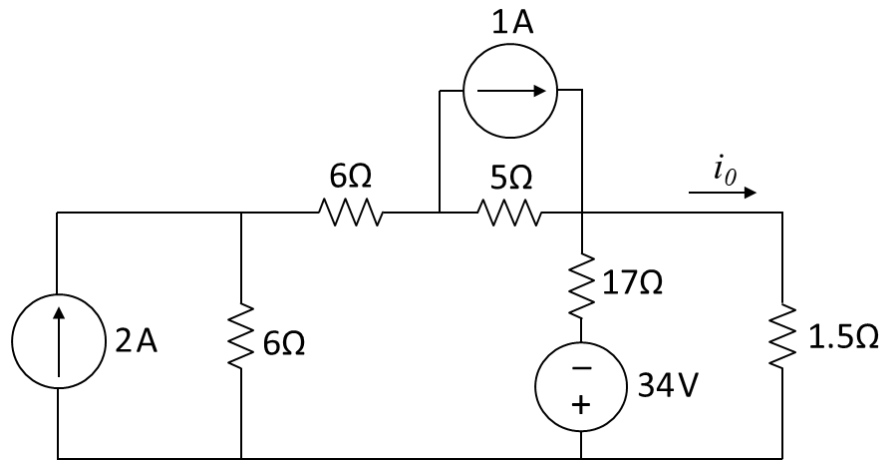


Figure 3

QUESTION 4 [20 marks]

The system shown in Figure 4 is being used to power a load.

- (15 marks) Find the Thevenin equivalent of the system.
- (5 marks) Find the power in the load using the Thevenin equivalent model from part (a).

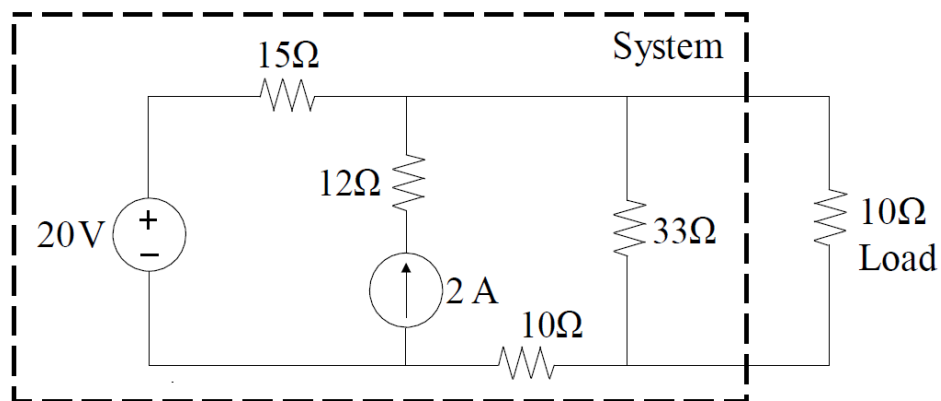


Figure 4

QUESTION 5 [30 marks]

- a. **(15 marks)** The circuit shown in Figure 5 is used to test a “touch-switch” (Sw B), which detects the touch of a finger by the capacitance of the human body. The body can be modelled as a 100 pF capacitor relative to ground, and the resistance of the arm can be modelled as a $1.5\text{ k}\Omega$ resistor.
- (5 marks)** A person is charged to 2000 V as it walks across a carpet towards the touch-switch (Sw B). It stops in front of the touch-switch at time $t = 0\text{ s}$ (Sw A opens). What energy is stored in the body?
 - (10 marks)** At time $t = 0\text{ s}$, the person touches the touch-switch (Sw B closes). Calculate and plot the current through the $100\text{ k}\Omega$ resistor for the first $50\text{ }\mu\text{s}$. Ensure your plot is to scale and has at least three labelled values.

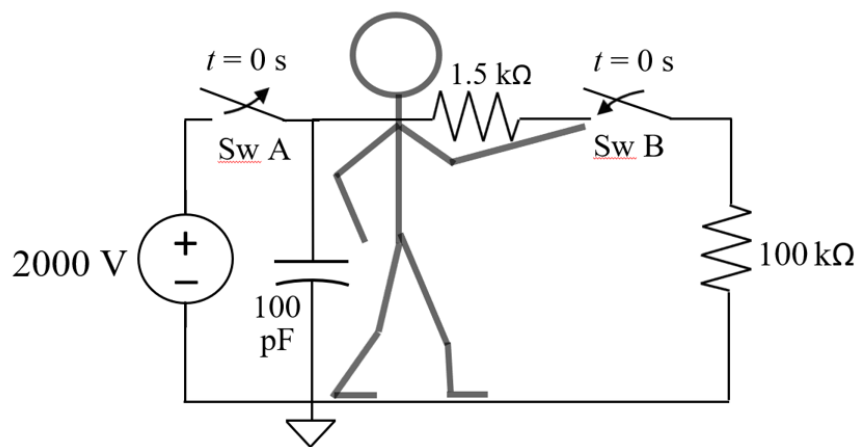


Figure 5

- b. **(15 marks)** In the circuit shown in Figure 6, the switch has been closed for a long time before it is opened at $t = 0$.
- (4 marks)** Find the initial voltage $v_c(0^-)$ across the capacitor.
 - (4 marks)** Find the final voltage $v_c(\infty)$ across the capacitor.
 - (4 marks)** Derive an expression for the voltage of the capacitor $v_c(t)$ for all time (i.e., for both $t < 0$ and $t \geq 0$).
 - (3 marks)** Sketch the voltage $v_c(t)$ obtained in part (iii) as a function of time.

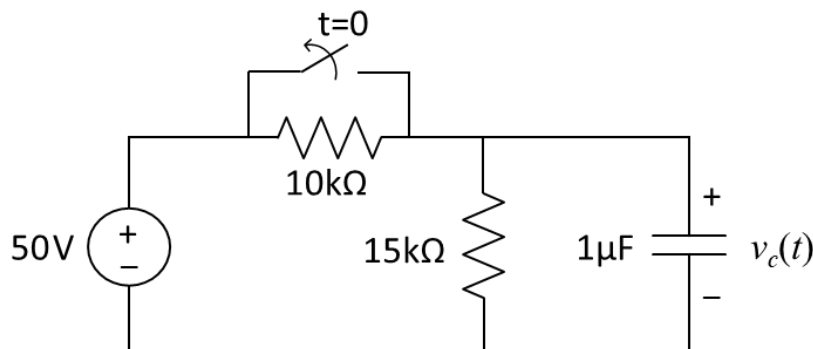


Figure 6

END OF PAPER