

Topic 8 recap

- **Nodal** and **mesh analysis** are applied to AC circuits the same way as in DC circuits.
 - Nodal equations (KCL) and mesh equations (KVL) should be written for an AC circuit in phasor domain when it is operated in steady state sinusoidal conditions.
- **Superposition** can also be applied to AC circuits with multiple independent sources in phasor domain.
 - When having sources with **different frequencies only superposition** can be used to find the steady state response of the circuit.
 - A separate phasor circuit must be solved for each frequency independently.
 - The overall response is the sum of the time domain responses of all individual phasor circuits.
 - If the **frequencies are the same**, the sum of the phasor responses will be used as the final response and then transformed back to time domain if needed.
- The concept of **source transformation** is also applicable in the frequency domain.

Topic 8 recap

- **Thevenin** and **Norton equivalent** circuits can also be used for AC circuits in phasor domain.
 - The Thevenin equivalent circuit consists of a voltage source \mathbf{V}_{Th} in series with the Thevenin equivalent impedance \mathbf{Z}_{Th} :
 - $\mathbf{V}_{Th} = \mathbf{V}_{oc}$: Open-circuit phasor voltage across the given terminals.
 - $\mathbf{Z}_{Th} = \mathbf{Z}_{eq}$: Equivalent impedance as seen from the given terminals.
 - The Norton equivalent circuit consists of a current source \mathbf{I}_N in parallel with the Norton equivalent impedance \mathbf{Z}_N :
 - $\mathbf{I}_N = \mathbf{I}_{sc}$: Short-circuit current through the given terminals.
 - $\mathbf{Z}_N = \mathbf{Z}_{Th} = \mathbf{Z}_{eq}$: Equivalent impedance as seen from the given terminals.
 - **Thevenin-Norton transformation** is the same as in DC:

$$\mathbf{I}_N = \frac{\mathbf{V}_{Th}}{\mathbf{Z}_{Th}} \text{ and } \mathbf{V}_{Th} = \mathbf{Z}_N \mathbf{I}_N$$