



Faculty of Engineering

School of Electrical Engineering and Telecommunications

# ELEC 1111 – Topic 3

## Circuit Theorems

**Dr. Inmaculada (Inma) Tomeo-Reyes**

Lecturer

School of Electrical Engineering and Telecommunications, UNSW

# Topic 3 Content

## **This lecture covers:**

- Linearity and Superposition
- Source Transformation
- Thevenin's and Norton's theorems
- Maximum Power Transfer

**Corresponds to Chapter 4  
of your textbook**

# Linear property


- A system is called **linear** if it follows two main properties:

- **Homogeneity:**


If the input ( $x$ ) is multiplied by a constant ( $k$ ), the output/response ( $y$ ) is multiplied by the **same** constant.

- **Additivity:**

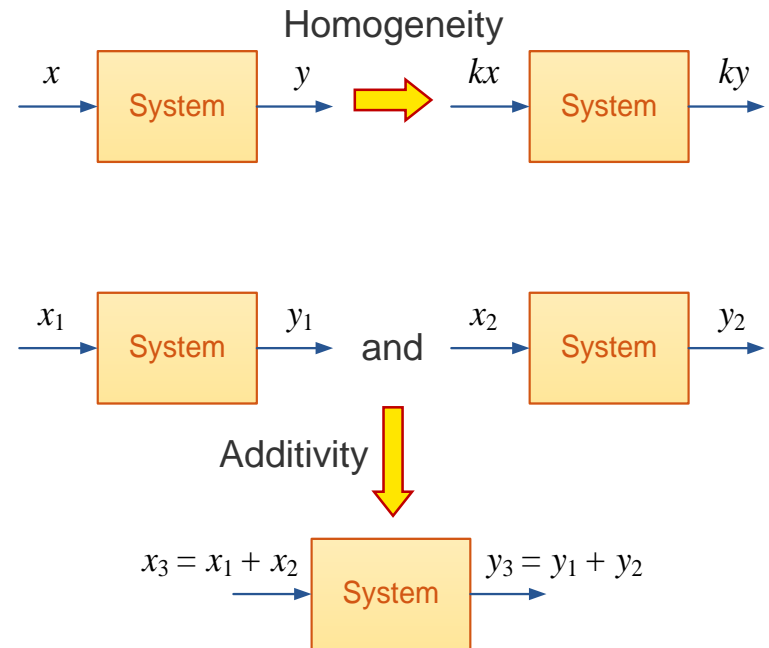The response to the sum of the inputs is the sum of the individual responses to each input.




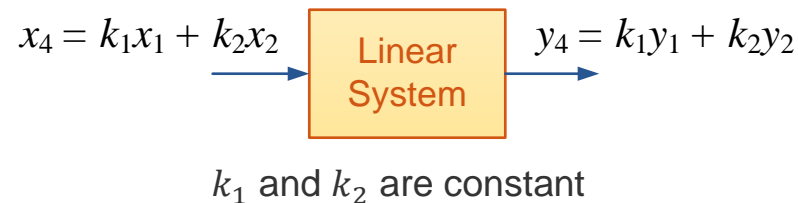- Together, the response to the **linear combination** of inputs is equal to the **linear combination** of individual responses to each input.


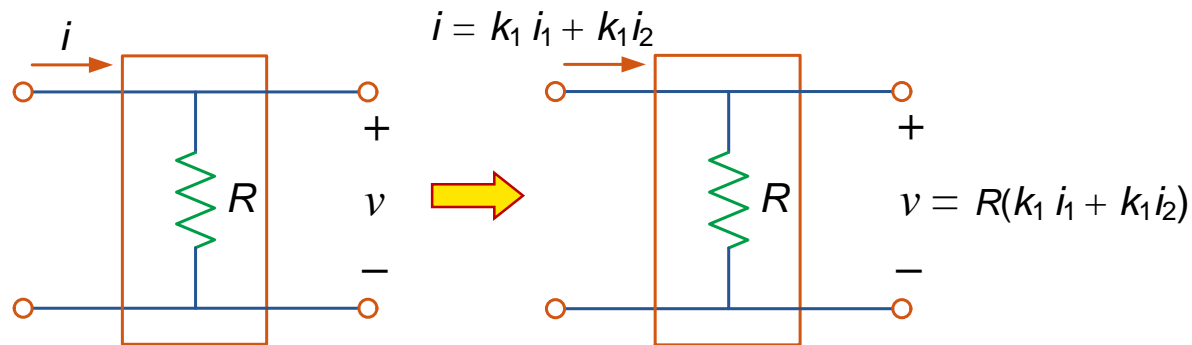
# Linear property

- Resistor is a **linear electrical element** since the voltage-current relationship satisfies both the **homogeneity** and **additivity** properties.



$$v = R(k_1 i_1 + k_2 i_2)$$

$$v = k_1 \underbrace{R i_1}_{v_1} + k_2 \underbrace{R i_2}_{v_2}$$

$$v = k_1 v_1 + k_2 v_2$$

# Linear property

A **linear circuit** is one whose **output** is **linearly related** (or directly proportional) to its **input**.

Example: Find the voltage  $v_o$  when  $i_s = 30$  A and  $i_s = 60$  A.


$$i_2 = \frac{4 \parallel 20}{20} i_s = \frac{20/6}{20} i_s = \frac{1}{6} i_s \quad (\text{current division})$$

$$v_o = 8i_2 = 8 \times \frac{1}{6} i_s = \frac{4}{3} i_s \quad (\text{Ohm's law})$$

$$\text{If } i_s = 30 \text{ A} \quad \Rightarrow \quad v_o = \frac{4}{3} i_s = 40 \text{ V}$$

$$\text{If } i_s = 60 \text{ A} \quad \Rightarrow \quad v_o = \frac{4}{3} i_s = 80 \text{ V}$$
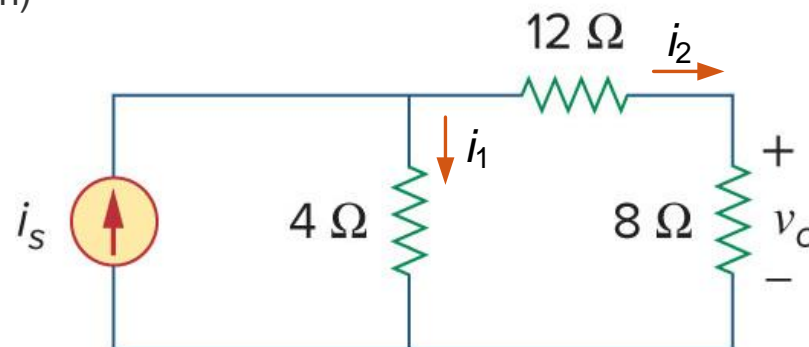
$$\text{If } i_s = k_1 30 + k_1 60 \text{ A} \quad \Rightarrow \quad v_o = \frac{4}{3} i_s = \frac{4}{3} (k_1 30 + k_1 60) = k_1 40 + k_1 80 \text{ V}$$



# Superposition

If there are **two** or **more independent** sources in a circuit, there are different ways to solve for the circuit parameters:

- Nodal or mesh analyses.
- **Superposition.**
  - It is based on the **linear property** of circuits.
  - Only **one independent** source is considered at a time.
  - The **rest** of the independent sources are **set to zero** (turned off).
  - **Dependent** sources are **left intact** since they are controlled by circuit variables.


The **superposition** principle states that the voltage across (or current through) an element in a **linear circuit** is the **algebraic sum** of the voltages across (or currents through) that element due to each **independent source** acting **alone**.

# Superposition


Steps to apply superposition principle:

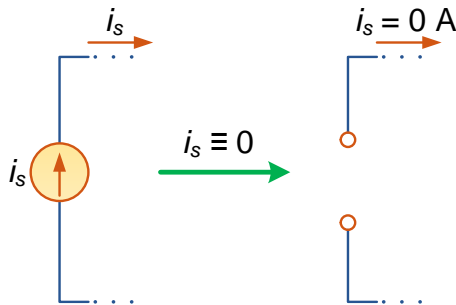1. Turn off all **independent** sources except **one** by setting them to **zero**.
2. Find the output (voltage or current in question) using methods covered in Topics 2 and 3.
3. Repeat step 1 for each of the other independent sources.
4. Find the total contribution by **adding** algebraically all the contributions due to the **independent** sources.

Turning off a **current source** means replacing it with an **open circuit**




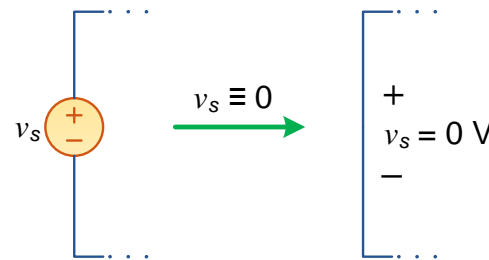Turning off a **voltage source** means replacing it with a **short circuit**


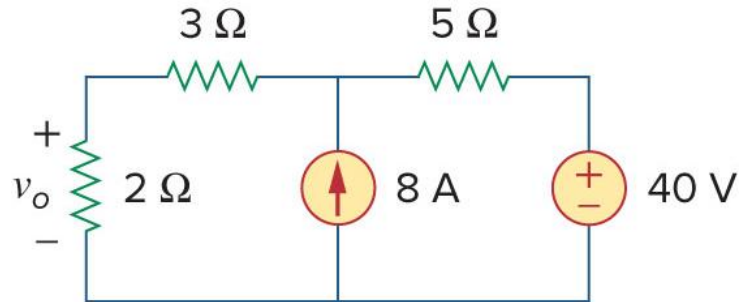
# Exercise


Using the superposition theorem, find  $v_o$  in the circuit below.





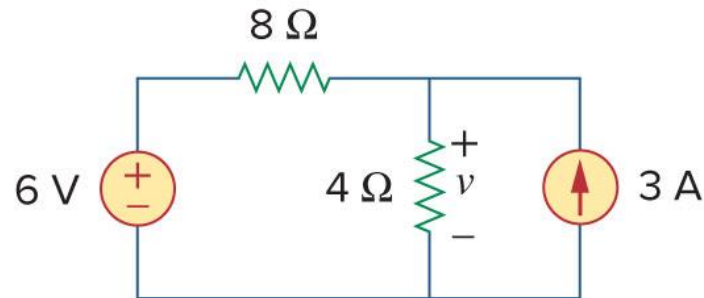
# Exercise

Using the superposition theorem, find  $v$  in the circuit below.


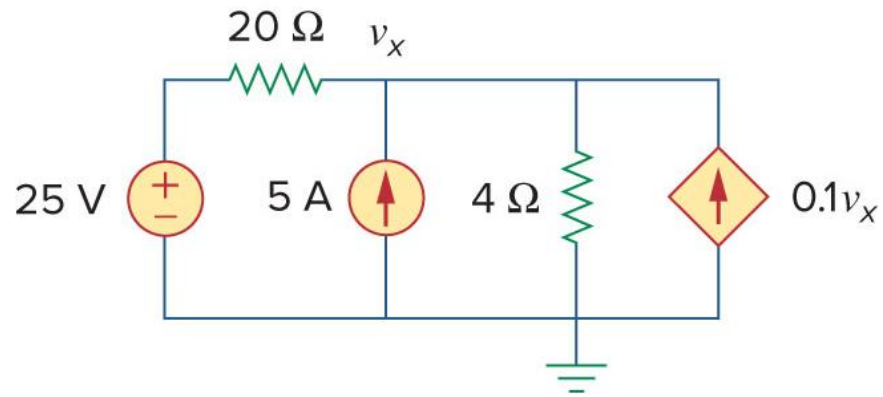
# Exercise

Using the superposition theorem, find  $v_x$  in the circuit below.




# Superposition

Superposition is only applicable to **linear responses**.


E.g. power in resistors is a nonlinear response.

$$p = vi = i^2 R = \frac{v^2}{R}$$

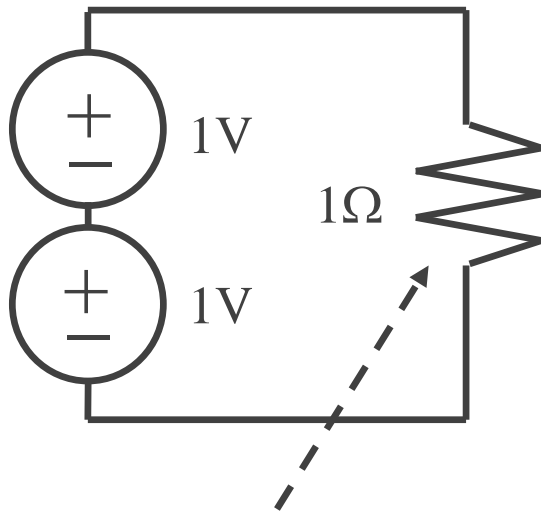


4W delivered  
to resistor

≠

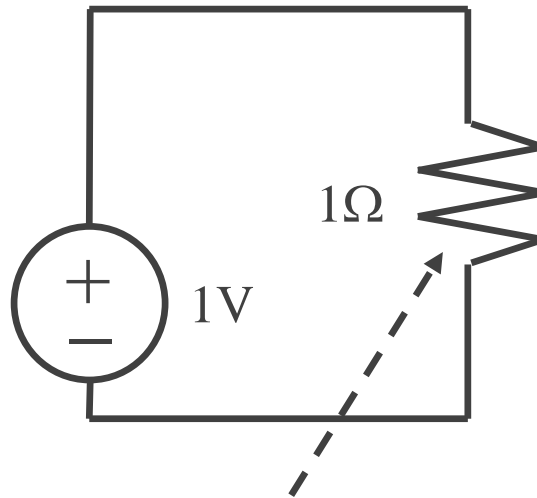

1W delivered  
to resistor

+

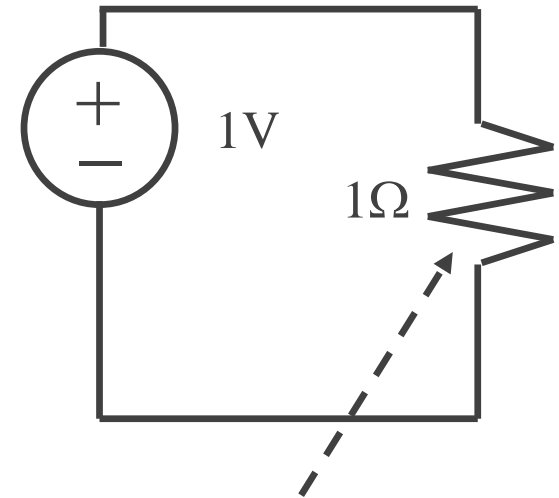


1W delivered  
to resistor
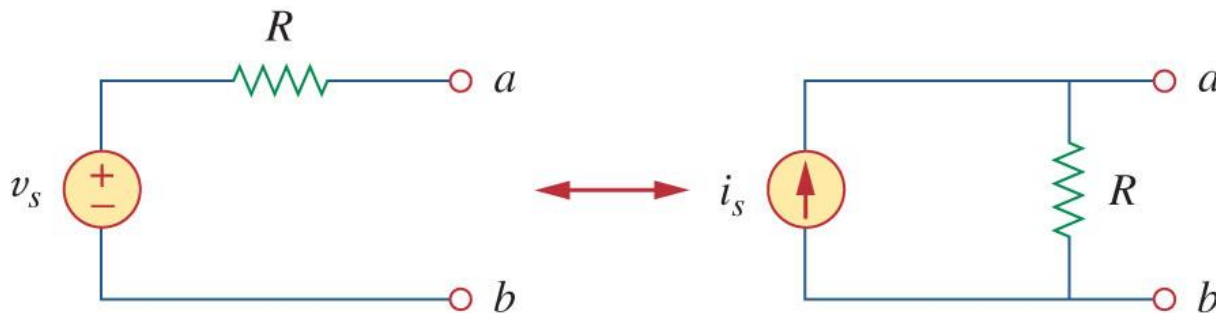
# Source transformation

- It is possible to transform a source from one form to another. This can be useful for **simplifying** circuits.
- The principle behind this transformation is the concept of **equivalence**, where two circuits are called equivalent if their  **$v$ - $i$  characteristics** are **identical** at the terminal.
- The **direction** of current and **polarity** of voltage should follow the **passive sign convention**.


A **source transformation** is the process of **replacing** a voltage source  $v_s$  in **series** with a resistor  $R$  by a current source  $i_s$  in **parallel** with a resistor  $R$  or vice versa




# Source transformation
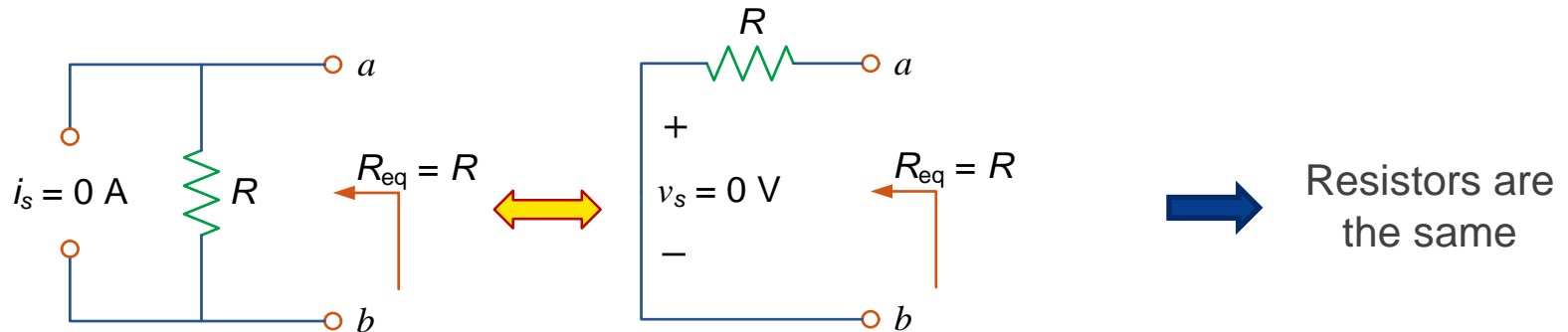
## Terminal equivalency


- If we turn off the sources, the **equivalent resistance** ( $R_{eq}$ ) at terminal  $a$ - $b$  must be the **same**.



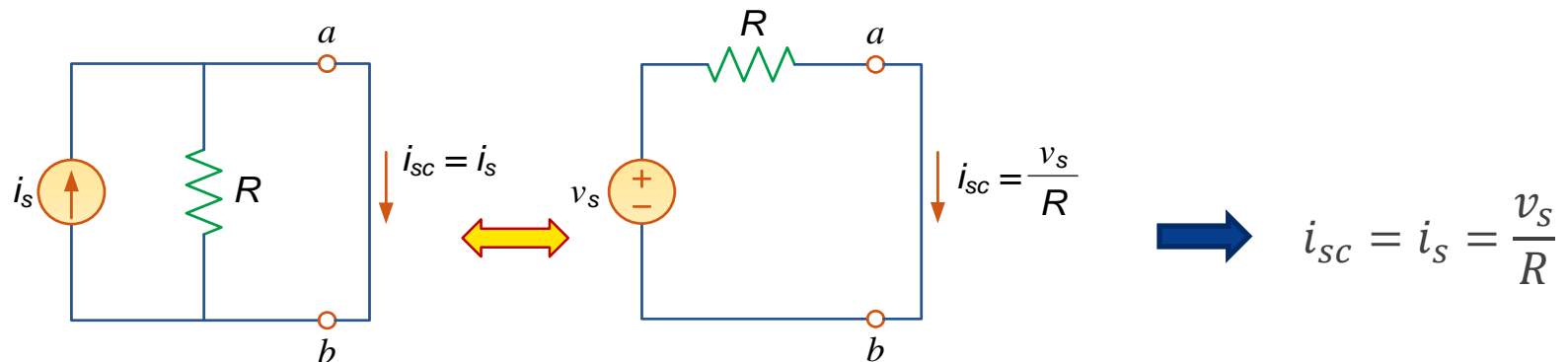- Short-circuit current** ( $i_{sc}$ ) flowing from  $a$  to  $b$  must be the **same**.




# Source transformation

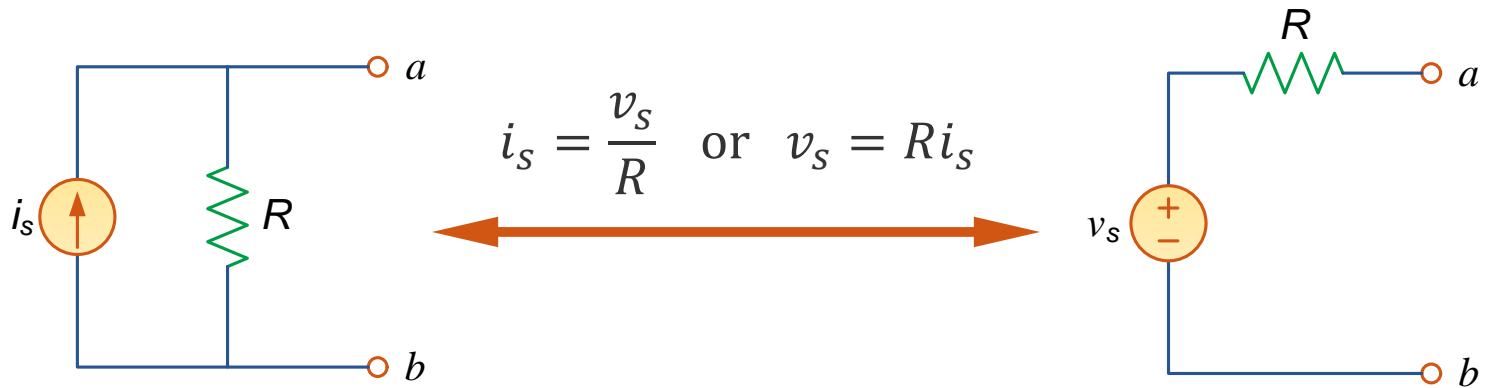
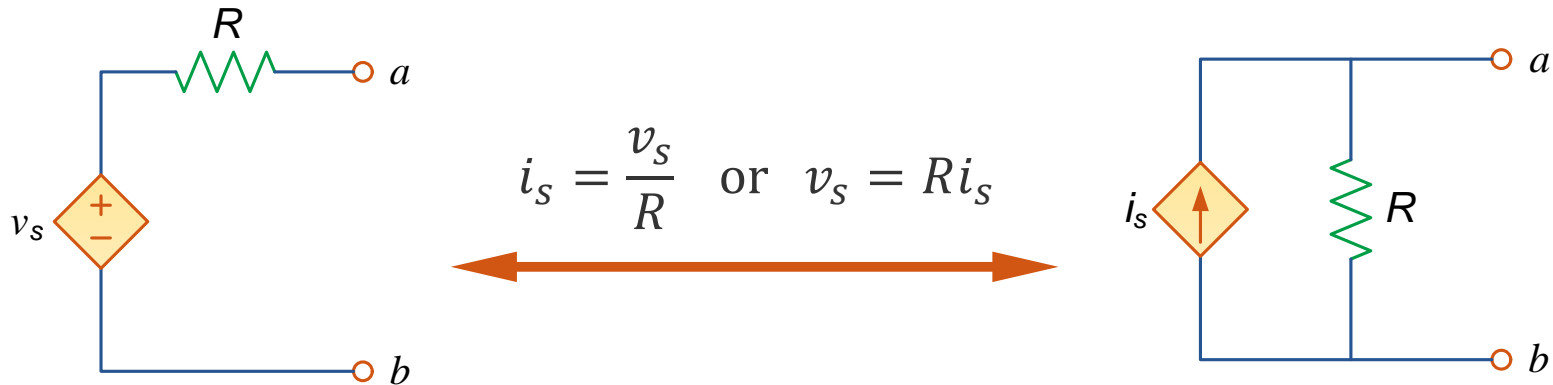
# Source transformation

- Source transformation can also be applied to **dependent** sources, provided that the dependent **variable** is handled **carefully**.




Some limitations:

- Source transformation is **not** possible when  $R = 0$  for an **ideal voltage source** (for a practical voltage source  $R \neq 0$ )
- Source transformation is **not** possible when  $R = \infty$  for an **ideal current source** (for a practical current source  $R \neq \infty$ )
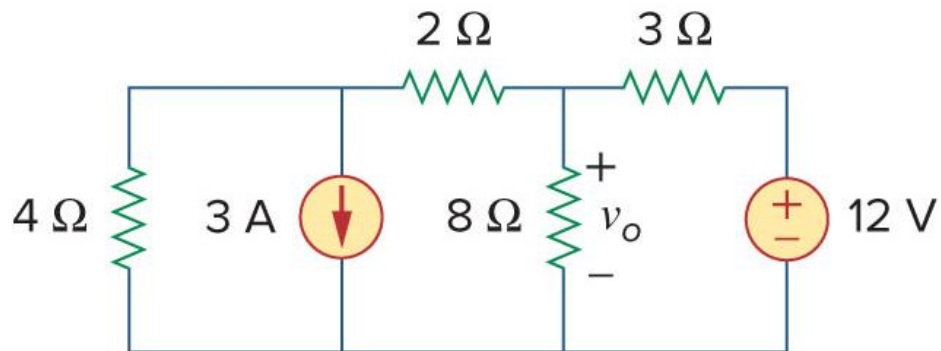
# Exercise


Use source transformation to find  $v_o$  in the circuit below.





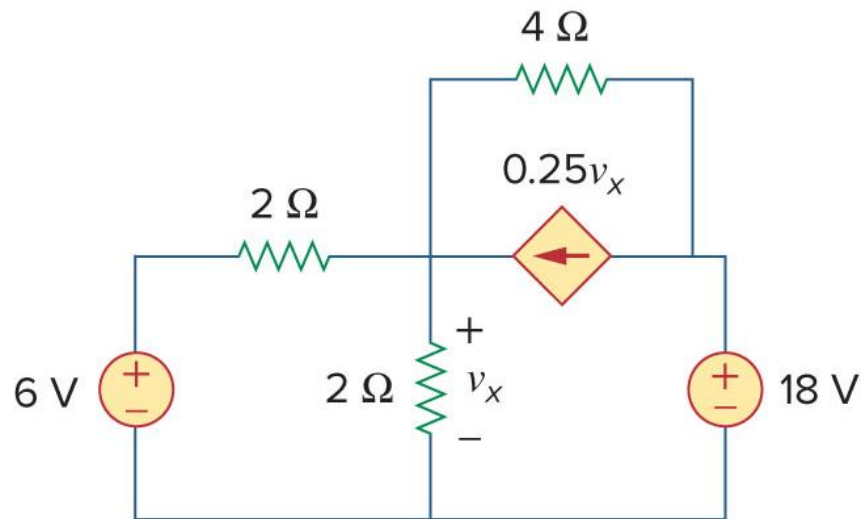
# Exercise

Use source transformation to find  $v_x$  in the circuit below.



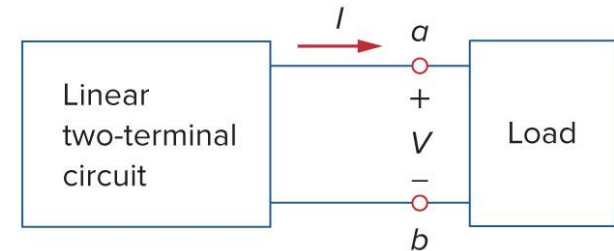
# Thevenin's theorem

- In many circuits, one element can be variable (e.g. house hold appliances consuming different powers – hairdryer, fridge, etc.). This variable element is called the **load**.
- Every time the load changes, the circuit would have to be analyzed again.
- Thevenin's theorem provides a technique to simplify the analysis by **replacing the fixed part** of the circuit with an equivalent one known as **Thevenin equivalent circuit**.



(a)

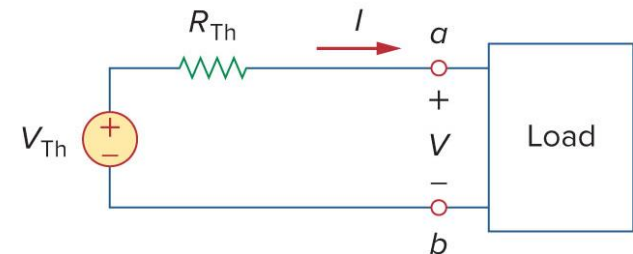


(b)

**Thevenin's theorem** states that a **linear** two-terminal circuit (Fig. (a)) can be replaced by an **equivalent circuit** consisting of a **voltage source  $V_{Th}$**  in **series** with a **resistor  $R_{Th}$**  (Fig. (b))
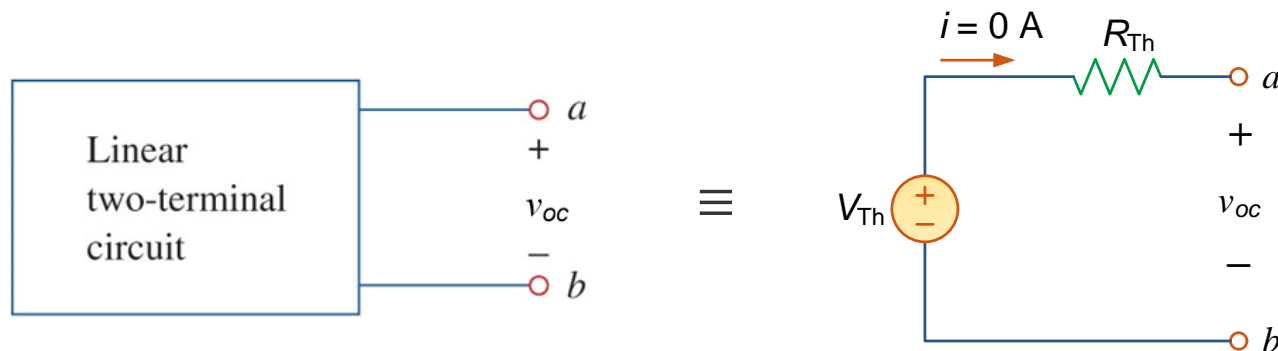
# Thevenin's theorem


- The voltage source's value, known as **Thevenin voltage**  $V_{Th}$ , is equal to the **open-circuit voltage** at the terminals.




$$V_{Th} = v_{oc}$$
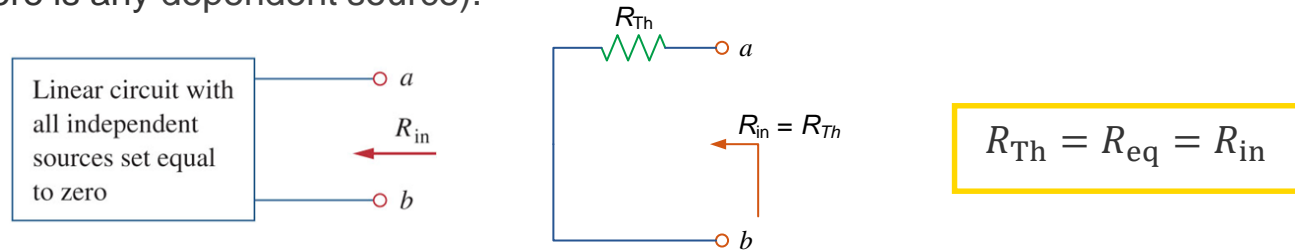
# Thevenin's theorem


- $R_{Th}$  can be obtained using different methods:
  1. Input **resistance** measured at the terminal pair when **all independent sources are turned off** (not valid if there is any dependent source).



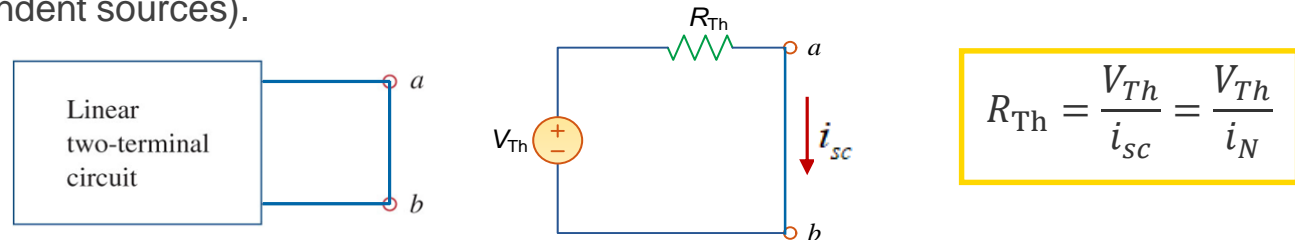2. Ratio of the open-circuit voltage to the short-circuit current at the terminal pair (not valid if there are only dependent sources).




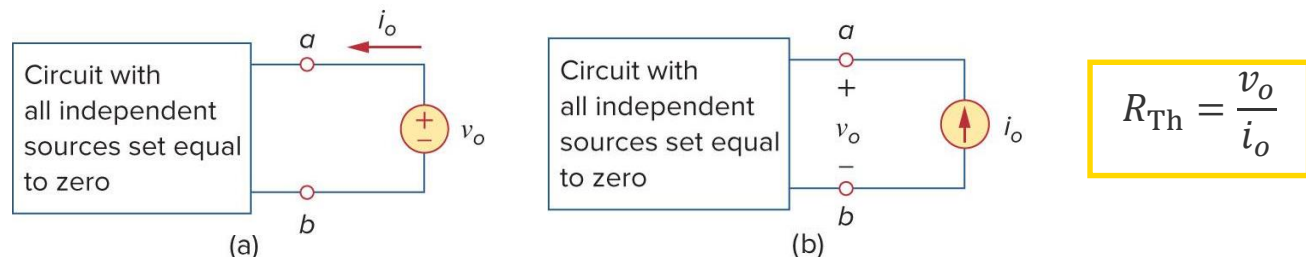3. Turn off independent sources and (a) attach a voltage source  $v_o$  to the terminals  $a$ - $b$  and find the resulting current  $i_o$ , or (b) attach a current source  $i_o$  and find the resulting voltage  $v_o$ . For simplicity:  $v_o = 1$  V or  $i_o = 1$  A (valid always).



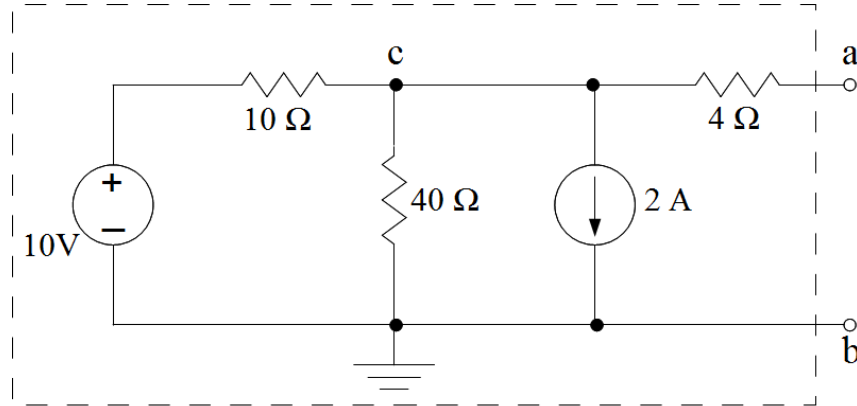
# Exercise

Calculate the Thevenin equivalent of the circuit, as seen from terminals a-b.



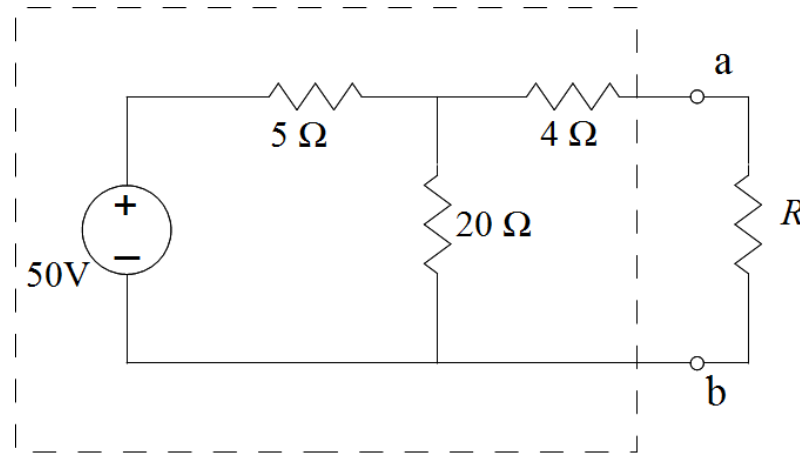
# Exercise

Replace the circuit in the box with its Thevenin equivalent circuit.


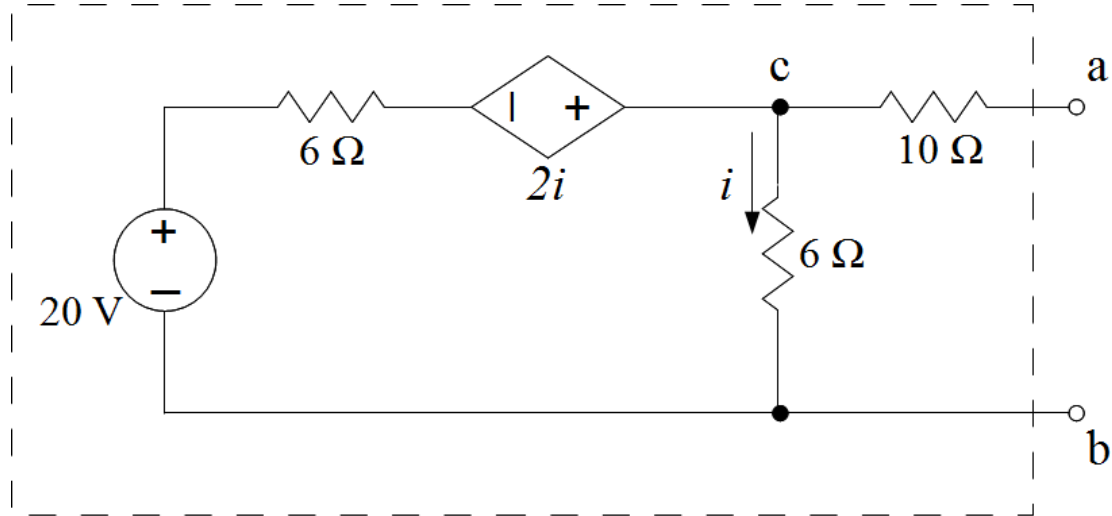
# Exercise

Calculate the Thevenin equivalent of the circuit, as seen from terminals a-b.



# Thevenin's theorem


When we have a circuit with **dependent sources but not independent ones**, we have a “dead network”, i.e. all voltages and currents are equal to zero.

- Thevenin voltage  $V_{Th}$ :

$$V_{Th} = v_{oc} = 0$$

- Thevenin resistance  $R_{Th}$ :


- All currents and voltages in the circuit are equal to zero, including  $i_{sc}$ .
- The only possible method to calculate  $R_{Th}$  in this case is method 3, i.e. attach a **voltage source**  $v_o$  to the terminals **a-b** and find the resulting **current**  $i_o$  (Fig. (a)), or attach a **current source**  $i_o$  and find the resulting **voltage**  $v_o$  (Fig. (b)).
- Note: In this case it is possible for  $R_{Th}$  to be negative ( $R_{Th} < 0$ ). This implies that the circuit is supplying power.

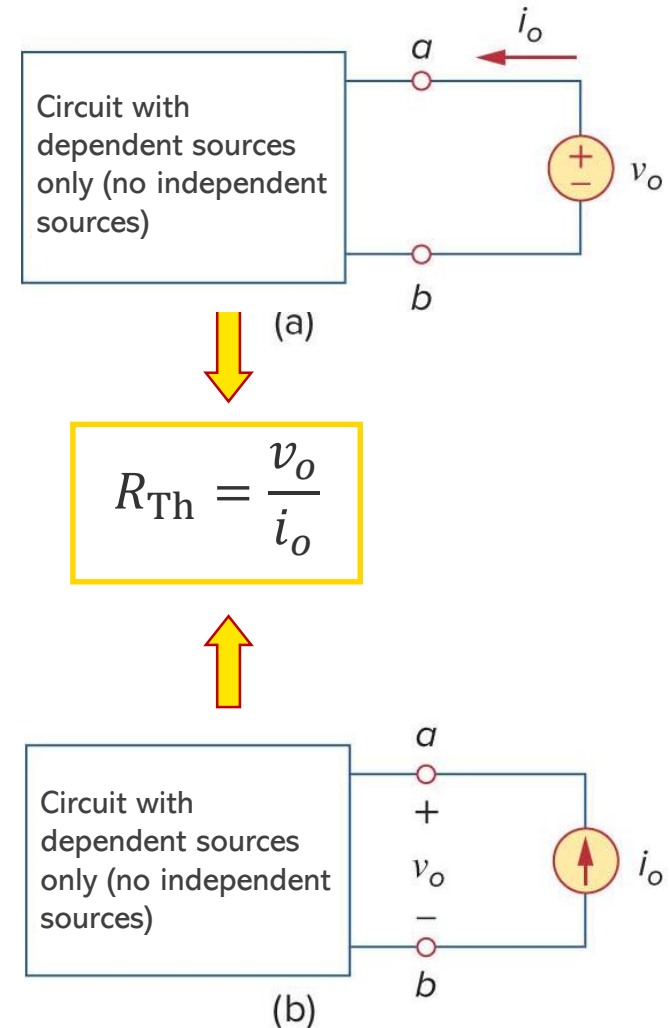




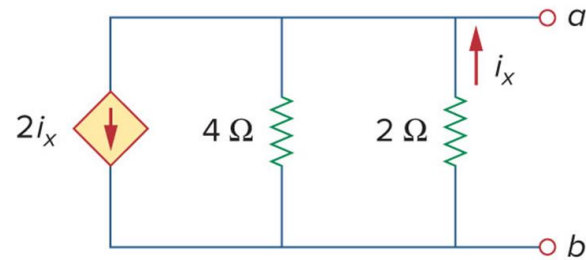
# Exercise

Find the Thevenin equivalent of the circuit below at the terminals  $a$ - $b$ .


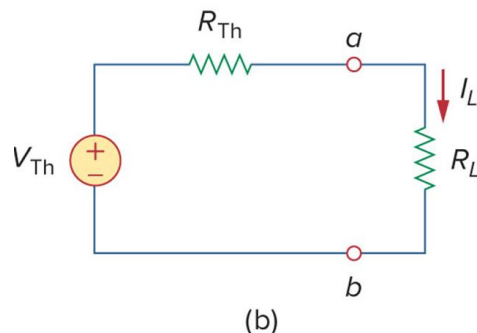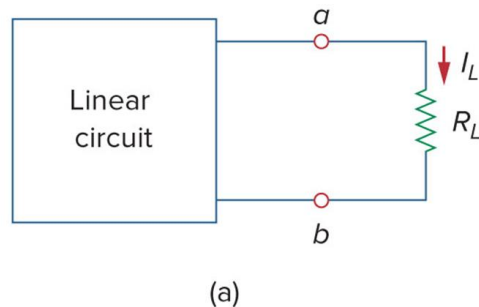
# Thevenin's theorem

- Thevenin's theorem is a powerful technique in circuit analysis with variable loads.
- It allows to **simplify** a large linear circuit.
- The **equivalent circuit** behaves externally **exactly the same** as the original circuit.
- The current through the **load**  $R_L$  (**load current**  $I_L$ ) and the voltage across the load (**load voltage**  $V_L$ ) is obtained using simple voltage division or KVL/KCL.




$$I_L = \frac{V_{Th}}{R_{Th} + R_L}$$
$$V_L = \frac{R_L}{R_{Th} + R_L} V_{Th}$$

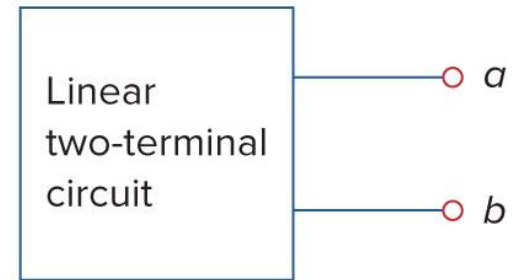
# Norton's theorem

- Norton's theorem is the **dual** form of Thevenin's theorem.
- It provides a similar technique to **simplify** the analysis by **replacing a linear circuit** with an equivalent one known as **Norton's equivalent circuit**.

**Norton's theorem** states that a **linear** two-terminal circuit (Fig. (a)) can be replaced by an **equivalent circuit** consisting of a **current source  $I_N$**  in **parallel** with a **resistor  $R_N$**  (Fig. (b)).




(a)

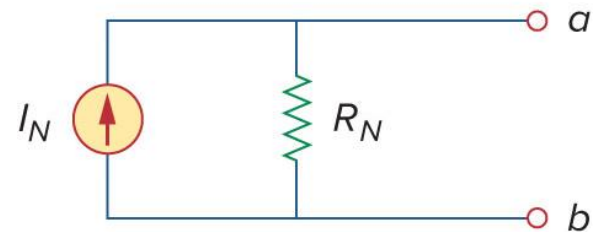


(b)
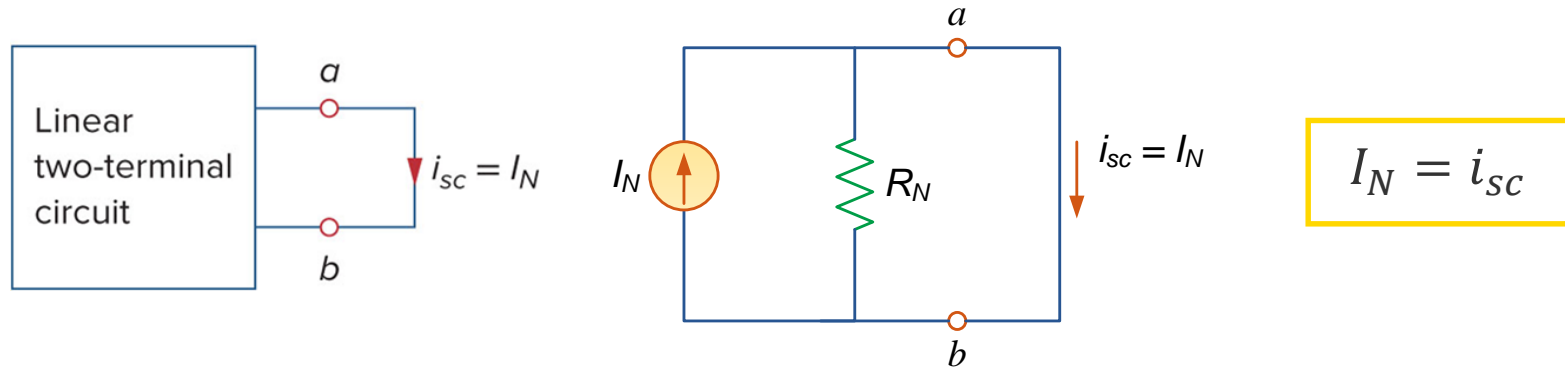
# Norton's theorem

- The current source's value, known as Norton current  $I_N$ , is equal to the short-circuit current at the terminals.




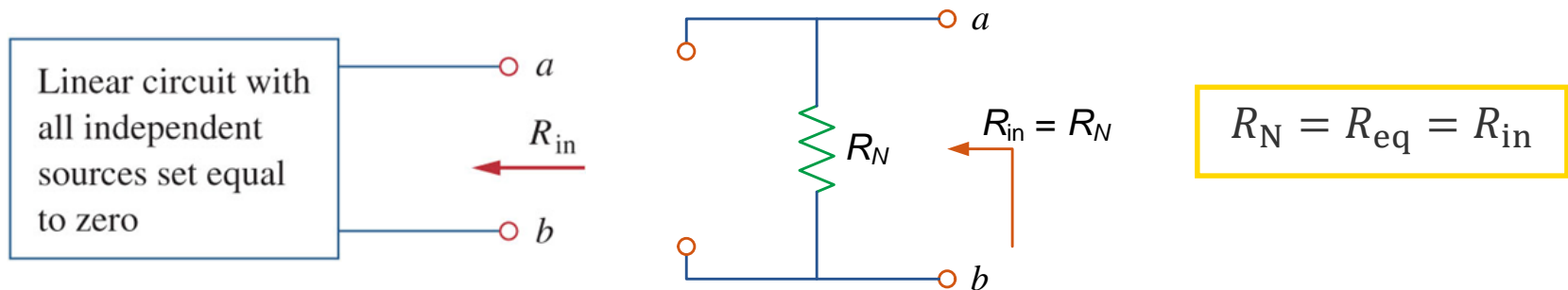- The **Norton resistance  $R_N$**  is **same** as the **Thevenin resistance  $R_{Th}$** , which is the **input resistance** measured at the terminals when **all independent sources are turned off**.



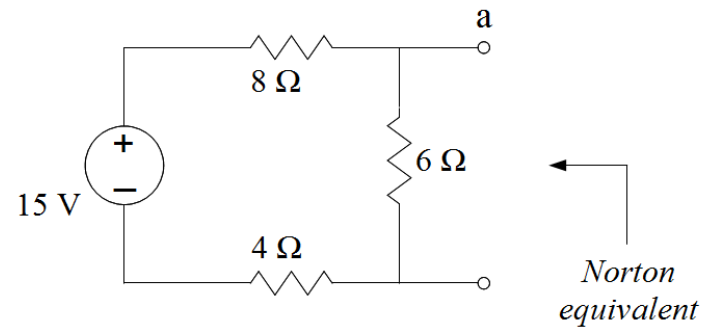
# Exercise

Calculate the Norton equivalent of the following circuit:




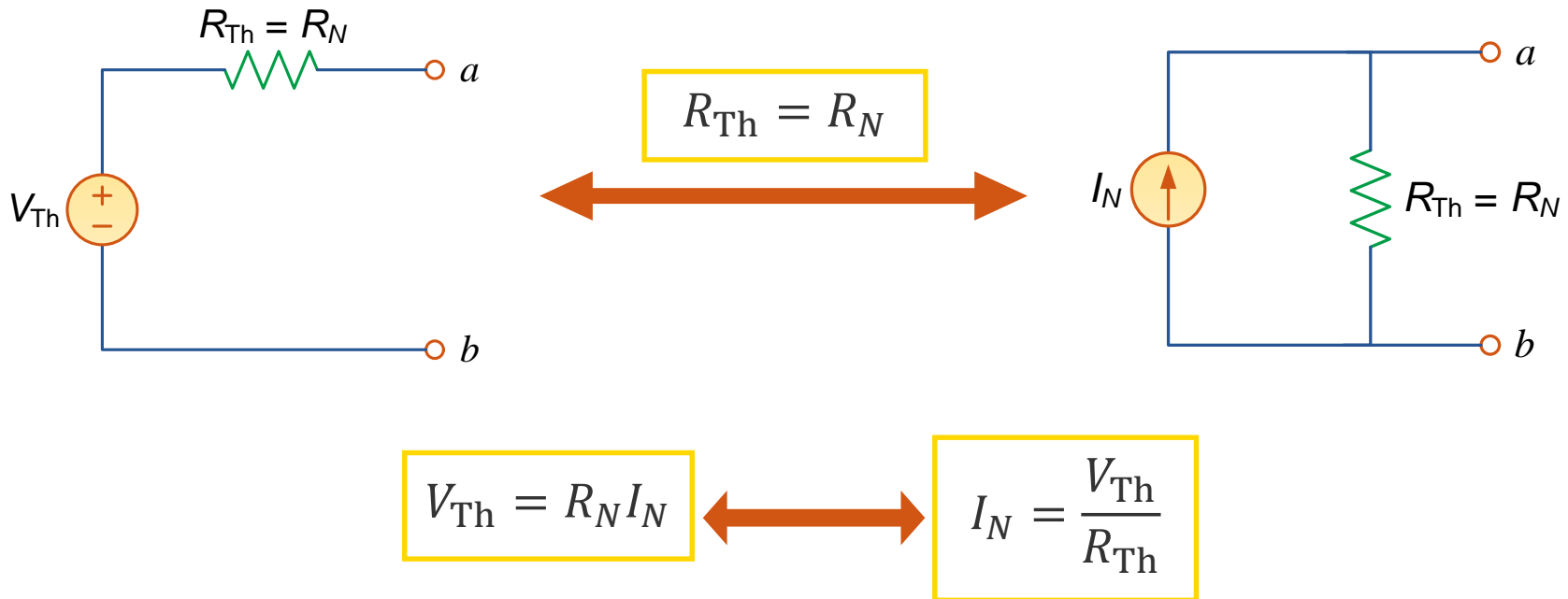
# Thevenin-Norton transformation

- Thevenin's and Norton's theorems are **related** to each other through **source transformation**.
- Thevenin and Norton resistances are **exactly the same** and equal to **input resistance** measured from the terminals of the circuit.


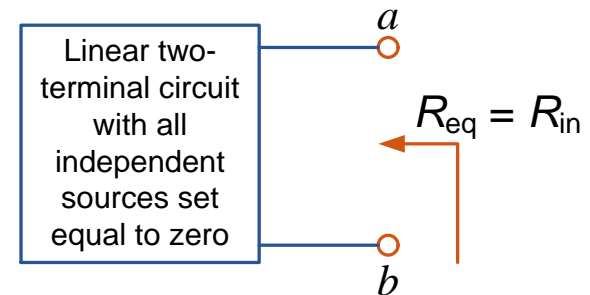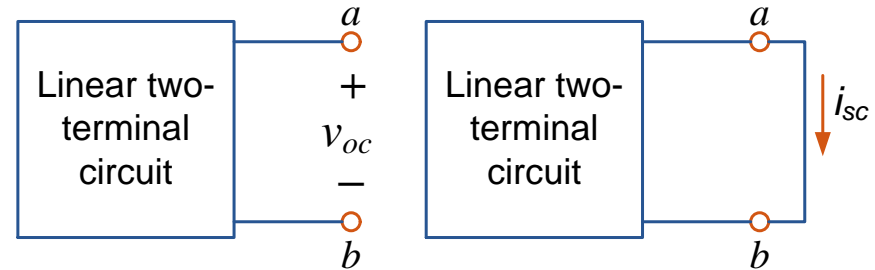
# Thevenin-Norton transformation


- **Dependent** sources in Norton equivalent circuit are handled in **the same way** as Thevenin equivalent circuit.
- Since  $V_{Th}$ ,  $I_N$  and  $R_{Th} = R_N$  are related based on source transformation, finding the Thevenin or Norton equivalent circuit requires **two** of the following:
  1. The **open-circuit voltage**  $v_{oc}$  across terminals  $a$  and  $b$ .
  2. The **short-circuit current**  $i_{sc}$  at terminals  $a$  and  $b$ .
  3. The **equivalent or input resistance**  $R_{eq} = R_{in}$  at terminals  $a$  and  $b$  when all **independent** sources are **turned off**.



$$\begin{aligned} V_{Th} &= v_{oc} \\ I_N &= i_{sc} \\ R_{Th} &= \frac{v_{oc}}{i_{sc}} = R_N \end{aligned}$$
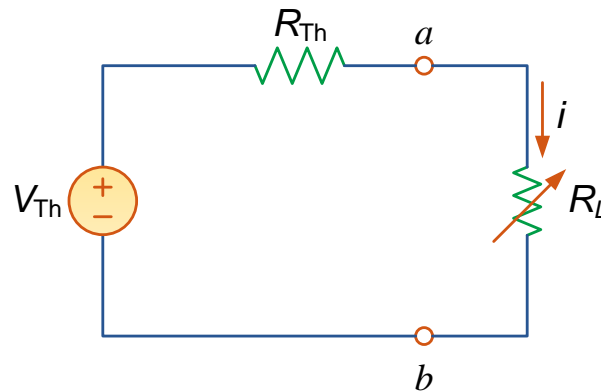
# Maximum power transfer

- In many practical applications, a circuit is designed to provide **maximum power** to a **load**.
- Unlike ideal sources, **internal resistance** of real sources **restricts** the amount of power that can be transferred to a load.
- The power consumption of that internal resistance is known as **power loss**.
- Using the **Thevenin equivalent circuit** we can find the **maximum power** that can be transferred to a load based on **fixed**  $V_{Th}$  and  $R_{Th}$  and **variable**  $R_L$ .



$$p(R_L) = R_L i^2 = R_L \left( \frac{V_{Th}}{R_{Th} + R_L} \right)^2$$



# Maximum power transfer

- To find for which value of  $R_L$  the power would be maximum, differentiate  $p$  with respect to  $R_L$  and set the result to zero.


$$\begin{aligned}\frac{dp}{dR_L} &= V_{Th}^2 \left[ \frac{(R_{Th} + R_L)^2 - 2R_L(R_{Th} + R_L)}{(R_{Th} + R_L)^4} \right] \\ &= V_{Th}^2 \left[ \frac{(R_{Th} + R_L - 2R_L)}{(R_{Th} + R_L)^3} \right] = 0 \quad \Rightarrow \quad (R_{Th} + R_L - 2R_L) = 0\end{aligned}$$

- Maximum power** is transferred to the load when the **load resistance  $R_L$**  is **equal** to the **Thevenin resistance  $R_{Th}$**  as seen from the load terminals

$R_L = R_{Th}$

➔

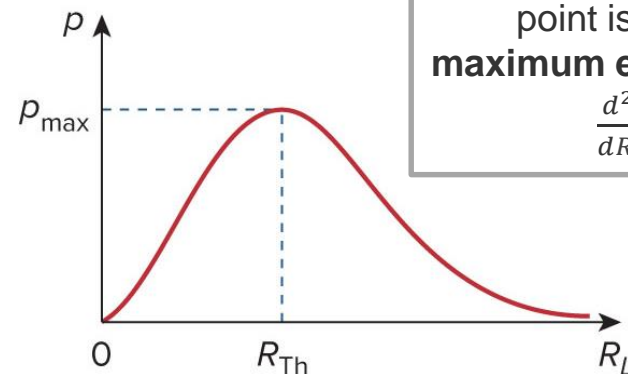
$p_{\max} = \frac{V_{Th}^2}{4R_{Th}}$   
 $v_L = \frac{V_{Th}}{2}$



It can be shown that this point is the global **maximum extremum** since  $\frac{d^2p}{dR_L^2} < 0$
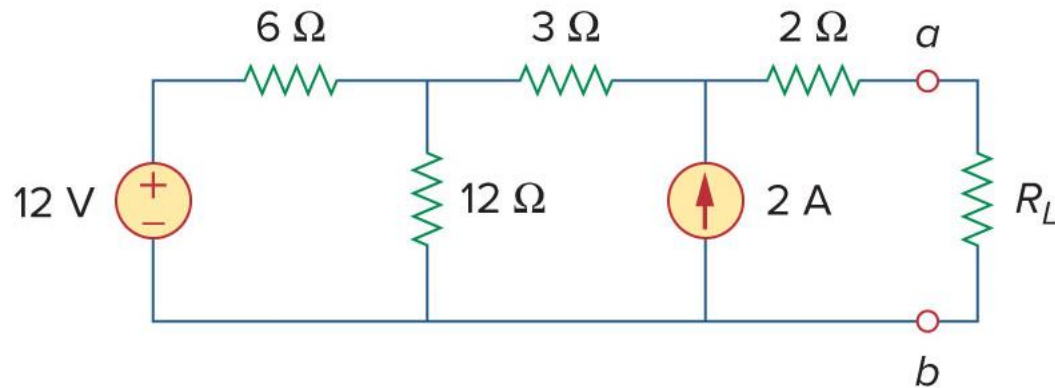
# Exercise

Find the value of load resistance  $R_L$  for maximum power transfer in the circuit below, and then find the maximum power  $p$ .





# Source Modeling – Voltage source

Thevenin and Norton equivalent circuits can be useful in modeling **realistic** voltage and current sources that deliver maximum power to a load.

- With a load connected to the voltage source, the terminal voltage drops in magnitude, which is known as **loading effect**.
- The internal resistance  $R_s$  of the voltage source  $v_s$  in series with the load  $R_L$  acts as **voltage divider**.

$$v_L = \frac{R_L}{R_s + R_L} v_s$$

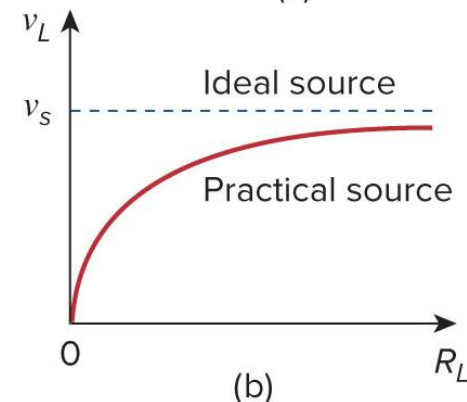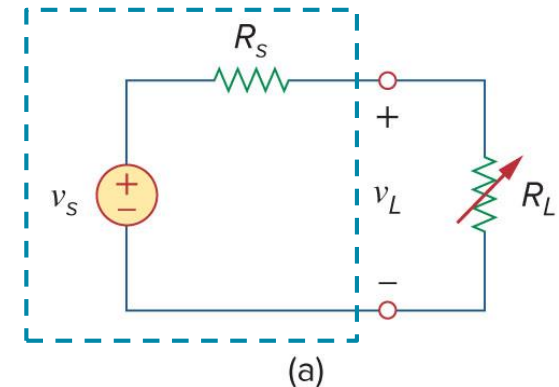- The load voltage will be constant if  $R_s$  is **zero** or **very small** compared to the load  $R_s \ll R_L$ .
- Without load,  $R_L \rightarrow \infty$ ,  $v_{oc} = v_s$  which is known as **unloaded voltage source**.





Note that  $v_{oc} = v_s = V_{Th}$ , Thevenin voltage, they are all equivalent.

# Source Modeling – Current source

- Similarly, with a load connected to the current source, the terminal current drops in magnitude, which is known as **loading effect**.
- The internal resistor  $R_p$  in parallel with the load  $R_L$  acts as **current divider**.

$$i_L = \frac{R_p}{R_p + R_L} i_s$$

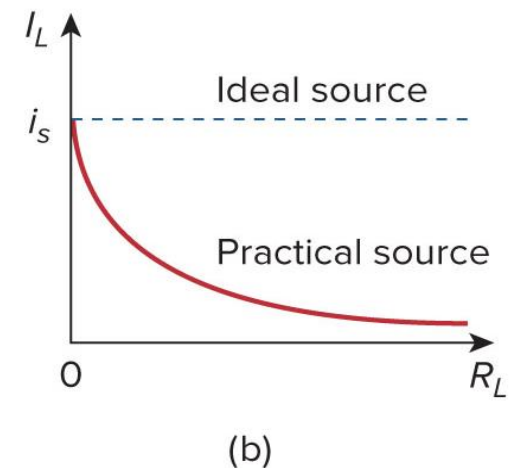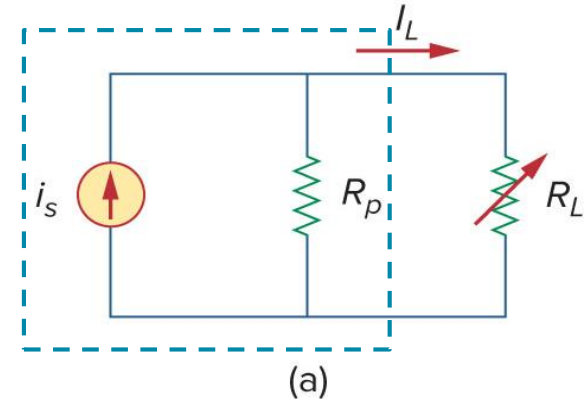- The load current will be constant if  $R_p$  is **infinite** or **very large** compared to the load  $R_p \gg R_L$ .
- Without load,  $R_L = 0$ ,  $i_{sc} = i_s$  which is known as **unloaded current source**.



Note that  $i_{sc} = i_s = I_N$ , Norton current, they are all equivalent.

# Source Modeling

- The following steps can be followed to determine the unloaded source voltage  $v_s$  and internal resistance  $R_s$  of **voltage source** model in **practice**:

1. Measure the open-circuit voltage (Fig. (a)).


$$v_s = v_{oc}$$

2. Connect a variable load  $R_L$  (Fig. (b)) and adjust its resistance until  $v_L = \frac{v_s}{2}$ .

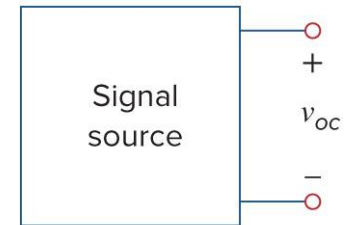
3. Disconnect  $R_L$  and measure its resistance as it should be **equal** to internal resistance  $R_s$  based on maximum power transfer principle.

$$v_L = \frac{v_s}{2} \Rightarrow R_s = R_L = R_{Th}$$

- Use source transformation to identify  $i_s$  and  $R_p$  for current source model.



(a)


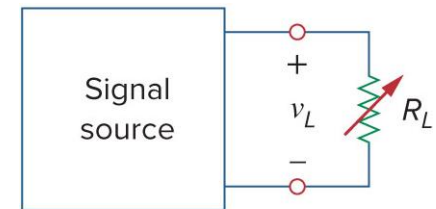


(b)

Note: In the laboratory, you will be doing a similar experiment but with constant load  $R_L$  to identify  $v_s$  and  $R_s$  and not necessarily following maximum power transfer principle.
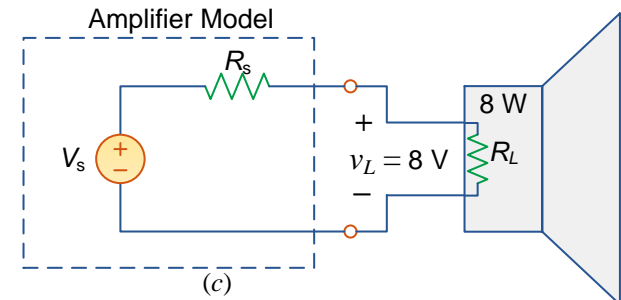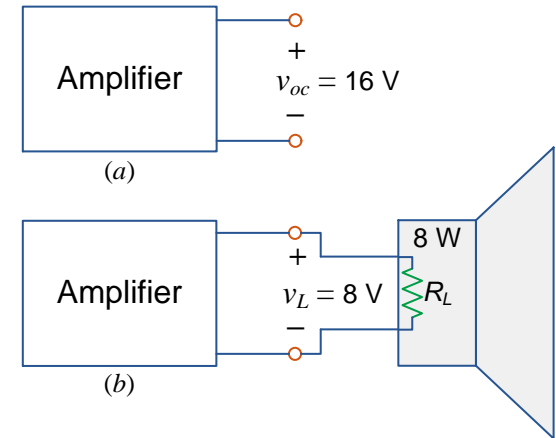
# Exercise

The open-circuit voltage across a certain amplifier is 16 V. The voltage drops to 8 V when an 8-W speaker is connected to the amplifier. Determine the internal resistance of the amplifier and calculate the load voltage when a 24-Ω speaker is used instead.



# Questions?

