

## Topic 5: Inductors and RL Circuits

1. For the circuits shown in Fig. 1 and 2,

- a) Find  $v_c$ ,  $i_L$ , and the energy stored in the capacitor and inductor in Fig. 1 under DC conditions.

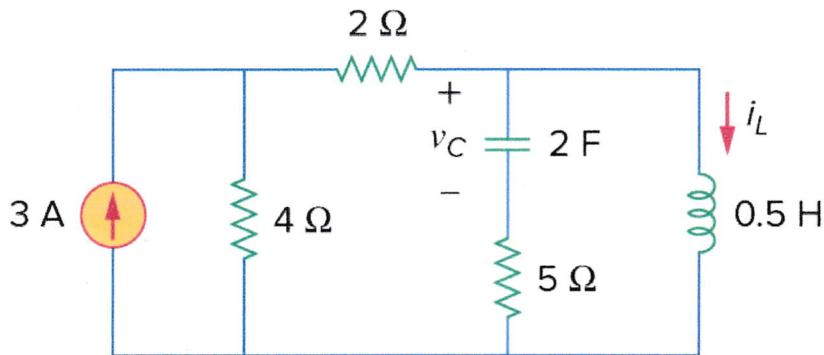


Fig. 1.

- b) Find  $v_c$ ,  $i_L$ ,  $i$ , and the energy stored in the capacitor and inductor in Fig. 2 under DC conditions.


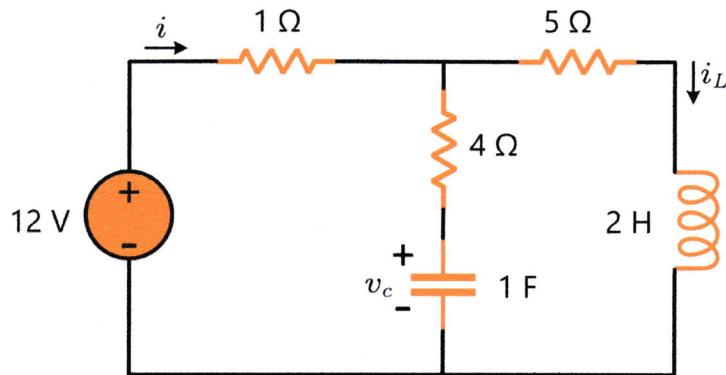


Fig. 2.

**Answer:**

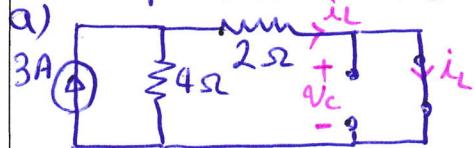- a)  $v_c = 0 \text{ V}$ ,  $i_L = 2 \text{ A}$ ,  $w_c = 0 \text{ J}$ , and  $w_L = 1 \text{ J}$   
 b)  $v_c = 10 \text{ V}$ ,  $i_L = i = 2 \text{ A}$ ,  $w_c = 50 \text{ J}$ , and  $w_L = 4 \text{ J}$

**Solution:** Draw the circuit in DC conditions by replacing the capacitor with open-circuit and the inductor with short circuit




Using Current Division

$$i_L = \frac{4}{4+2} \times 3 = 2 \text{ A}$$

$V_C = 0$  parallel with short circuit

$$W_L = \frac{1}{2} L i_L^2 = \frac{1}{2} \times 0.5 \times 4 = 1 \text{ J}$$
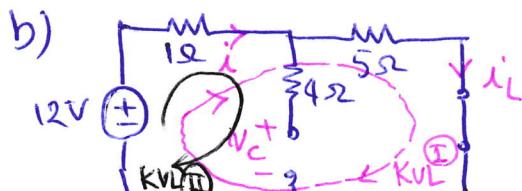
$$W_C = \frac{1}{2} C V_C^2 = 0 \text{ J}$$



No current is going through 4-Ω resistor.

$$\text{Thus } i = i_L = \frac{12}{1+5} = 2 \text{ A} \quad (\text{Simple KVL})$$


$$\text{KVL II: } -12 + i + V_C \rightarrow V_C = 10 \text{ V}$$

\*  $V_C$  is also the same as the voltage across 5-Ω resistor  $\rightarrow V_C = 5 \times i_L = 10 \text{ V}$

$$W_L = \frac{1}{2} L i_L^2 = \frac{1}{2} \times 2 \times 4 = 4 \text{ J}$$

$$W_C = \frac{1}{2} C V_C^2 = \frac{1}{2} \times 1 \times 100 = 50 \text{ J}$$

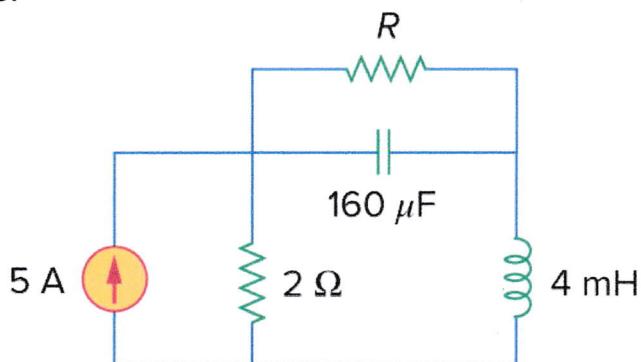
2. In the following circuit, Calculate the value of  $R$  that will make the energy stored in the capacitor the same as that stored in the inductor under steady-state conditions.



**Answer:**  $R = 5 \Omega$ ,

**Hint:** Find the capacitor and inductor energies in term of  $R$ .

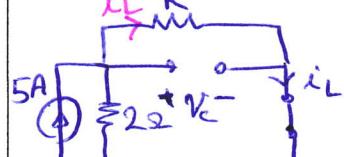**Solution:** Draw the circuit under Steady-State Conditions



Using current division  $\rightarrow i_L = \frac{2}{2+R} \times 5 = \frac{10}{2+R} \text{ A}$

$$W_L = \frac{1}{2} L i_L^2 = \frac{1}{2} \times 4 \times 10 \times \left( \frac{10}{2+R} \right)^2 \quad V_C = R i_L = \frac{10R}{2+R}$$

$$W_C = \frac{1}{2} C V_C^2 = \frac{1}{2} \times 160 \times 10^{-6} \times \frac{(10R)^2}{(2+R)^2}$$

$$= 80 \times 10^{-6} \times \frac{100R}{(2+R)^2}$$


$$W_L = W_C \rightarrow \frac{2 \times 10 \times 100}{(2+R)^2} = \frac{80 \times 10^{-6}}{(2+R)^2} \times 100R^2$$

$$\Rightarrow R^2 = \frac{1}{40 \times 10^{-3}} = \frac{100}{4} = 25$$

$$\Rightarrow R = \sqrt{25} \rightarrow R = 5 \Omega$$


only the positive value is acceptable.

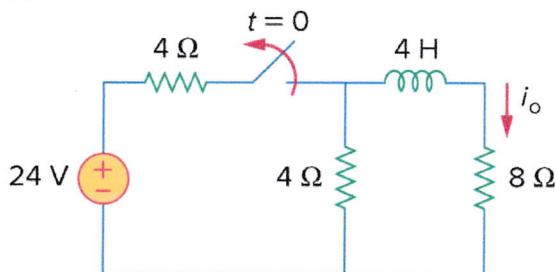3. The switch in the following circuit has been closed for a long time. At  $t = 0$ , the switch is opened. Calculate  $i_o(t)$  for all time (i.e., for both  $t < 0$  and  $t > 0$ ), and sketch the current  $i_o(t)$  as a function of time showing all critical points in the sketch.



**Answer:**  $i_o(t) = \begin{cases} 1.2 \text{ A} & t \leq 0 \\ 1.2e^{-3t} \text{ A} & t \geq 0 \end{cases}$

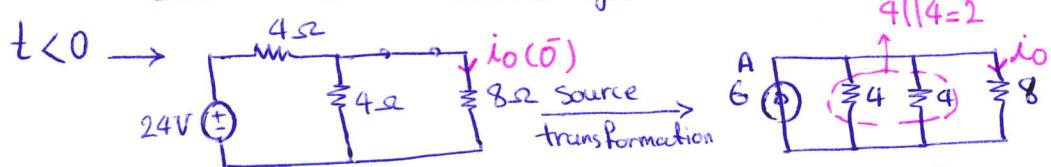
**Solution:** Draw the circuit before changes in the circuit.



Using Current division  $\rightarrow i_o = \frac{2}{2+8} \times 6 = 1.2 \text{ A}$   $\rightarrow i(\bar{0}) = 1.2 \text{ A} = i(0^+) = I_0$

After changes

$t > 0$  Switch is opened

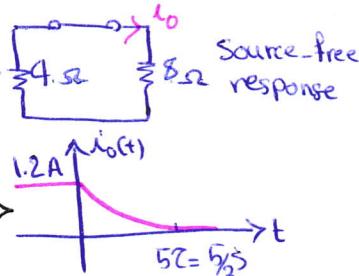

$\Rightarrow i_o(t) = \begin{cases} 1.2 \text{ A} & t \leq 0 \\ 1.2e^{-3t} \text{ A} & t > 0 \end{cases}$


Current of inductor cannot change suddenly.

$$i_o(t) = I_0 e^{-\frac{t}{T}}$$

$$T = \frac{L}{R_{Th}} = \frac{4}{12} = \frac{1}{3} \text{ s}$$

$$R_{Th} = 4 + 8 = 12 \Omega$$

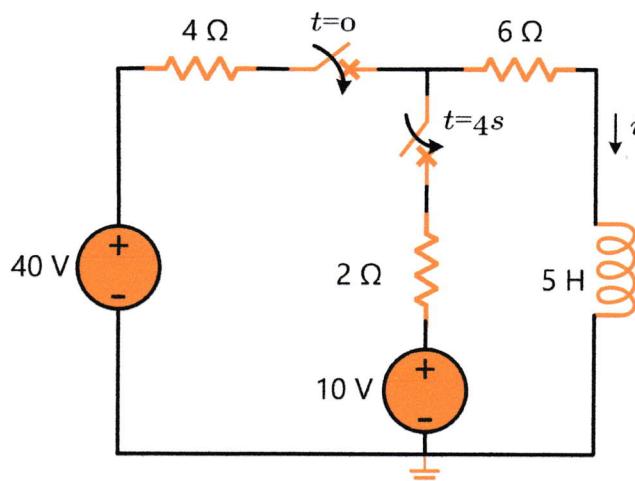4. In the following circuit, at  $t = 0$ , switch 1 is closed (next to 4-Ω resistor), and switch 2 is closed 4 seconds later. Find  $i(t)$  for all time (i.e., for both  $t < 0$  and  $t > 0$ ), and calculate  $i(t)$  at  $t = 2 \text{ s}$  and  $t = 5 \text{ s}$ . Sketch  $i(t)$  waveform showing all critical points in the sketch.






**Answer:**  $i_L(t) = 1e^{-50t}u(t)$  A,  $v(t) = -5e^{-50t}u(t)$  V

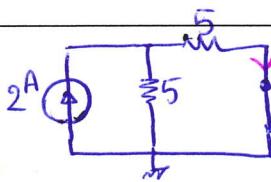**Solution:**

Before changes  $t < 0$   
 $S_1$ : closed,  $S_2$ : opened




$$i(\bar{0}) = i(0^+) = 1 \text{ A} = I_0$$

$$i_L = \frac{5}{5+5} \times 2 = 1 \text{ A}$$

After changes

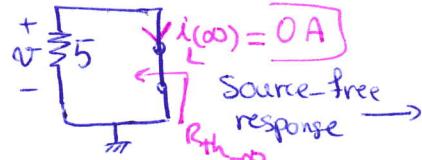$t > 0$   
 $S_1$ : open  
 $S_2$ : closed



$$\Rightarrow i(t) = I_0 e^{-\frac{t}{T}} \rightarrow T = L_{\text{Th}\infty} = \frac{100 \times 10^{-3}}{5} = 0.02 = \frac{1}{50} \text{ s}$$


Thus  $\Rightarrow v(t) = -5 \times i_L(t) = -5 e^{-50t} \quad t > 0$   
based on given polarity

$$\Rightarrow i(t) = 1 e^{-50t} \quad t > 0$$

$$= 1 e^{-50t} u(t)$$

You can use step function

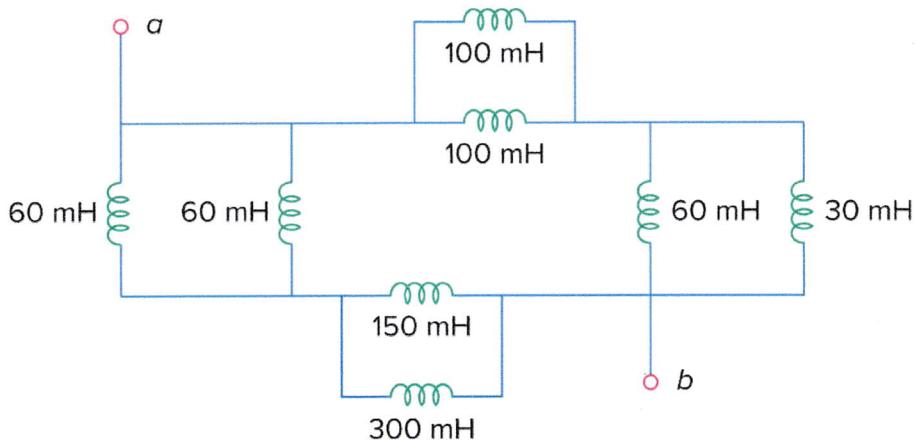
6. Find the equivalent inductance as seen from the terminals  $a-b$  in the circuit below.



**Answer:**  $L_{\text{eq}} = 45.5 \text{ mH}$

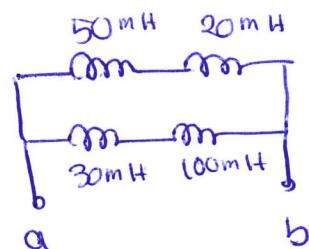
**Solution:**

$$\begin{aligned} & 100/(100) = 50 \text{ mH} \\ & 60/(160) = 30 \text{ mH} \\ & 150/(300) = 100 \text{ mH} \\ & 60/(130) = 20 \text{ mH} \end{aligned}$$



$$\Rightarrow L_{\text{eq}} = (50 + 20) \parallel (30 + 100) = \frac{70 \times 130}{70 + 130} = 45.5 \text{ mH}$$

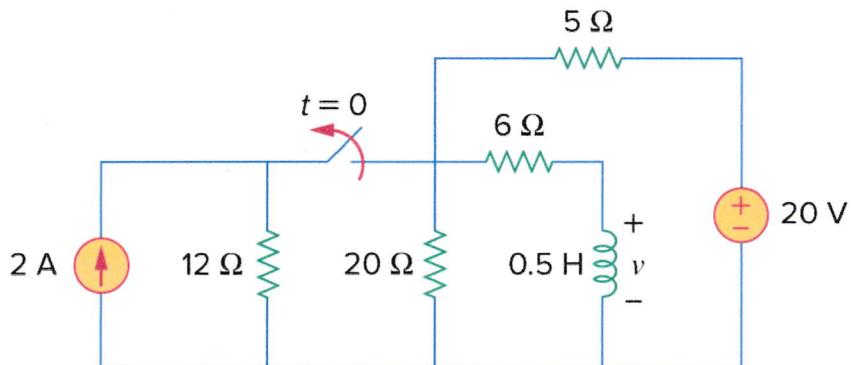7. Find the voltage across inductor  $v(t)$  for  $t > 0$ .




**Answer:**  $v(t) = -4e^{-20t}u(t)$  V

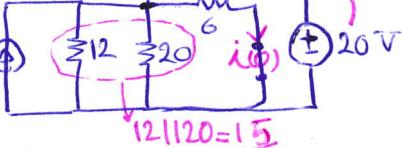
**Solution:**

Before changes  $t < 0$   
switch closed →  
use source transformation

current division  
 $\Rightarrow L = \frac{3}{3+6} \times 6 = 2 \text{ A} = i(0)$





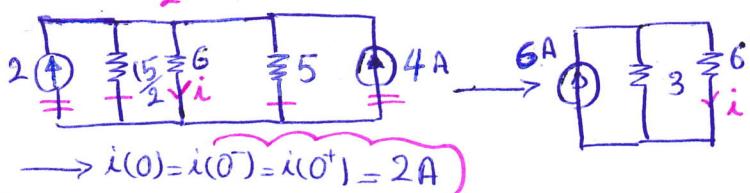
$V = L \frac{di}{dt}$  → So find the current through inductor first



After changes  $t > 0$



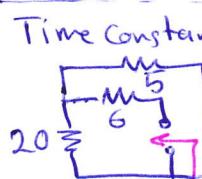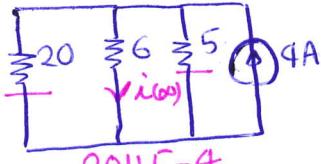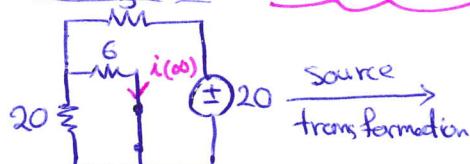Current division  
 $i(\infty) = \frac{4}{4+6} \times 4 = 1.6 \text{ A}$



$\Rightarrow i(t) = i(\infty) + (i(0) - i(\infty)) e^{-\frac{t}{T}}$


$= 1.6 + (2 - 1.6) e^{-\frac{t}{\frac{10}{20}}} = 1.6 + 0.4 e^{-20t} + 0$

Thus  $V = L \frac{di}{dt} = 0.5 \times 0.4 \times (-20) e^{-20t}$

$\Rightarrow V(t) = -4e^{-20t} + 0$

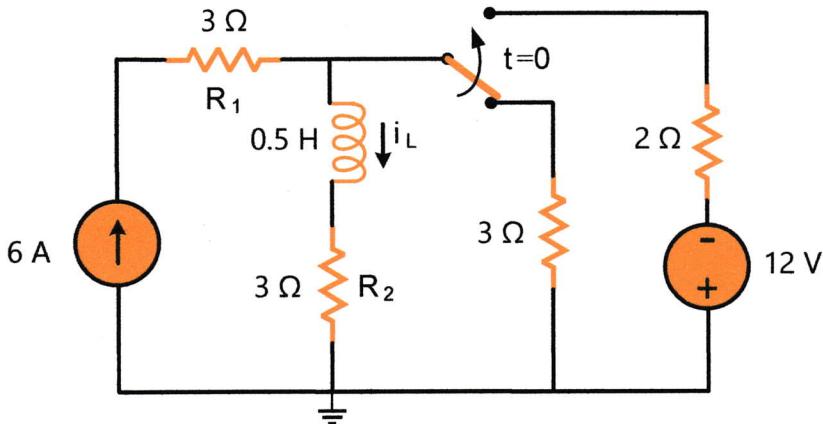8. (Final Exam – S1 2017) In the circuit below,

- Find the energy stored in the inductor under steady-state when the switch is in the open position (connected to 3-Ω resistor).
- If the switch has been in the open position for a long time and closes at  $t = 0$ , derive an analytical expression for the current  $i_L(t)$  through the inductor for  $t > 0$ .
- Plot the current through the inductor as a function of time.
- Derive an analytical expression for the voltages across resistors  $R_1$  and  $R_2$  ( $v_{R_1}$  and  $v_{R_2}$ ) as a function of time for  $t > 0$ .



**Answer:**


- $w_L(0) = 2.25 \text{ J}$
- $i_L(t) = 3e^{-10t}u(t) \text{ A}$
- $v_{R_1}(t) = 18 \text{ V}, v_{R_2}(t) = 9e^{-10t}u(t) \text{ V}$

**Solution:**

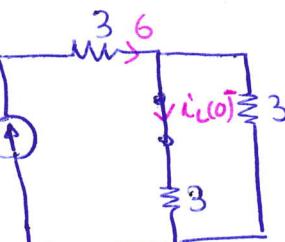a)  $W_L(0) = \frac{1}{2}L i_L^2(0) \rightarrow \text{Before changes}$

Current division  $\rightarrow i_L = \frac{3}{3+3} \times 6 = 3 \text{ A} = i_L^-(0) = i_L^+(0) = i_L(0)$

$$\Rightarrow W_L(0) = \frac{1}{2} \times 0.5 \times 3^2 = \frac{9}{4} = 2.25 \text{ J}$$



b)  $i_L^+(0) = 3 \text{ A}$  After changes  $i_L(t) = i_L(\infty) + (i_L(0) - i_L(\infty)) e^{-\frac{t}{T}}$   $T = \frac{L}{R_{\text{Th}\infty}}$

Nodal Analysis:  $6 = \frac{V}{3} + \frac{V}{2} + 6 \rightarrow V = 0 \text{ V} \Rightarrow i_L(\infty) = 0 \text{ A}$  Current sources cancel each other

$$R_{\text{Th}\infty} = \frac{3+2}{3+2} = \frac{5}{5} = 1 \Omega$$

$$R_{\text{Th}\infty} = 2+3=5 \Omega \rightarrow T = \frac{L}{R_{\text{Th}\infty}} = \frac{0.5}{5} = \frac{1}{10} \text{ s}$$

$$\Rightarrow i_L(t) = 0 + (3-0)e^{-\frac{t}{10}} = 3e^{-\frac{10t}{10}} = 3e^{-10t} \text{ A} \quad t > 0 \quad (\text{Source-free response})$$

c)  $v_{R_1} = 3 \times 6 = 18 \text{ V} \rightarrow \text{Constant current flowing through } 3 \Omega \text{ resistor}$

$$v_{R_2} = 3 \times i_L(t) = 9e^{-10t} \text{ V} \quad t > 0 \text{ or } 9e^{-10t} u(t)$$


Passive sign  $\downarrow i_L(t)$   
Convention  $\frac{+}{-}$

$f(t)$

Note that any function valid for only  $t > 0$

can be written as  $f(t)u(t)$  showing that it only exists after  $t > 0$   
where  $u(t)$  is unit step function.

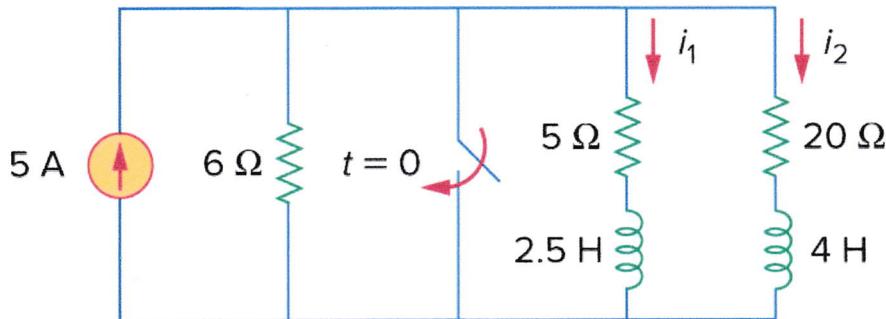9. Derive an expression for  $i_1(t)$  and  $i_2(t)$  for  $t > 0$ .




**Answer:**  $i_1(t) = 2.4e^{-2t}u(t)$  A,  $i_2(t) = 0.6e^{-5t}u(t)$  A

**Solution:**

Before changes

$t < 0$   
switch: opened

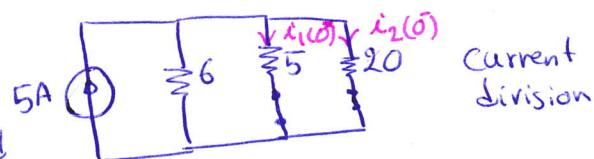

current division

for  $i_1 \rightarrow$  5A is divided between  $5\Omega$  and  $(20+6)\Omega$


$$i_1 = \frac{20+6}{5+20+6} \times 5 = \frac{26}{31} \times 5 = \frac{130}{31} = \frac{120}{25} = \frac{12}{5} = 2.4 \text{ A} = i_1(0)$$

for  $i_2 \rightarrow$  5A is divided between  $20\Omega$  and  $(5+6)\Omega$

$$i_2 = \frac{5+6}{20+5+6} \times 5 = \frac{11}{31} \times 5 = \frac{55}{31} = \frac{150}{250} = \frac{15}{25} = 0.6 \text{ A} = i_2(0)$$

After changes

$t > 0$  switch: closed

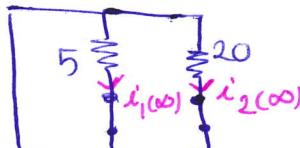

Source-free response

$$i_1(t) = i_1(0) e^{-\frac{t}{T_1}}$$

$$i_2(t) = i_2(0^+) e^{-\frac{t}{T_2}} \rightarrow i_1(0) = i_1(0^-) = 2.4 \text{ A}$$

$$T_1 = \frac{L_1}{R_{Th1}} \rightarrow \text{from } L_1 \text{ terminals}$$



Note that both inductors will discharge through their resistors and short circuit


$$i_1(\infty) = i_2(\infty) = 0$$

$$R_{Th1} = 5 \Omega \rightarrow T_1 = \frac{2.5}{5} = 0.5 \text{ s}$$

$$T_2 = \frac{L_2}{R_{Th2}} \rightarrow \text{from } L_2 \text{ terminals}$$

$$i_1(t) = 2.4e^{-2t} \quad t > 0$$

$$i_2(t) = 0.6e^{-5t} \quad t > 0$$

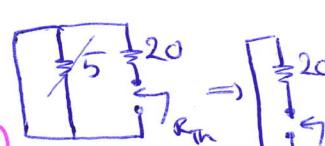

$$R_{Th2} = 20 \Omega \rightarrow T_2 = \frac{4}{20} = 0.2 \text{ s}$$

or write them with  $u(t)$