

Topic 10: Digital Logic Circuits

1. Convert the following unsigned binary numbers to decimal:
 1. 101
 2. 10111
 3. 1101
2. Convert the following decimal numbers to binary:
 1. 9
 2. 45
 3. 255
3. How many binary digits are required to allow a variable to range between 0 and 1000?
4. Write a Boolean expression for the following statement: “Z is TRUE if either A or B is FALSE, otherwise Z is FALSE”. Write a truth table for this expression.
5. Consider the functions $X(A,B,C)$ and $Y(A,B,C)$ specified in the truth table

A	B	C	$X(A, B, C)$	$Y(A, B, C)$
0	0	0	1	0
0	0	1	0	0
0	1	0	0	0
0	1	1	0	1
1	0	0	1	0
1	0	1	1	1
1	1	0	0	1
1	1	1	1	1

1. Write a logic expression corresponding to the functions $X(A,B,C)$ and $Y(A,B,C)$.
2. Implement $X(A,B,C)$ using logic gates.
3. Implement $Y(A,B,C)$ using logic gates.
4. Using DeMorgan's Theorem, implement $X(A,B,C)$ using only two-input NAND gates.

6. Complete the truth tables of the following logic equations:

1. Output = $A \cdot \bar{B}$

2. Output = $A \cdot \bar{B} \cdot C$

3. Output = $\bar{A} + B$

4. Output = $A \cdot \bar{B} + C$

7. Draw the logic diagrams which represent the function of these logic equations using NAND Gates only:

1. Output = $A \cdot \bar{B}$

2. Output = $A \cdot \bar{B} \cdot C$

3. Output = $\bar{A} + B$

4. Output = $A \cdot \bar{B} + C$

8. Draw the logic diagram which represent the function of this logic equation

$$X = A \cdot \bar{B} \cdot C + A \cdot B \cdot \bar{C}$$