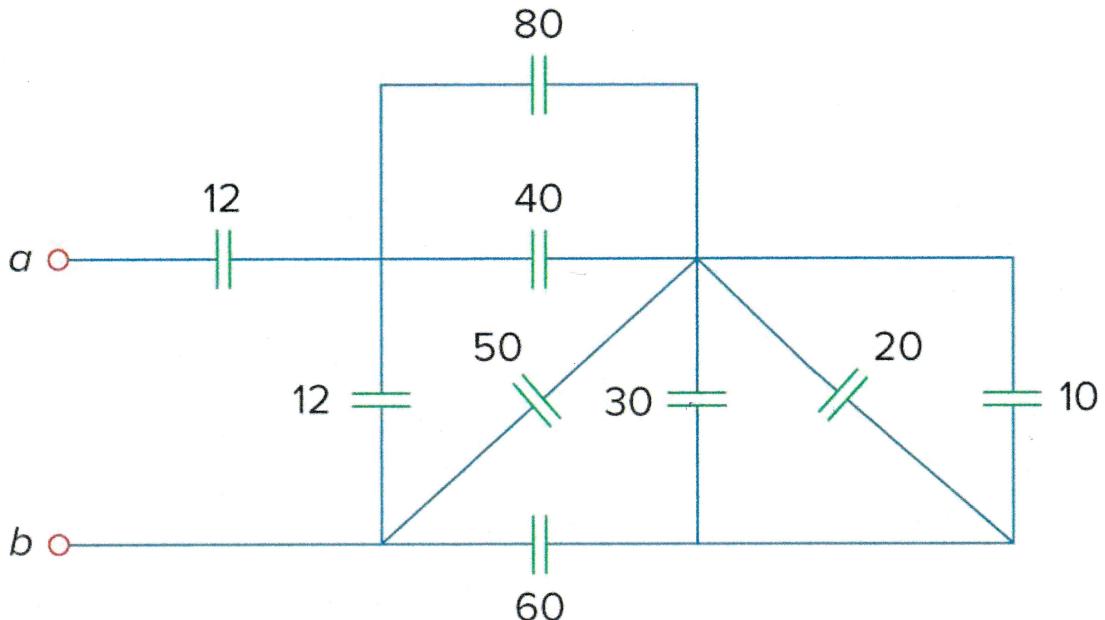


1. (Final Exam – S2, 2015) The circuit below shows a network of supercapacitors in a hybrid energy storage system where all capacitances are in μF

- Find the equivalent capacitance at terminals a-b.
- What is the energy stored if the voltage of terminals a-b is equal to 100 V.



Answer:

a) $C_{eq} = 10 \mu\text{F}$.

b) $w = 50 \text{ mJ}$

Hint: since nothing is mentioned about initial conditions, they are assumed to be zero.

Solution:

From right-hand-side: $10 \parallel 20 \parallel 30 \rightarrow 10 + 20 + 30 = 60 \mu\text{F}$

a) C_{eq}

Series combination of 12 and 20: $12 + 20 = 32 \mu\text{F}$

Parallel combination of 32 and 60: $\frac{32 \times 60}{32 + 60} = 19.2 \mu\text{F}$

Series combination of 19.2 and 50: $19.2 + 50 = 69.2 \mu\text{F}$

Parallel combination of 69.2 and 30: $\frac{69.2 \times 30}{69.2 + 30} = 48 \mu\text{F}$

Series combination of 12 and 48: $12 + 48 = 60 \mu\text{F}$


Parallel combination of 60 and 60: $\frac{60 \times 60}{60 + 60} = 30 \mu\text{F}$

$C_{eq} = \frac{12 \times 60}{72} = 10 \mu\text{F}$

b) $W(t) = \frac{1}{2} C V_c^2(t)$ $\xrightarrow[V=100 \text{ Constant}]{} W = \frac{1}{2} \times 10 \times 100^2 = 0.05 \text{ J or } 50 \text{ mJ}$

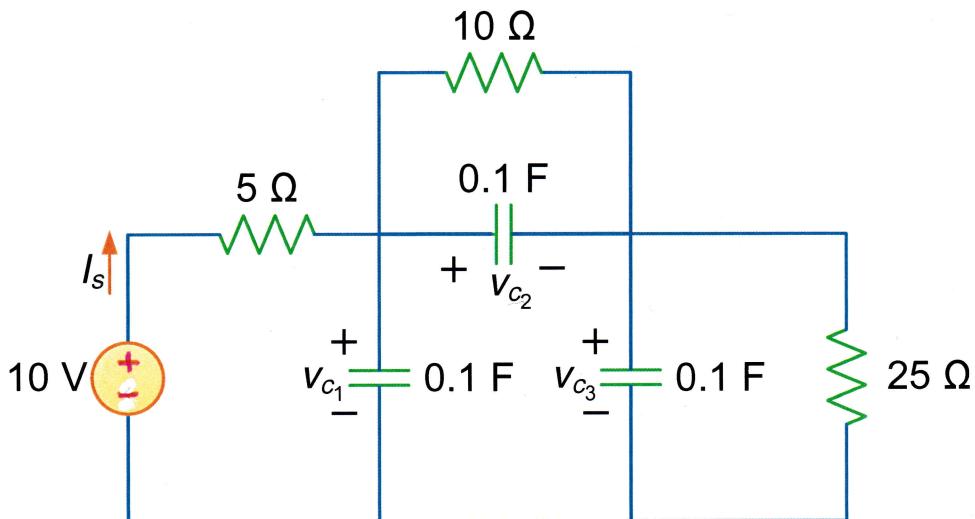2. (Final Exam – S2, 2015) For the circuit below,

- Determine the current I_s after the circuit has reached steady state.
- Determine the capacitor voltages V_{c_1} , V_{c_2} and V_{c_3} after the circuit has reached steady state.



Answer:

- $I_s = 0.25 \text{ A}$
- $V_{c_1} = 8.75 \text{ V}$, $V_{c_2} = 2.5 \text{ V}$, $V_{c_3} = 6.25 \text{ V}$

Hint: The steady state means that the capacitors are fully charged and under DC conditions.

Solution: Replace all capacitors with open circuit.

a)

$$KVL_1 \rightarrow I_s = \frac{10}{5+10+25} = \frac{10}{40} = 0.25 \text{ A}$$


b) V_{c_3} : It is parallel with $25\Omega \rightarrow V_{c_3} = 25 \times I_s = 6.25 \text{ V}$ (I)

V_{c_2} : It is parallel with $10\Omega \rightarrow V_{c_2} = 10 \times I_s = 2.5 \text{ V}$ (II)

V_{c_1} : Write KVL in m1 $\rightarrow -V_{c_1} + V_{c_2} + V_{c_3} = 0$ (I) (II) $V_{c_1} = 8.75 \text{ V}$

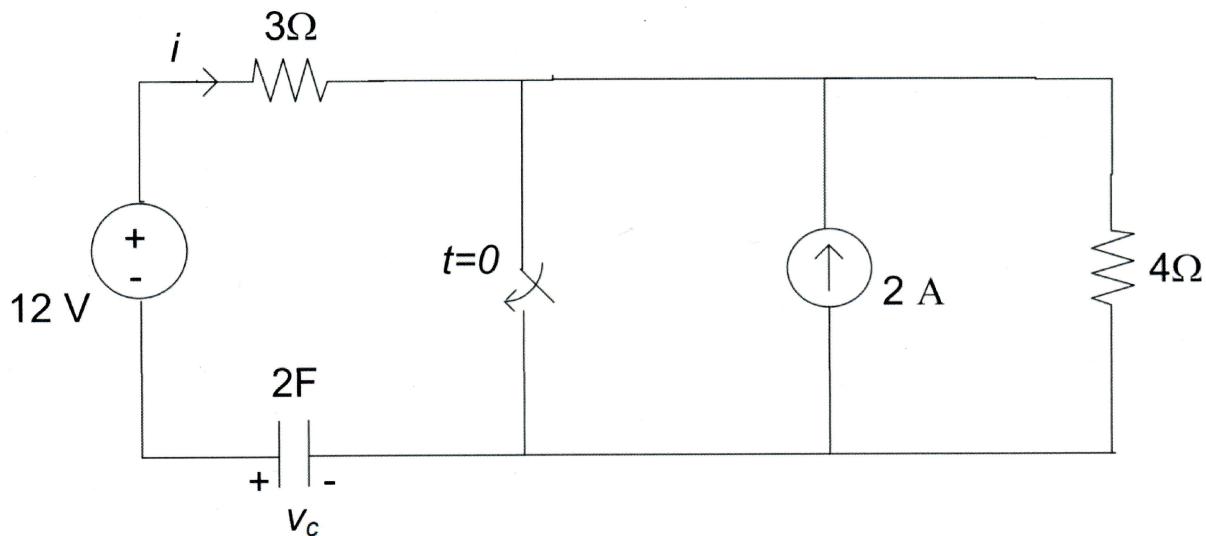3. (Final Exam – S2, 2015) For the circuit below, the switch has been in open position for a long time before changing position as shown at time $t = 0$.


- Find the voltage v_c and the current i when $t < 0$, i.e., $v_c(0^-)$ and $i(0^-)$.
- Find v_c and i when $t > 0$ and in steady state condition, i.e., $v_c(+\infty)$ and $i(+\infty)$.



Answer:

- $v_c(0^-) = -4 \text{ V}$ and $i(0^-) = 0 \text{ A}$
- $v_c(+\infty) = -12 \text{ V}$ and $i(+\infty) = 0 \text{ A}$

Solution:

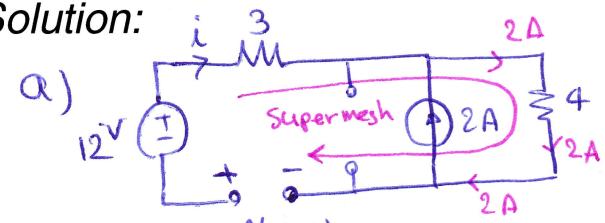

$t=0^-$ means just before zero when the switch is still open


$$i(t=0^-) = 0 \text{ open circuit}$$

$v_c(0^-)$: write KVL in δ Supermesh


$$-12 + 3 \times 0 + 4 \times 2 - v_c(0^-) = 0 \rightarrow v_c(0^-) = -4 \text{ V}$$

Note that 2A current source sends its current only through 4Ω resistor

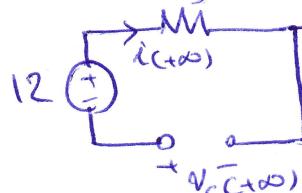b) $t > 0$ Switch is closed for a long time $t \rightarrow \infty$, thus capacitor is again fully charged with new voltage




short circuit bypasses the right side

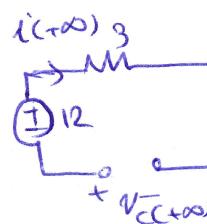

$i(+\infty) = 0$ again open circuit

$$v_c(+\infty) = -12 \text{ V}$$

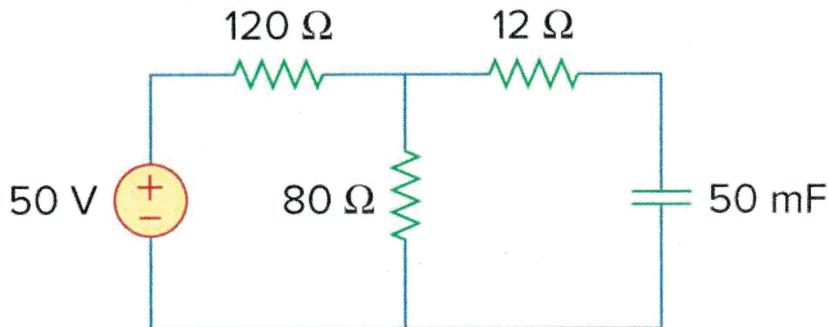4. Find the time constant for the RC circuit given below.



Answer: $\tau = 3 \text{ s}$


Solution: Time constant $\tau = R_{\text{Th}} \cdot C$ where R_{Th} is the equivalent / Thevenin resistance seen from Capacitor \rightarrow

$$R_{\text{Th}} = (120 \parallel 80) + 12 = 48 + 12 = 60 \Omega$$

$$\Rightarrow \tau = 60 \times 50 \times 10^{-3} = 3 \text{ s}$$

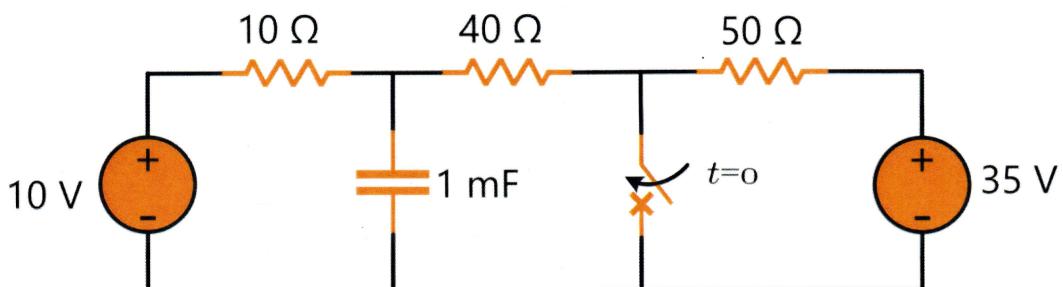5. (Mid-semester Exam - Summer 2017) In the circuit below, the switch has been in the open position for a long time before closing at time $t = 0$.

- Give an expression for the capacitor voltage $v_c(t)$ (i.e., as a function of time) for $t > 0$.
- Give an expression for the capacitor current $i_c(t)$ for $t > 0$
- Give an expression for the current of the $40\text{-}\Omega$ resistor $i_{R40}(t)$ for $t > 0$.



Answer:

$$\text{a) } v_c(t) = 8 + 4.5e^{\frac{-t}{8 \times 10^{-3}}} \text{ V}$$

$$\text{b) } i_c(t) = -\frac{4.5}{8} e^{\frac{-t}{8 \times 10^{-3}}} = -0.5625 e^{\frac{-t}{8 \times 10^{-3}}} \text{ A}$$

$$\text{c) } i_{R40}(t) = \frac{8}{40} + \frac{4.5}{40} e^{\frac{-t}{8 \times 10^{-3}}} = 0.2 + 0.1125 e^{\frac{-t}{8 \times 10^{-3}}} \text{ A}$$

Solution:


First find τ : $V_c(t) = V(\infty) + (V(0) - V(\infty)) e^{\frac{-t}{\tau}}$

$V(0)$: initial voltage $t < 0$
 $V(\infty)$: final voltage at $t \rightarrow \infty$

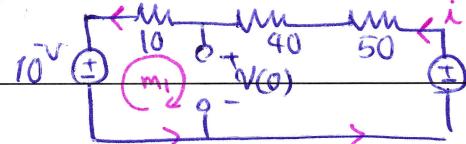a) $\tau = R_{\text{Th}} \cdot C \rightarrow R_{\text{Th}}$ after the switch
 $\rightarrow \tau = 8 \times 10^{-3} \text{ s}$ is closed

τ ; time constant

Then, find $V(0)$ when switch is open and capacitor is fully charged



$$\text{Find } i \text{ via KVL: } i = \frac{35-10}{10+40+50} = 0.25 \text{ A}$$


* Now find $V(0)$ via KVL in m_1 : $+V(0) + 10i - 10 = 0 \Rightarrow V(0) = 12.5 \text{ V}$

* Close the switch and find $V(\infty)$ as capacitor is now fully charged with new voltage

$$i = \frac{10}{10+40} = 0.2 \text{ A}$$

$$\text{KVL in } m_1: -10 + (0i + V(\infty)) = 0 \Rightarrow V(\infty) = 8 \text{ V}$$


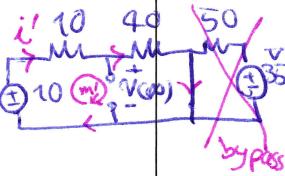
$$\Rightarrow V_C(t) = 8 + (12.5 - 8)e^{-\frac{t}{RC}} = 8 + 4.5e^{-\frac{t}{8 \times 10^3}} \text{ V}, t > 0$$



$$\text{b) } i_C = C \frac{dV_C}{dt} \rightarrow i_C = 10^{-3} \times -\frac{1}{8 \times 10^{-3}} \times 4.5e^{-\frac{t}{8 \times 10^{-3}}} = -\frac{4.5}{8} e^{-\frac{t}{8 \times 10^{-3}}} \text{ A}, t > 0$$

$$\text{c) After switch is closed: } i_{40}(+) \text{ is parallel with capacitor} \rightarrow i_{40} = \frac{V_C(t)}{40} = \frac{8}{40} + \frac{4.5}{40} e^{-\frac{t}{8 \times 10^{-3}}} \text{ V}, t > 0$$

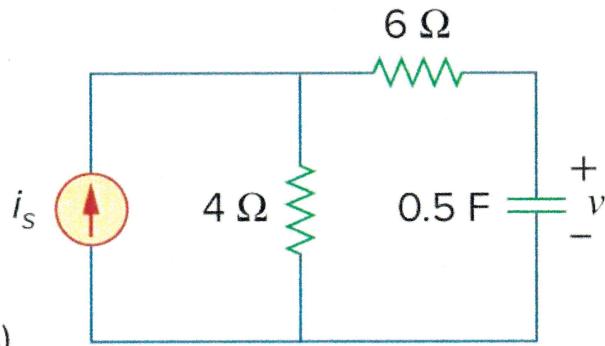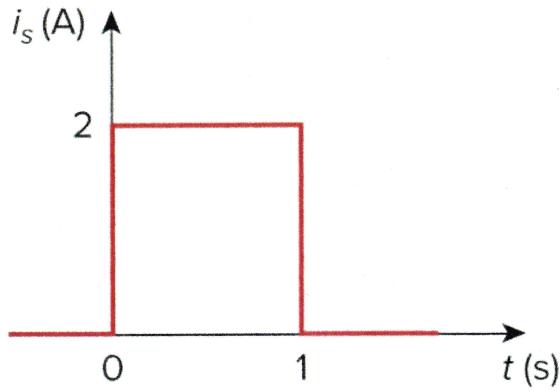6. If the waveform given in Fig. (a) is applied to the circuit of Fig. (b), find the expression for $v(t)$ assuming $v(0) = 0$.



(a)


(b)

$$\text{Answer: } v(t) = \begin{cases} 8\left(1 - e^{-\frac{t}{5}}\right) \text{ V}, & 0 < t < 1 \\ 1.4502e^{-\frac{(t-1)}{5}} \text{ V}, & t \geq 1 \end{cases}$$


Solution: $V(t) = V(\infty) + (V(0) - V(\infty))e^{-\frac{t}{RC}}$ Note that here we have a pulse

as input, which means that for $0 < t < 1$, $V(t)$ will change up to a voltage according to its time constant, initial voltage, and a final voltage value (if $i_s = 2$ was permanent). Then, it starts discharging its energy through resistors starting from initial voltage at $t=1$.

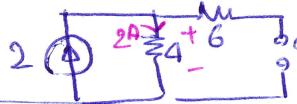for $0 < t < 1$: $V(0) = 0 \rightarrow V(\infty)$ assuming it would fully charge under $i_s = 2 \text{ A}$


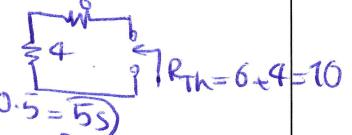
$$V(\infty) = V_4 = 2 \times 4 = 8 \text{ V}$$



$$\Rightarrow V(t) = 8(0 - 8)e^{-\frac{t}{5}} = 8(1 - e^{-\frac{t}{5}}) \text{ V}, 0 < t < 1$$

$$V(0) \triangleq V(1) = 8(1 - e^{-\frac{1}{5}}) = 1.4502 \text{ initial voltage after current switch to zero}$$


$$V(\infty) = 0 \text{ fully discharged}$$

$$\Rightarrow V(t) = 0 + (1.45 - 0)e^{-\frac{t-1}{5}} \text{ But this is only valid for } t > 1$$

$$\text{Thus: } V(t) = \begin{cases} 8(1 - e^{-\frac{t}{5}}) \text{ V} & 0 < t < 1 \\ 1.45e^{-\frac{(t-1)}{5}} \text{ V} & t > 1 \end{cases}$$

Apply time shift because $V(1) = 1.45$ from second function.

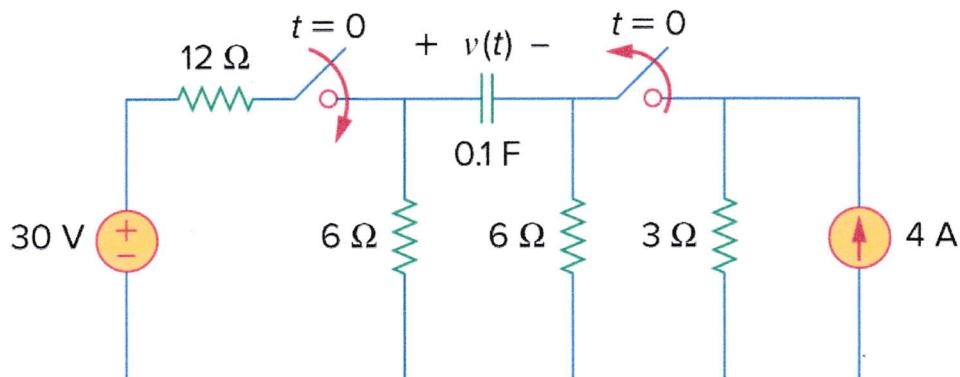7. In the circuit below, determine the response $v(t)$ for all time (i.e., for both $t < 0$ and $t > 0$), and sketch $v(t)$ waveform showing all critical points in the sketch.




$$\text{Answer: } v(t) = \begin{cases} -8 & t \leq 0 \\ 10 - 18e^{-t} & t \geq 0 \end{cases}$$

Solution:


Before changes $t < 0$

Switch on the left: opened

Switch on the right: closed

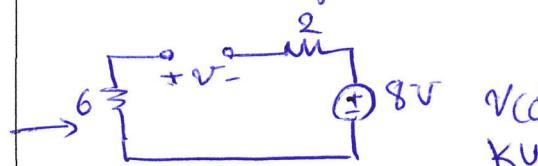

$$KVL \uparrow$$

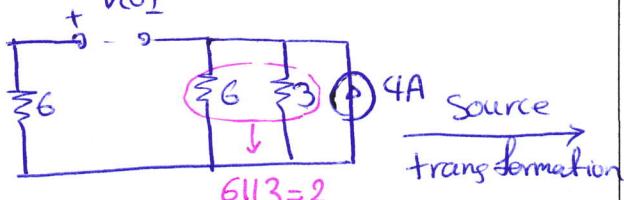


$$v(0+) = v(0-) = -8V$$


After the changes

$t > 0$ switch on the left: closed

switch on the right: opened

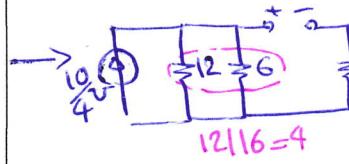


$$KVL \uparrow$$

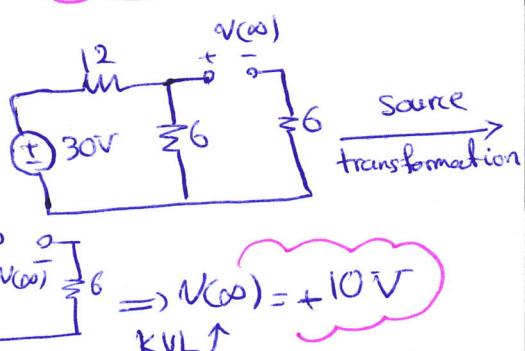

$$v(00) = +10V$$
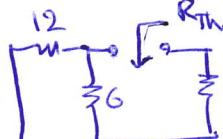
$$\text{Time Constant } \tau = R_{Th\infty} C$$



$$R_{Th\infty} = 6 + (6||12) = 6 + 4 = 10\Omega$$

$$\Rightarrow \tau = 10 \times 0.1 = 1s$$

$$\Rightarrow v(t) = v(00) + (v(0) - v(00)) e^{-\frac{t}{\tau}}$$

$$\text{for all time } v(t) = \begin{cases} -8V & t \leq 0 \\ 10 - 18e^{-t} & t > 0 \end{cases}$$

$$\text{or } v(t) = -8u(-t) + [10 - 18e^{-t}]u(t)$$

