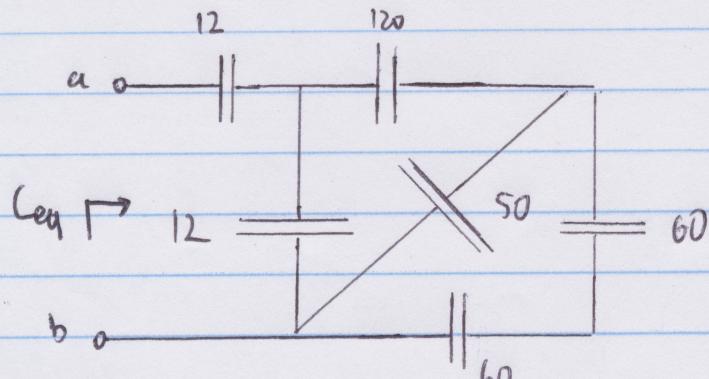


2015 Semester 2 Final Exam

Q.1 i) $80//40 = 120 \mu F$ Note: $// \Rightarrow$ Parallel
 $10//20//30 = 60 \mu F$ $+ \Rightarrow$ In Series



$$[(60+60)//50 + 12] // 12 + 12$$

$$(30//50 + 12) // 12 + 12$$


$$(80+120)//12 + 12$$

$$= 48//12 + 12$$

$$= 60 + 12$$

$$= 10 \mu F$$

ii) a)

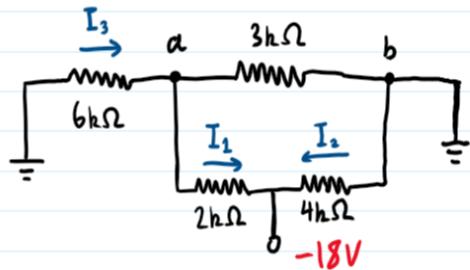

KCL at node 'a':

$$\frac{0-V_A}{6} + \frac{0-V_A}{3} = \frac{V_A - (-18)}{2}$$

$$-V_A - 2V_A = 3V_A + 54$$

$$-6V_A = 54$$

$$V_A = -9V$$

$$I_1 = \frac{V_A - (-18)}{2000} = \frac{-9 + 18}{2000} = 4.5 \text{ mA}$$

$$I_2 = \frac{0 - (-18)}{4000} = 4.5 \text{ mA}$$

$$I_3 = \frac{0 - V_A}{6000} = \frac{0 - (-9)}{6000} = 1.5 \text{ mA}$$

$$b) V_{ab} = V_a - V_b = -9V$$

c) Power dissipated

$$P_{6k\Omega} = I_3^2(6000) = 13.5 \text{ mW}$$

$$P_{2k\Omega} = I_1^2(2000) = 40.5 \text{ mW}$$

$$P_{4k\Omega} = I_2^2(4000) = 81 \text{ mW}$$

$$P_{3k\Omega} = \frac{V_{ab}^2}{3000} = 27 \text{ mW}$$

iii) KCL at node a:

$$\frac{V_a}{2} + \frac{V_a - V_b}{5} + 3 + 2 = 0$$

$$5V_a + 2V_a - 2V_b + 50 = 0$$

$$7V_a - 2V_b = -50 \quad \textcircled{1}$$

KCL at node b:

$$\frac{V_b - V_a}{5} + \frac{V_b}{4} = 2$$

$$4V_b - 4V_a + 5V_b = 40$$


$$9V_b - 4V_a = 40 \quad \textcircled{2}$$

$$\left(\begin{array}{cc|c} V_a & V_b \\ -4 & 9 & 40 \\ 7 & -2 & -50 \end{array} \right) \quad R_2 = 4R_2 + 7R_1$$

$$\left(\begin{array}{cc|c} -4 & 9 & 40 \\ 0 & 55 & 80 \end{array} \right) \quad \therefore V_b = \frac{80}{55} = \frac{16}{11} \text{ V}$$

$$V_a = \frac{40 - 9 \left(\frac{16}{11} \right)}{-4} = -\frac{74}{11} \text{ V}$$

Q.2 i)

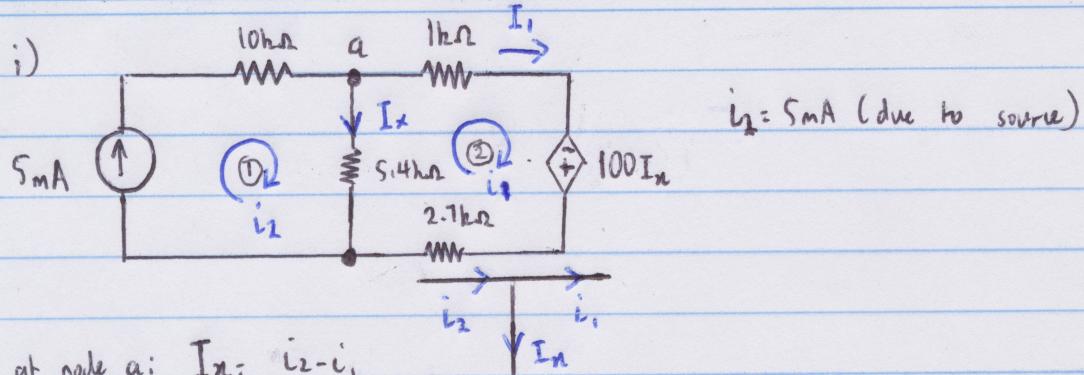

$$i_2 = 5mA \text{ (due to source)}$$


KCL at node a : $I_n = i_2 - i_1$

$$\text{KVL in mesh } ②: 3.7 \times 10^3 i_1 - 100(i_2 - i_1) + 5.4 \times 10^3(i_1 - i_2) = 0$$

$$9.2 \times 10^3 i_1 - 5.5 \times 10^3(5 \times 10^{-3}) = 0$$

$$i_1 = \frac{27.5}{9.2 \times 10^3} = \underline{\underline{11}} \text{ A} = 2.989 \text{ mA}$$

ii) Turning off $4A$:

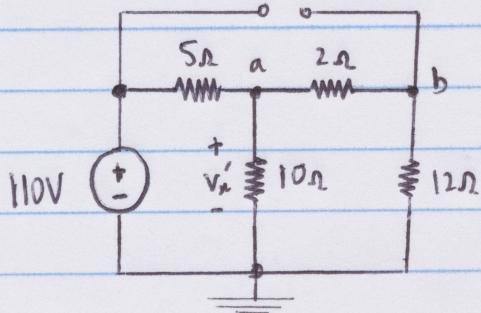

KCL at node a :

$$\frac{V_a - 110}{5} + \frac{V_a}{10} + \frac{V_a - V_b}{2} = 0$$

$$2V_a - 220 + V_a + 5V_a - 5V_b = 0$$

$$8V_a - 5V_b = 220 \quad ①$$

KCL at node b :

$$\frac{V_b - V_a}{2} + \frac{V_b}{12} = 0$$

$$-6V_a + 7V_b = 0 \quad ②$$


$$\left(\begin{array}{cc|c} V_a & V_b \\ -6 & 7 & 0 \\ 8 & -5 & 220 \end{array} \right) \quad R_2 = 3R_2 + 4R_1$$

$$\left(\begin{array}{cc|c} -6 & 7 & 0 \\ 0 & 13 & 660 \end{array} \right) \quad \therefore V_b = \frac{660}{13} \text{ V} = 50.77 \text{ V}$$

$$\therefore V_a = -7\left(\frac{660}{13}\right), \quad \frac{770}{13} \text{ V} = 59.23 \text{ V}$$

$$\therefore V_a' = V_a = \frac{770}{13} \text{ V}$$

Turning off 100V:

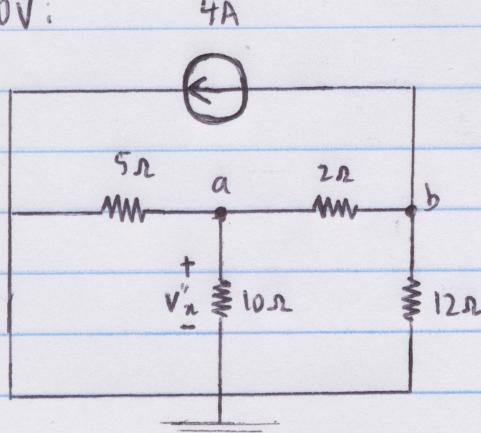

KCL at node a:

$$\frac{V_a}{5} + \frac{V_a}{10} + \frac{V_a - V_b}{2} = 0$$

$$8V_a - 5V_b = 0 \quad (1)$$

KCL at node b:

$$\frac{V_b - V_a}{2} + \frac{V_b}{12} + 4 = 0$$

$$-6V_a + 7V_b = -48 \quad (2)$$

$$\left(\begin{array}{cc|c} V_a & V_b \\ 8 & -5 & 0 \\ -6 & 7 & -48 \end{array} \right) \quad R_2 = 4R_2 + 3R_1$$

$$\left(\begin{array}{cc|c} 8 & -5 & 0 \\ 0 & 13 & -192 \end{array} \right) \quad \therefore V_b = \frac{-192}{13} \text{ V}$$


$$V_a = \frac{5}{8} \left(\frac{-192}{13} \right) = \frac{-120}{13} \text{ V}$$

$$\therefore V''_a = V_a = \frac{-120}{13} \text{ V}$$

By superposition:

$$V_n = V'_n + V''_n$$
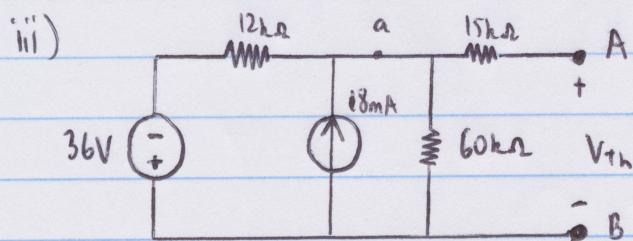
$$= \frac{770}{13} - \frac{120}{13} = 50 \text{ V}$$




KCL at node a:


$$\frac{V_a + 36}{12 \times 10^3} + \frac{V_a}{60 \times 10^3} = 18 \times 10^{-3}$$

$$6V_a + 180 = 1080$$
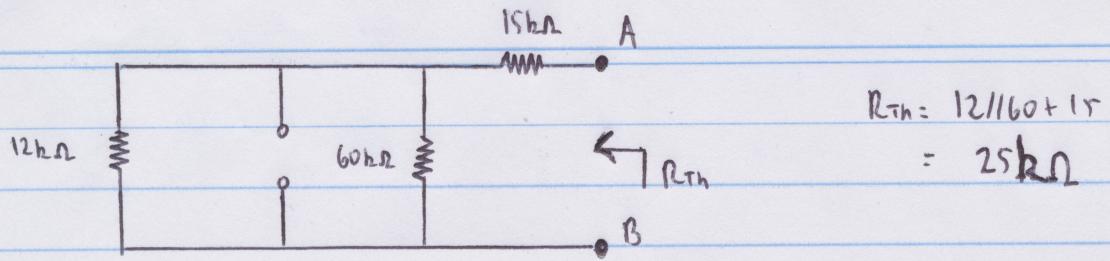
$$\therefore V_{Th} = V_a = 150 \text{ V}$$




Thevenin equivalent circuit

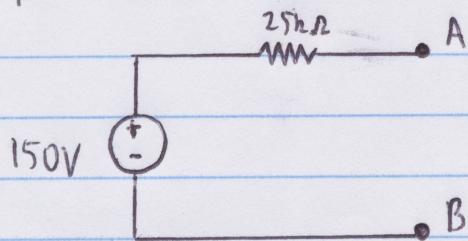

Q.3 i)

a) Under steady-state condition:

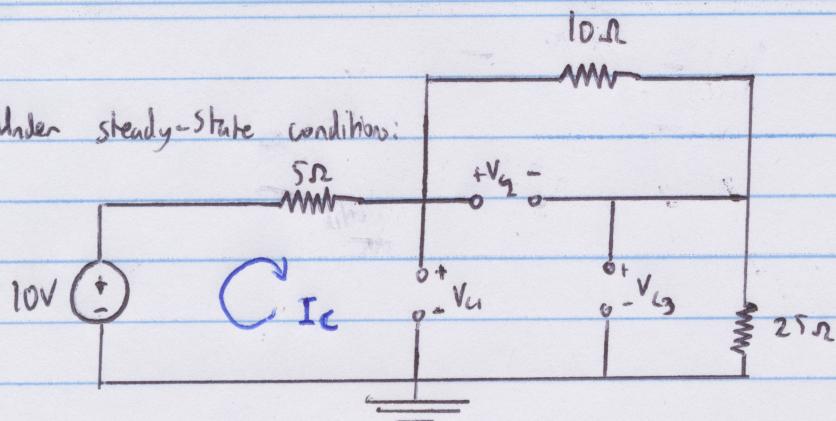

KVL in mesh:

$$-10 + (5 + 10 + 25) I_{LC} = 0$$

$$I_{LC} = 0.25 \text{ A}$$

b) Current across 5Ω :

$$\frac{10 - V_{L1}}{5} = 0.25$$

$$10 - V_{L1} = 1.25$$

$$\therefore V_{L1} = 8.75 \text{ V}$$

Current across 10Ω :

$$\frac{8.75 - V_{L3}}{10} = 0.25$$


$$8.75 - V_{L3} = 2.5$$

$$\therefore V_{L3} = 6.25 \text{ V}$$

$$V_{L2} = V_{L1} - V_{L3}$$

$$\approx 8.75 - 6.25 = 2.5 \text{ V}$$

ii) At $t=0^-$

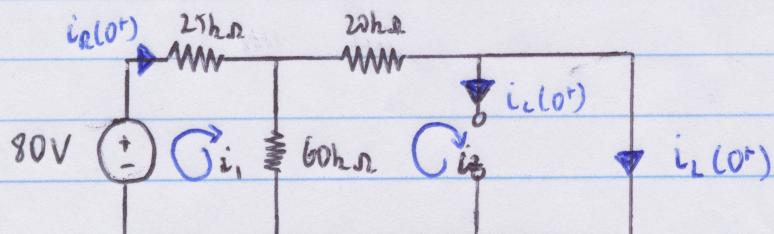

KVL in mesh ①:

$$0 = -80 + 25 \times 10^3 i_1 + 60 \times 10^3 (i_1 - i_2)$$

$$85 \times 10^3 i_1 - 60 \times 10^3 i_2 = 80 \quad ①$$

KVL in mesh ②:

$$0 = 20 \times 10^3 i_2 + 60 \times 10^3 (i_2 - i_1)$$

$$-60 \times 10^3 i_1 + 80 \times 10^3 i_2 = 0 \quad ②$$

$$\left(\begin{array}{cc|c} -60 & 80 & 0 \\ 85 & -60 & 80 \end{array} \right) \quad R_1 = R_1 \div 20 \Rightarrow \left(\begin{array}{cc|c} -3 & 4 & 0 \\ 17 & -12 & 16 \end{array} \right) \quad R_2 = R_2 \div 5$$

$$R_2 = 3R_1 + 17R_1$$


$$\left(\begin{array}{cc|c} -3 & 4 & 0 \\ 0 & 32 & 48 \end{array} \right) \quad \therefore i_2 = 1.5A \times 10^{-3} = 1.5mA$$

$$i_1 = \frac{-4 \times 1.5}{-3} = 2A \times 10^{-3} = 2mA$$

$$\therefore i_R(0^+) = 2mA$$

$$i_L(0^+) = 1.5mA$$

$$i_C(0^+) = 0A$$

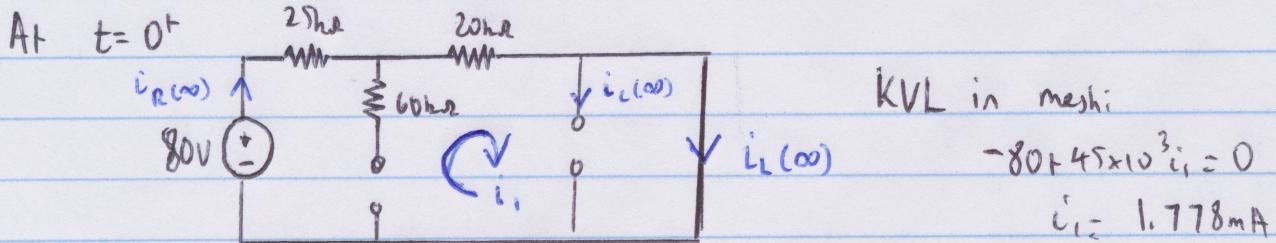


$$\therefore i_R(\infty) = 1.778mA$$

$$i_L(\infty) = 1.778mA$$


$$i_C(\infty) = 0A$$

iii) At $t = 0^-$

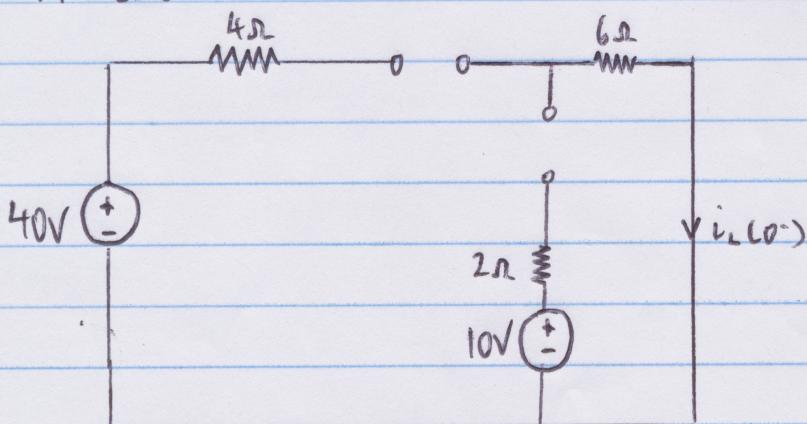

$i_L(0^-) = 0A$ due to no source connected

At $0 < t < 4$

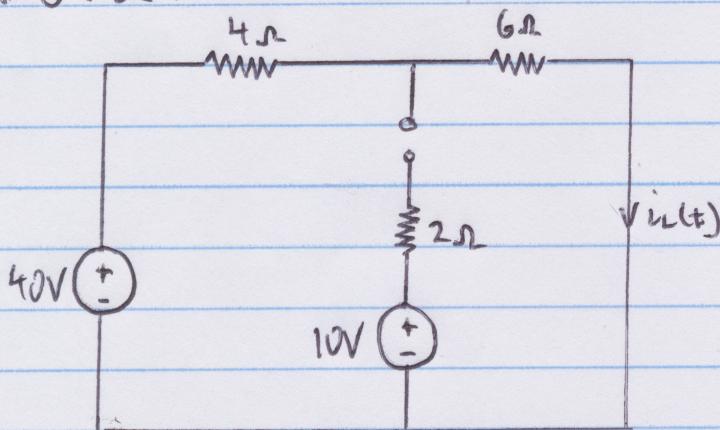

KVL:

$$10i_L(t) = 40$$


$$i_L(t) = 4A$$

$$R_{Th} = 4 + 6 = 10\Omega$$

$$T = \frac{L}{R_{Th}} = \frac{5}{10} = \frac{1}{2} s$$

$$\begin{aligned} \therefore i_L(t) &= 4 + (0 - 4)e^{-2t} A \\ &\approx 4(1 - e^{-2t}) A \quad \text{for } 0 < t < 4 \end{aligned}$$

At $t > 4$

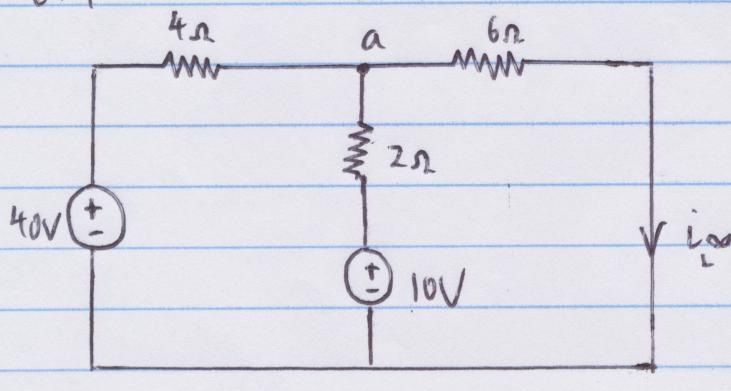

KCL at node 'a':

$$\frac{Va - 40}{4} + \frac{Va - 10}{2} + \frac{Va}{6} = 0$$

$$11Va - 180 = 0$$

$$Va = \frac{180}{11} = 16.364 V$$

Current across 6Ω

$$\frac{Va}{6} = i_{L\infty}$$

$$\therefore i_{L\infty} = \frac{30}{11} A$$

and $i_{L0} = 4(1 - e^{-8})$ at $t = 4s$

$$R_{Th} = 4/12 + 6 = \frac{22}{3} \Omega$$

$$T = \frac{L}{R_{Th}} = \frac{5}{\frac{22}{3}} s$$

$$\therefore i_L(t) = \frac{30}{11} + \left(4 - 4e^{-\frac{8}{11}} - \frac{30}{11}\right) e^{-\frac{22}{15}t} \Rightarrow = \frac{30}{11} + \left(\frac{14}{11} - 4e^{-\frac{8}{11}}\right) e^{-\frac{22}{15}t}, t > 4$$


$$Q.4 \text{ i) } Z_{eq}(\frac{1}{12}F) = -\frac{j}{4(\frac{1}{12})} = -j3\Omega$$

$$Z_{eq}(2H) = j(4)(2) = j8\Omega$$

Sources:

$$16\sin 4t \Rightarrow 16\cos(4t - 90^\circ)V = 16\angle -90^\circ V$$
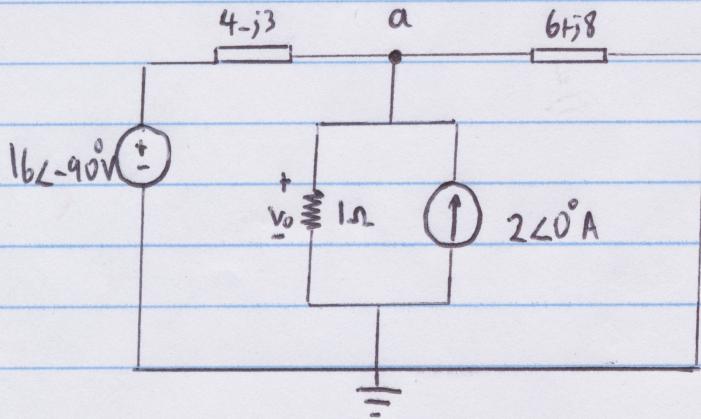
$$2\cos 4t \Rightarrow 2\angle 0^\circ A$$



KCL at node 'a':

$$\frac{V_0 - 16\angle -90^\circ}{4-j3} + \frac{V_0}{1} + \frac{V_0}{6+j8} = 2$$

$$V_0 \left(\frac{1}{4-j3} + 1 + \frac{1}{6+j8} \right) = 2 + \frac{16\angle -90^\circ}{4-j3}$$

$$\therefore V_0 = 3.836 \cos(4t - 35^\circ) V$$

$$\text{i') } Z_{eq}(10mH) = j(10 \times 10^{-3})(100) = j1\Omega$$

$$Z_{eq}(20 \times 10^{-6}F) = -\frac{j}{20 \times 10^{-6} \times 100} = -j500\Omega$$

For the circuit:

$$\begin{aligned} Z_{eq} &= (40\angle 0^\circ) \parallel 60 \parallel 30 - j500 \\ &= \left(\frac{1}{40\angle 0^\circ} + \frac{1}{60} + \frac{1}{30} \right)^{-1} - j500 = 500 \angle -88.5^\circ \Omega \end{aligned}$$

$$Y_{in} = \frac{1}{Z_{eq}} = 2 \angle 88.5^\circ \text{ ms}$$

Z_{in}


$$\text{i'')} \quad i_1 = 100 \sin(50t + 10^\circ) = 100 \cos(50t + 10^\circ) = 100\angle 10^\circ A$$

$$i_T = 50 \sin(50t - 40^\circ) = 50 \cos(50t - 130^\circ) = 50\angle -130^\circ A$$


KLL:

$$i_T = i_1 + i_2$$
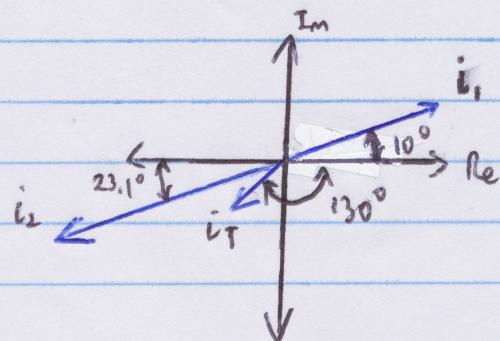
$$\begin{aligned} i_2 &= 50\angle -130^\circ - 100\angle 10^\circ \\ &= -141.99\angle -156.9^\circ \end{aligned}$$



Q.5.i)

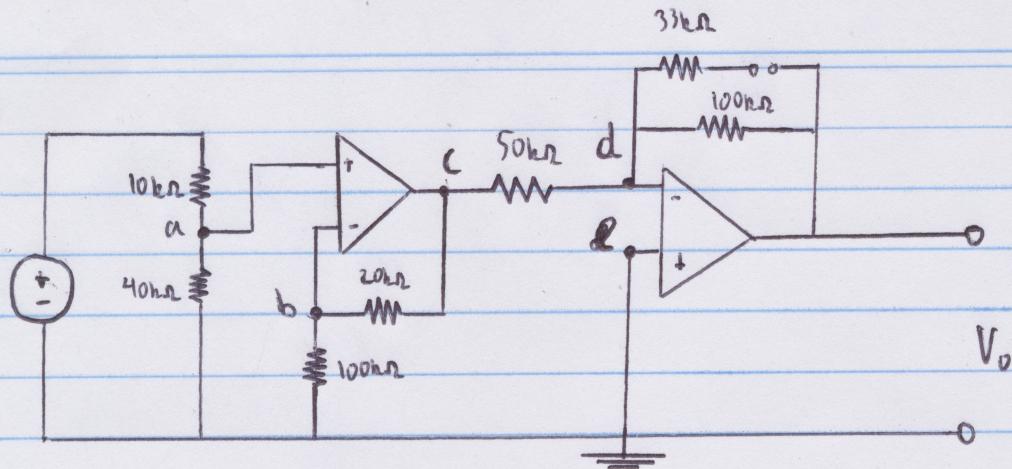

KCL at node a_i :

$$\frac{V_a - 10}{10,000} + \frac{V_a}{40,000} = 0$$

$$5V_a = 40$$

$$V_a = 8V = V_b \text{ (Op amp principle)}$$

KCL at node b_i :

$$\frac{8}{100,000} + \frac{8 - V_c}{20,000} = 0$$

$$8 + 40 - 5V_c = 0$$

$$V_c = 9.6V$$


$$V_e = V_d = 0V$$

KCL at node d_i :

$$\frac{0 - 9.6}{50,000} + \frac{0 - V_o}{100,000} = 0$$

$$2V_o = V_o = -19.2V$$

ii)

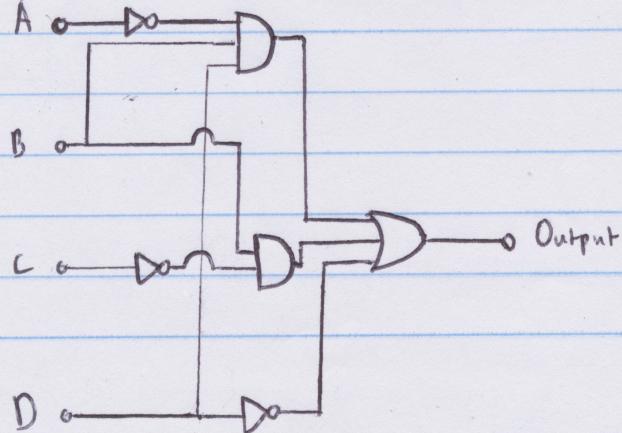

iii)	A	B	C	\bar{A}	\bar{B}	\bar{C}	$\bar{A} + \bar{B}$	$\bar{B} + \bar{C}$	Output
	0	0	0	1	1	1	1	1	0
	0	0	1	1	1	0	1	0	1
	0	1	0	1	0	1	1	1	0
	0	1	1	1	0	0	1	1	0
	1	0	0	0	1	1	1	1	0
	1	0	1	0	1	0	1	0	1
	1	1	0	0	0	1	0	1	1
	1	1	1	0	0	0	0	1	1