

Family Name .....

Given Name .....

Student No. ....

Signature .....

**THE UNIVERSITY OF NEW SOUTH WALES**  
**School of Electrical Engineering & Telecommunications**  
**MID-SESSION EXAMINATION**

**S1 2016**

**ELEC1111**  
**Electrical Circuits**

<b>TIME ALLOWED:</b>	<b>55 minutes</b>
<b>TOTAL MARKS:</b>	<b>40</b>
<b>TOTAL NUMBER OF QUESTIONS:</b>	<b>5</b>

**THIS EXAM CONTRIBUTES 20% TO THE TOTAL COURSE ASSESSMENT**

Reading Time: 5 minutes.

This paper contains 3 pages.

Candidates must **ATTEMPT ALL** questions.

Answer all questions in the answer booklet provided.

Marks for each question are indicated beside the question.

This paper **MAY** be retained by the candidate.

Print your name, student ID and question number on the front page of each answer book.

Authorised examination materials:

Candidates should use their own UNSW-approved electronic calculators.

This is a closed book examination.

Assumptions made in answering the questions should be stated explicitly.

All answers must be written in ink. Except where they are expressly required, pencils **may only be used** for drawing, sketching or graphical work.

### QUESTION 1 [4 marks]

For the circuit in Figure 1 below, calculate the equivalent resistance  $R_{eq}$  of the network as seen from the terminals shown.

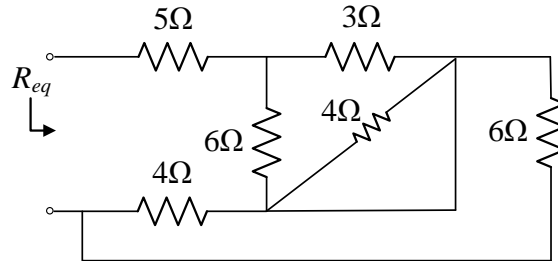


Figure 1

### QUESTION 2 [8 marks]

For the circuit below in Figure 2, apply nodal analysis, and write down the node voltage equations using the labels shown in Fig. 2. Note: You should NOT solve them.

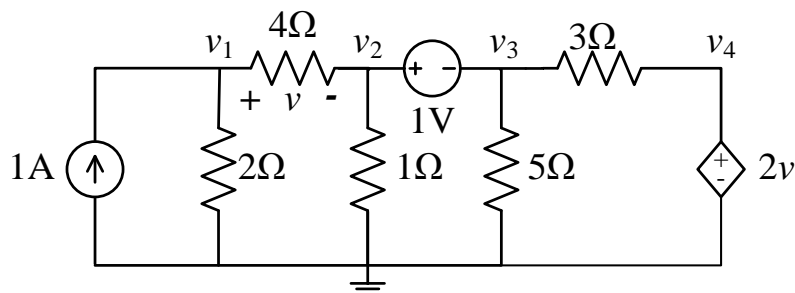


Figure 2

### QUESTION 3 [8 marks]

For the circuit shown below in Figure 3, use mesh analysis to write down mesh equations and solve for the mesh currents labelled  $i_1$ ,  $i_2$ , and  $i_3$ .

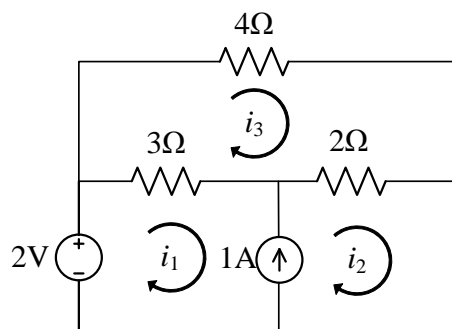


Figure 3

### QUESTION 4 [12 marks]

- (a) (6 marks) For the circuit below in Figure 4, showing sketches in your working, use the superposition principle to determine the current  $i$  that flows in the  $20\ \Omega$  resistor.
- (b) (6 marks) Using source transformation, find the Norton equivalent of the circuit to the left of the terminal pair A-B in Figure 4.

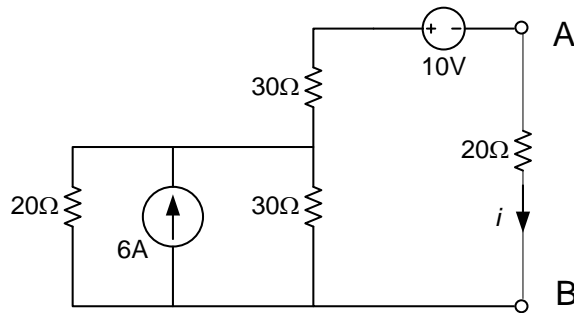


Figure 4

### QUESTION 5 [8 marks]

For the circuit below in Figure 5, the switch has been in the same position for a long time before changing position as shown at time  $t = 0$ .

- (a) (4 marks) Calculate the capacitor voltage  $v_C(t)$
- immediately after the switch closes, i.e.  $v_C(0^+)$ , and
  - as  $t \rightarrow \infty$ , i.e.  $\lim_{t \rightarrow \infty} v_C(t)$ .
- (b) (4 marks) Give an expression for the capacitor voltage  $v_C(t)$  (i.e. as a function of time) for  $t > 0$ . Explain how you arrived at this expression.

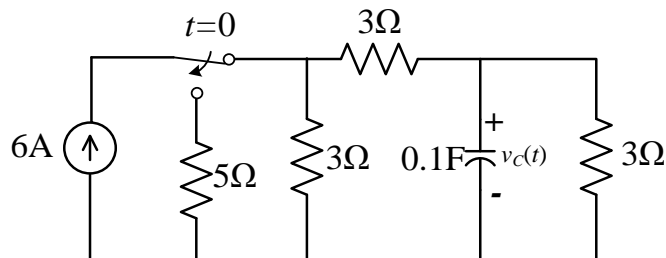


Figure 5

END OF PAPER