



Family Name .....

Given Name .....

Student No. ....

Signature .....

## THE UNIVERSITY OF NEW SOUTH WALES

### School of Electrical Engineering & Telecommunications

### FINAL EXAMINATION

Semester 2, 2017

**ELEC1111**

**Electrical and Telecommunications Engineering**

**TIME ALLOWED: 2 hours**

**TOTAL MARKS: 100**

**TOTAL NUMBER OF QUESTIONS: 5**

**THIS EXAM CONTRIBUTES 50% TO THE TOTAL COURSE ASSESSMENT**

Reading Time: 10 minutes.

This paper contains 6 pages.

Candidates must **ATTEMPT ALL** questions.

Answer each question in a **separate answer booklet**.

Marks for each question are indicated beside the question.

This paper **MAY NOT** be retained by the candidate.

Students must achieve **a minimum of 40 marks** to pass the course.

Print your name, student ID and question number on the front page of each answer book.

Authorised examination materials:

Candidates should use their own UNSW-approved electronic calculators.

This is a closed book examination.

Assumptions made in answering the questions should be stated explicitly.

All answers must be written in ink. Except where they are expressly required, pencils **may only be used** for drawing, sketching or graphical work.

For the **numerical solutions**, you can use either **fraction** form or floating-point form (maximum **2 digits** after decimal point is enough)

## QUESTION 1 [20 marks]

(i) [10 marks] For the circuit shown in Figure 1,

a. (8 marks) Apply mesh analysis and show that the mesh equations are given as below,

$$\begin{cases} i_1 + 3i_2 - 2i_3 = 8 \\ i_1 + i_2 - 4i_3 = -1 \\ i_1 - i_2 = -4 \end{cases}$$

b. (2 marks) Given the values of mesh currents as  $i_1 = -0.5$  A,  $i_2 = 3.5$  A, and  $i_3 = 1$  A, find the voltage  $v$  across 4-A current source.

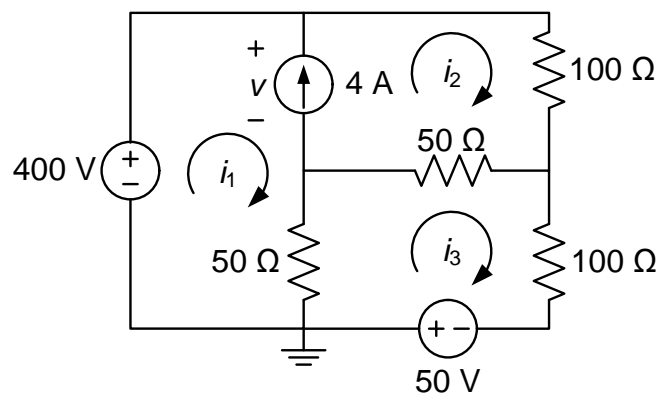


Figure 1

(ii) [10 marks] For the circuit shown in Figure 2,

a. (8 marks) Apply nodal analysis and show that the nodal equations are given as below,

$$\begin{cases} 11v_1 - 6v_2 = 108 \\ 4v_1 - 3v_2 = -54 \end{cases}$$

b. (2 marks) Given the values of node voltages as  $v_1 = 72$  V and  $v_2 = 114$  V, Calculate the power of the dependent current source.

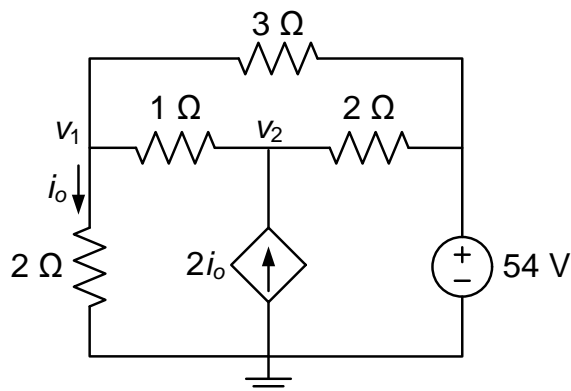


Figure 2

## QUESTION 2 [20 marks]

(i) [10 marks] For the circuit shown in Figure 3,

- (4 marks) Calculate the open-circuit voltage  $v_{oc}$  and short-circuit current  $i_{sc}$  at the terminals  $a$ - $b$ .
- (4 marks) Obtain the Norton equivalent circuit with respect to the terminals  $a$ - $b$  and draw the equivalent circuit.
- (2 marks) Determine the value of the load resistance  $R_L$  for maximum power transfer, and then calculate the maximum power that can be delivered to  $R_L$ .

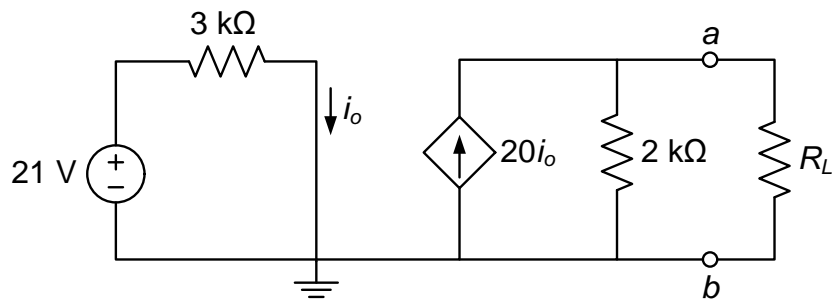


Figure 3

(ii) [10 marks] In circuit shown in Figure 4, the switch has been in position A for a long time. At  $t = 0$ , the switch moves to position B.

- (4 marks) Find the voltage  $v(t)$  across the capacitor immediately after the switch changes to position B,  $v(0^+)$ , and its final voltage when  $t \rightarrow \infty$ ,  $v(\infty)$ .
- (4 marks) Derive an expression for the capacitor voltage  $v(t)$  for all time (i.e., for both  $t < 0$  and  $t > 0$ ).
- (2 marks) Find the current  $i(t)$  through 3-kΩ resistor for  $t > 0$ .

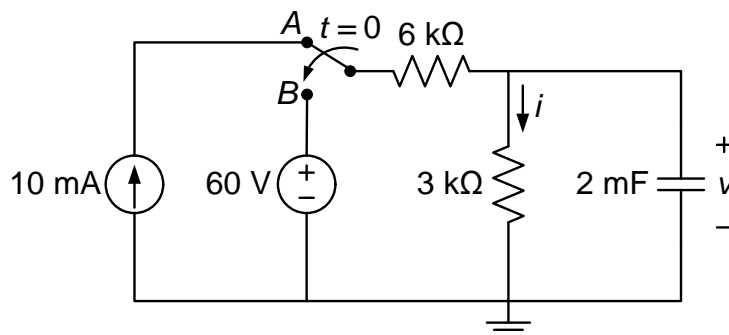


Figure 4

### QUESTION 3 [20 marks]

- (i) **[8 marks]** For the Op Amp circuit shown in Figure 5 show that the output  $v_o$  can be given by the following equation,

$$v_o = a_1 v_1 - a_2 v_2$$

and determine the parameters  $a_1$  and  $a_2$  in terms of resistors  $R_1$  to  $R_5$ .

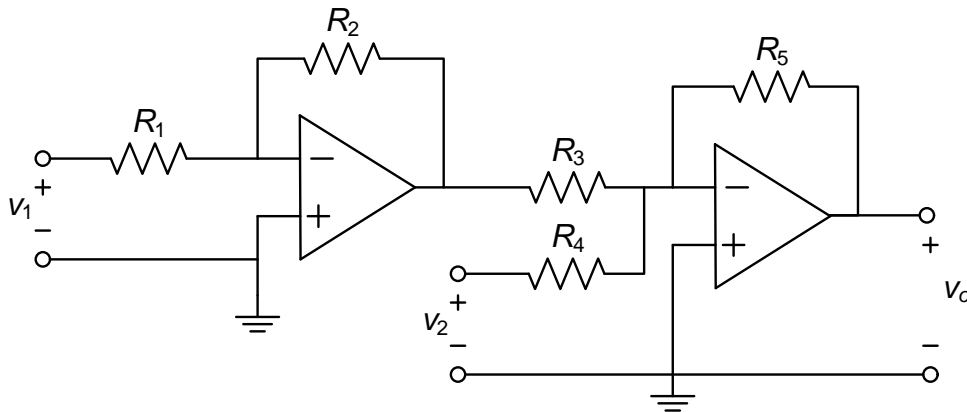


Figure 5

- (ii) **[12 marks]** In the circuit of Figure 6, the switch has been in position A for a long time before changing its position to B at  $t = 0$ .

- (10 marks)** Derive an expression for the inductor current  $i_L(t)$  for all time (i.e., for both  $t < 0$  and  $t > 0$ ) and sketch  $i_L(t)$  as a function of time showing all critical points in the sketch.
- (2 marks)** Find the voltage  $v(t)$  across the  $2\text{-}\Omega$  resistor for  $t > 0$ .

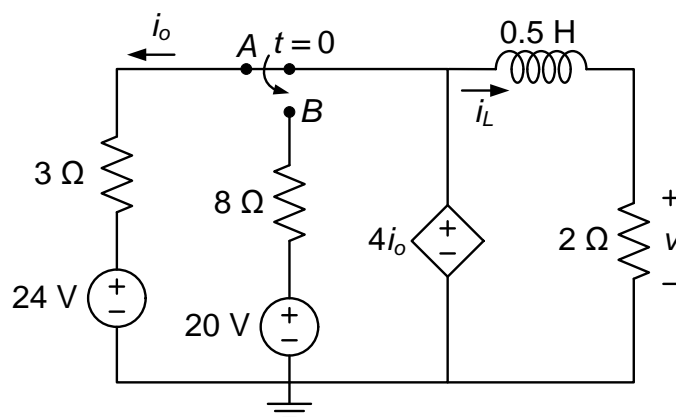


Figure 6

## QUESTION 4 [20 marks]

(i) [10 marks] For the circuit shown in Figure 7,

- (4 marks) Find the equivalent impedance  $Z_{eq}$  seen from terminals  $a$ - $b$
- (6 marks) Apply phasor analysis and source transformation to calculate the voltage  $v_x$  across the  $80\text{-}\Omega$  resistor.

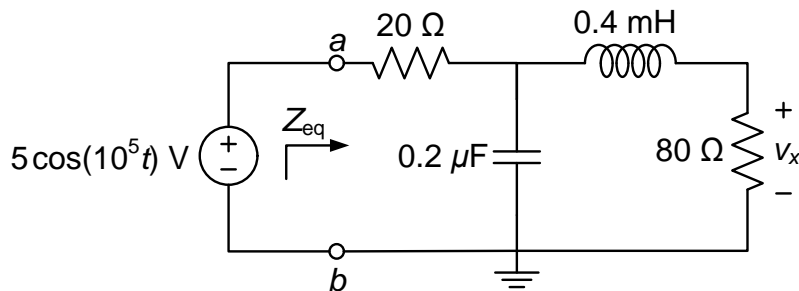


Figure 7

(ii) [10 marks] For the circuit shown in Figure 8,

- (6 marks) Find the Thevenin equivalent circuit as seen from the terminals  $a$ - $b$ , and draw the equivalent circuit.
- (2 marks) Determine the value of the load impedance  $Z_L$  for maximum average power transfer.
- (2 marks) Calculate the maximum average power that can be delivered to the load  $Z_L$  from this circuit.

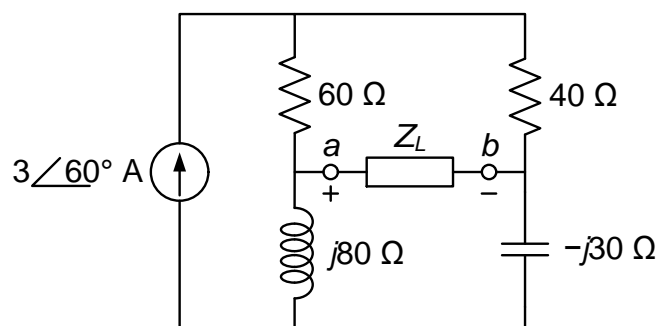


Figure 8

## QUESTION 5 [20 marks]

- (i) [10 marks] For the circuit shown in Figure 9,
- (6 marks) Find the output voltage  $v_x$  using phasor analysis and superposition principle.
  - (4 marks) Sketch the phasors of voltage source  $V$  and current source  $I$  along with phasor of voltage  $V_x$  on a phasor diagram.

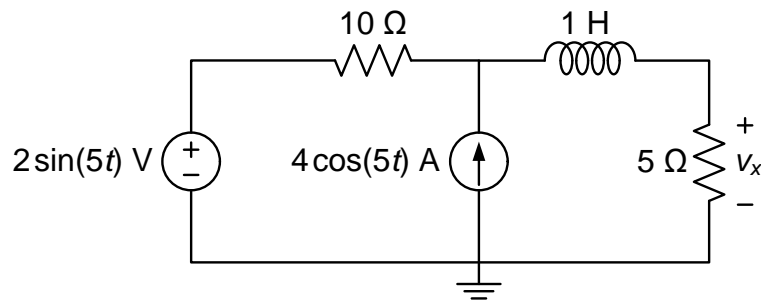


Figure 9

- (ii) [10 marks] Consider the following logical diagram shown in Figure 10.
- (4 marks) Derive and simplify the logical expression for  $Z$ .
  - (4 marks) Construct the truth table relating  $Z$  to inputs  $A$ ,  $B$ , and  $C$ .
  - (2 marks) Using part a. and/or part b., show that  $Z$  can be realised using exactly one 3-input AND gate and one 1-input NOT gate showing all working.

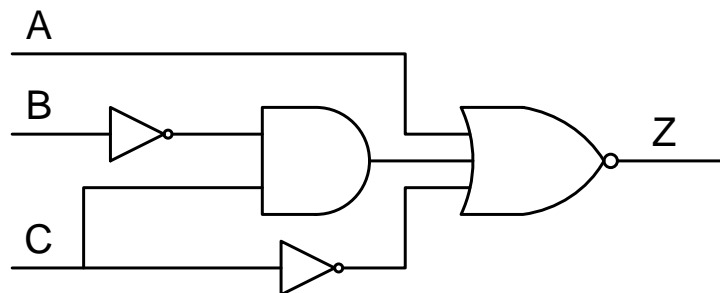


Figure 10

**END OF PAPER**