



Family Name .....

Given Name .....

Student No. ....

Signature .....

**THE UNIVERSITY OF NEW SOUTH WALES**  
**School of Electrical Engineering & Telecommunications**

**MID-SEMESTER EXAMINATION**

**Semester 2, 2017**

**ELEC1111**  
**Electrical and Telecommunications Engineering**

**TIME ALLOWED: 1 hour**  
**TOTAL MARKS: 100**  
**TOTAL NUMBER OF QUESTIONS: 4**

**THIS EXAM CONTRIBUTES 20% TO THE TOTAL COURSE ASSESSMENT**

Reading Time: 5 minutes.

This paper contains 6 pages.

Candidates must **ATTEMPT ALL** questions.

Answer each question in a **separate answer booklet**.

Marks for each question are indicated beside the question.

This paper **MAY NOT** be retained by the candidate.

Print your name, student ID and question number on the front page of each answer book.

Authorised examination materials:

Candidates should use their own UNSW-approved electronic calculators.

This is a closed book examination.

Assumptions made in answering the questions should be stated explicitly.

All answers must be written in ink. Except where they are expressly required, pencils **may only be used** for drawing, sketching or graphical work.

For the **numerical solutions**, you can use either **fraction** form or **floating-point** form (maximum **2 digits** after decimal point is enough)

### QUESTION 1 [20 marks]

- (i) For the circuit shown in Figure 1,
- (15 marks) Calculate the equivalent resistance  $R_{eq}$  as seen from terminals  $a$ - $b$ .
  - (5 marks) Find the current  $i$  through the network using the result of part (a).

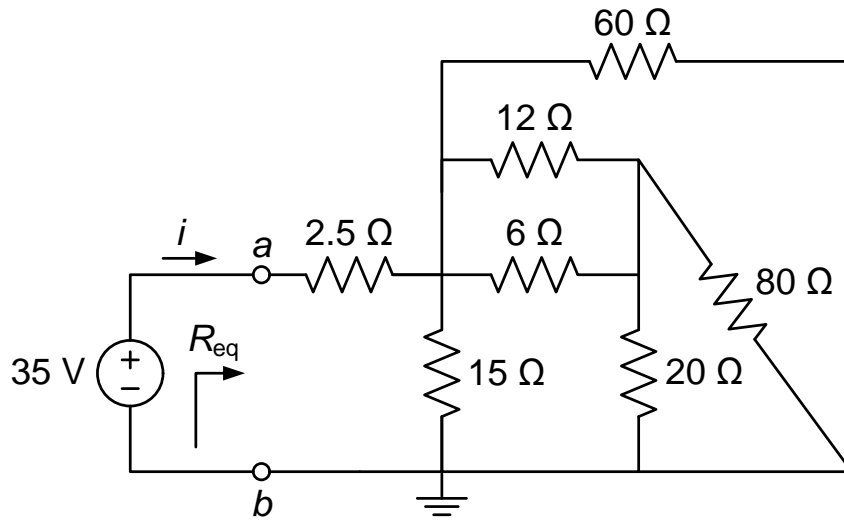


Figure 1

## QUESTION 2 [40 marks]

(i) [24 marks] For the circuit shown in Figure 2,

- (10 marks) Apply nodal analysis to obtain the node voltage at nodes  $v_1$  and  $v_2$ , and show that  $v_1 = 20\text{ V}$  and  $v_2 = 12\text{ V}$
- (12 marks) Calculate all the powers absorbed/supplied by resistors and sources and specify which element supplies power and which element absorbs power.
- (2 marks) Verify the law of conservation of energy for this circuit.

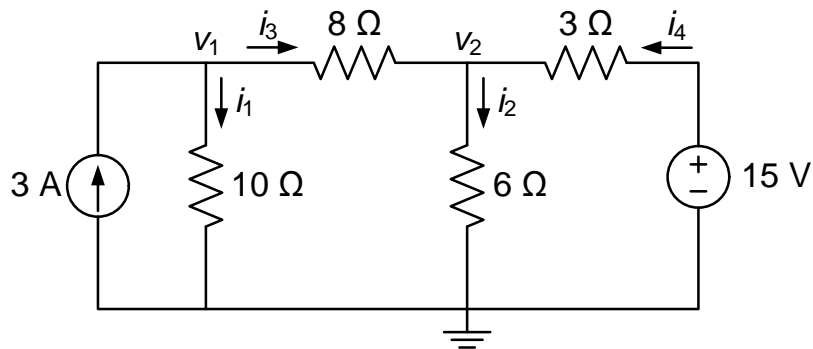


Figure 2

(ii) [16 marks] For the circuit shown in Figure 3,

- (10 marks) Apply mesh analysis to obtain the mesh currents  $i_1$ ,  $i_2$  and  $i_3$ , and show that  $i_1 = 25\text{ A}$  and  $i_2 = 12.5\text{ A}$
- (2 marks) Find the voltage  $v$  across 4-Ω resistor.
- (4 marks) Calculate the power of the 50-V voltage source and explain whether it supplies or absorbs power.

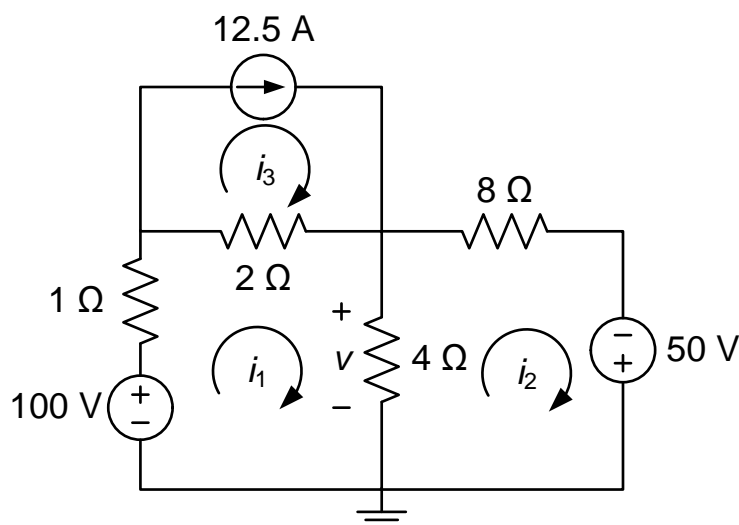


Figure 3

### QUESTION 3 [20 marks]

- (i) [10 marks] For the circuit shown in Figure 4,
- (6 marks) Use source transformation to obtain Thevenin equivalent circuit from terminals  $a$ - $b$  and draw the Thevenin equivalent circuit.
  - (4 marks) Determine the value of load resistance  $R_L$  for maximum power transfer, and then calculate the maximum power that can be delivered to  $R_L$ .

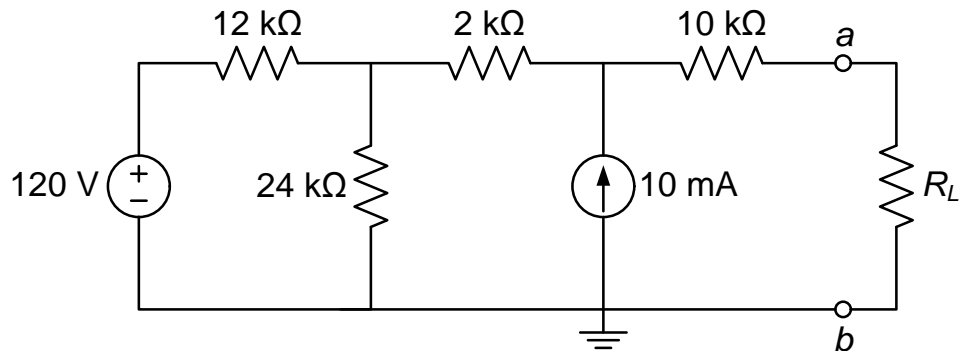


Figure 4

- (ii) [10 marks] Find the equivalent resistance  $R_{eq}$  in the circuit given in Figure 5.

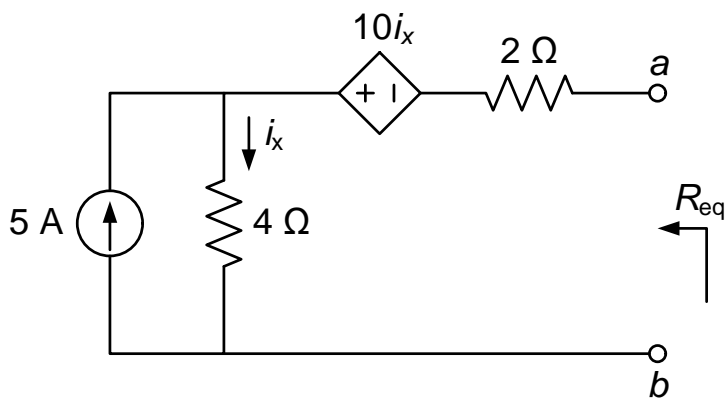


Figure 5

#### QUESTION 4 [20 marks]

- (i) In the circuit shown in Figure 6, the switch has been closed for a long time before it is opened at  $t = 0$ . The voltage source is given a step function.
- (4 marks)** Find the initial voltage  $v(0^-)$  across the capacitor under steady-state condition.
  - (2 marks)** Calculate the initial energy  $w_C(0)$  stored in the capacitor.
  - (4 marks)** Find the final voltage  $v(\infty)$  across the capacitor under steady-state condition.
  - (4 marks)** Derive an expression for the voltage of the capacitor  $v(t)$  for all time (i.e., for both  $t < 0$  and  $t > 0$ ).
  - (2 marks)** Sketch the obtained voltage  $v(t)$  in part (d) as a function of time.
  - (4 marks)** Derive an expression for the current  $i(t)$  through the  $5\text{-}\Omega$  resistor for all time (i.e., for both  $t < 0$  and  $t > 0$ ).

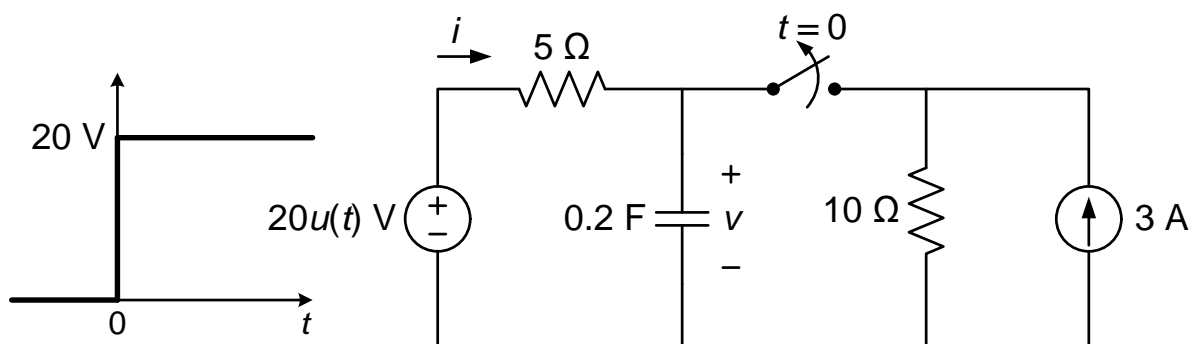


Figure 6

END OF PAPER

This page is intentionally left blank

This page is intentionally left blank