
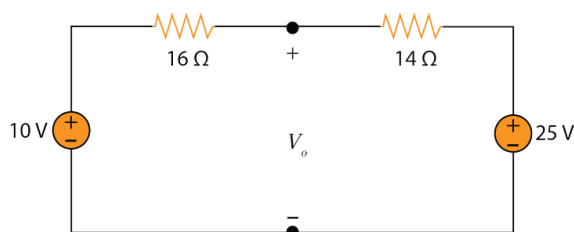


Topic 2 (part 1): Kirchhoff's Laws

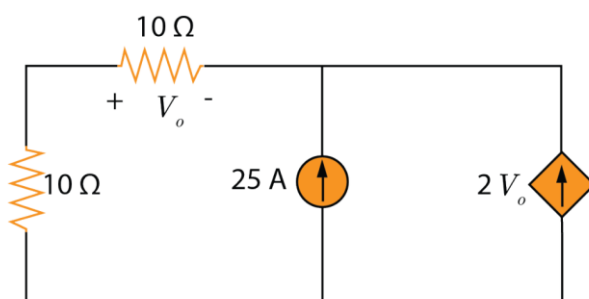1. Determine the voltage v_o in the following circuit.




2. In the following circuit:



- (a) Calculate the voltage v_o .
(b) Calculate the power supplied/absorbed by the dependent source.

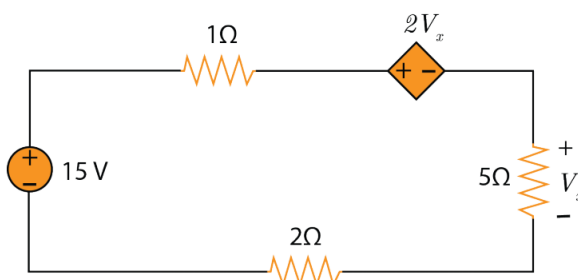3. Find voltage v_x in the following circuit.



4. Calculate the equivalent resistance R_{ab} between terminals a and b in the following two circuits.

