

ELEC 1111 - Electric Circuits

Tutorial 9 - AC Power

Never Stand Still

Faculty of Engineering

School of Electrical Engineering and Telecommunications

- Find the average power absorbed in the 50Ω resistor of the following circuit, if $i_s = 6 \cos 10^3 t$.

