
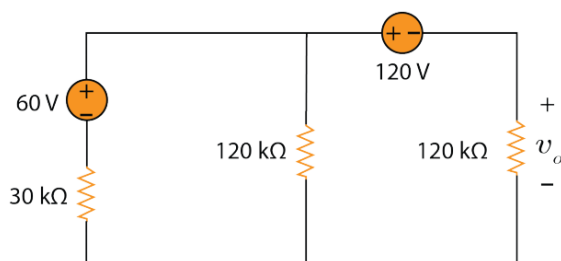


Topic 2 (part 2): Nodal and Mesh Analysis

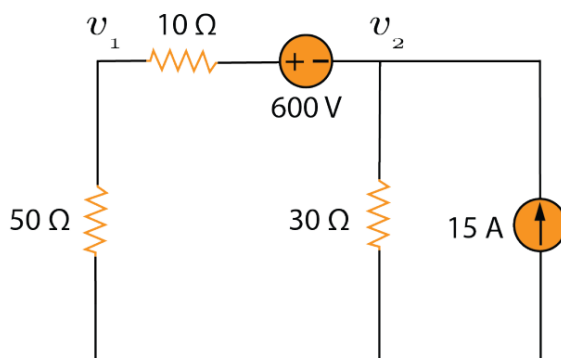1. Obtain the voltage v_o in the following circuit.



2. Using nodal analysis, calculate the voltages v_1 and v_2 of the nodes.



3. Find the voltage v_o and the current i_o of the following circuit.

