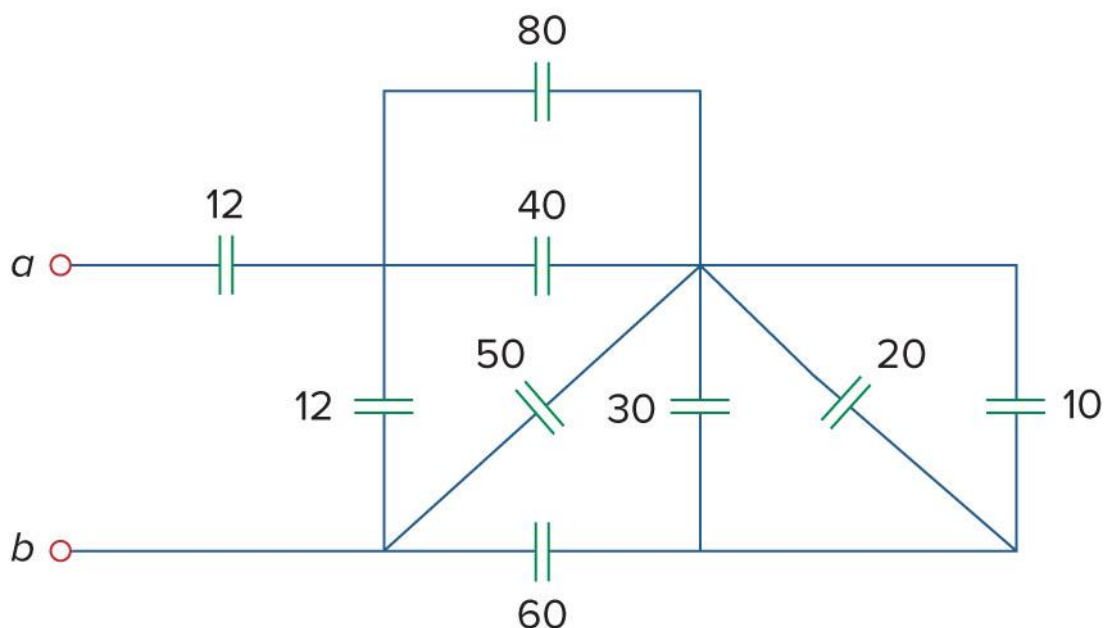


Topic 4: Capacitors and RC Circuits

1. (**Final Exam – S2, 2015**) The circuit below shows a network of supercapacitors in a hybrid energy storage system where all capacitances are in μF
- Find the equivalent capacitance at terminals a-b.
 - What is the energy stored if the voltage of terminals a-b is equal to 100 V.



Answer:


a) $C_{eq} = 10 \mu\text{F}$.

b) $w = 50 \text{ mJ}$

Hint: since nothing is mentioned about initial conditions, they are assumed to be zero.

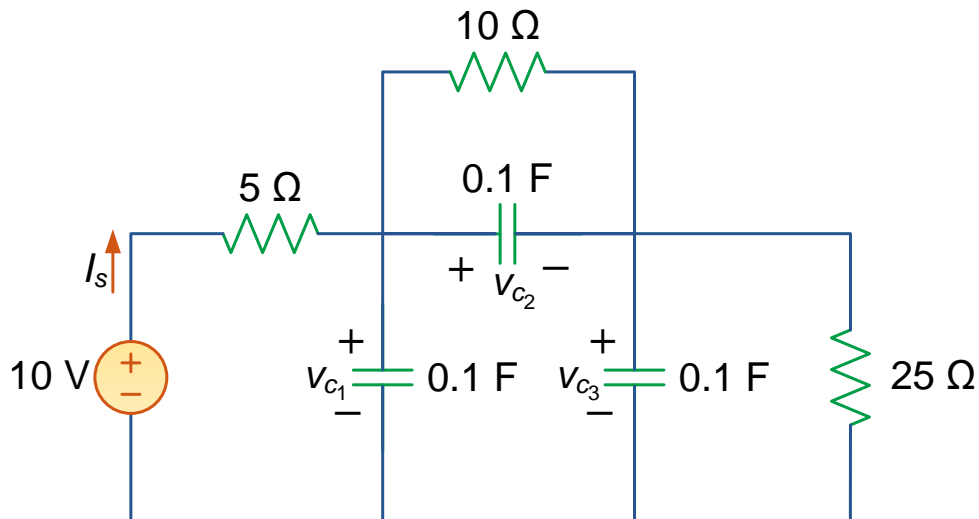2. (Final Exam – S2, 2015) For the circuit below,

- Determine the current I_s after the circuit has reached steady state.
- Determine the capacitor voltages V_{c_1} , V_{c_2} and V_{c_3} after the circuit has reached steady state.



Answer:


a) $I_s = 0.25 \text{ A}$

b) $V_{c_1} = 8.75 \text{ V}$, $V_{c_2} = 2.5 \text{ V}$, $V_{c_3} = 6.25 \text{ V}$

Hint: The steady state means that the capacitors are fully charged and under DC conditions.

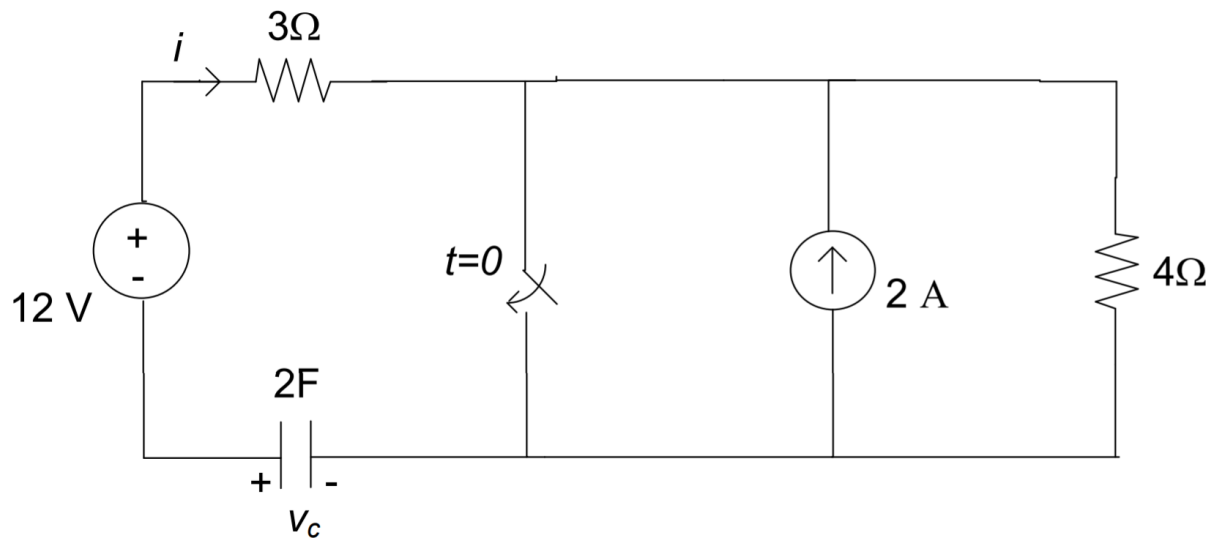3. (Final Exam – S2, 2015) For the circuit below, the switch has been in open position for a long time before changing position as shown at time $t = 0$.


- Find the voltage v_c and the current i when $t < 0$, i.e., $v_c(0^-)$ and $i(0^-)$.
- Find v_c and i when $t > 0$ and in steady state condition, i.e., $v_c(+\infty)$ and $i(+\infty)$.



Answer:

- $v_c(0^-) = -4 \text{ V}$ and $i(0^-) = 0 \text{ A}$
- $v_c(+\infty) = -12 \text{ V}$ and $i(+\infty) = 0 \text{ A}$

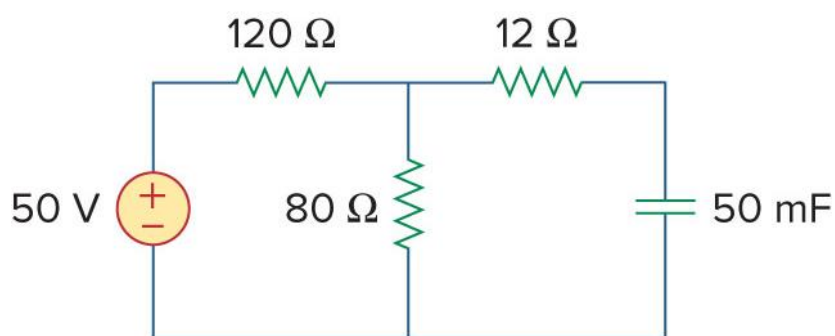
4. Find the time constant for the RC circuit given below.



Answer: $\tau = 3 \text{ s}$

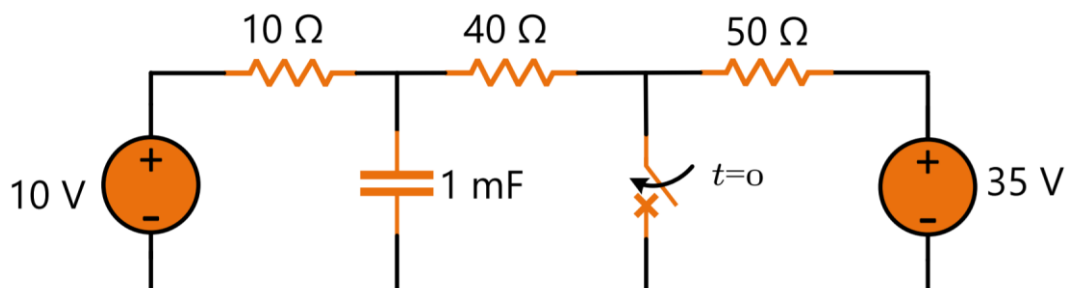5. (Mid-semester Exam - Summer 2017) In the circuit below, the switch has been in the open position for a long time before closing at time $t = 0$.

- Give an expression for the capacitor voltage $v_c(t)$ (i.e., as a function of time) for $t > 0$.
- Give an expression for the capacitor current $i_c(t)$ for $t > 0$
- Give an expression for the current of the 40-Ω resistor $i_{R40}(t)$ for $t > 0$.




Answer:

$$\text{a) } v_c(t) = 8 + 4.5e^{\frac{-t}{8 \times 10^{-3}}} \text{ V}$$

$$\text{b) } i_c(t) = -\frac{4.5}{8}e^{\frac{-t}{8 \times 10^{-3}}} = -0.5625e^{\frac{-t}{8 \times 10^{-3}}} \text{ A}$$


$$\text{c) } i_{R40}(t) = \frac{8}{40} + \frac{4.5}{40}e^{\frac{-t}{8 \times 10^{-3}}} = 0.2 + 0.1125e^{\frac{-t}{8 \times 10^{-3}}} \text{ A}$$

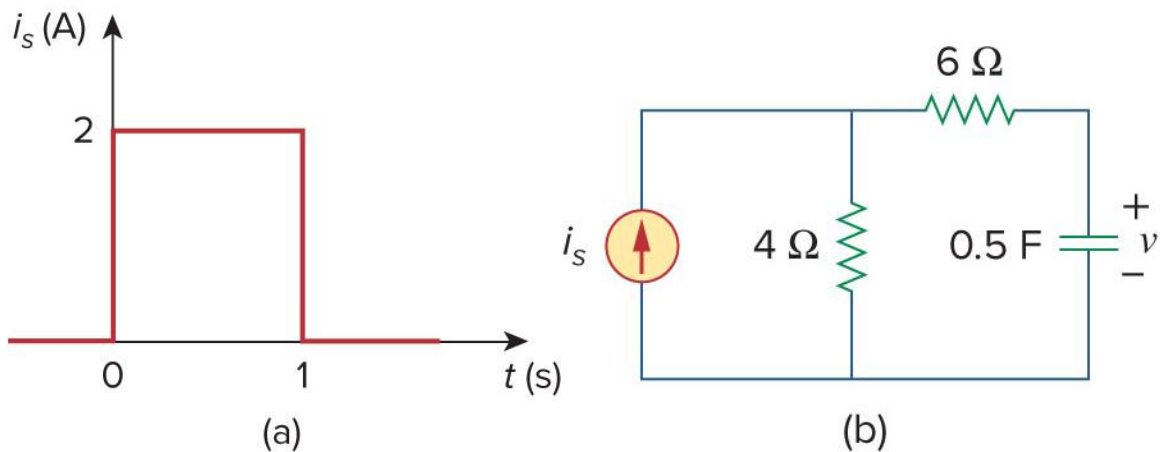6. If the waveform given in Fig. (a) is applied to the circuit of Fig. (b), find the expression for $v(t)$ assuming $v(0) = 0$.



Answer:
$$v(t) = \begin{cases} 8 \left(1 - e^{-\frac{t}{5}}\right) \text{ V}, & 0 < t < 1 \\ 1.4502 e^{-\frac{-(t-1)}{5}} \text{ V}, & t \geq 1 \end{cases}$$

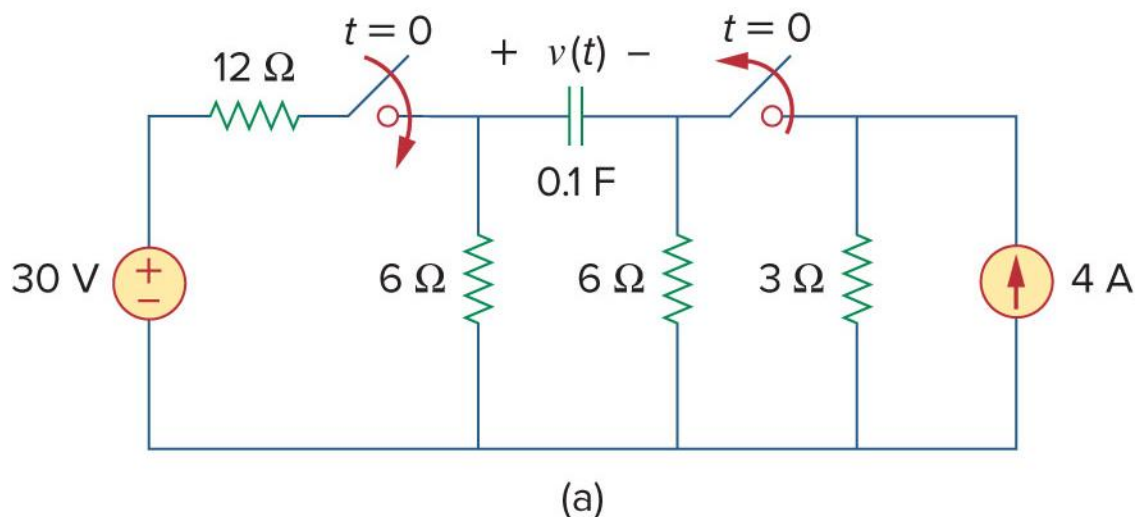7. In the circuit below, determine the response $v(t)$ for all time (i.e., for both $t < 0$ and $t > 0$), and sketch $v(t)$ waveform showing all critical points in the sketch.



Answer:
$$v(t) = \begin{cases} -8 \text{ V} & t \leq 0 \\ 10 - 18e^{-t} \text{ V} & t \geq 0 \end{cases}$$