

Family Name

Given Name

Student No.

Signature

THE UNIVERSITY OF NEW SOUTH WALES

School of Electrical Engineering & Telecommunications

FINAL EXAMINATION

Session 2, 2015

ELEC1111

Electrical and Telecommunications Engineering

TIME ALLOWED: 3 hours

TOTAL MARKS: 100

TOTAL NUMBER OF QUESTIONS: 5

THIS EXAM CONTRIBUTES 60% TO THE TOTAL COURSE ASSESSMENT

Reading Time: 10 minutes.

This paper contains 7 pages.

Candidates must **ATTEMPT ALL** questions.

Answer each question in a **separate answer book**.

Marks for each question are indicated beside the question.

This paper **MAY NOT** be retained by the candidate.

Print your name, student ID and question number on the front page of each answer book.

Authorised examination materials:

Candidates should use their own UNSW-approved electronic calculators.

This is a closed book examination.

Assumptions made in answering the questions should be stated explicitly.

All answers must be written in ink. Except where they are expressly required, pencils **may only be used** for drawing, sketching or graphical work.

QUESTION 1 [20 marks]

- (i) [6 marks] Find the equivalent capacitance at terminals a - b of the circuit in Figure 1. All capacitances are in μF .

 


Figure 1

- (ii) [7 marks] For the circuit shown in Figure 2:
- Find the indicated currents I_1 , I_2 and I_3 .
 - Find the voltage V_{ab} .
 - Find the total power dissipated by the resistors.

 


Figure 2

- (iii) [7 marks] For the circuit shown in Figure 3, use nodal analysis to find the nodal voltages V_a and V_b .

 


Figure 3

QUESTION 2 [20 marks]

- (i) **[6 marks]** For the circuit shown in Figure 4, use mesh analysis to calculate the current I_I .

 


Figure 4

- (ii) **[8 marks]** For the circuit shown in Figure 5 use the principle of superposition to find the voltage v_x .

 


Figure 5

- (iii) **[6 marks]** Find and draw the Thevenin equivalent circuit with respect to the terminals A-B for the circuit in Figure 6.

 


Figure 6

QUESTION 3 [20 marks]

(i) [4 marks] For the circuit shown in Figure 7:

- Determine the current I_C after the circuit has reached steady state.
- Determine the capacitor voltages V_{C1} , V_{C2} and V_{C3} after the circuit has reached steady state.

 


Figure 7

(ii) [6 marks] Refer to the circuit shown in Figure 8. The switch has been closed for a long time before opening at time $t=0$. Calculate the values $i_R(0^+)$, $i_L(0^+)$ and $i_C(0^+)$, immediately after the switch opens. Calculate the values $i_R(\infty)$, $i_L(\infty)$ and $i_C(\infty)$, after the switch has been open for a long time.

 


Figure 8

QUESTION 3 CONTINUES ON NEXT PAGE

- (iii) **[10 marks]** In the circuit shown in Figure 9, switch S_1 is closed at $t=0$ and switch S_2 is closed at $t=4$. Find the current $i(t)$ for $t>0$.

 


Figure 9

QUESTION 4 [20 marks]

- (i) **[10 marks]** Determine v_o in the circuit shown in Figure 10:


 


Figure 10

 - (ii) **[5 marks]** Find the input admittance, Y_{in} , of the circuit shown in Figure 11 at $\omega = 100 \text{ rad/s}$. Express answer in polar form.



(b)

Figure 11

- (iii) **[5 marks]** For Figure 12, $i_1 = 100 \sin(50t + 100^\circ) \text{ A}$ and $i_T = 50 \sin(50t - 40^\circ) \text{ A}$. Determine phasors I_1 , I_2 and I_T and draw the phasor diagram showing I_1 , I_2 and I_T .

 


Figure 12

QUESTION 5 [20 marks]

- (i) **[8 marks]** Calculate the voltage v_o after the op amp circuit of Figure 13 has reached steady state.

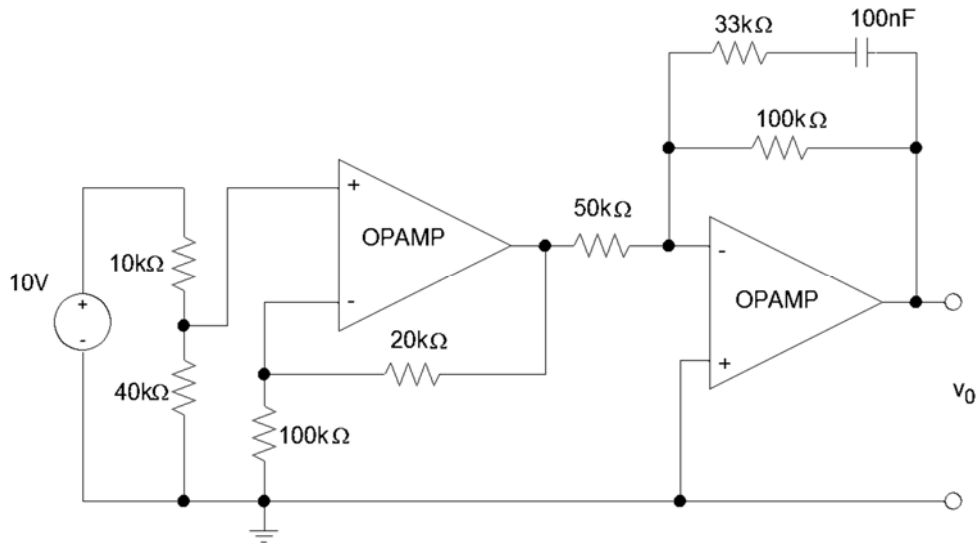


Figure 13

- (ii) **[6 marks]** Draw the logic diagram which represents the function of this logic equation:

$$Output = \bar{A}.B.D + B.\bar{C} + \bar{D}$$

- (iii) **[6 marks]** For the logic circuit shown in Figure 14, draw up a truth table that describes the operation of this circuit.

 


Figure 14

END OF PAPER