

Family Name .....

Given Name .....

Student No. ....

Signature .....

**UNSW SYDNEY**

**School of Electrical Engineering & Telecommunications**

**FINAL EXAMINATION**

**Semester 1, 2017**

**ELEC1111**

**Electrical and Telecommunications Engineering**

<b>TIME ALLOWED:</b>	<b>2 hours</b>
<b>TOTAL MARKS:</b>	<b>100</b>
<b>TOTAL NUMBER OF QUESTIONS:</b>	<b>5</b>

**THIS EXAM CONTRIBUTES 50% TO THE TOTAL COURSE ASSESSMENT**

Reading Time: 10 minutes.

This paper contains 6 pages.

Candidates must **ATTEMPT ALL** questions.

Answer each question in a **separate answer booklet**.

Marks for each question are indicated beside the question.

This paper **MAY NOT** be retained by the candidate.

Students must achieve a **minimum of 40 marks** to pass the course.

Print your name, student ID and question number on the front page of each answer book.

Authorised examination materials:

Candidates should use their own UNSW-approved electronic calculators.

This is a closed book examination.

Assumptions made in answering the questions should be stated explicitly.

All answers must be written in ink. Except where they are expressly required, pencils **may only be used** for drawing, sketching or graphical work.

## QUESTION 1 [20 marks]

- (i) [10 marks] In the circuit of Figure 1,
- [5 marks] Calculate the voltage  $V_x$ .
  - [3 marks] Calculate the power dissipated in the  $4\ \Omega$  resistor.
  - [2 marks] Does the dependent voltage source in this circuit supply or absorb power? Explain your answer.

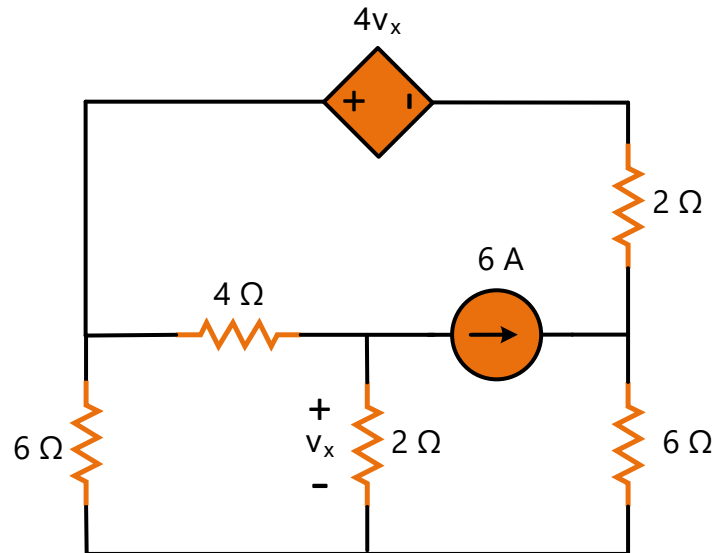


Figure 1

- (ii) [10 marks] For the circuit of Figure 2
- [4 marks] Calculate the Thevenin voltage for terminals a-b
  - [4 marks] Find the Thevenin resistance  $R_{th}$  for terminals a-b and draw the equivalent Thevenin circuit.
  - [2 marks] What is the maximum power that can be delivered to a load from this circuit?

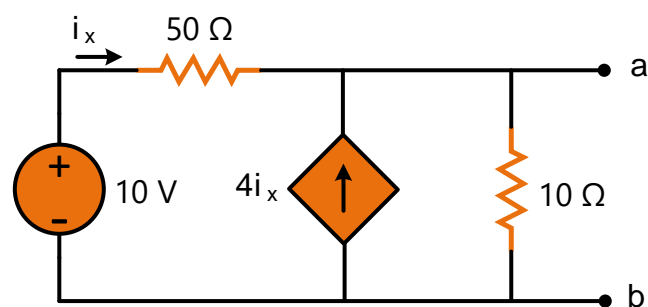


Figure 2

## QUESTION 2 [20 marks]

(i) [8 marks] Operational Amplifiers

- a. [5 marks] Demonstrate, deriving the required equations, that the gain of a *non-inverting amplifier* circuit is given by

$$\frac{V_{out}}{V_{in}} = 1 + \frac{R_f}{R_{in}}$$

where  $R_f$  and  $R_{in}$  are the feedback and input resistances, respectively.

- b. [1 mark] From the following set of resistors select  $R_f$  and  $R_{in}$  to achieve a gain of 12.

1 $\Omega$	5 $\Omega$	8 $\Omega$	10 $\Omega$	20 $\Omega$	50 $\Omega$
60 $\Omega$	80 $\Omega$	100 $\Omega$	110 $\Omega$	120 $\Omega$	150 $\Omega$
100 $\Omega$	220 $\Omega$	240 $\Omega$	330 $\Omega$	470 $\Omega$	600 $\Omega$

- c. [2 marks] What resistors from the ones above should be used if you would like to construct an *inverting amplifier* where  $\frac{V_{out}}{V_{in}} = -12$ .

- (ii) [12 marks] Find the output voltage  $v_{out}$  of the following Operational Amplifier circuit. Plot the voltages  $v_{in}$  and  $v_{out}$  in the same phasor diagram.

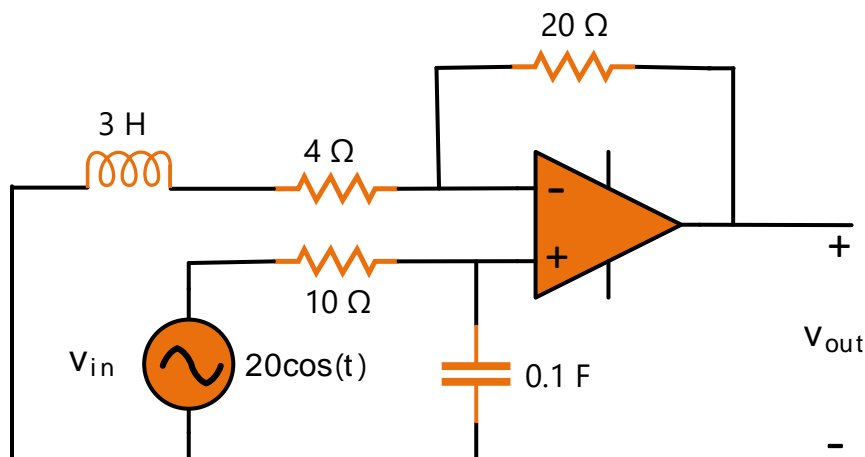


Figure 3

### QUESTION 3 [20 marks]

- (i) [10 marks] Find the voltage  $v_x(t)$  in the circuit of Figure 4.

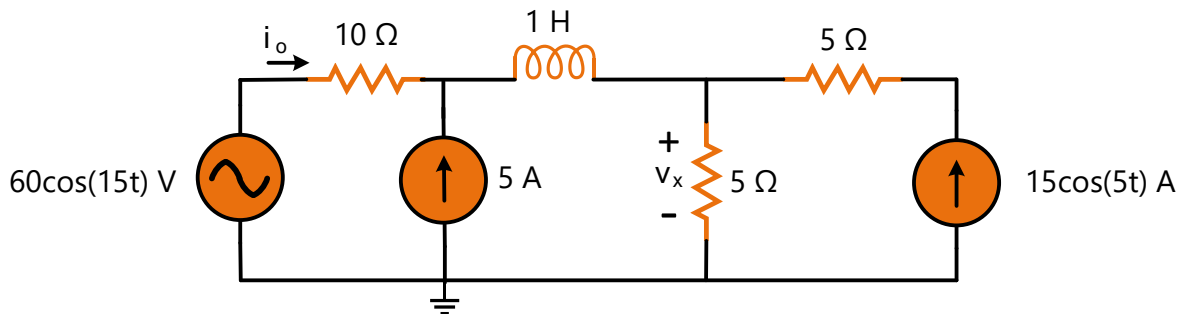


Figure 4

- (ii) [10 marks] In the following circuit of Figure 5,
- [2 marks] Find the energy stored in the inductor under steady-state when the switch is in the open position.
  - [4 marks] If the switch has been in the open position for a long time and closes at  $t=0$ , derive an analytical expression for the current  $i_L$  through the inductor for  $t>0$ .
  - [2 marks] Plot the current through the inductor as a function of time.
  - [2 marks] Derive an analytical expression for the voltages across resistors  $R_1$  and  $R_2$  ( $v_{R_1}$  and  $v_{R_2}$ ) as a function of time for  $t>0$ .

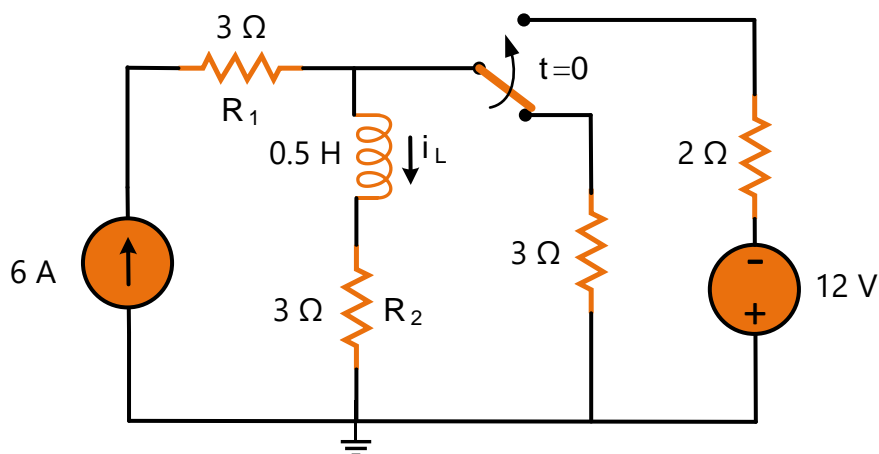


Figure 5

## QUESTION 4 [20 marks]

- (i) [8 marks] Calculate the equivalent impedance of the circuit of Figure 6 as seen by:
- (2 marks) a *dc* voltage source
  - (6 marks) an *ac* voltage source with a frequency of  $\omega = 2$  rad/sec. (Provide your answer in rectangular or polar form)

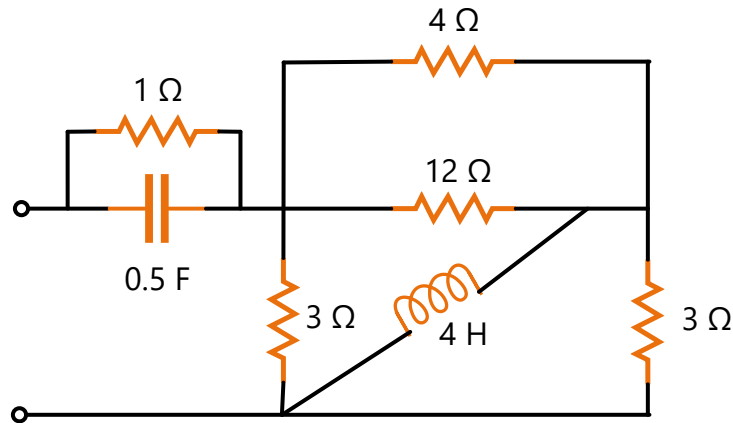


Figure 6

- (ii) [10 marks] For the circuit shown in Figure 7
- [7 marks] Calculate and draw the Thevenin equivalent of the circuit for terminals a-b
  - [3 marks] Calculate and draw the Norton equivalent of the circuit for terminals a-b

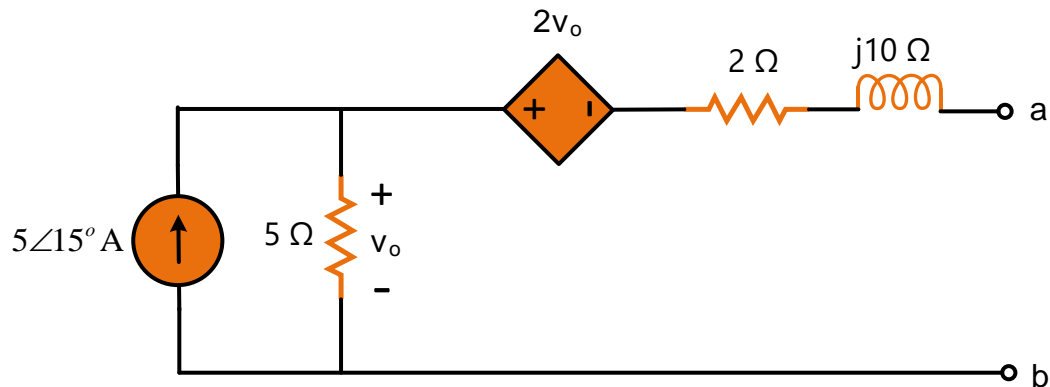


Figure 7

- (iii) [2marks] Consider the Thevenin equivalent of a circuit that consists of a voltage source and an impedance  $Z_{Th}$ . What is the value of the load impedance  $Z_L$  that should be connected to its terminals for maximum power transfer?

### QUESTION 5 [20 marks]

- (i) [8 marks] Two loads are connected in parallel and are supplied by a  $230\text{ V}_{\text{rms}}$ , 50 Hz voltage source.

**Load 1** consumes 20 kVA of power at a power factor of 0.8 leading (capacitive)

**Load 2** consumes 6 kW at a power factor of 0.6 lagging (inductive)

Calculate:

- [2 marks] The total complex power of the two loads.
  - [2 marks] The total apparent power.
  - [2 marks] The combined power factor of the two loads, and
  - [2 marks] The rms value of the current supplied by the source.
- (ii) [6 marks] A ideal 500V:100V transformer is rated at 20 kVA and is supplied by a  $500\text{ V}_{\text{rms}}$ , 50 Hz voltage source in its primary windings. A load of  $10+j10\ \Omega$  is connected in its secondary windings. Draw the circuit and calculate:
- [2 marks] The currents through the primary and secondary windings
  - [2 marks] The power consumed by the load
  - [2 marks] The loading of the transformer (Transformer loading is the ratio of power through the transformer over the rated power of the transformer.)
- (iii) [6 marks] Consider the following logical diagram
- [3 marks] Derive and simplify the logical expression for Z.
  - [3 marks] Write the truth table of the circuit.

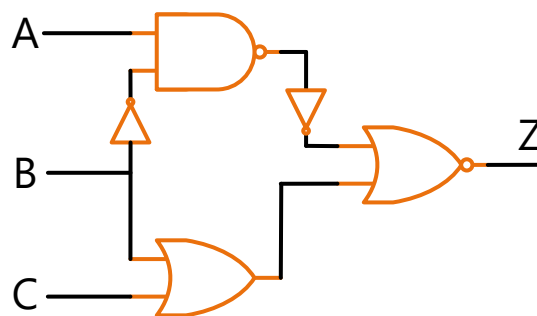


Figure 8

**END OF PAPER**