

2016 Semester 2 Final Exam

Question 1

a)

i) KCL at node a:

$$\frac{V_a}{12} + \frac{V_a - V_b}{2} + 2i_n = 0$$

$$\text{But } i_n = \frac{V_c}{2}$$

$$V_a + 6V_a - 6V_b + 12V_c = 0$$

$$7V_a - 6V_b + 12V_c = 0 \quad (1)$$

KCL at node b:

$$\frac{V_b - V_a}{2} + 1 + \frac{V_b - V_c}{5} = 0$$

$$5V_b - 5V_a + 10 + 2V_b - 2V_c = 0$$

$$-5V_a + 7V_b - 2V_c = -10 \quad (2)$$

KCL at node c:

$$\frac{V_c}{2} + \frac{V_c - V_b}{5} = 2i_n = 2\left(\frac{V_c}{2}\right) = V_c$$

$$5V_c + 2V_c - 2V_b = 10V_c$$

$$2V_b + 3V_c = 0 \quad (3)$$

ii)
$$\left(\begin{array}{ccc|c} 7 & -6 & 12 & 0 \\ -5 & 7 & -2 & -10 \\ 0 & 2 & 3 & 0 \end{array} \right) \quad R_2 = 7R_2 + 5R_1$$

$$\left(\begin{array}{ccc|c} 7 & -6 & 12 & 0 \\ 0 & 19 & 46 & -70 \\ 0 & 2 & 3 & 0 \end{array} \right) \quad R_3 = 19R_3 - 2R_2$$

$$\left(\begin{array}{ccc|c} 7 & -6 & 12 & 0 \\ 0 & 19 & 46 & -70 \\ 0 & 0 & -35 & 140 \end{array} \right) \quad \therefore V_C = -4V$$

$$V_B = \frac{-70 - 46(-4)}{19} = 6V$$


$$V_A = \frac{6 \times 6 - 12(-4)}{7} = 12V$$

iii) $i_3 = 2i_1 = 2i_2$
 $\therefore 2i_2 - i_3 = 0 \quad \textcircled{1}$

KCL at supermesh:

$$i_2 + 1 = i_1$$

$$i_1 - i_2 = 1 \quad \textcircled{2}$$

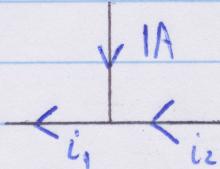

KVL in supermesh:

$$12i_1 + 2(i_1 - i_3) + 5(i_2 - i_3) + 2i_2 = 0$$

$$14i_1 + 7i_2 - 7i_3 = 0$$

$$2i_1 + i_2 - i_3 = 0 \quad \textcircled{3}$$

iv) $\left(\begin{array}{ccc|c} 1 & -1 & 0 & 1 \\ 0 & 2 & -1 & 0 \\ 2 & 1 & -1 & 0 \end{array} \right) \quad R_3 = R_3 - 2R_1$

$$\left(\begin{array}{ccc|c} 1 & -1 & 0 & 1 \\ 0 & 2 & -1 & 0 \\ 0 & 3 & -1 & -2 \end{array} \right) \quad R_3 = 2R_3 - 3R_2$$

$$\left(\begin{array}{ccc|c} 1 & -1 & 0 & 1 \\ 0 & 2 & -1 & 0 \\ 0 & 0 & 1 & -4 \end{array} \right) \quad \therefore i_3 = -4A$$

$$i_2 = -4 = -2A$$

$$i_1 = -1A$$

v) Power absorbed:

$$P_{12\Omega} = \frac{V_a^2}{R} = \frac{12^2}{12} = 12W \text{ absorbed}$$

$$P_{2\Omega} = \frac{(V_a - V_b)^2}{R} = \frac{(12 - 6)^2}{2} = 18W \text{ absorbed}$$

$$P_{5\Omega} = \frac{(V_b - V_c)^2}{R} = \frac{(6 - 4)^2}{5} = 20W \text{ absorbed}$$

$$P_{1\Omega} = \frac{V_c^2}{R} = \frac{(-4)^2}{2} = 8W \text{ absorbed}$$

$$P_{1A} = 1 \times V_b = 1 \times 6 = 6W \text{ absorbed}$$

Power supplied:

$$2i_n = 2i_2 = -4A$$

$$V_a - V_c = 12 + 4 = 16V$$


$$P_{2i_n} = -4 \times 16 = 64W \text{ supplied}$$

$$\sum P = 64 - 6 - 8 - 20 - 18 - 12$$

$\approx 0W \quad \therefore \text{Power is conserved}$

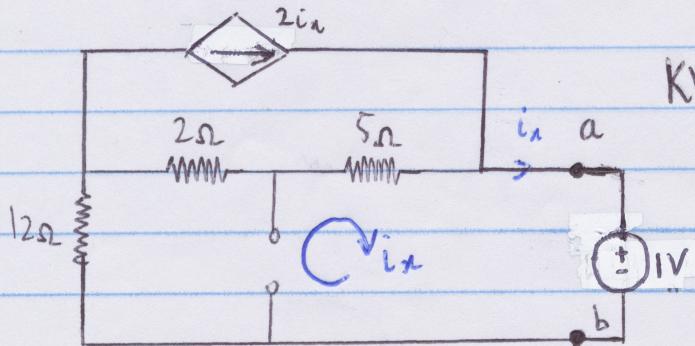b) Finding R_{Th}

$i_n = 0A \Rightarrow \text{Open circuit}$



KVL in mesh


$$12i_n + 7(i_n - 2i_n) + 1 = 0$$

$$5i_n = -1$$

$$i_n = -0.2A$$

$$\therefore R_{Th} = \frac{1}{i_n} = -5\Omega$$

Finding V_{Th}

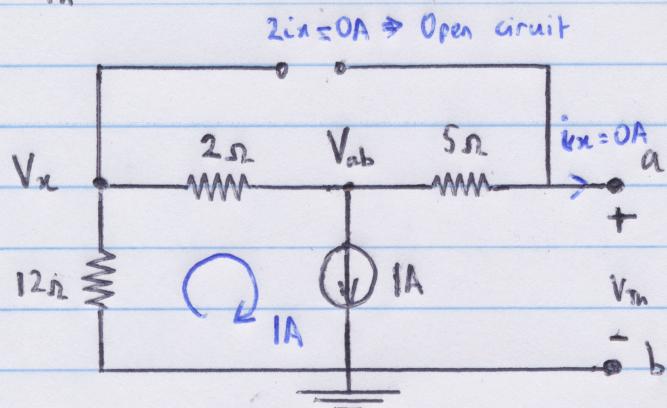

Current across 5Ω :

$$\frac{V_{ab} - V_{Th}}{5} = 0$$

$$\therefore V_{ab} = V_{Th}$$

Current across 12Ω :

$$\frac{0 - V_R}{12} = 1$$

$$V_R = -12V$$

KCL:

$$\frac{V_{ab} - (-12)}{2} + 1 + 0 = 0$$

$$V_{ab} + 12 + 2 = 0$$

$$\therefore V_{ab} = -14V$$


$$\text{Hence } V_{Th} = -14V$$

$$P_{max} = \left| \frac{V_{Th}^2}{4R_{Th}} \right| = \left| \frac{(-14)^2}{4 \times 5} \right| = 9.8W \text{ when } R_L = 5\Omega$$

c)

$$\text{By superposition } V_o = V'_o + V''_o + V'''_o$$

Only leaving 9V source on (V_o')

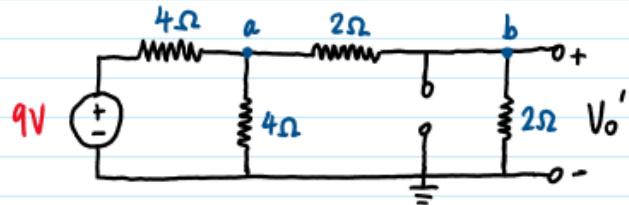

KCL at node a:

$$\frac{V_a - 9}{4} + \frac{V_a}{4} + \frac{V_a - V_b}{2} = 0$$

$$V_a - 9 + V_a + 2V_a - 2V_b = 0$$

$$4V_a - 2V_b = 9$$

$$V_a = \frac{9 + 2V_b}{4}$$

KCL at node b:

$$\frac{V_b - V_a}{2} + \frac{V_b}{2} = 0$$

$$2V_b - V_a = 0$$


$$2V_b - \left(\frac{9 + 2V_b}{4}\right) = 0$$

$$8V_b - 9 - 2V_b = 0$$


$$6V_b = 9$$

$$V_b = \frac{3}{2} = 1.5V = V_o'$$

Only leaving 2V source on (V_o'')

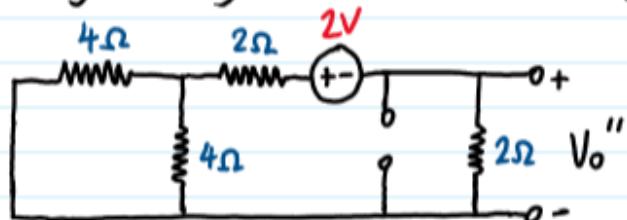

$$4/4 = 2\Omega$$

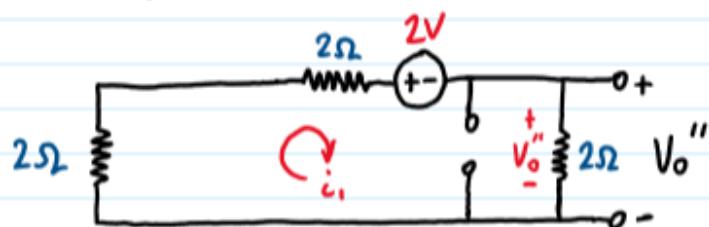

KCL in mesh

$$2i_1 + 2i_1 + 2 + 2i_1 = 0$$

$$6i_1 = -2$$


$$i_1 = -\frac{1}{3}$$

$$\therefore V_o'' = 2i_1 = -\frac{2}{3}V$$

Only leaving 0.5A source on (V_o''')



$$4//4 + 2 = 4\Omega$$

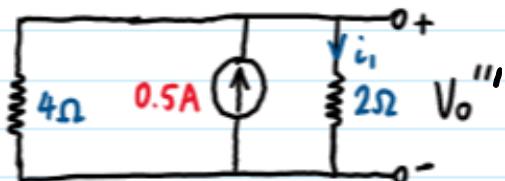

Current division

$$i_1 = \frac{4}{4+2} \times 0.5 = \frac{1}{3}A$$

$$\therefore V_o'' = 2i_1 = \frac{2}{3}V$$

$$\therefore V_o = V_o' + V_o'' + V_o'''$$

$$= 1.5 - \frac{2}{3} + \frac{2}{3}$$

$$= 1.5V$$


$$\therefore V_o = V'_o + V''_o + V'''_o$$

$$= 1.5 - \frac{2}{3} + \frac{2}{3}$$


$$= 1.5V$$

d) $V_{Th} = V_o = 3V$

Finding R_{Th}

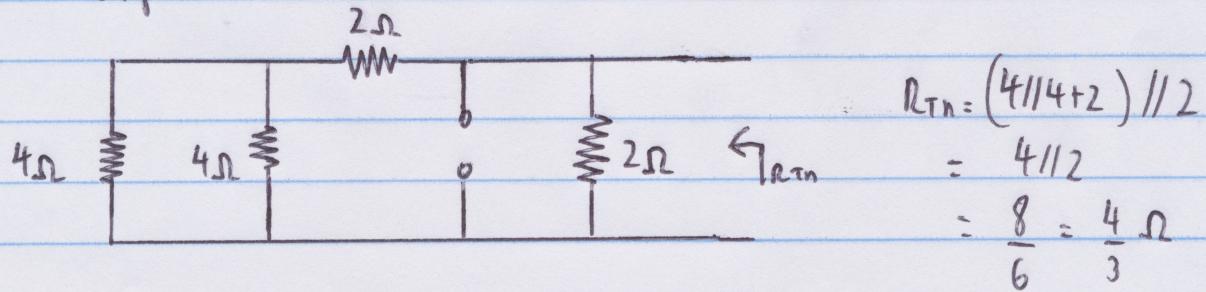


\therefore Thevenin equivalent circuit

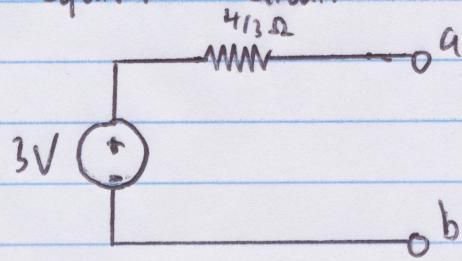

Question 2

a) At $t=0^-$

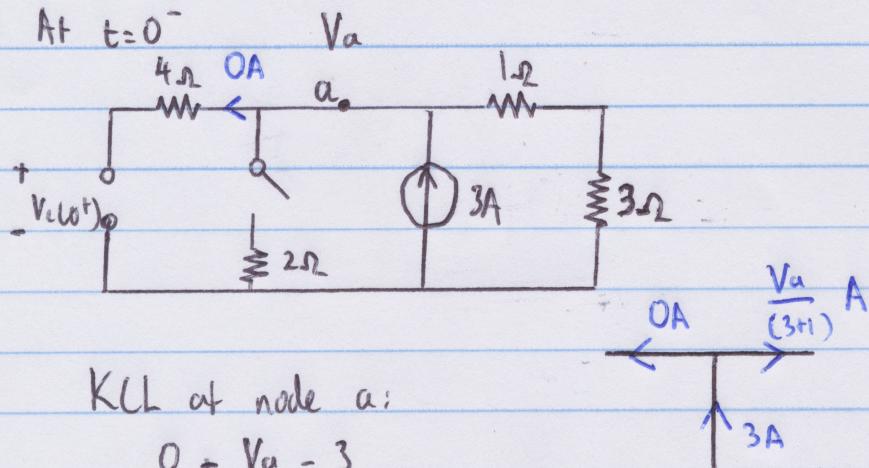


KCL at node a:

$$0 + \frac{V_a}{4} + 3 = \frac{V_a}{3+1}$$

$$V_a = 12V \Rightarrow \text{Current across } 4\Omega: 0 = \frac{V_a - V_c(0^+)}{4} \therefore V_a = V_c(0^+)$$

$$\therefore V_c(0^+) = 12V$$

b) At $0 \leq t \leq 1$

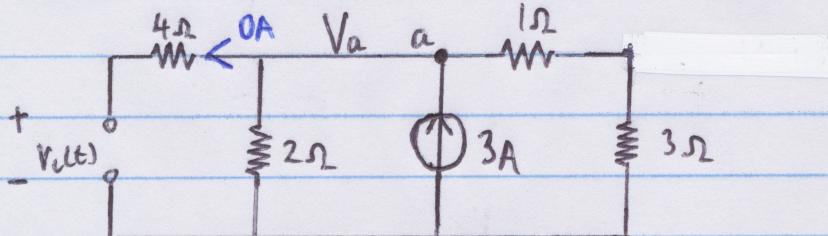

KCL at node a:

$$0 + \frac{V_a}{2} + \frac{V_a}{4} = 3$$

$$3V_a = 12$$

$$V_a = 4V \Rightarrow V_a = V_c(t)$$

$$\therefore V_c(t) = 4V$$

$$R_{Th} = 4 + (3+1)/2 \Rightarrow T = R_{Th}L = \left(\frac{16}{3}\right)(1) = \frac{16}{3}s$$


$$= \frac{16}{3}\Omega$$

$$V_c(t) = 4 + (12-4)e^{-\frac{3}{16}t} V$$

$$= 4(1 + 2e^{-\frac{3}{16}t}) V \text{ for } 0 \leq t \leq 1$$

c) For $t \geq 1$

$$V_c(t) = 4(1 + 2e^{-\frac{3}{10}})$$

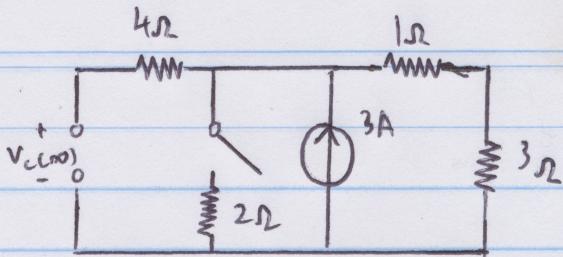

At $t \geq 1$ (Same figure as a))

$$\therefore V_c(\infty) = 12V$$

$$R_{Th} = 4 + 1 + 3 \\ = 8\Omega$$

$$T = R_{Th} C = 8(1) = 8s$$

$$\therefore V_c(t) = 12 + (4 + 8e^{-\frac{3}{10}} - 12) e^{-\frac{(t-1)}{8}} V \\ = 12 + 8(-1 + e^{-\frac{3}{10}}) e^{-\frac{(t-1)}{8}} V \quad \text{for } t \geq 1$$

d) From c)

$$V_c(\infty) = 12V \quad (\text{Similarly solve for } \lim_{t \rightarrow \infty} (V_c(t)) = 12V)$$

e) At $t=5$

$$W_c = \frac{1}{2} C(V(s))^2 = \frac{1}{2}(1)[12 + 8(-1 + e^{-\frac{3}{10}}) e^{-\frac{1}{2}}]^2 = 62.39J$$

Question 3

a)

$$\text{i) } Z_{eq}(L) = \frac{-j}{wC}$$

$$Z_{eq}(L) = jwL$$

$$Z_{eq AB} = R \parallel \left(\frac{-j}{wC} + jwL \right)$$

$$= R \parallel \left(\frac{jw^2 CL - j}{wC} \right)$$

$$= \left(\frac{1}{R} + \frac{wC}{jw^2 CL - j} \right)^{-1}$$

$$= \left(\frac{jw^2 CL - j + wCR}{R(jw^2 CL - j)} \right)^{-1} = \frac{jR(w^2 CL - 1)}{wCLR + j(w^2 CL - 1)}$$


$$\text{ii) } Z_{eq} = j6 \left(100^2 \times 2 \times 10^{-3} \times 0.1 - 1 \right) = 3.841 \cos(100t + 50.2^\circ) \Omega$$

$$100 \times 2 \times 10^{-3} \times 6 + j(100^2 \times 2 \times 10^{-3} \times 0.1 - 1) \quad \text{or } 3.841 \angle 50.2^\circ \Omega$$

$$\text{iii) } V_s = 240 \sin(100t) = 240 \omega_s (100t - 90^\circ) V = 240 \angle -90^\circ$$

$$i_s = \frac{V_s}{Z_{eq}} = \frac{240 \angle -90^\circ}{3.841 \angle 50.2^\circ} = -48 - j40 = 62.482 \omega_s (100t - 140^\circ) A$$


iv)

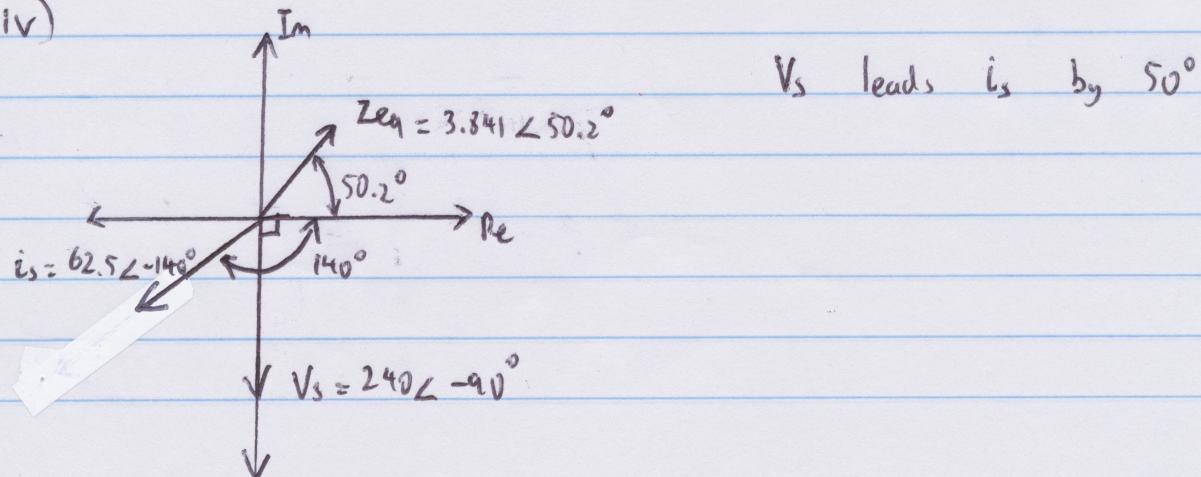

b)

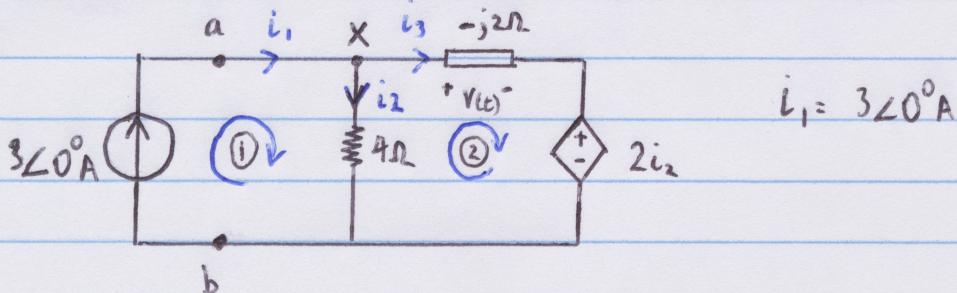i) $\omega = 4 \text{ rad/s}$

$$Z_{eq}(0,125\text{F}) = -j \frac{1}{4(0,125)} = -j2 \Omega$$



KCL at node X:

$$i_1 = i_2 + i_3$$

$$i_2 + i_3 = 3 \quad \textcircled{1}$$

KVL in mesh ②:

$$(-j2)i_3 + 2i_2 - 4i_2 = 0$$

$$-2i_2 - (j2)i_3 = 0 \quad \textcircled{2}$$

$$\textcircled{1} \times 2 \Rightarrow 2i_2 + 2i_3 = 6 \quad \textcircled{3}$$


$$\textcircled{2} + \textcircled{3} \Rightarrow (2-j2)i_3 = 6$$

$$i_3 = \frac{6}{2-j2} = 2.121 \cos(4t + 45^\circ) \text{ A}$$


$$\therefore i_2 = 3 - 2.121 \cos(4t + 45^\circ) = 2.121 \cos(4t - 45^\circ) \text{ A}$$

$$\therefore v(t) = (-j2) \left(\frac{6}{2-j2} \right) = 4.243 \cos(4t - 45^\circ) \text{ V}$$

ii)

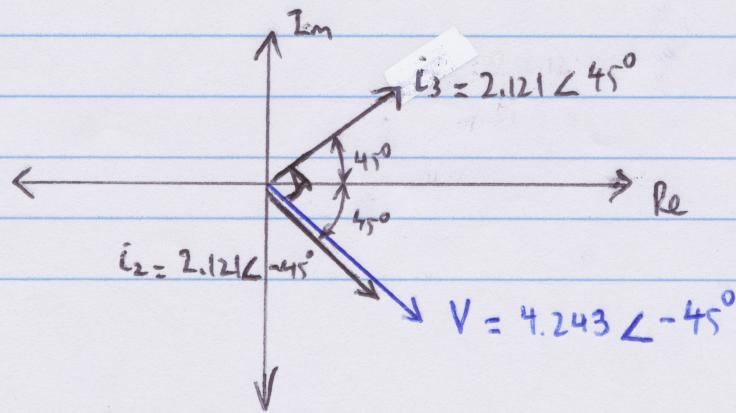

Question 4

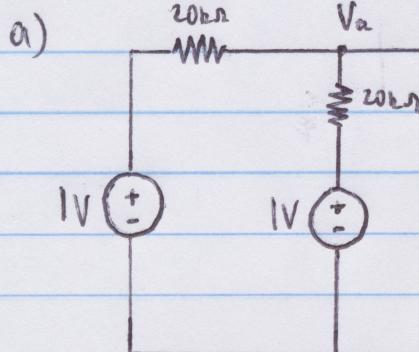

KCL at node a:


$$\frac{V_a - 1}{20 \times 10^3} + \frac{V_a - 1}{20 \times 10^3} + \frac{V_a}{10 \times 10^3} = 0$$

$$4V_a = 2$$

$$V_a = 0.5V$$

b)

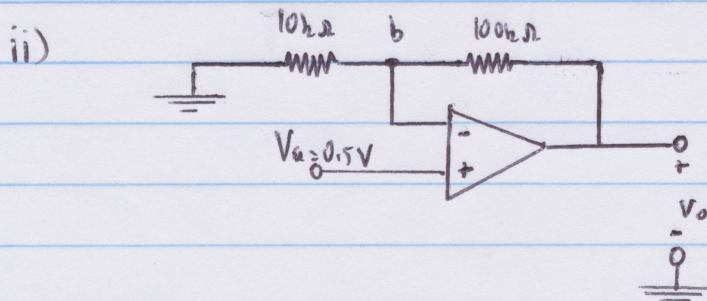i) $\frac{V_o}{V_a} = \frac{5.5}{0.5} = 11$



$$V_a = V_b = 0.5V \text{ (Op amp principle)}$$

KCL at node b:

$$\frac{0.5}{10,000} + \frac{0.5 - V_o}{100,000} = 0$$

$$5.5 = V_o$$

$$\therefore V_o = 5.5V$$

iii) The output ratio is greater than zero ($11 > 0$) so the circuit cannot be an inverting amplifier $\Rightarrow \frac{V_o}{V_a} = -\frac{R_f}{R_{in}}$ (Inverting amplifier formula)

Furthermore supply voltage is supplied through the positive terminal of the op amp.



Question 5

a) Binary value | 16 8 4 2 1
 Binary digit | 1 1 0 0 1

$$11001 \Rightarrow 16+8+1 = 25$$

b) Binary value | 32 16 8 4 2 1 $35 = 32 + 2 + 1$
 Binary digit | 1 0 0 0 1 1

$$100011 \Rightarrow 35$$

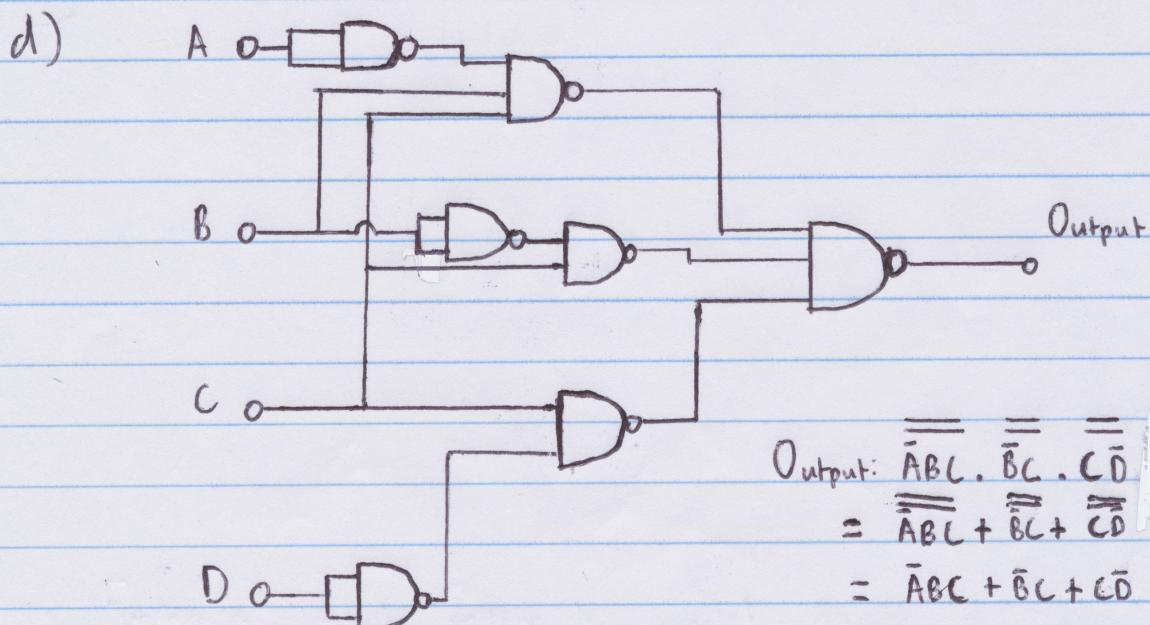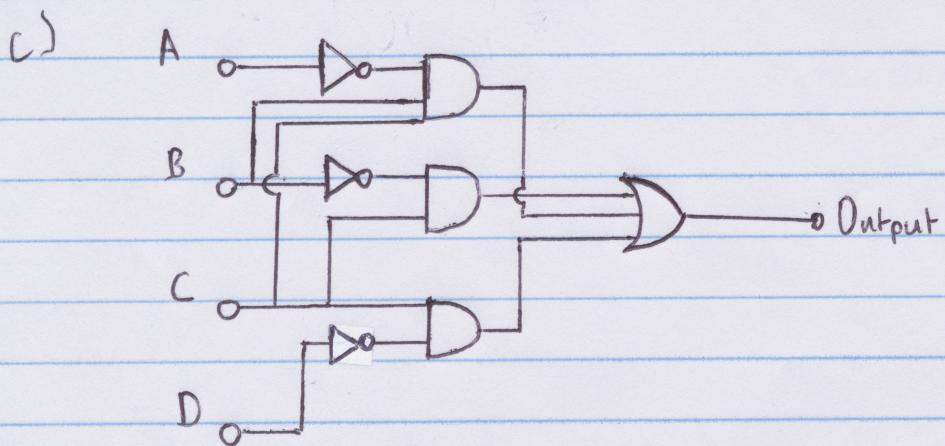

e)

$$\text{i) } f(A, B, C) = \overline{(A, B) + (\bar{B} + C)}$$

ii)	A	B	C	A, B	$\bar{B} + C$	$f(A, B, C)$
	0	0	0	0	1	0
	0	0	1	0	1	0
	0	1	0	0	0	1
	0	1	1	0	1	0
	1	0	0	0	1	0
	1	0	1	0	1	0
	1	1	0	1	0	0
	1	1	1	1	1	0

$$\text{iii) } \overline{(A, B) + (\bar{B} + C)}$$

$$= (\overline{A, B}) \cdot (\overline{\bar{B} + C})$$

$$= (\bar{A} + \bar{B}) \cdot (\bar{\bar{B}} \cdot \bar{C}) = (\bar{A} + \bar{B}) \cdot (B \cdot \bar{C})$$

$$= \bar{A} \cdot B \cdot \bar{C} + \cancel{\bar{B} \cdot B \cdot \bar{C}}$$

$$= \bar{A} \cdot B \cdot \bar{C}$$

