$$V_{s} = V_{o} + 1) \text{ Identify all nodes}$$

$$V_{s} = V_{o} + 120 \text{ k}\Omega$$

$$V_{s} = V_{o} + 120 \text{ or } V_{o} = V_{s} - 120 \text{ or } V_{o} = V_{o} - 120 \text{ or } V_{o} = V_{$$

3) Define currents so K(1 of nobe 1:
$$l_1 + l_2 + l_3 = 0$$

Because of series elements: $l_1 = \frac{V_2}{30k}$ $l_3 = \frac{V_0}{190k}$

KCL: $\frac{V_2}{30k} + \frac{V_1}{190k} + \frac{V_0}{190k} = 0 = 0$
 $\frac{V_1 - 60}{30k} + \frac{V_1}{190k} + \frac{V_1 - 190}{190k} = 0$

$$\Rightarrow 6V_1 = 360 \Rightarrow V_1 = 60V$$

$$V_0 = V_1 - 120 = 60 - 120 = -60V$$



$$\begin{array}{c|c}
v & 10 \Omega & \forall x & v \\
\hline
600 V & 30 \Omega
\end{array}$$

$$\begin{array}{c|c}
\hline
15 A & \\
\hline
Reference Node
\end{array}$$

1) From series connection

$$\frac{V_1}{50} = \frac{V_X}{60}$$

2) At nobe x


3) Nodal analysis at node 2

$$\Rightarrow \frac{V_{x}}{60} + \frac{V_{9}}{30} = 15 \Rightarrow$$

$$\Rightarrow \frac{V_x + 600}{60} + \frac{V_y}{30} = 15 \Rightarrow 3V_y + 600 = 300 \Rightarrow V_y = 100V$$

$$\frac{V_1}{50} = \frac{V_2 + 600}{60} \Rightarrow V_1 = \frac{50}{60} (100 + 600) = 583.3 \text{ V}$$



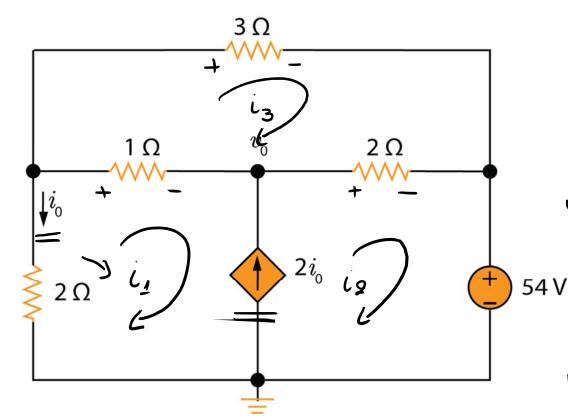


Mesh 3:
$$3i_3 - 2(i_2 - i_3) - 1(i_3 - i_3) = 0$$
 - => $6i_3 - 2i_2 - i_3 = 0$ (3)

Finally io = - L1


$$(1) \rightarrow i_{2} - i_{1} = 2i_{0} = -2i_{1}$$

$$\Rightarrow i_{2} = -i_{1} (4)$$

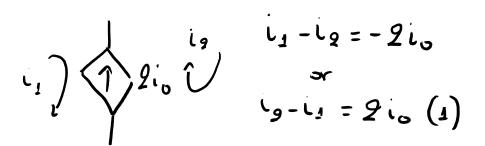i) (urrent source between two meshes: Supermesh:



Supermesh:

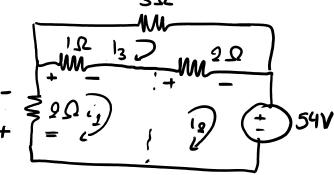

$$2i_1 + 3(i_1 - i_3) + 2(i_9 - i_3) + 54 = 0$$

=> $3i_1 + 2i_9 - 3i_3 = -54$ (2)



$$V_0 = 54 + 2 (i_2 - i_3) = 54 + 2 (36 - 6) = 54 + 60 = 114V$$

0/50

$$V_0 = -2i_1 - J(i_1 - i_3) = -2(-36) - J(-36 - 6) = 72 + 42 = 114V$$

